

EE 200 -03 Term Project

The Project

Design an adder circuit that adds two 2-digit decimal numbers and implement your design using Logicworks. Include means to enter the two decimal numbers and display the sum in your circuit.