

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
DEPARTMENT OF ELECTRICAL ENGINEERING

EE 200 DIGITAL LOGIC CIRCUIT DESIGN

EXAMINATION II

December 5, 2007

NAME :					
I.D. # :					
SECTION :	1	2	3	4	5

PROBLEM #	SCORE	MAXIMUM
1.		40
2.		30
3.		30
TOTAL		100

Q.# 1)

Design a combinational circuit that implements the following Boolean functions:

$$F_1(A, B, C, D) = \sum(0, 2, 8, 9, 10, 11, 13, 15)$$


$$F_2(A, B, C, D) = \prod(0, 2, 8, 10, 13, 15)$$

1. using a decoder made with NAND gates and external gates. Determine the type of external gates.
 2. Using a PLA with the minimum number of product terms. Determine the size of the PLA and its program table.
 3. Draw the logic circuit of the PLA showing the fuse pattern.
-
-

Q # 2)

In the logic circuit shown below, the inputs are x_2, x_1, x_0 and the final output is F .

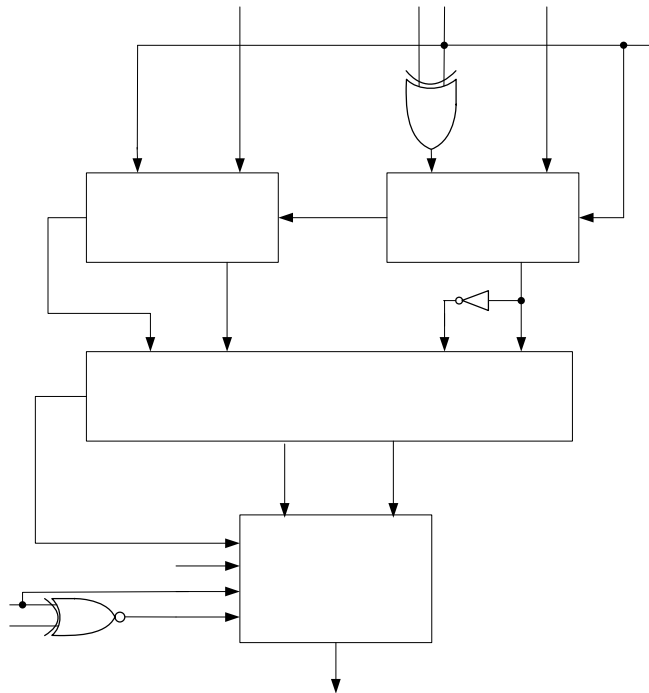- Derive the truth table that describes the operation of this circuit. Show the logic values at $D_0, D_1, D_2, D_3, A, B, V$ and F
 - Find out what the output function F represents in terms of the input variables.
-
-



Q # 3)

You would like to build a circuit that implements the function

$$F(A, B, C, D) = A'B + A'C + A'D + BD + AB'C'D$$

Only a 4x4 ROM and a 4x1 MUX are available. Program the ROM in the following circuit to implement the function F .

