

Section 3

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**  
Department of Electrical Engineering

**EE200 Digital Logic Circuit Design**

**Quiz # 4**

**12 November 2007**

**Student's Name:**

**I.D. #:**

Design a combinational circuit that will accept a three bit binary number (x, y, z) and generates the 2's complement of the input binary number (A, B, C). Implement the logic circuit using only NOR gates

---

---

Do not write below this line

---

---

*Instructor : Dr. M.M. Dawoud*

(071)

**Score : /10**