

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester I 2007/2008

Electronics II EE303

Quiz (1)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 MINUTES

Find the poles of the following circuit.

