

P 4.38

$$i_g = 4$$

$$50i_1 - 20i_2 - 25i_g = 0$$

$$-20i_1 + 120i_2 - 30i_\Delta = 0, \quad i_\Delta = i_1$$

$$\text{Solving, } i_1 = 4A, \quad i_2 = 5A$$

$$i_{25\Omega} = 4 - i_1 = 0, \quad i_{20\Omega} = i_2 - i_1 = 1A, \quad i_{100\Omega} = 4 - i_2 = -1A$$

$$i_{5\Omega} = i_1 = 4A, \quad V_1 = 100(i_g - i_2) = -100V, \quad V_2 = 25(i_g - i_1) = 0.$$

$$\therefore V_3 = V_2 + V_1 = 0 + (-100) = -100V$$

$$\therefore P_{4A} = -4V_3 = 400W \text{ (abs).}$$

$$30i_\Delta = 30i_1 = 120V \text{ (voltage of dependent source).}$$

$$\therefore P_{30i_\Delta} = -(30i_\Delta)i_2 = -600W \text{ (dev.)}$$


$$P_{5\Omega} = 16(5) = 80W, \quad P_{25\Omega} = 0, \quad P_{20\Omega} = 1(20) = 20W$$

$$P_{100\Omega} = 1(100) = 100W, \quad P_{4A}$$

$$\therefore \sum P_{abs} = P_{4A} + P_{5\Omega} + P_{25\Omega} + P_{20\Omega} + P_{100\Omega}$$

$$= 400 + 80 + 0 + 20 + 100 = 600W$$
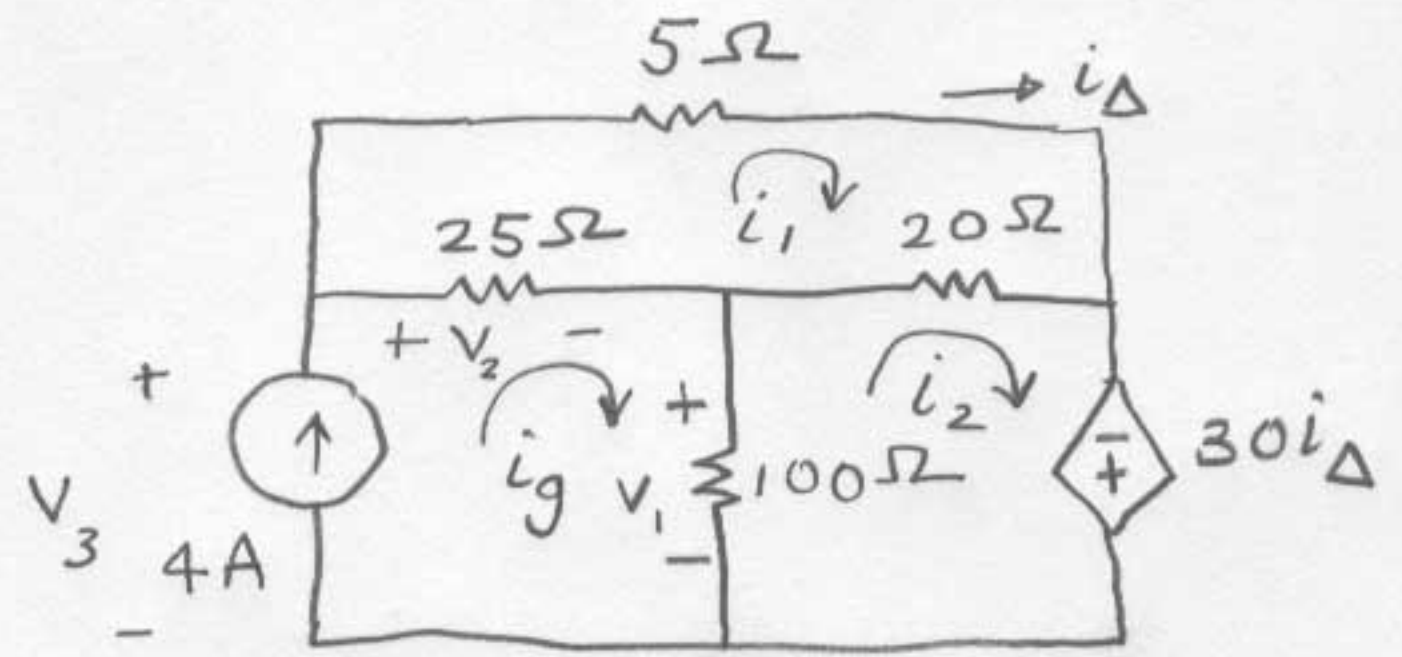
$$\therefore \sum P_{abs} = \sum P_{del.} = 600W$$



P 4.42 a)

$$15 = 30i_1 - 25i_2 - 2i_3$$

$$-10 = -25i_1 + 30i_2 - i_3$$

$$i_3 = 1.2 V_{\Delta}, \quad V_{\Delta} = 25(i_1 - i_3)$$

Solving, $i_1 = 10 \text{ A}$, $i_2 = 9 \text{ A}$, $i_3 = 30 \text{ A}$

$$i_{2\Omega} = i_1 - i_3 = 10 - 30 = -20 \text{ A}$$

$$P_{2\Omega} = (-20)^2 (2) = 800 \text{ W}$$

$$b) P_{15V} = -15(10) = -150 \text{ W (dev.)}$$


$$P_{10V} = 10i_2 = 10(9) = 90 \text{ W (abs.)}$$

$$V_o = 2(i_1 - i_3) + 1(i_2 - i_3) = -40 - 21 = -61 \text{ V}$$


$$P_{1.2V_{\Delta}} = i_3 V_o = 30(-61) = -1830 \text{ W (dev.)}$$

$$\sum P_{\text{dev.}} = 1830 + 150 = 1980 \text{ W}$$



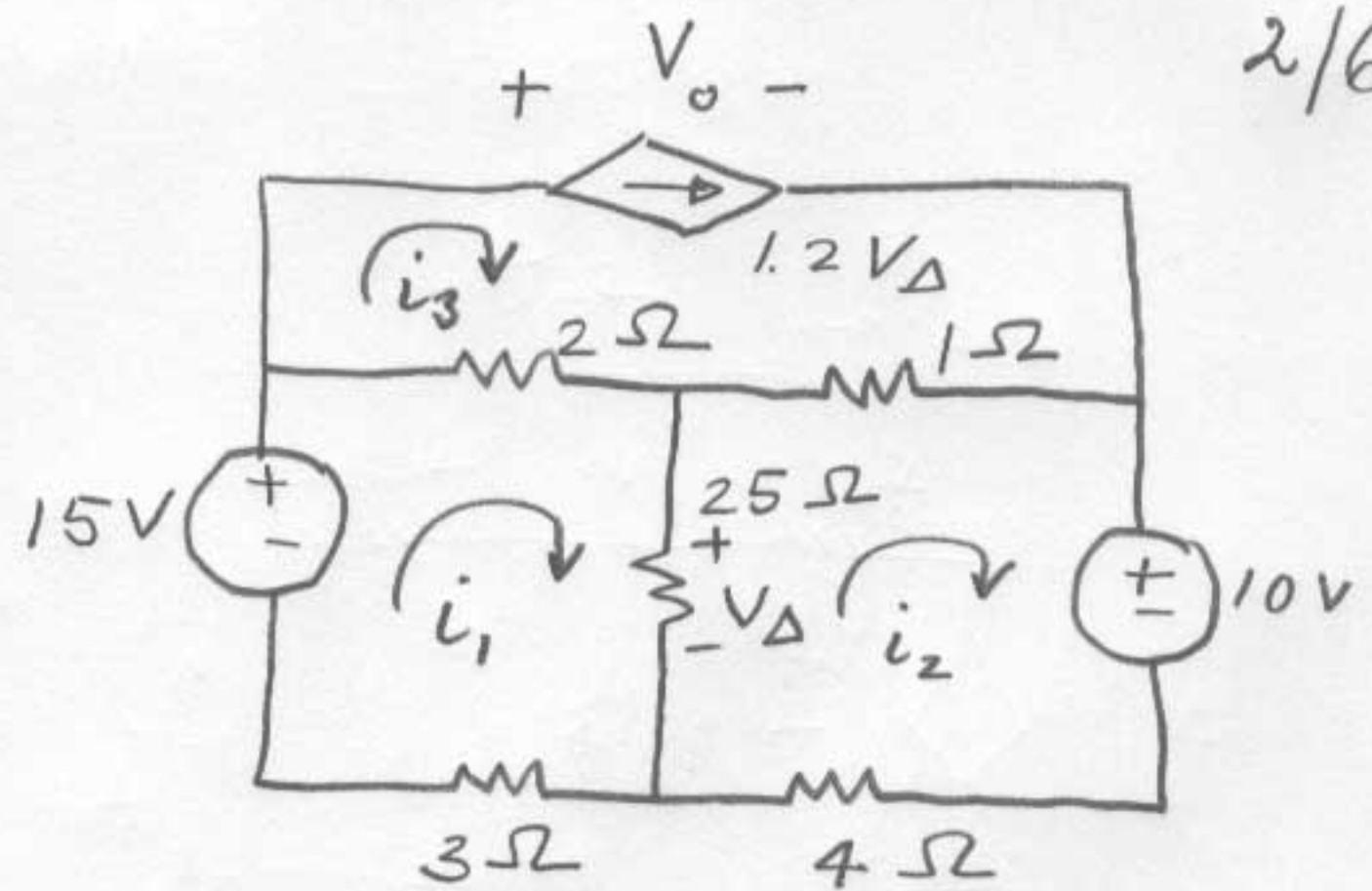
$$\% \text{ delivered to } 2\Omega = \frac{800}{19800} \times 100 = 40.4\%$$




P 4.5 a)

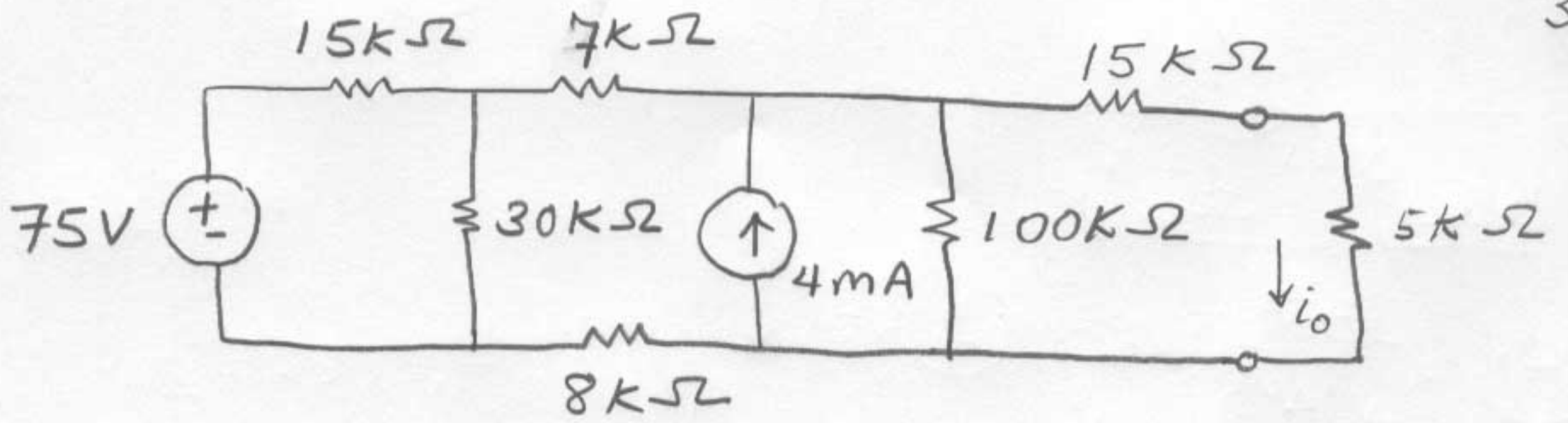

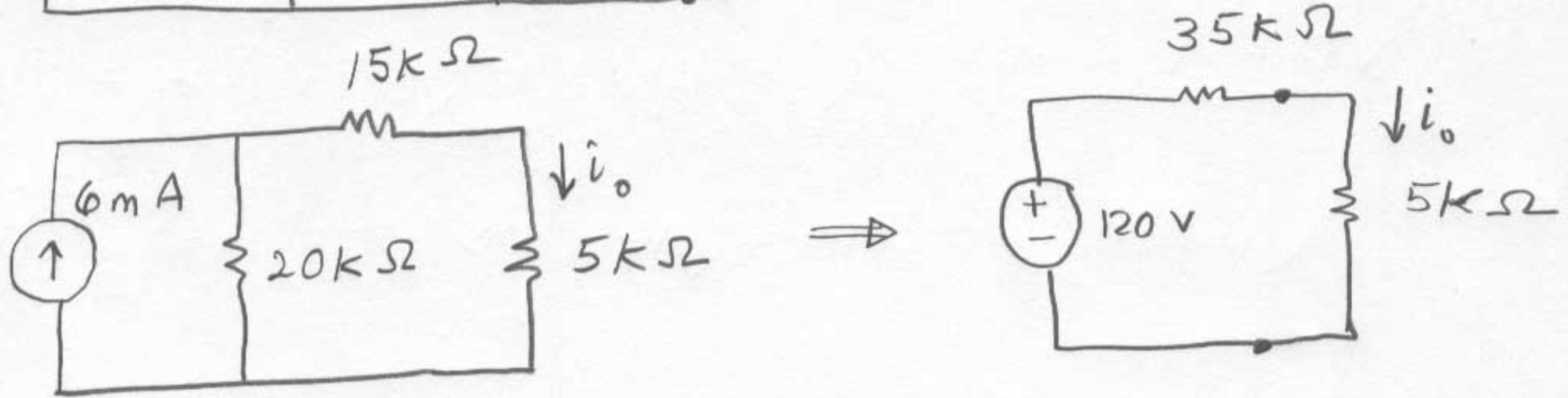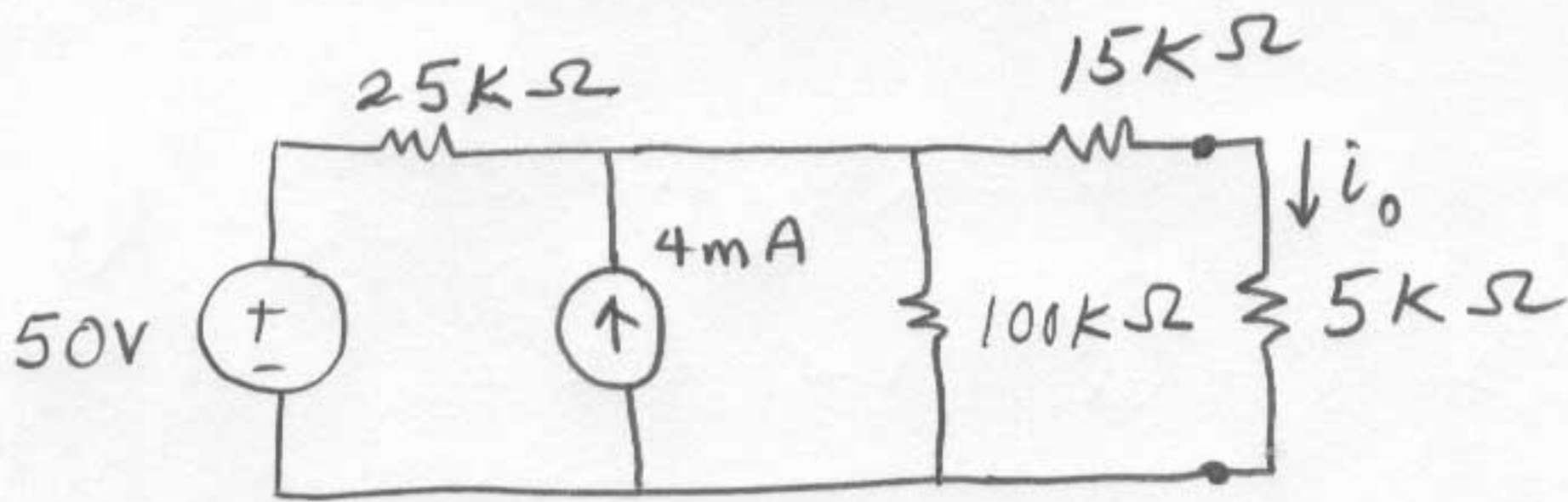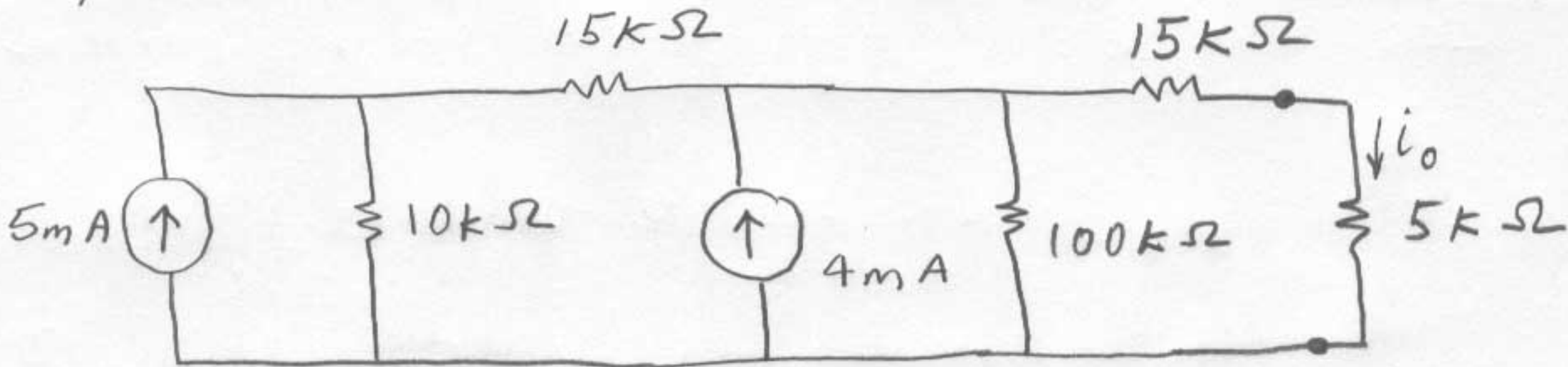$7k\Omega$ in series with $8k\Omega \Rightarrow 7+8 = 15k\Omega$.



$$i_o = \frac{120}{40} = 3mA$$

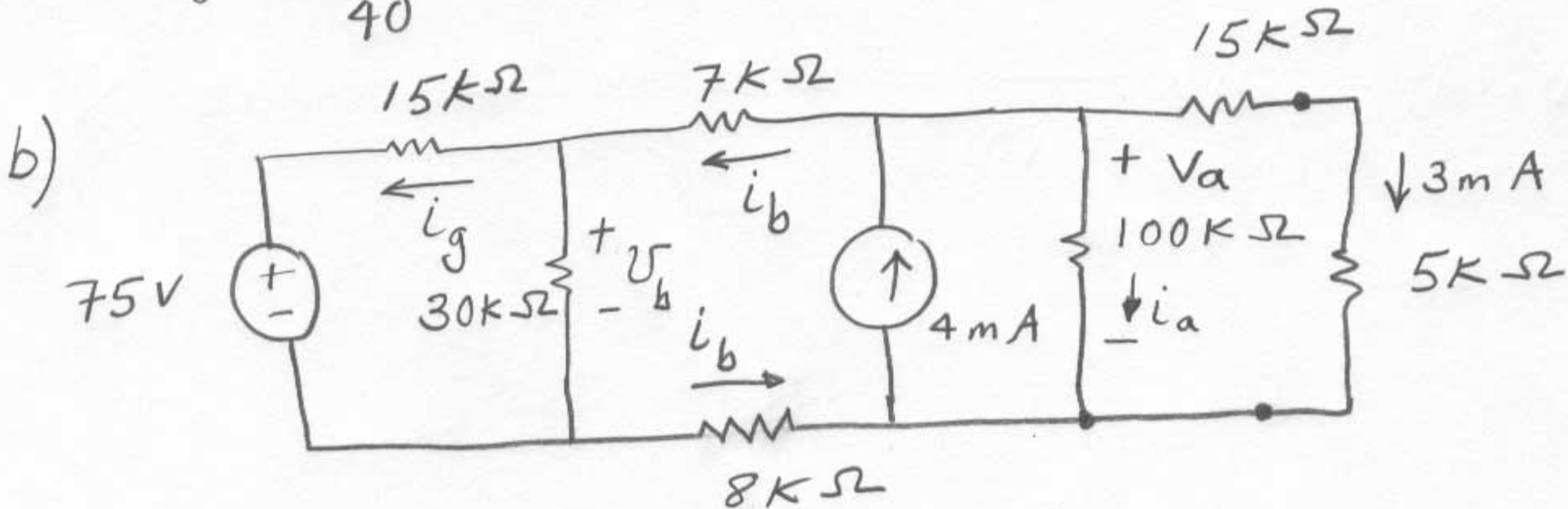

$$V_a = 3(20) = 60V, \quad i_a = \frac{V_a}{100} = 0.6mA$$

$$i_4 = 4 - 3.6 = 0.4mA$$

$$V_b = 60 - 0.4(15) = 54V$$

$$i_g = 0.4 - 54/30 = -1.4 \text{ mA}$$




$$P_{75V} = 75(-1.4) = -105 \text{ mW (dev.)}$$

Check: $P_{4mA} = -60(4) = -240 \text{ mW (dev.)}$

$$\sum P_{\text{dev.}} = 105 + 240 = 345 \text{ mW}$$


$$\begin{aligned} \sum P_{\text{dis}} &= (-1.4)^2(15) + (1.8)^2(30) + (0.4)^2(15) \\ &+ (0.6)^2(100) + (3)^2(20) = 345 \text{ mW} \end{aligned}$$

P 4.53 a)

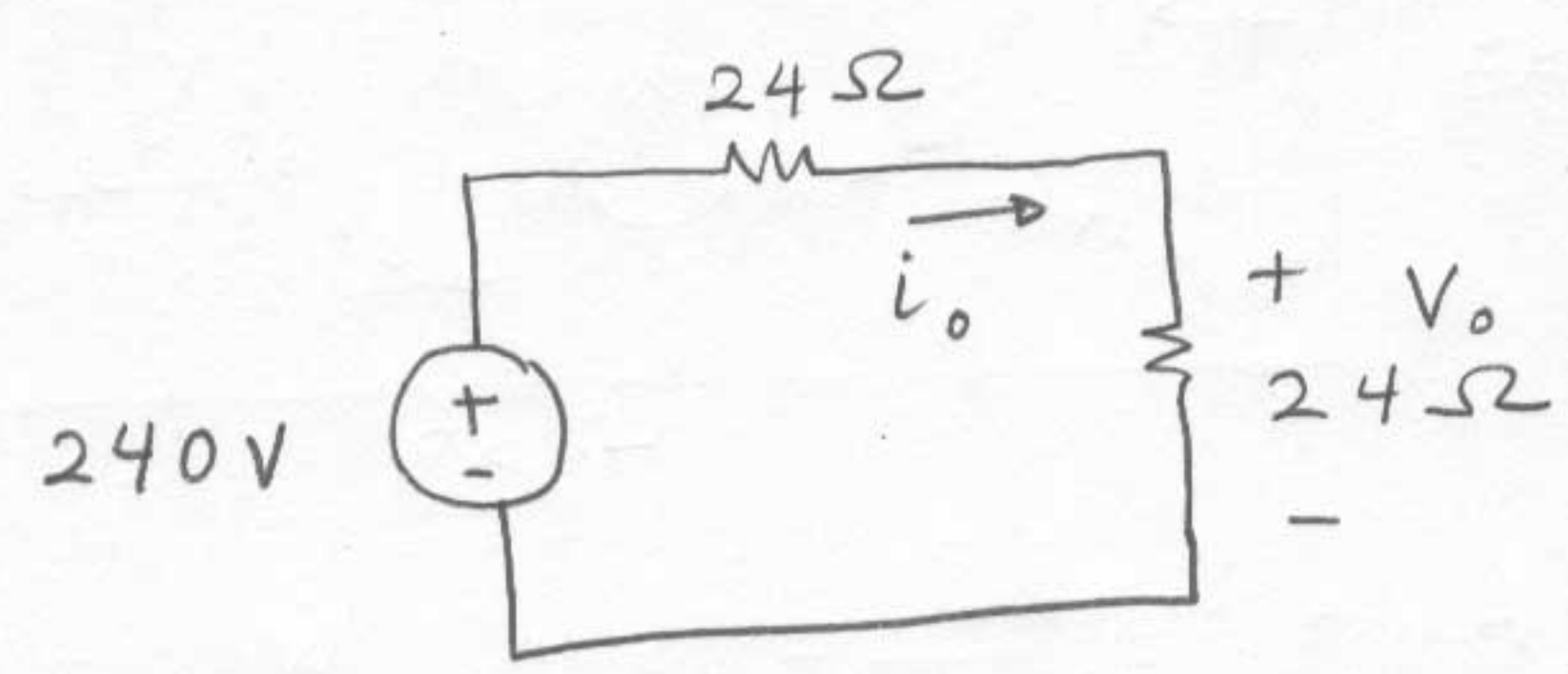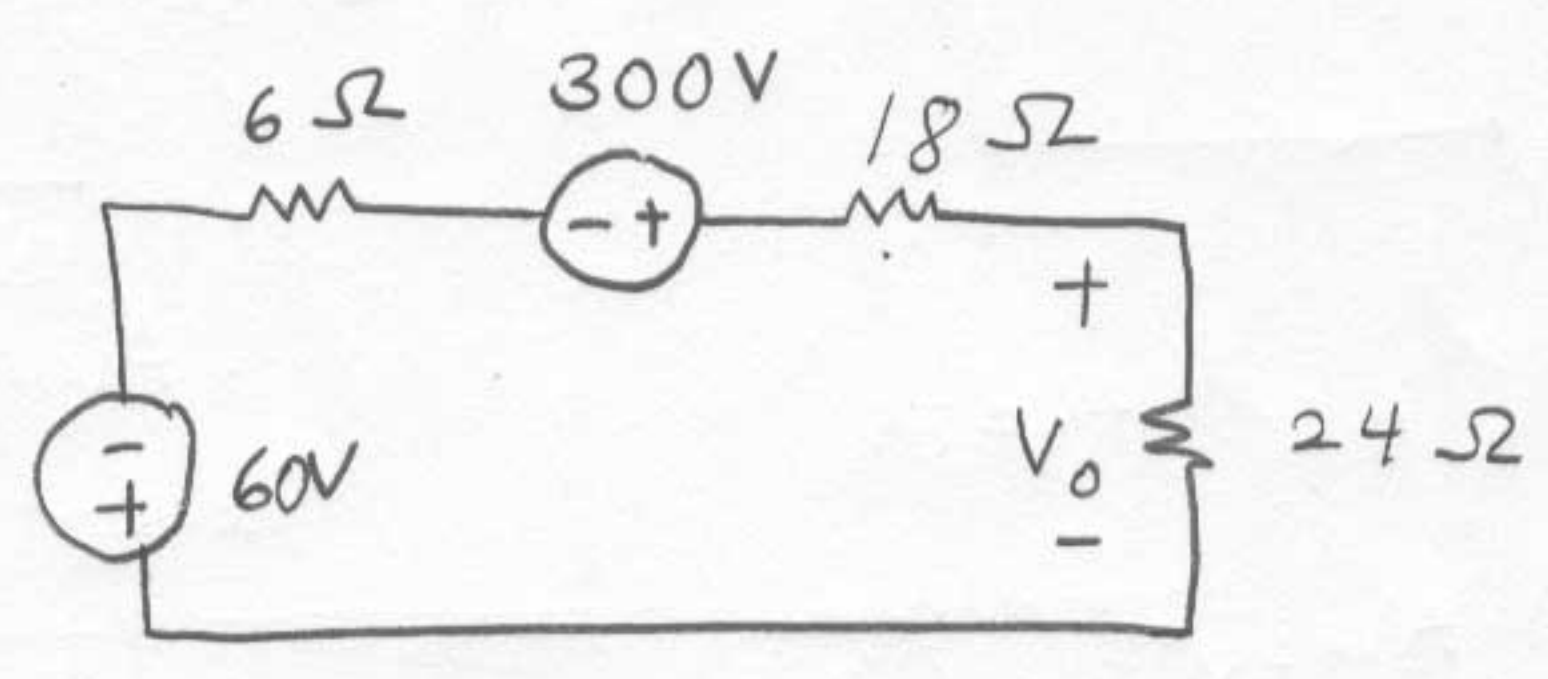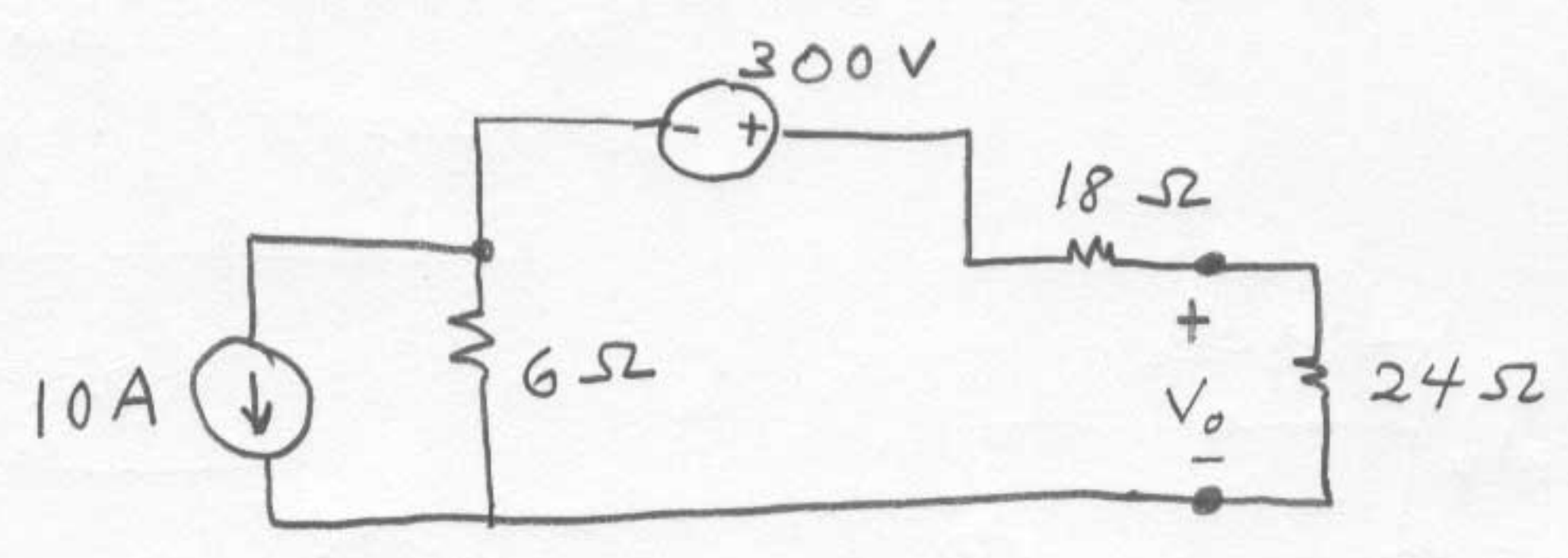

$$\therefore V_0 = \frac{1}{2}(240) = 120 \text{ V}, \quad i_0 = \frac{120}{24} = 5 \text{ A}$$

b)

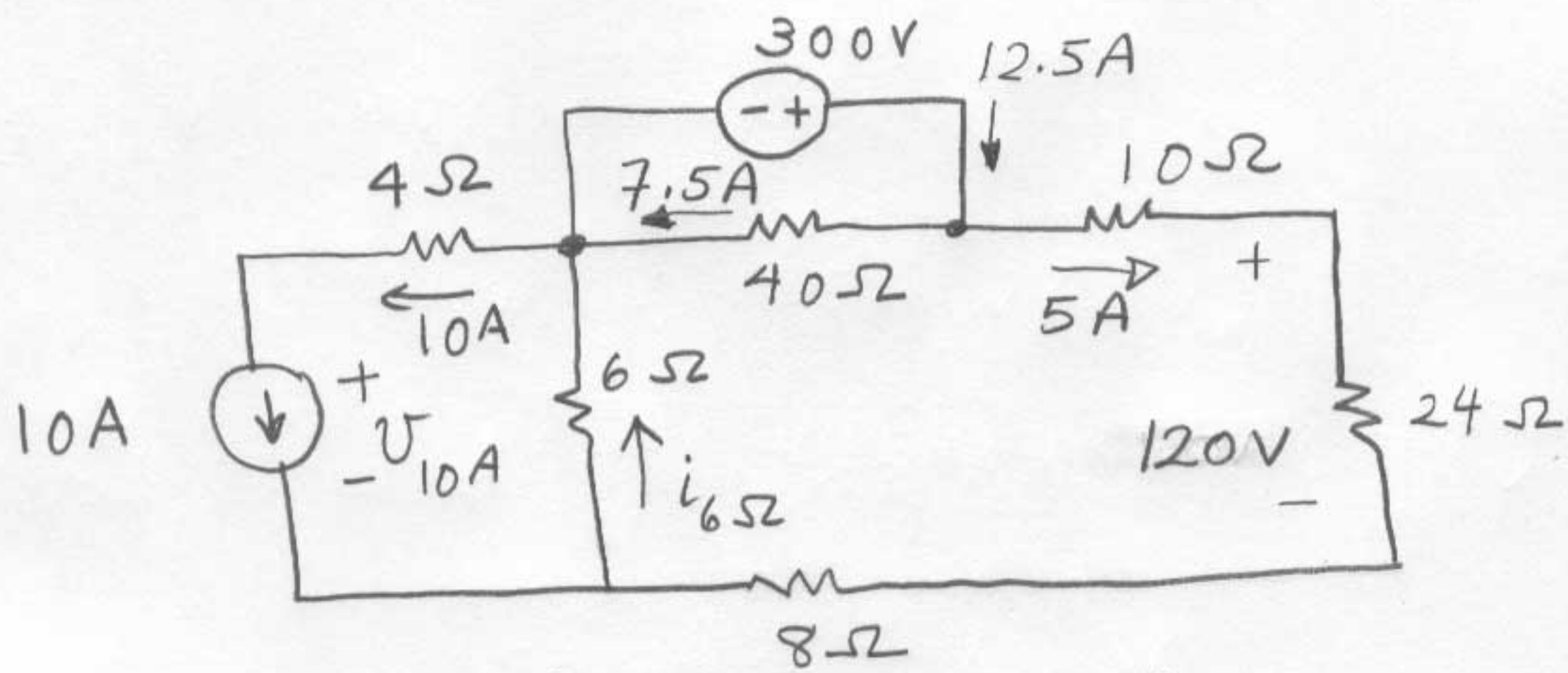

$$P_{300V} = -12.5(300) = -3750W$$

∴ The 300V source develops 3750W.

$$c) -10 + i_{6\Omega} + 7.5 - 12.5 = 0 \quad \therefore i_{6\Omega} = 15A$$

$$V_{10A} + 4(10) + 6(15) = 0 \quad \therefore V_{10A} = -130V$$



$$P_{10A} = 10V_{10A} = -1300W$$



∴ The 10A source develops 1300W.

$$d) \sum P_{del} = 3750 + 1300 = 5050W$$


$$\begin{aligned} \sum P_{dis} &= 100(4) + (7.5)^2(40) + (15)^2(6) + (5)^2(42) \\ &= 5050W \end{aligned}$$

P 4.54 a)

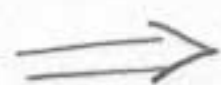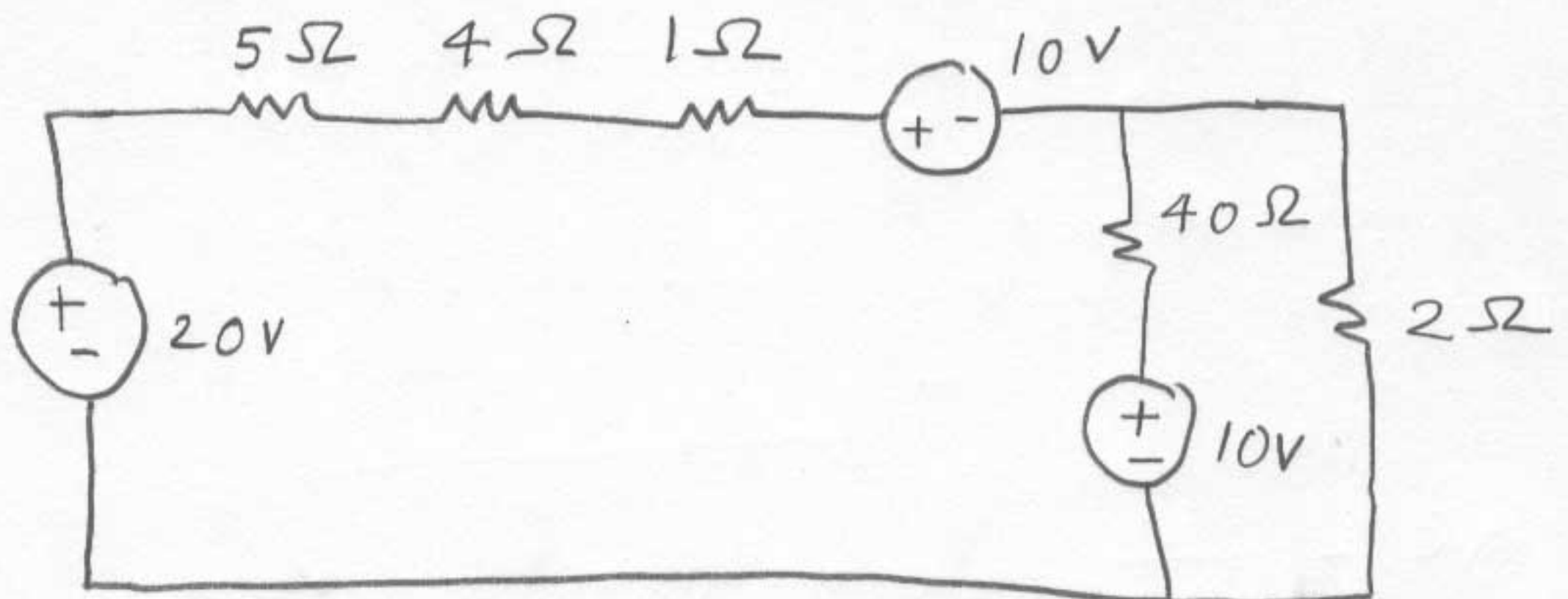

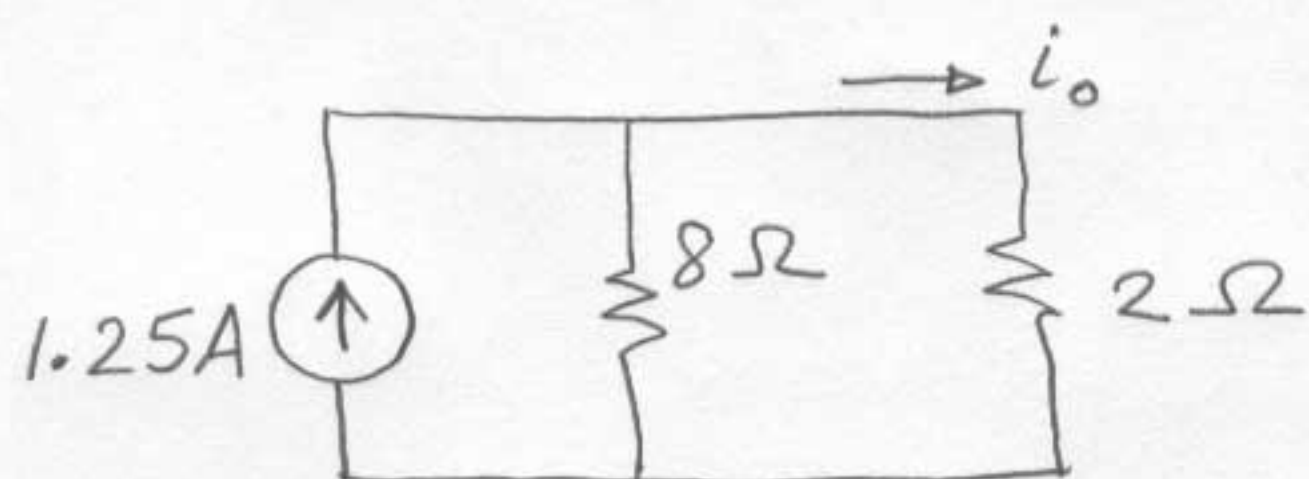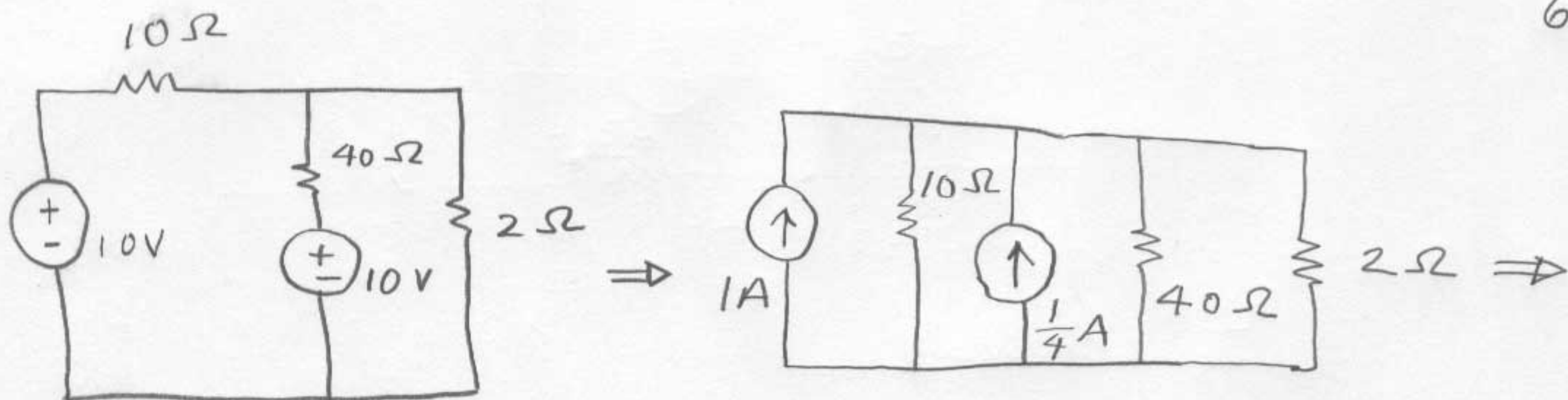
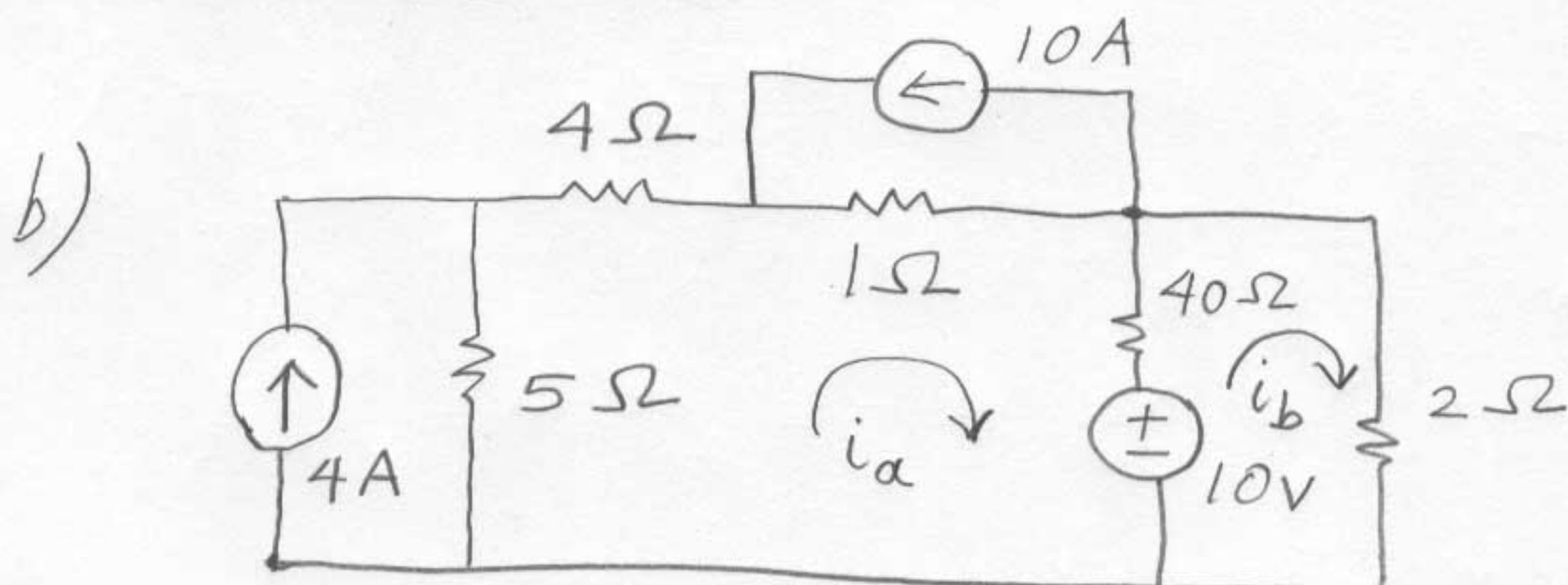
$$\therefore i_o = \frac{1.25(8)}{10} = 1A$$



$$50i_a - 40i_b = 20 - 10 - 10 = 0 \quad (\text{from mesh a})$$

$$-40i_a + 42i_b = 10 \quad (\text{from mesh b})$$

$$\therefore i_b = 1A = i_o$$