
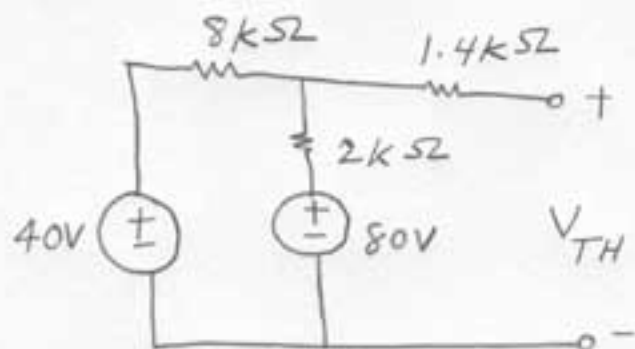


P4.75 a)

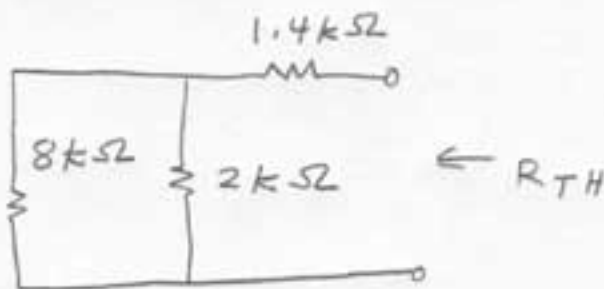


$$\frac{V_{TH} - 40}{80} + \frac{V_{TH} - 80}{2} = 0$$

$$\therefore V_{TH} = 72V$$




$$R_{TH} = 8 \parallel 2 + 1.4 = 3k\Omega$$

b)

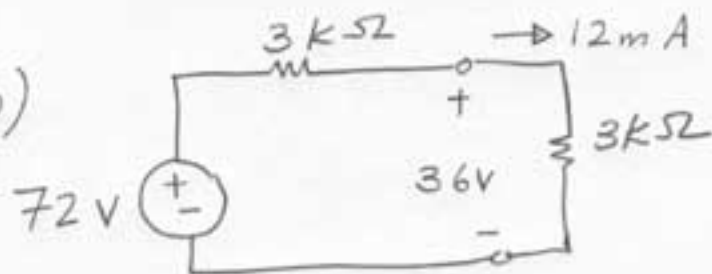

$$P_{max} = \frac{(36)^2}{3k} = 432mW$$
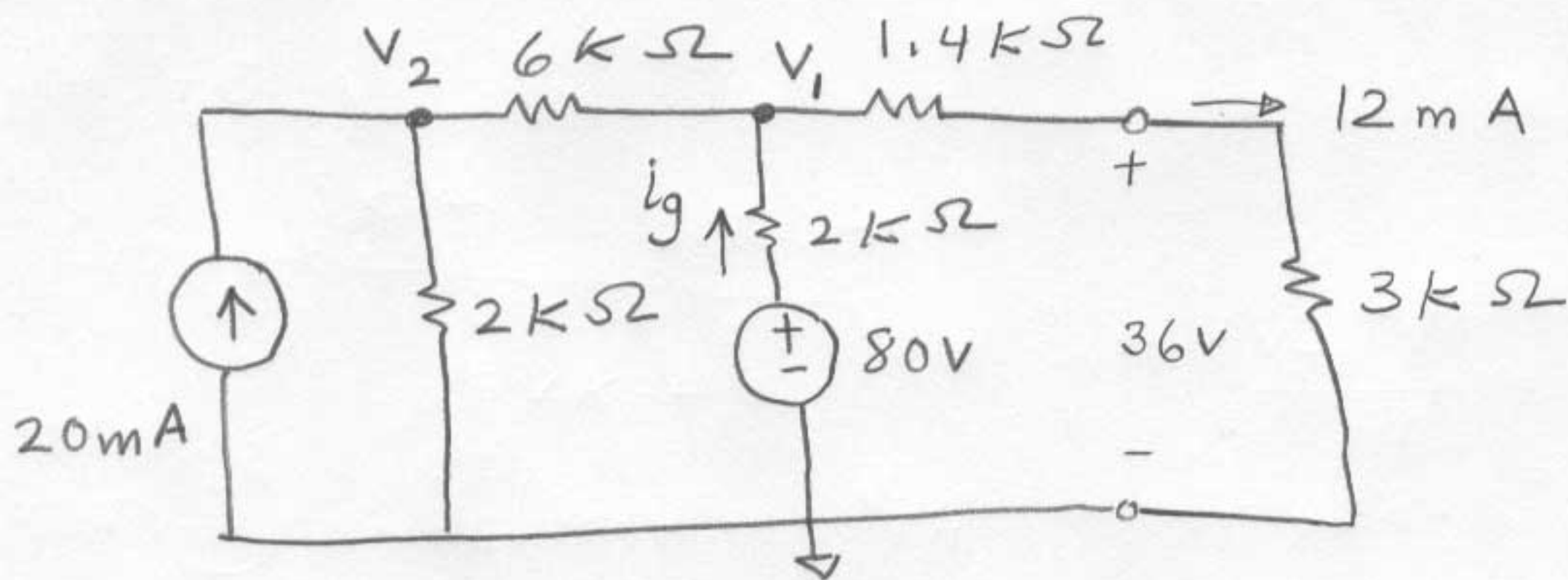
$$\text{or } P_{max} = \frac{(72)^2}{4 \times 3k} = 432mW$$



$$V_1 = (12 \times 10^{-3})(1.4 + 3) \times 10^3 = 12(4.4) = 52.8 \text{ V}$$

$$i_g = \frac{80 - 52.8}{2 \text{ k}} = 13.6 \text{ mA}$$

$$P_{80 \text{ V}} = -80(13.6 \text{ mA}) = -1088 \text{ mW} \text{ (actually delivered).}$$


$$-20 + \frac{v_2}{2} + \frac{v_2 - 52.8}{6} = 0$$

$$\therefore v_2 = 43.2 \text{ V}$$

$$P_{20 \text{ mA}} = (-20 \text{ mA})v_2 = -(20 \text{ mA})(43.2) = -864 \text{ mW} \text{ (actually del.)}$$

$$\sum P_{\text{dev.}} = 1088 + 864 = 1952 \text{ mW}$$
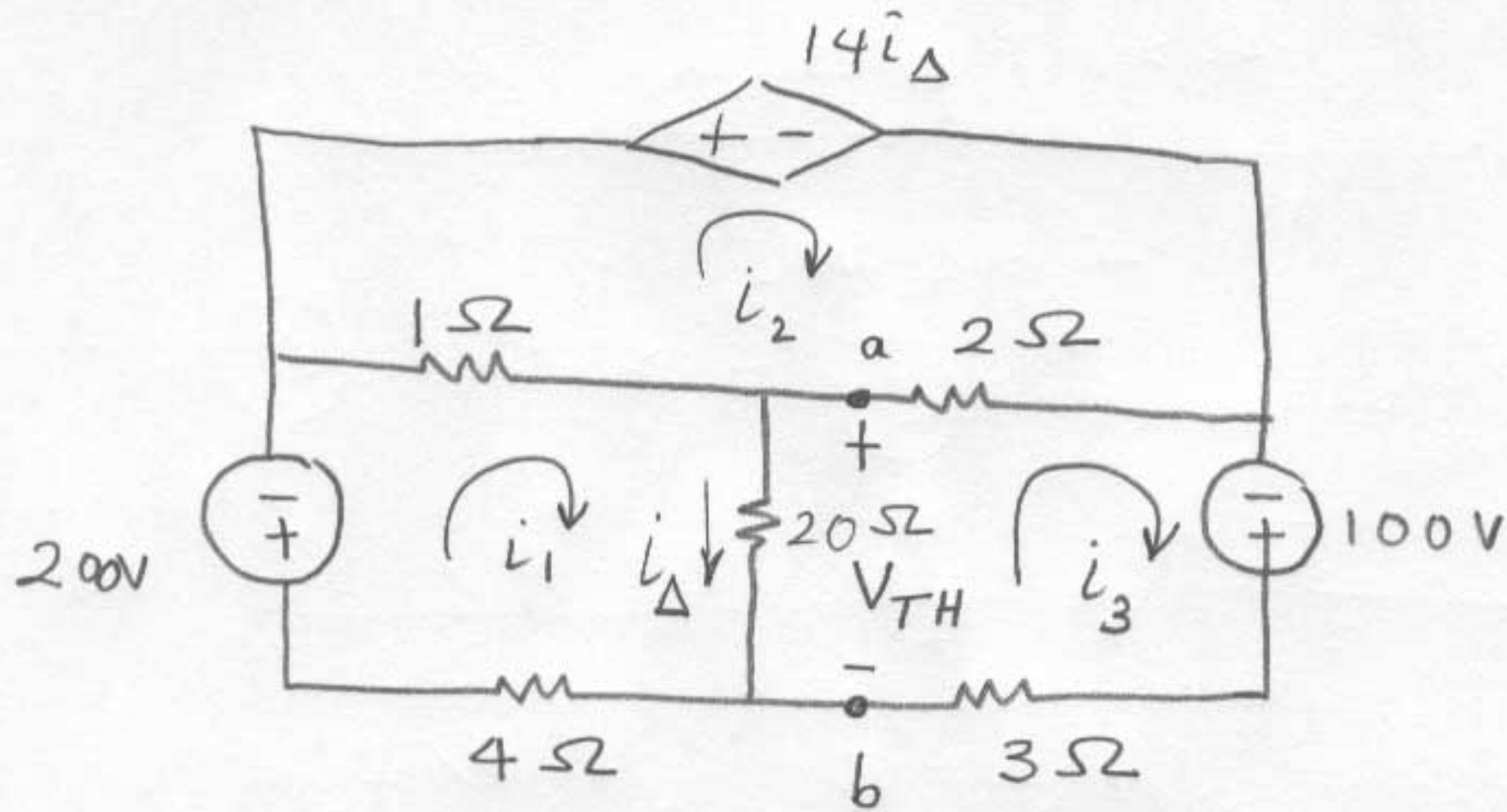
$$\% \text{ delivered to } R_o = \frac{432}{1952} \times 100 = 22.13 \%$$




$$\text{Mesh 1} \Rightarrow -200 = 25i_1 - i_2 - 20i_3$$

$$\text{Mesh 2} \Rightarrow 0 = 13i_1 + 3i_2 - 16i_3$$

$$\text{Mesh 3} \Rightarrow 100 = -20i_1 - 2i_2 + 25i_3$$

$$\text{Solving } i_1 = -2.5, i_3 = 5 \text{ A}$$
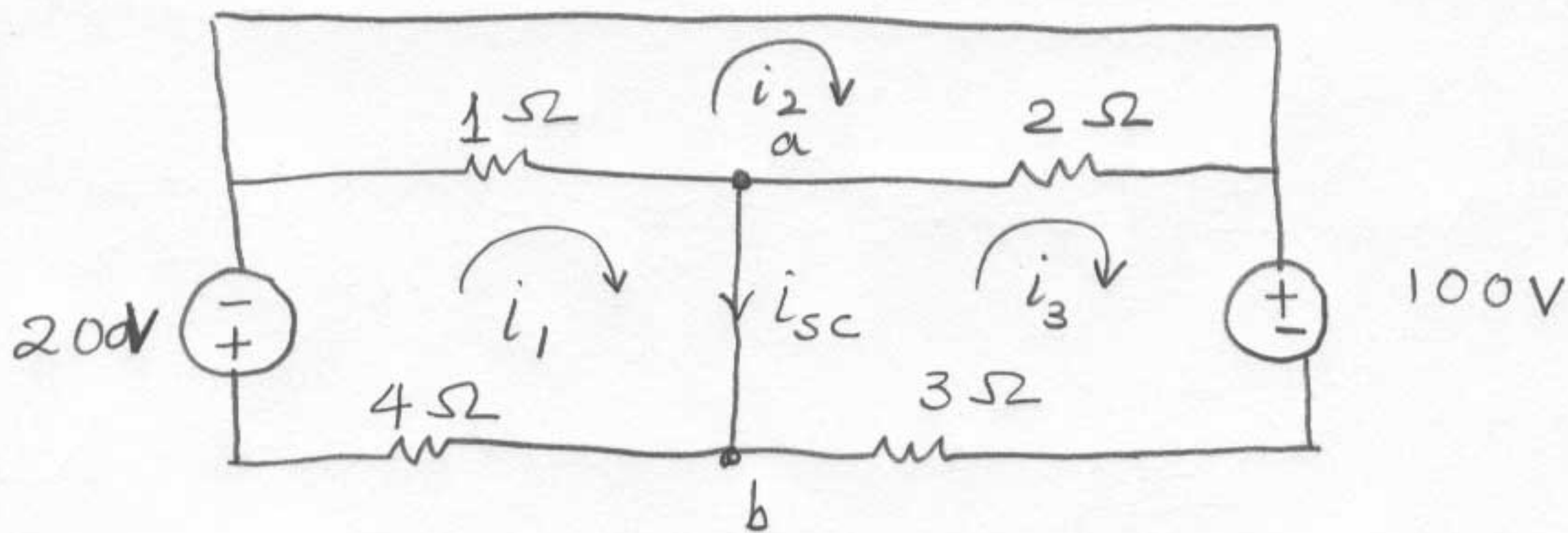
$$V_{TH} = 20(i_1 - i_3) = 20(-7.5) = -150 \text{ V}$$



Because the short circuit is in //  $20\Omega$ ,

$$\therefore i_{\Delta} = 0, 14i_{\Delta} = 0$$

$$\text{Mesh 1} \Rightarrow -200 = 5i_1 - i_2 + 0i_3$$

$$\text{Mesh 2} \Rightarrow 0 = -i_1 + 3i_2 - 2i_3$$

$$\text{Mesh 3} \Rightarrow 100 = 0i_1 - 2i_2 + 5i_3$$

Solving  $i_1 = -40 \text{ A}$  &  $i_3 = 20 \text{ A}$


$$\therefore i_{sc} = i_1 - i_3 = -60 \text{ A}$$

$$R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{-150}{-60} = 2.5 \Omega$$

For maximum power transfer  $R_o = R_{TH} = 2.5 \Omega$

$$b) P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(-150)^2}{4(2.5)} = 2250 \text{ W}$$

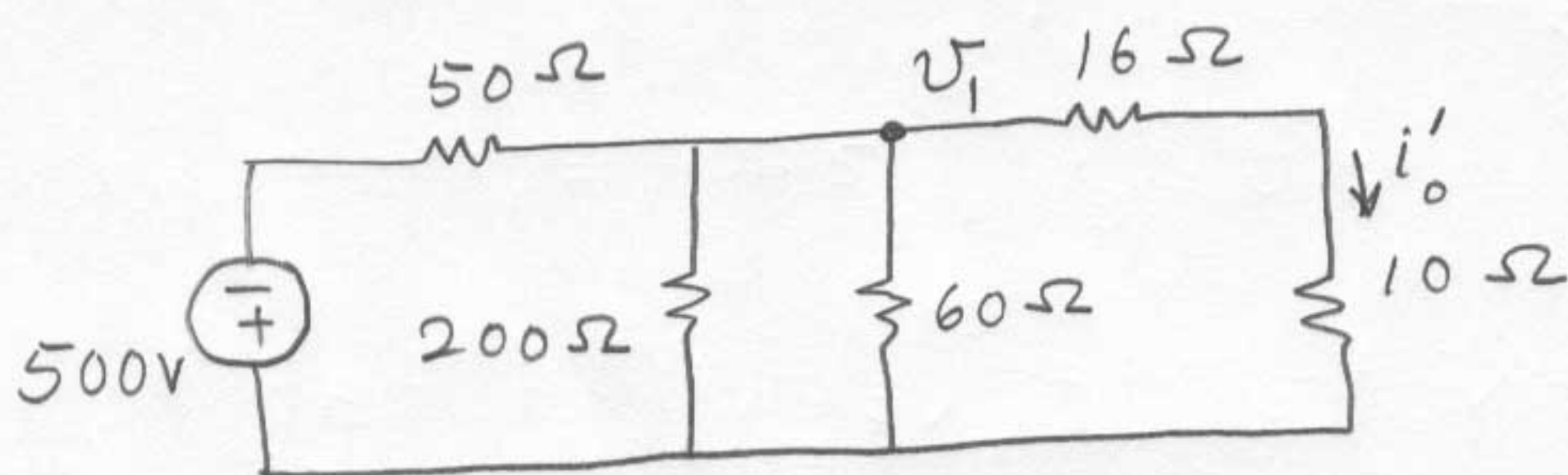P-4.90 a)  $i_o' = i_o \mid_{500 \text{ V}}$



$$\frac{v_1 + 500}{50} + \frac{v_1}{200} + \frac{v_1}{60} + \frac{v_1}{26} = 0$$

$$\therefore v_1 = -124.8 \text{ V}$$


$$i_o' = \frac{v_1}{26} = \frac{-124.8}{26} = -4.8 \text{ A}$$


$$i_o'' = i_o \mid_{20 \text{ A}}$$

$$\frac{v_1}{50} + \frac{v_1}{200} + \frac{v_1}{60} + \frac{v_1}{26} = 20$$

$$\therefore v_1 = 249.60 \text{ V}$$
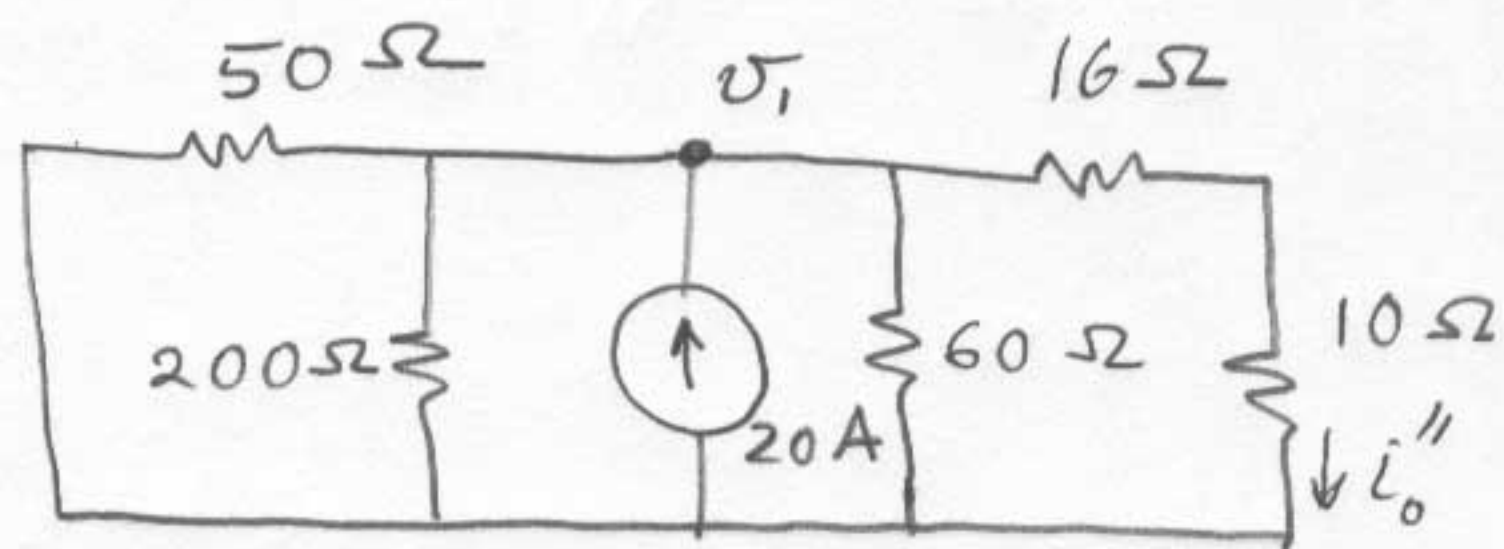
$$i_o'' = \frac{249.60}{26} = 9.6 \text{ A}$$




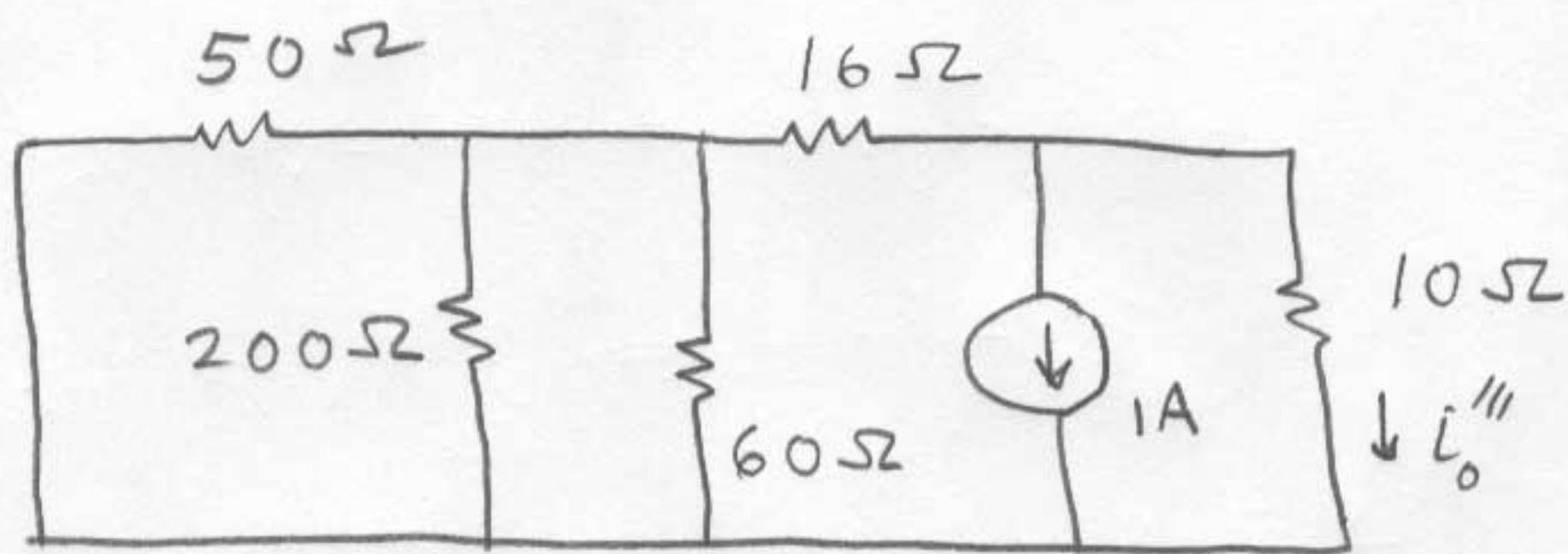

$$i_o''' = i_o |_{1A}$$

$$50 // 200 // 60 = 24 \Omega$$

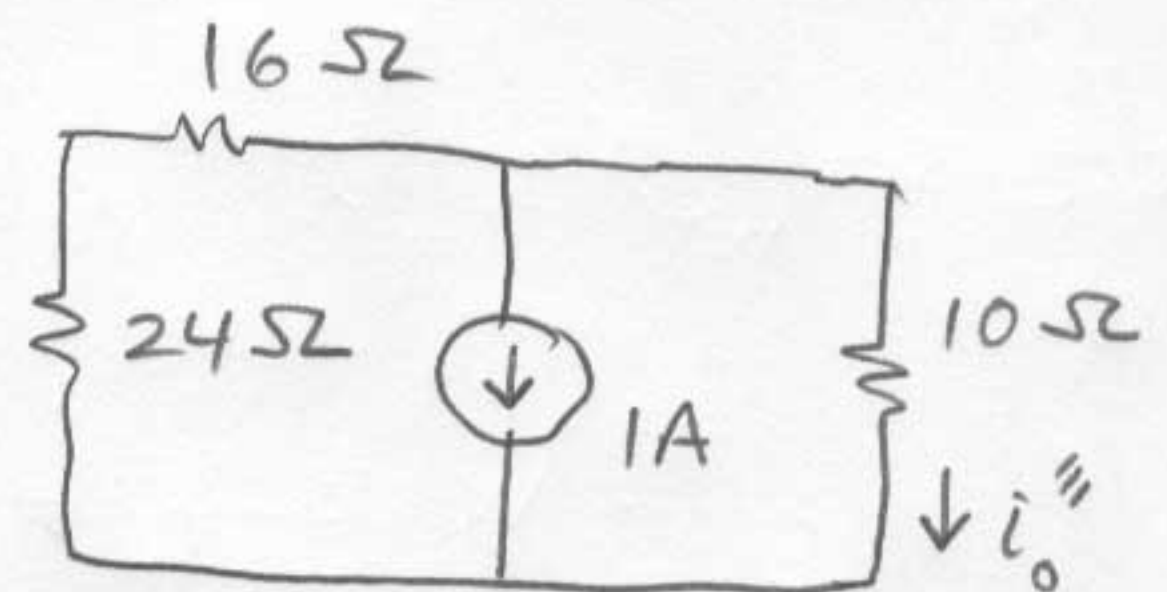
$$i_o''' = - \left( \frac{40}{50} \right) = -0.80 \text{ A}$$



$$i_o = i_o' + i_o'' + i_o''' = -4.8 + 9.6 - 0.8 = 4 \text{ A}$$

$$b) P = 10 i_o^2 = 160 \text{ W}$$

P-4.92 a)

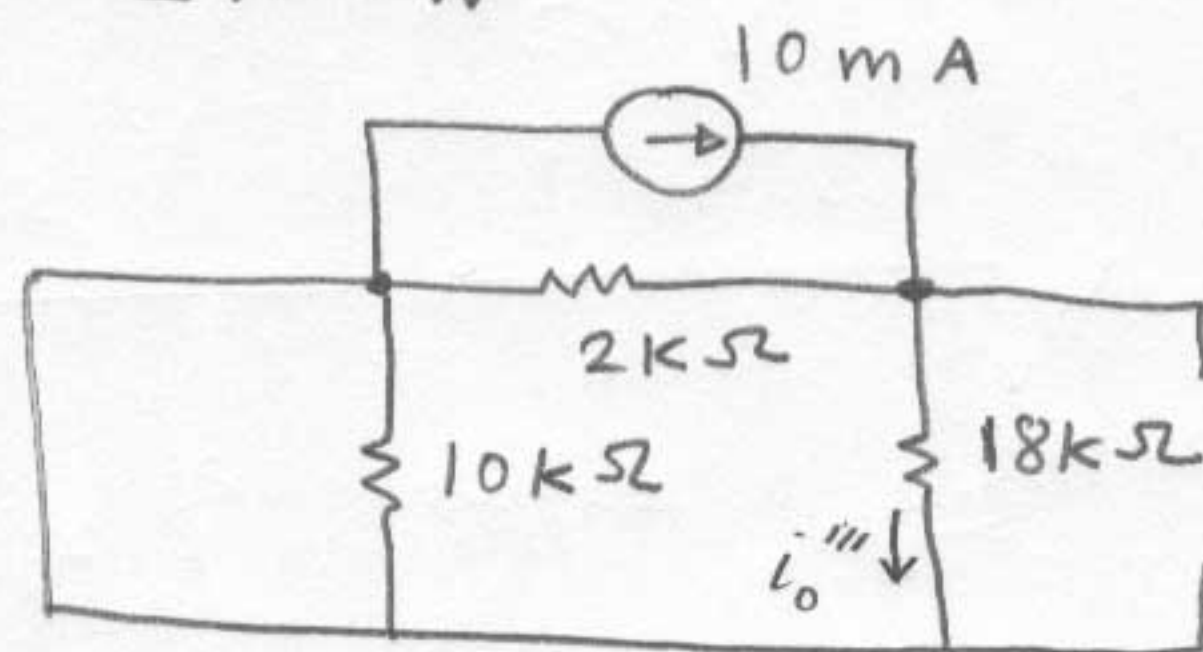

By hypothesis  $i_o' + i_o'' = 1.5 \text{ mA}$

$$i_o''' = 10 \left( \frac{2}{20} \right) = 1 \text{ mA}, \therefore i_o = 1.5 + 1 = 2.5 \text{ mA}$$

b) With all three sources in the circuit, write a single node voltage equation:

$$\frac{v_b}{18} + \frac{v_b - 20}{2} - 5 - 10 = 0$$

$$\therefore v_b = 45 \text{ V}$$

$$\therefore i_o = \frac{v_b}{18} = \frac{45}{18} = 2.5 \text{ mA}$$