


ID# KEY

Quiz

Name _____

EE 201-06 (032)

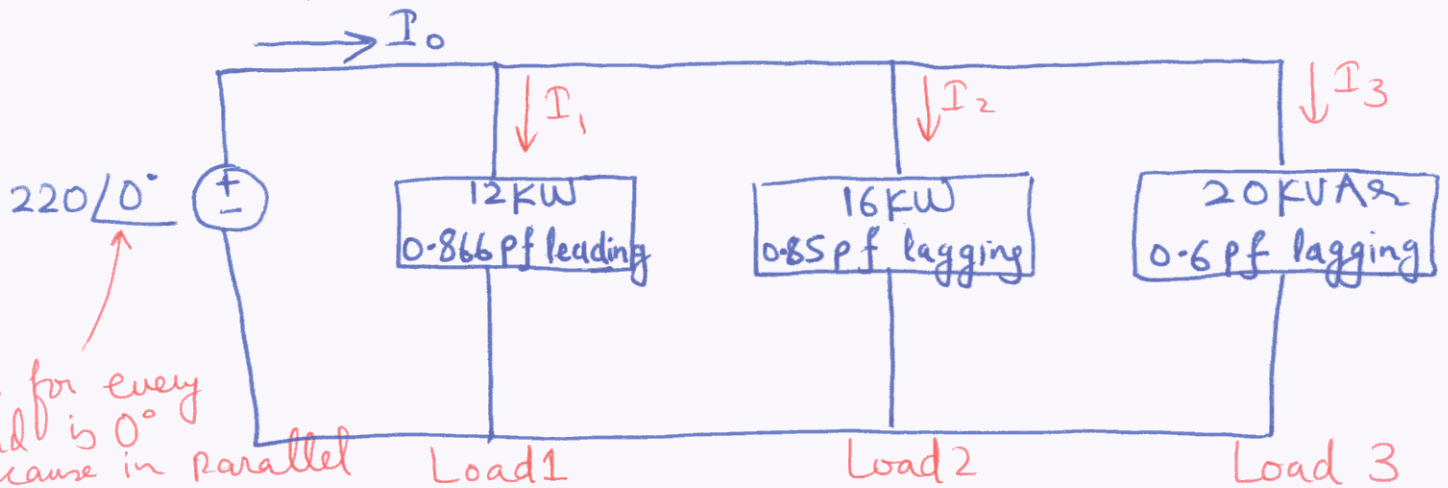- (a) Find I_0
- (b) Power factor of source (indicate if leading or lagging).
- (c) What should be connected in parallel to make the source power factor to unity. (Don't find the value, just name the component and write the reason for your selection).



θ_v for every load is 0° because in parallel

For Load 1

$$P = VI \cos \theta \Rightarrow I_1 = \frac{12,000}{220 \times 0.866}$$

$$\Rightarrow |I_1| = 63 \text{ A}$$

$$\text{Also } \theta_v - \theta_I = -\cos^{-1}(0.866)$$

$$\Rightarrow \theta_I = 30^\circ$$

$$\therefore I_1 = |I_1| \angle 30^\circ = 63 \angle 30^\circ$$

For Load 2

$$P = VI \cos \theta \Rightarrow I_2 = \frac{16,000}{220 \times 0.85}$$

$$\Rightarrow |I_2| = 85.56 \text{ A}$$

$$\text{Also } \theta_v - \theta_I = +\cos^{-1}(0.85) \Rightarrow \theta_I = -31.7^\circ$$

$$I_2 = |I_2| \angle -31.7^\circ = 85.56 \angle -31.7^\circ$$

For Load 3

$$Q = VI \sin \theta \Rightarrow I_3 = \frac{20,000}{220 \times \sin(\cos^{-1} 0.6)}$$

$$|I_3| = 113.63 \text{ A}$$

$$\text{Also } \theta_v - \theta_I = +\cos^{-1}(0.6) \Rightarrow \theta_I = -53.13^\circ$$

$$I_3 = |I_3| \angle -53.13^\circ = 113.63 \angle -53.13^\circ$$

$$I_0 = I_1 + I_2 + I_3$$

$$= 63 \angle 30^\circ + 85.56 \angle -31.7^\circ + 113.63 \angle -53.13^\circ$$

$$= 54.56 + j31.5 + 72.7 - j45 + 68.12 - j91$$

$$= 195.38 - j104.5$$

$$= 221.57 \angle -28.14^\circ$$

$$(b) \text{ p.f.} = \cos(\theta_v - \theta_I)$$

$$= \cos(0 - (-28.14))$$

$$\text{p.f.} = 0.882 \text{ lagging}$$

because θ_I is lagging θ_v

$$\theta_v - \theta_I = +ve$$

(c) Therefore we will connect a capacitor in parallel.