

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

FIRST SEMESTER 2012-2013 (S121)



Course Title:	Electronics II
Course Number:	EE 303

Exam Type:	Exam II
Date:	Wednesday November 28, 2012
Time:	6:00PM-7:30PM

Student Name: _____

Student ID: _____

Section # _____

GRADING		
Question 1	10	
Question 2	15	
Question 3	15	
Question 4	20	
Total:	60	


Show all your work and results. Do not give more than one answer otherwise the wrong one will be considered.

Question No.1: (10 points)

It is required to design a non-inverting amplifier with a closed loop gain of 100 V/V, given that the op-amp used has a dc gain of 10^5 V/V and a unity-gain frequency of 10^6 Hz, draw the closed-loop gain frequency response.

Label all the critical points on x and y axis

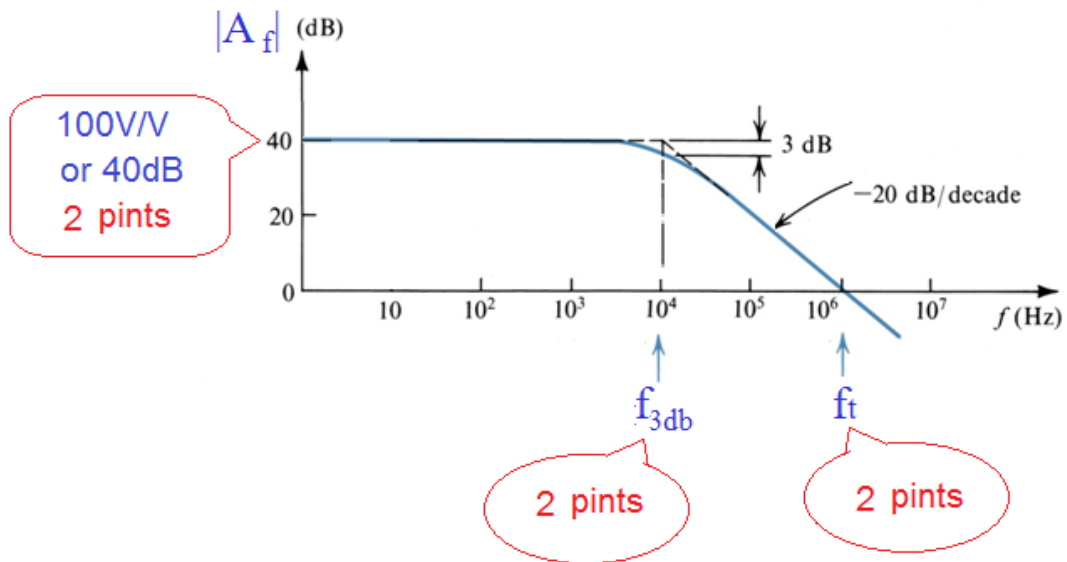
$BW_{CLG} = f_t / CLG = 10^4 \text{ Hz} \rightarrow (4 \text{ Points})$



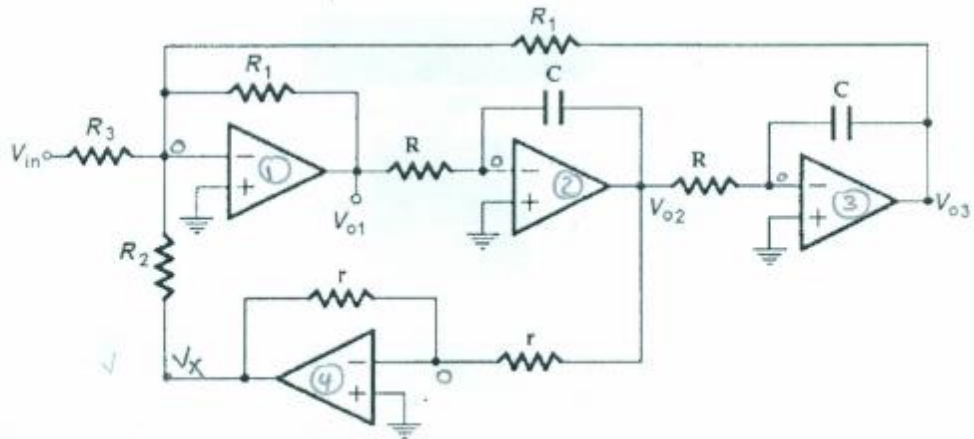Question No.2: (15 points)

For the active filter circuit shown below:

- Derive the transfer function for output (V_{o1}/V_{in}).
- Identify the order and the type of the filter.



a) KCL at (-) of opamp 1

$$\frac{V_{in}}{R_3} + \frac{V_{o3}}{R_1} + \frac{V_x}{R_2} + \frac{V_{o1}}{R_1} = 0 \quad \textcircled{1} \quad \underline{3 \text{ Points}}$$

$$V_x = -\frac{r}{r} V_{o2} = -V_{o2} \quad \& \quad V_{o2} = -\frac{1}{sCR} V_{o1}$$

$$\textcircled{2} \quad V_x = -\frac{1}{sCR} V_{o1} \quad \underline{3 \text{ Points}} \quad ; \quad V_{o3} = -\frac{1}{sCR} V_{o2} = \frac{1}{s^2 C^2 R^2} V_{o1} \quad \textcircled{3} \quad \underline{3 \text{ Points}}$$

From ①, ②, ③ $\Rightarrow \frac{V_{in}}{R_3} + \frac{1}{s^2 C^2 R^2} \frac{V_{o1}}{R_1} + \frac{V_{o1}}{R_2} \frac{1}{sCR} + \frac{V_{o1}}{R_1} = 0$

$$V_{o1} \left[\frac{1}{R_1 s^2 C^2 R^2} + \frac{1}{R_2 sCR} + \frac{1}{R_1} \right] = \frac{V_{in}}{R_3}$$

$$V_{o1} \left[\frac{1}{C^2 R^2} + \frac{R_1}{R_2 C R} s + s^2 \right] = \frac{s^2 R_1}{R_3} V_{in}$$

$$\frac{V_{o1}}{V_{in}} = \frac{\frac{R_1}{R_3} s^2}{s^2 + \frac{R_1}{C R_2 R} s + \frac{1}{C^2 R^2}} \quad \textcircled{*} \textcircled{*} \quad \underline{3 \text{ Points}}$$

b) 2nd order high pass filter 3 points

Question No.3: (15 points)

Consider the following filter transfer function:

$$T(s) = \frac{\left(\frac{1}{C_2 R_2}\right)s}{s^2 + \left(\frac{1}{C_1 R_2}\right)s + \frac{1}{C_1 C_2 R_1 R_2}}$$

Design the filter such that it has a center frequency of 1 krad/s, a bandwidth of 200 rad/s, and a center-frequency gain of 2 V/V. Assume $C_1 = 0.5 \mu\text{F}$.

Center Freq. = $\omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} = 1 \text{ k rad/s}$ 3 points

BW = $\frac{1}{C_1 R_2} = 200 \text{ rad/s}$ (2) 3 points

Center Freq. gain = $\frac{C_1}{C_2} = 2 \text{ V/V}$ (3) 3 points

C_1 is given $0.5 \mu\text{F}$ From (3) $C_2 = 0.25 \mu\text{F}$ 2 points

From (2) $\frac{1}{0.5 \mu \times R_2} = 200 \Rightarrow R_2 = 10 \text{ k}\Omega$ 2 points

From (1) $\omega_0^2 = \frac{1}{0.5 \mu \times 0.25 \mu \times R_1 \times 10 \text{ k}}$ 2 points

$R_1 = 800 \Omega$

Question No. 4: (20 points)

A series-shunt feedback amplifier employ a basic amplifier with input and output resistance each of $1k\Omega$ and gain $A = 2000$ V/V. The feedback factor $\beta = 0.1$ V/V. Find:

- the closed loop gain (A_f).
- the input resistance for the closed loop amplifier.
- the output resistance for the closed loop amplifier.
- If a manufacturing error results in a reduction of A to 1800 V/V, What is the new value for the closed loop gain (A_f)? Comment on your result.

a) $A_f = \frac{A}{1+\beta A}$

$$A_f = \frac{2000}{1+(0.1)(2000)} = 9.950 \frac{V}{V} \rightarrow (4 \text{ Points})$$

b) $R_{if} = R_i(1 + \beta A)$

$$R_{if} = (1)(201) = 201k\Omega \rightarrow (4 \text{ Points})$$

c) $R_{of} = \frac{R_o}{1+\beta A}$

$$R_{of} = \frac{1}{1+200} = 5\Omega \rightarrow (4 \text{ Points})$$

d) $A_{f(new)} = \frac{A_{new}}{1+\beta A_{new}} = \frac{1800}{1+(0.1)(1800)} = 9.945 \frac{V}{V} \rightarrow (4 \text{ Points})$

The % change in A_f is less than the % change in A by the amount of the feedback.
 $\rightarrow (4 \text{ Points})$