

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**

**ELECTRICAL ENGINEERING DEPARTMENT**

**FIRST SEMESTER 2012-2013 (S121)**



<b>Course Title:</b>	<b>Electronics II</b>
<b>Course Number:</b>	<b>EE 303</b>

<b>Exam Type:</b>	<b>Major Exam I</b>
<b>Date:</b>	<b>Saturday Oct. 6<sup>th</sup>, 2012</b>
<b>Time:</b>	<b>6:00PM-7:30PM</b>

**Student Name:** \_\_\_\_\_

**Student ID:** \_\_\_\_\_


**Section #** \_\_\_\_\_

GRADING		
<b>Question 1</b>	<b>25</b>	
<b>Question 2</b>	<b>15</b>	
<b>Question 3</b>	<b>20</b>	
<b>Total:</b>	<b>60</b>	

**Show all your work and results. Do not give more than one answer otherwise the wrong one will be considered.**

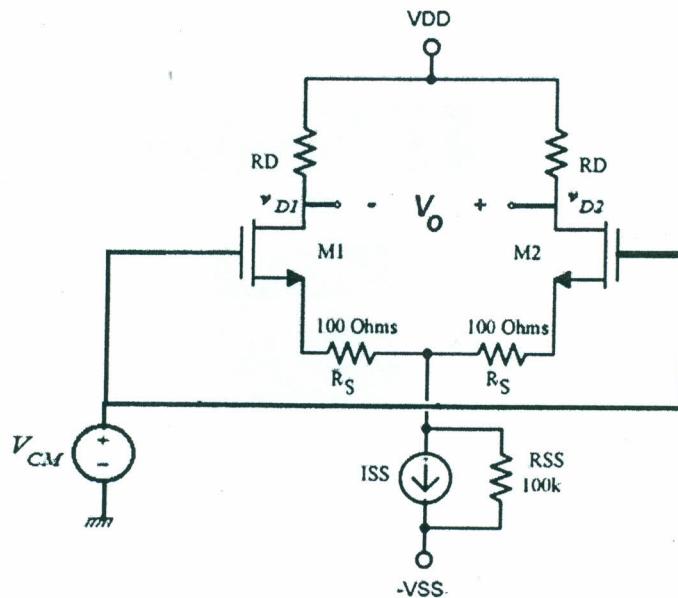**Question No.1 [25 points]**

For the MOS pair with a common-mode voltage  $V_{CM}$  applied as shown below. Assume  $V_{DD} = 5 \text{ V}$ ,  $V_{SS} = 5 \text{ V}$ ,  $k'(W/L) = 5 \text{ mA/V}^2$ ,  $V_t = 0.5 \text{ V}$ ,  $I_{SS} = 1.5 \text{ mA}$ , and  $R_D = 2 \text{ k}\Omega$ , and neglect channel-length modulation.




- a- Find the highest permitted value of  $V_{CM}$ . [4 points]
- b- Develop the **differential** and **common** mode half circuits for the given Differential amplifier. [10 points]
- c- Calculate Common-Mode Rejection Ratio (CMRR). [6 points]
- d- What is the function of  $R_S$  (i.e. the main difference compared with the case of  $R_S = 0$ ). [5 points]

a)  $V_{GD} < V_t \Rightarrow V_G < V_t + V_D \Rightarrow V_{CM_{max}} < V_t + V_{DD} - I_{D1}R_D$  [5 points]


$$I_{D1} = \frac{1}{2} I_{SS} = 0.75 \text{ mA} \quad \textcircled{4} \quad \Rightarrow V_{CM_{max}} < 0.5 + 5 - 0.75 \times 2$$

$$V_{CM_{max}} = \underline{\underline{4 \text{ V}}}$$

b) Differential half

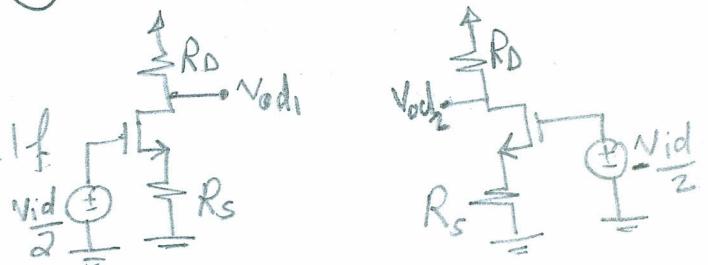

Common mode half

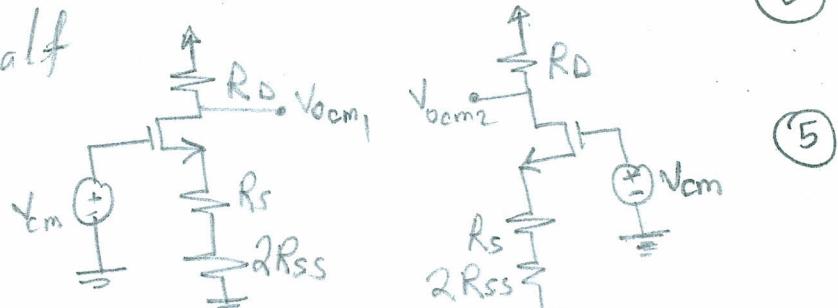

c)  $\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right| ; A_d = \frac{V_o}{V_{id}} = \frac{2R_D}{2 + 2R_c} = \frac{R_D}{1 + R_c} ; A_{cm} = 0$  [6]



d)  $R_S$  will increase input Differential Range. [5]

**Question No. 2 [15 points]**

In the circuit shown,  $g_m = 1 \text{ ms}$ ,  $C_{gs} = 10 \text{ pF}$ ,  $C_{gd} = 1 \text{ pF}$ ,  $C_1 = C_2 = 10 \mu\text{F}$ ,  $R_{sig} = 1 \text{ k}\Omega$ ,  $R_{G1} = 8.6 \text{ M}\Omega$ ,  $R_{G2} = 8.6 \text{ M}\Omega$ ,  $R_D = 12 \text{ k}\Omega$ , and  $R_L = 24 \text{ K}\Omega$ .

Determine and then calculate all of the high frequency poles.

[15 points]

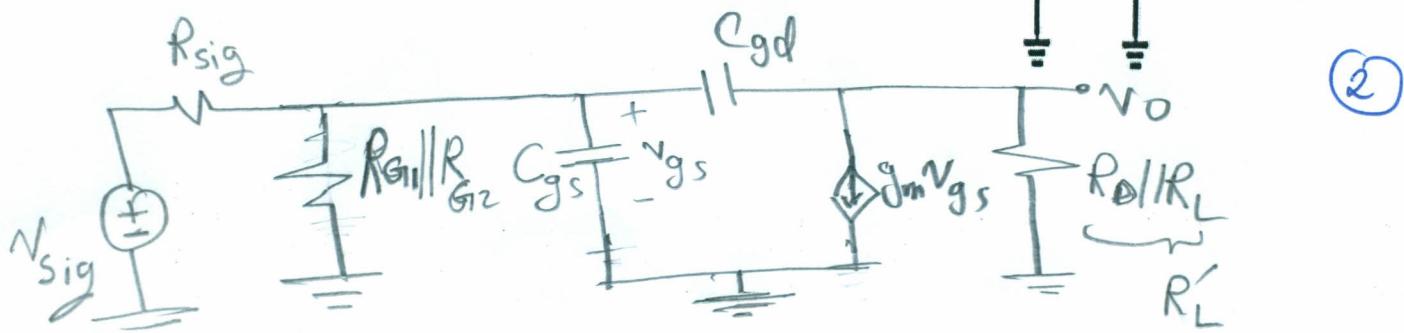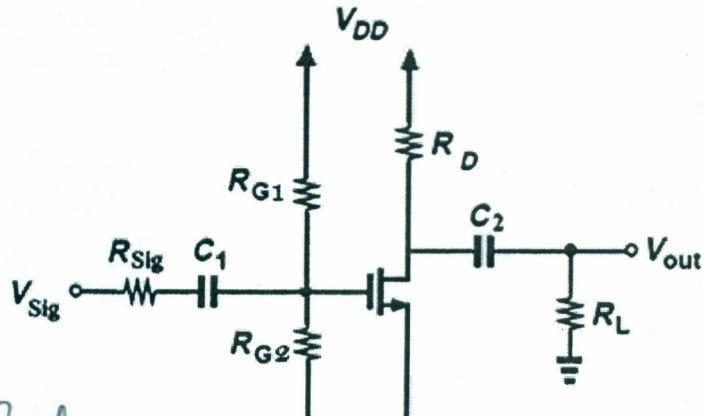

$$\text{Miller theorem } K = -g_m R'_L = -8 \text{ V/V}$$

$$C_1 = C_{gd} (1 + g_m R'_L) = 9 C_{gd} = 9 \text{ pF}$$

$$C_2 = C_{gd} \left(1 + \frac{1}{g_m R'_L}\right) = 1.125 \text{ pF}$$

$$C_{eq} = C_{gs} + C_1 = 19 \text{ pF}$$

$$= 52.6 \text{ M rad/s}$$

Pole due  $C_{eq}$ :

$$\omega_{H1} = \frac{1}{C_{eq} [R_{sig} || R_{G1} || R_{G2}]} \quad (5)$$

Pole due  $C_2$ :


$$\omega_{H2} = \frac{1}{C_2 (R_L || R_D)} = 111.1 \text{ M rad/s} \quad (6)$$

**Question No. 3 [20 points]**

For the common emitter amplifier shown; assumes  $r_x$  and  $r_o$  are neglected:

a- Drive the expressions for all low frequency poles. [15 points]

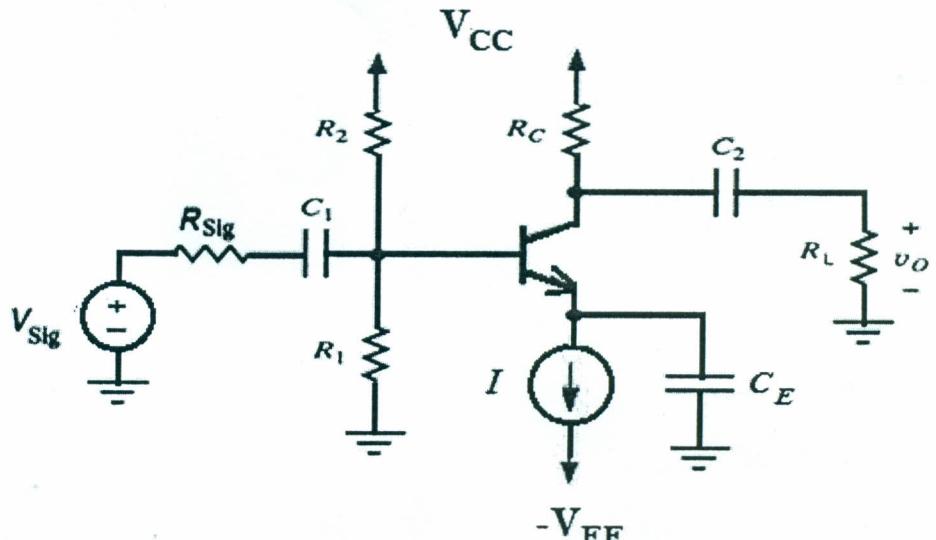b- Find an expression for the low corner frequency  $f_L$  (*do not neglect any pole*). [5 points]



$$\text{a) } \omega_{L1} = \frac{1}{C_1 [R_{\text{Sig}} + (R_1 || R_2 || r_\pi)]}$$

5

$$\omega_{L2} = \frac{1}{C_E \left[ r_e + \frac{R_1 || R_2 || R_{\text{Sig}}}{\beta + 1} \right]}$$

5

$$\omega_{L3} = \frac{1}{C_2 [R_C + R_L]}$$

5

$$\text{b) } \omega_L = \omega_{L1} + \omega_{L2} + \omega_{L3} \quad \textcircled{3}$$

$$f_L = \frac{\omega_L}{2\pi} \quad \textcircled{2}$$