

# EE 204

## Lecture 05


### Circuit Solution by Circuit Reduction

Sources Connected in Series and in Parallel :


Both circuits are invalid. Why?

Circuit (a) violates KVL  $\Rightarrow$  *ideal* voltage sources cannot be combined in *parallel*  
(unless they have the same voltage)

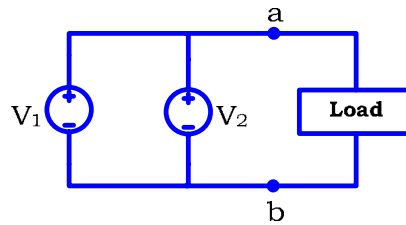Circuit (b) violates KCL  $\Rightarrow$  *ideal* current sources cannot be combined in *series*  
(unless they have the same current)



(a)

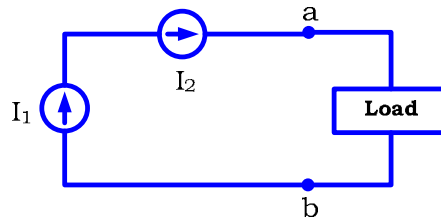

(b)

Figure 1

We can connect ideal voltage sources in *series*.

Voltage sources in *series* can be reduced to a single voltage source

$$V_{eq} = V_1 - V_2 + V_3 + V_4$$

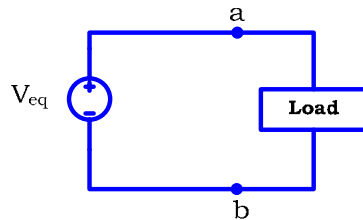
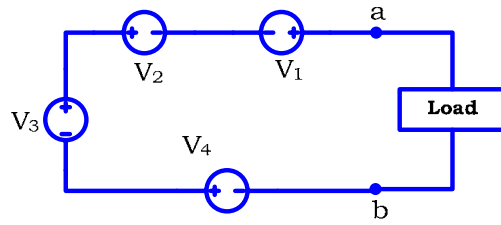


Figure 2

We can connect ideal current sources in *parallel*.

Current sources in *parallel* can be combined as a single current source

$$I_{eq} = -I_1 - I_2 + I_3 - I_4$$

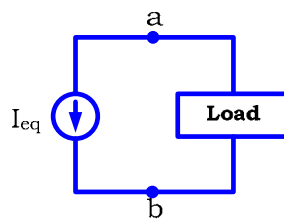
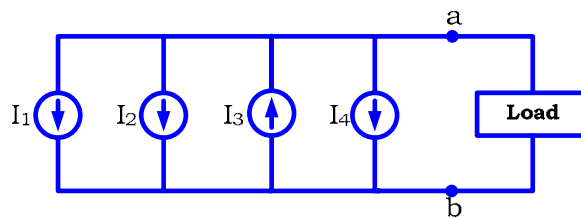
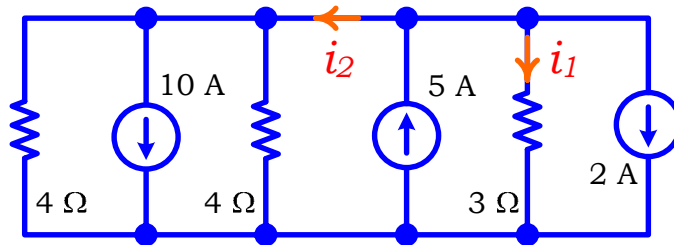
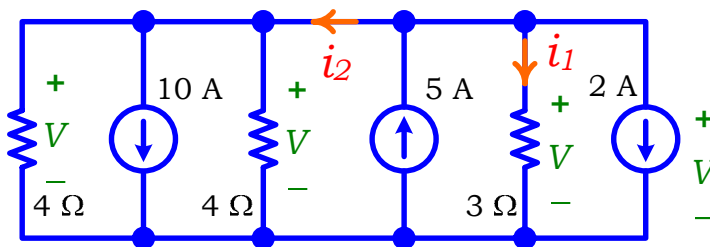


Figure 3

**Example 1**

Determine the currents  $i_1$  and  $i_2$  in the circuit of Fig. ...

**(a)****(b)****Solution:**

$$V = \frac{-10A + 5A - 2A}{\frac{1}{4}S + \frac{1}{4}S + \frac{1}{3}S}$$

$$= \frac{-7A}{\frac{5}{6}S} = -8.4V$$

Ohm's law gives the currents through the resistors. Current  $i_1$  is labeled with the passive sign convention with respect to voltage  $V$ . Hence

$$i_1 = \frac{V}{3\Omega}$$

$$= \frac{-8.4A}{3\Omega} = -2.8A$$

Circuit  $i_2$  is the sum of the currents through the 3 ohm resistor, the 5-A current source, and the 2-A current source. Applying KCL yields:




$$i_2 = 5A - i_1 - 2A = 5.8A$$

This can also be calculated as the sum of the currents through the 4-ohm resistors and the 10-A source:

$$i_2 = \frac{V}{4\Omega} + \frac{V}{4\Omega} + 10 = 5.8A$$
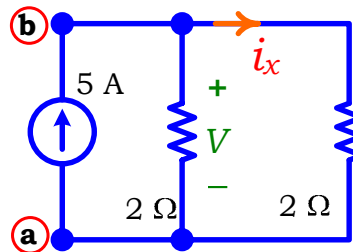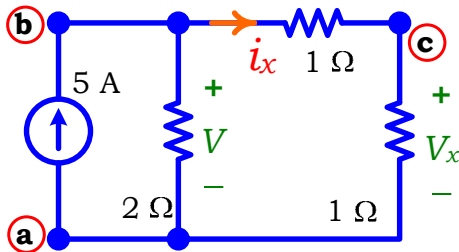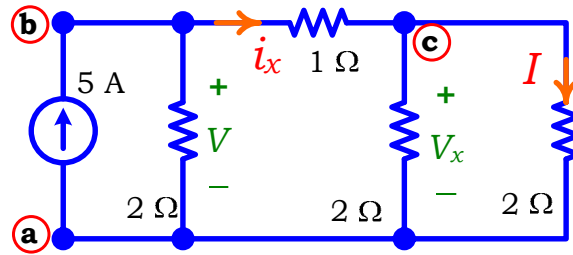
### Example 2

Determine voltages  $V$  and  $v_x$  and currents  $I$  and  $i_x$  in the circuit of Fig. ...



### Solution:

Combine the 2 resistors in // (2 ohm resistors) to get a resistor of 1 Ohm. Circuit in step 1. Note that to find the current  $I$  which has been lost, we have to come back to the original circuit once we find  $v_x$  which remains after circuit reduction. Similarly  $i_x$  remains.

Finally add the equivalent resistor to the 1 Ohm series resistor to get 1 + 1 or 2 Ohm resistor, circuit in step2. Note that node  $c$  and voltage  $v_x$  have disappeared in this reduction, but voltage  $V$  remains since it is across the parallel combination. Also current  $i_x$  remains. No more reduction is required since we have a single node now and we can therefore determine  $V$  as:

$$V = \frac{5A}{\frac{1}{2}\Omega + \frac{1}{2}\Omega} = 5V$$

The current  $i_x$  can also be determined using Ohm's law as:

$$i_x = \frac{V}{2\Omega} = \frac{5}{2} A$$

Moving back to Step 1, we determine the voltage  $v_x$  using Ohm's law as:

$$v_x = i_x \times 1\Omega = \frac{5}{2} V$$

The current  $I$  can now be determined from the original circuit as

$$I = \frac{v_x}{2\Omega} = \frac{5}{4} A$$

**Equivalent Resistance of  $N$  Resistors in Series:**

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{i=1}^N R_i$$

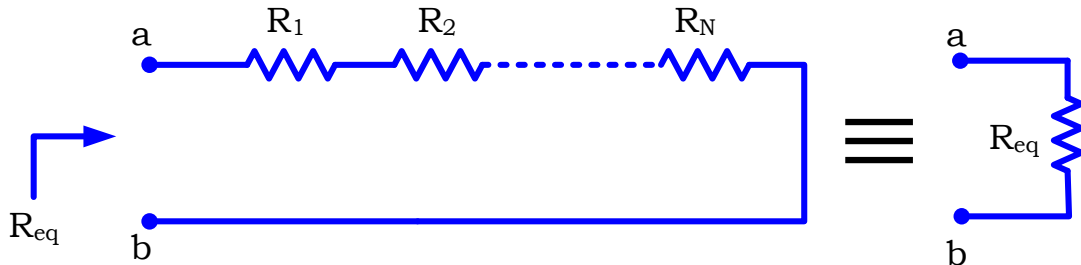


Figure 3

**Equivalent Resistance of  $N$  Resistors in Parallel:**

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \sum_{i=1}^N \frac{1}{R_i}$$

Special Case: If *two* resistors  $R_1$  &  $R_2$  are in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow R_{eq} = \frac{\text{Product}}{\text{Sum}}$$

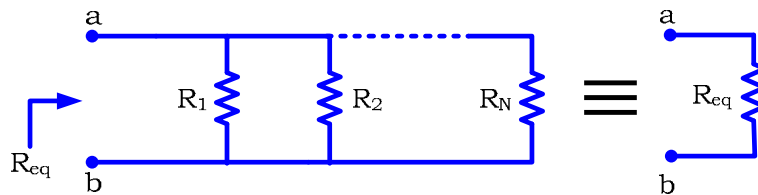


Figure 4

**Example 1:**

Calculate the equivalent resistance seen to the right of  $a-b$ .

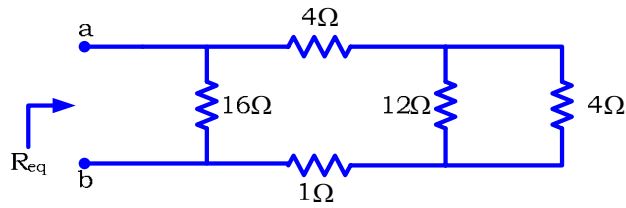


Figure 5

Solution:

$$12\Omega \text{ \& \ } 4\Omega \text{ in parallel} \Rightarrow \frac{12 \times 4}{12 + 4} = \frac{48}{16} = 3\Omega$$

$$4\Omega \text{ \& \ } 3\Omega \text{ \& \ } 1\Omega \text{ in series} \Rightarrow 4 + 3 + 1 = 8\Omega$$

$$16\Omega \text{ \& \ } 8\Omega \text{ in parallel} \Rightarrow \frac{16 \times 8}{16 + 8} = \frac{16 \times 8}{24} = \frac{16}{3} = 5.33\Omega$$

$$\therefore R_{eq} = 5.33\Omega$$

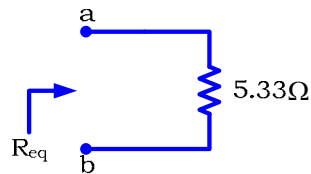
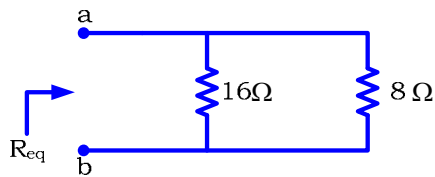
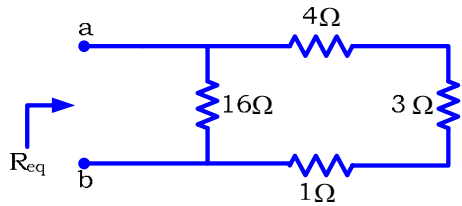


Figure 6

### Conductance

The conductance  $G$  of a resistor is the reciprocal of the resistance  $R$

$$G = \frac{1}{R}$$

Unit of  $G$  is  $\frac{1}{\Omega}$  or Semen [ $S$ ]  $\Rightarrow \frac{1}{\Omega} \equiv S$

For  $N$  conductances in series

$$\frac{1}{G_{eq}} = \sum_{i=1}^N \frac{1}{G_i}$$

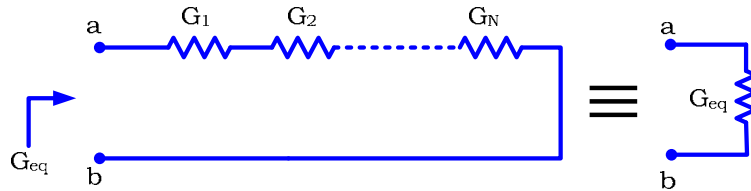


Figure 7

For  $N$  conductances in parallel

$$G_{eq} = \sum_{i=1}^N G_i$$

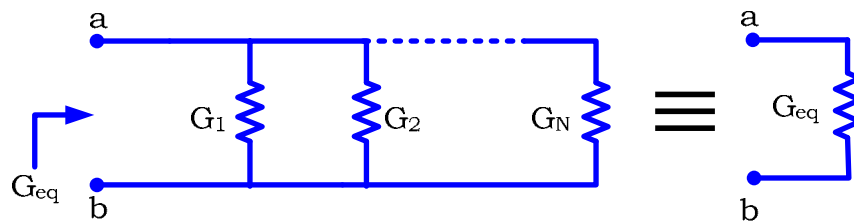


Figure 8


**Power absorbed by a resistor:**

Using circuit a)  $p_R = +iv = +i(iR) = i^2R = \frac{v^2}{R}$


Using circuit b)  $p_R = -iv = -i(-iR) = i^2R = \frac{v^2}{R}$

$\therefore p_R = \frac{v^2}{R} = i^2R$  (regardless of the direction of  $i$  and the polarity of  $v$ )

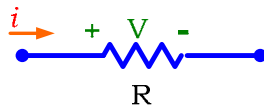$\therefore p_R \geq 0 \Rightarrow$  a resistor *does not generate* electric power, it *always absorbs* it.



(a)

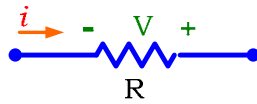

(b)

Figure 9

**Example 2:**

In the given circuit, calculate:

- a)  $G_{eq}$  seen by the voltage source
- b)  $R_{eq}$
- c) the power absorbed by the load

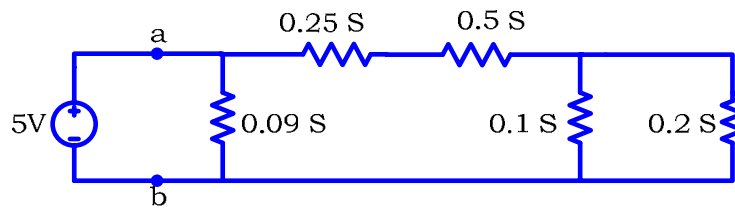


Figure 10

Solution

a)

$$0.1S \text{ \& } 0.2S \text{ (parallel)} \Rightarrow 0.1 + 0.2 = 0.3S$$

$$0.25S \text{ \& } 0.5S \text{ \& } 0.3S \text{ (series)} \Rightarrow \frac{1}{0.25} + \frac{1}{0.5} + \frac{1}{0.3} = 4 + 2 + 3.33 = 9.33 \Rightarrow$$

$$\frac{1}{9.33} = 0.107S$$

$$0.107S \text{ \& } 0.09S \text{ (parallel)} \Rightarrow 0.107 + 0.09 = 0.197S$$

$$\therefore G_{eq} = 0.197S$$



$$b) R_{eq} = \frac{1}{G_{eq}} = \frac{1}{0.197} = 5.08\Omega$$

$$c) P_{5.08\Omega} = \frac{v^2}{R} = \frac{(5)^2}{5.08} = 4.97W$$

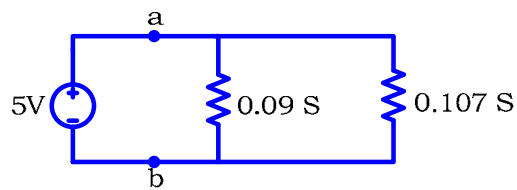
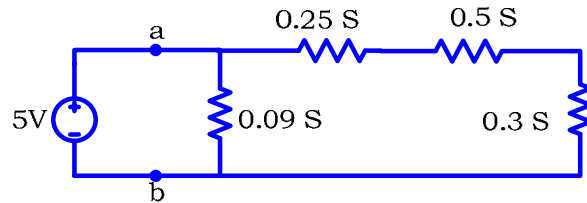


Figure 11

### The meaning of the series connection

$3\Omega$  &  $6V$  are in series.

$10V$  &  $5A$  are in series.

$4\Omega$  &  $20V$  &  $5\Omega$  are in series.

Why?

$6V$  &  $2\Omega$  are *not* in series.

$2\Omega$  &  $11V$  are *not* in series.

Why?

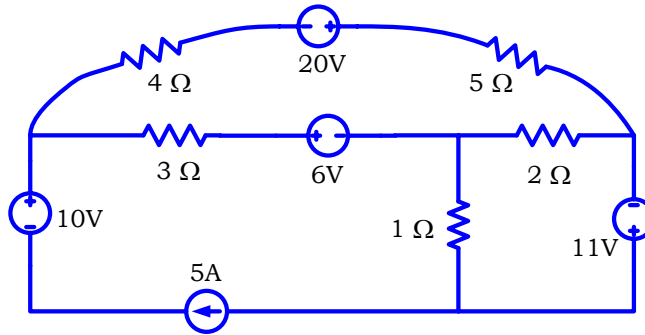


Figure 12

$3\Omega$  &  $6V$  are in series  $\Rightarrow$  the same current  $I_1$  passes through them.

$10V$  &  $5A$  are in series  $\Rightarrow$  the same current  $5A$  passes through them.

$4\Omega$  &  $20V$  &  $5\Omega$  are in series  $\Rightarrow$  the same current  $I_4$  passes through them.

$6V$  &  $2\Omega$  are not in series  $\Rightarrow$  different currents  $I_1$  &  $I_3$  pass through them.

$2\Omega$  &  $11V$  are not in series.  $\Rightarrow$  different currents  $I_3$  &  $I_5$  pass through them.

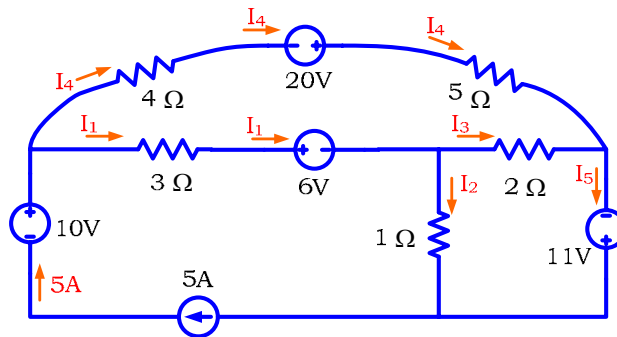


Figure 13

### The meaning of the parallel connection

$3A$  &  $4\Omega$  are in parallel

$6\Omega$  &  $8\Omega$  are in parallel

$2V$  &  $8\Omega$  are not in parallel

Why?

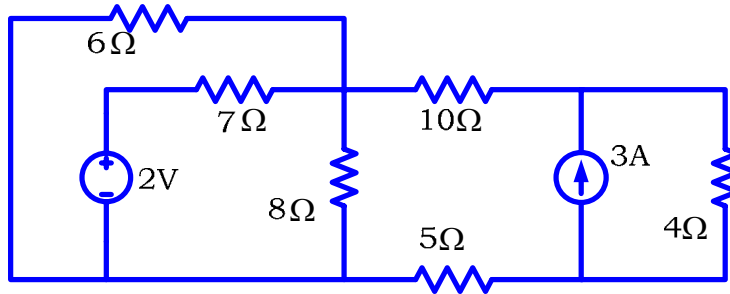


Figure 14

The *same voltage* appears across 3A & 4Ω  $\Rightarrow$  they are in parallel

The *same voltage* appears across 6Ω & 8Ω  $\Rightarrow$  they are in parallel

*Different voltages* appear across 2V & 8Ω  $\Rightarrow$  they are *not* in parallel

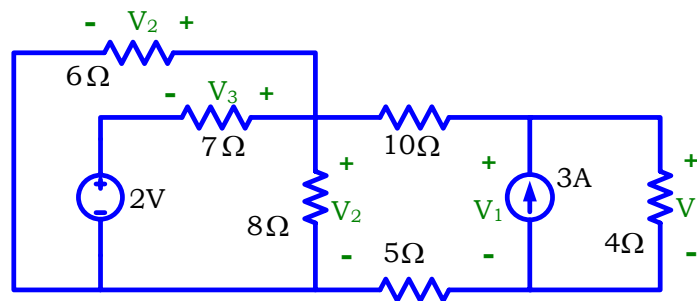


Figure 15

**Example 3:**

Calculate:

- a) the power absorbed by the 3Ω resistor
- b) the *equivalent resistance* seen by the 10V voltage source

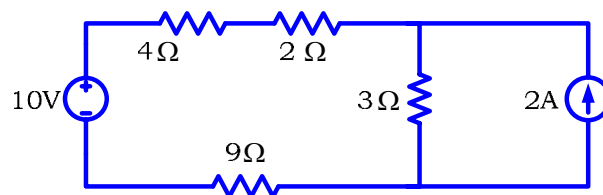


Figure 16

Solution:

a)

$2\Omega$  &  $4\Omega$  &  $9\Omega$  are in series  $\Rightarrow 2+4+9=15\Omega$

Define  $v_1$  &  $v_2$  &  $i_1$  &  $i_2$  (*arbitrary choice of voltage polarity and current direction*)

$$\text{KVL} \quad \Rightarrow \quad -10 + v_1 + v_2 = 0$$

$$\text{Ohm's Law} \quad \Rightarrow \quad -10 + 15i_1 + 3i_2 = 0 \quad (1)$$

$$\text{KCL} \quad \Rightarrow \quad i_1 + 3 = i_2 \quad (2)$$

$$\text{Solving (1) \& (2)} \quad \Rightarrow \quad -10 + 15(i_2 - 3) + 3i_2 = 0 \quad \Rightarrow \quad 18i_2 = 55 \quad \Rightarrow$$

$$i_2 = \frac{55}{18} = 3.056\text{A}$$

$$\therefore p_{3\Omega} = 3i_2^2 = 3(3.056)^2 = 28.02\text{W}$$

b)

$$\text{Using (3)} \quad \Rightarrow \quad i_1 = i_2 - 3 = 3.056 - 3 = 0.056\text{A}$$

$$\therefore R_{eq} = +\frac{v}{i_1} = +\frac{10}{0.056} = 178.57\Omega$$

