

# EE 204

## Lecture 08

### Superposition

#### The Superposition Principle:

Consider a multi-input multi-output general circuit.

The inputs  $S_1, S_2, S_3, \dots, S_N$  represent either *independent* voltage or current sources

The outputs  $O_1, O_2, O_3, \dots, O_M$  represent the remaining voltages and currents

For instance,  $O_1$  may be current through a resistor, and  $O_2$  may be voltage across a current source

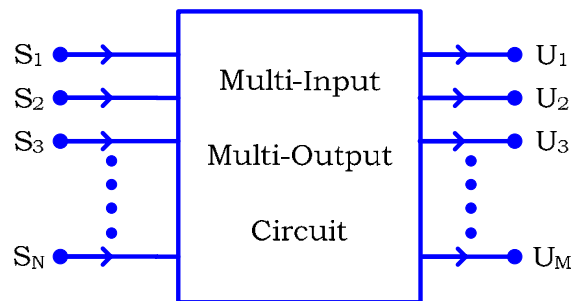


Figure 1

For simplicity, let us consider a *single-output* circuit, with one output quantity,  $U$

All the inputs  $S_1, S_2, S_3, \dots, S_N$  affect the output  $U$

In other words,  $U$  has *some contribution* from *each* of the sources  $S_1, S_2, S_3, \dots, S_N$


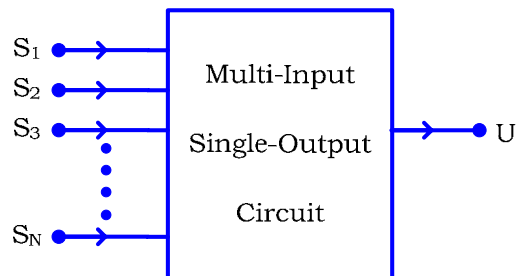


Figure 2

The contribution of  $S_1$  to  $U$  is labeled  $U_1$

The contribution of  $S_2$  to  $U$  is labeled  $U_2$

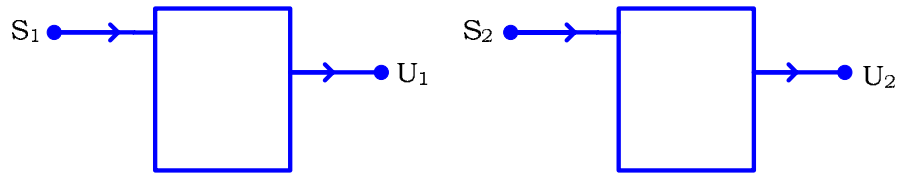

**Figure 3**

In general, the contribution of  $S_i$  to  $U$  is labeled  $U_i$


↓

$$U = U_1 + U_2 + U_3 + \dots + U_N$$

This is called the *Superposition Principle*.

This principle is valid for *linear circuits only*.

All the circuits covered in this course are linear circuits.

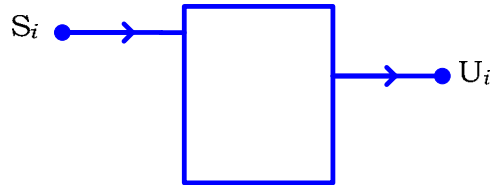


**Figure 4**

The output  $U$  may be *current or voltage*, but it *cannot be power or energy*.


Thus, the SP principle *applies* to currents and voltages, but it *does not* apply to power or energy.

To calculate  $U_1 \Rightarrow$  set *all independent* sources to zero *except*  $S_1$

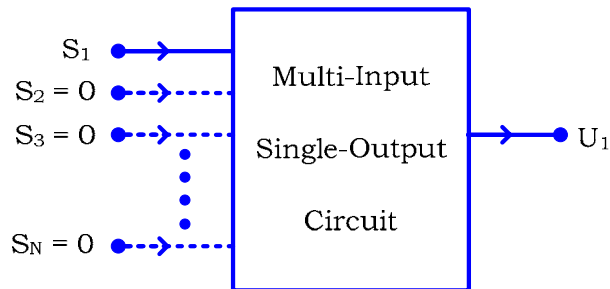


**Figure 5**

To calculate  $U_2 \Rightarrow$  set *all independent* sources to zero *except*  $S_2$

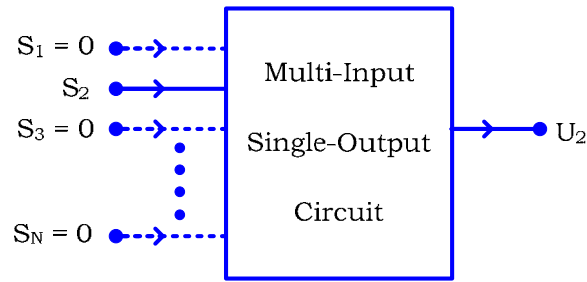

**Figure 6**

To calculate  $U_i \Rightarrow$  set *all independent* sources to zero *except*  $S_i$

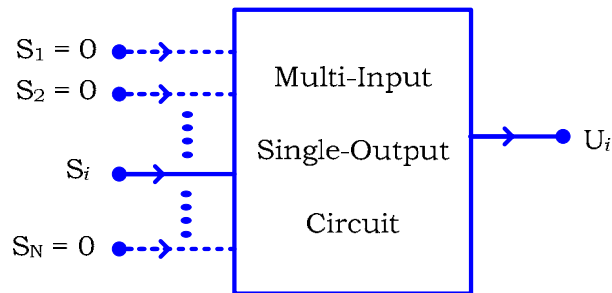

**Figure 7**


To set a voltage source to zero  $\Rightarrow$  replace it with a short circuit

To set a current source to zero  $\Rightarrow$  replace it with an open circuit

Extension of SP to multi-output circuits is straightforward.

**Example 1:**

Calculate  $I$  using SP.

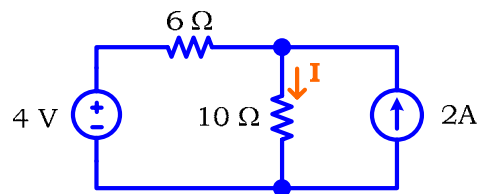


**Figure 8**

Solution:

First calculate  $I' = I|_{4V}$  (current  $I$  due to only the 4V source)

Set the remaining independent sources to zero  $\Rightarrow$  replace 2A with an open circuit

$$I' = \frac{4}{6+10} = 0.25A$$

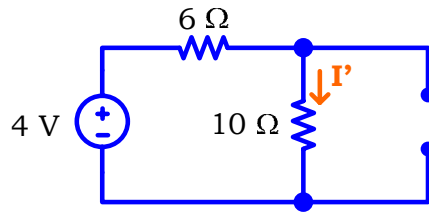


**Figure 9**

Next calculate  $I'' = I|_{2A}$  (current  $I$  due to only the 2A source)

Set the remaining independent sources to zero  $\Rightarrow$  replace 4V with a short circuit

$$\text{CDR} \Rightarrow I'' = \frac{6}{6+10} \times 2 = \frac{12}{16} = 0.75A$$

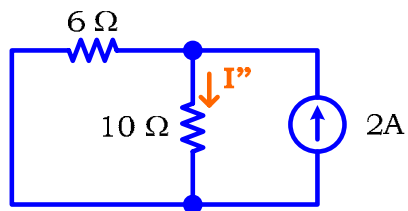


**Figure 10**

$$\therefore I = I' + I'' = 0.25 + 0.75 = 1.00A$$

**Example 2:**

Calculate  $I$  using SP.

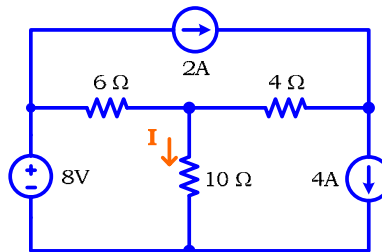

**Figure 11**

Solution:


$$\text{Calculate: } I' = I|_{8V}$$

2A & 4A  $\Rightarrow$  replaced by open circuits

Current through  $4\Omega$  is zero (why?)

The  $4\Omega$  has no effect  $\Rightarrow$   $6\Omega$  &  $10\Omega$  are *in series*

$$\therefore I' = \frac{8}{6+10} = 0.5A$$

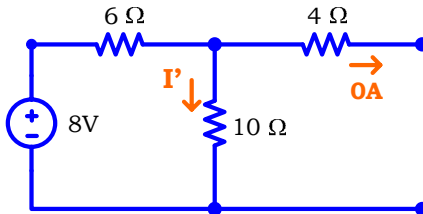

**Figure 12**


Next calculate:  $I' = I|_{4A}$

8V  $\Rightarrow$  replaced by a short circuit

2A  $\Rightarrow$  replaced by an open circuit

$4\Omega$  *in series* with 4A  $\Rightarrow$  equivalent to 4A

$$\text{CDR} \Rightarrow I'' = -\frac{6}{6+10} \times 4 = -1.5A$$

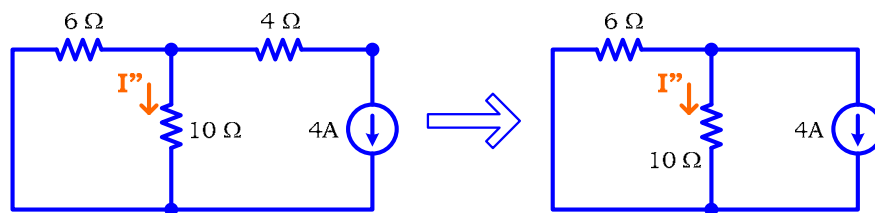

**Figure 13**

Finally calculate:  $I'' = I|_{2A}$

8V  $\Rightarrow$  replaced by a short circuit

4A  $\Rightarrow$  replaced by an open circuit

$4\Omega$  *in series* with 2A  $\Rightarrow$  equivalent to 2A

$$\text{CDR} \Rightarrow I'' = \frac{6}{6+10} \times 2 = 0.75A$$

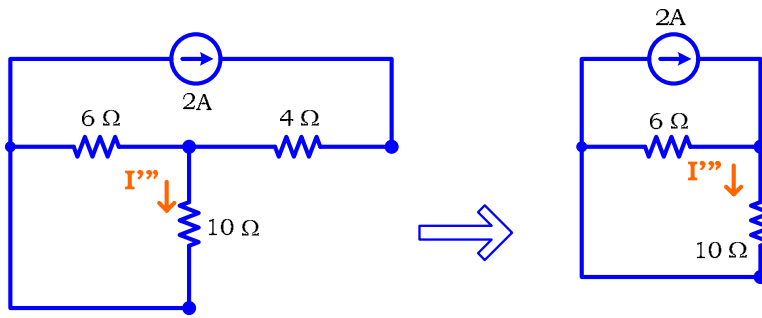


Figure 14

$$\therefore I = I' + I'' + I''' = (0.5) + (-1.5) + (0.75) = -0.25A$$

**Example 3:**

Calculate:

- a)  $P' = P_{5\Omega}|_{8V}$  (Power absorbed by the  $5\Omega$  resistor due only the  $8V$  source)
- b)  $P'' = P_{5\Omega}|_{10V}$  (Power absorbed by the  $5\Omega$  resistor due only the  $10V$  source)
- c) Show that  $P \neq P' + P''$

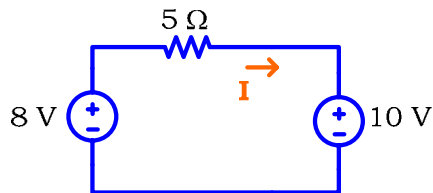


Figure 20

Solution:


$$a) I' = \frac{8}{5} = 1.6A \quad \Rightarrow \quad P' = (1.6)^2 5 = 12.8W$$

$$b) I'' = -\frac{10}{5} = -2A \quad \Rightarrow \quad P'' = (-2)^2 5 = 20W$$

$$c) I = I' + I'' = 1.6 - 2 = -0.4A \quad \Rightarrow \quad P = (-0.4)^2 5 = 0.8W$$

$$P' + P'' = 12.8 + 20 = 32.8$$

$$\therefore P \neq P' + P''$$

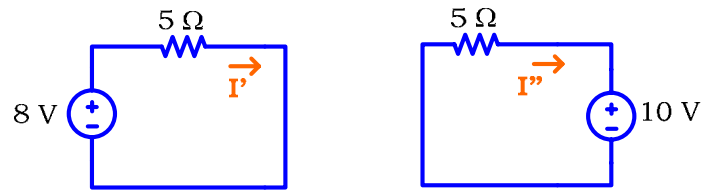

**Figure 21**

Therefore, for power calculation, we can use SP to calculate *total* currents and voltages, from which we can calculate the power.

From the previous examples we can draw the following conclusions:

- 1- The number of partial-circuits *equals* the number of *independent* sources.
- 2- The *algebraic sign* of the unknown *must be* accounted for.
- 3- The voltage *polarity* and the current *direction* remain the *same* in *all* partial-circuits.
- 4- *Dependent* sources are *never* set to zero.
- 5- SP is *not* applicable to Power (or to energy).