

EE 204

Lecture 13

Mesh Analysis - Introduction

Definition of Mesh

The circuit contains four windows (meshes).

A mesh is simply a *window* in an electric circuit

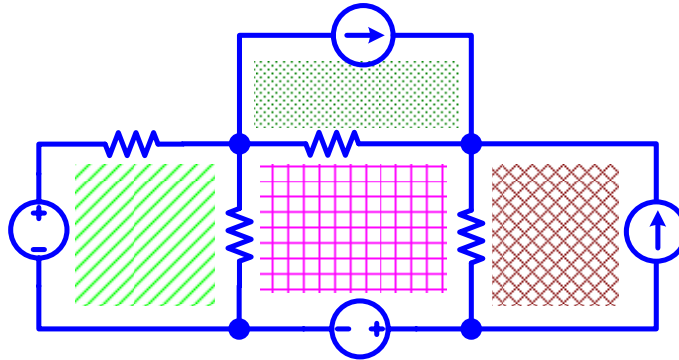


Figure 1

Currents through Elements & Mesh Currents:

The currents i_a , i_b , i_c are currents through elements

$$\text{KCL at node 1} \Rightarrow i_a = i_b + i_c \Rightarrow i_b = i_a - i_c$$

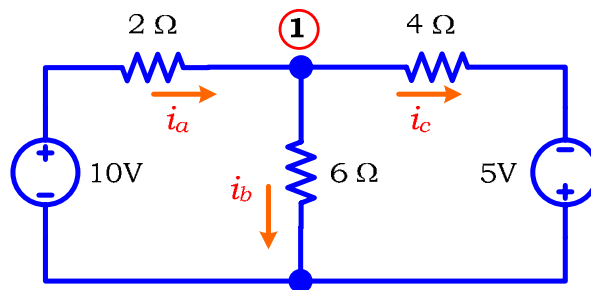


Figure 2

The *imaginary* currents i_1 & i_2 are *mesh* currents

We imagine i_1 to circulate around mesh 1 (CW)

We imagine i_2 to circulate around mesh 2 (also CW)

$i_a = i_1$ (because only mesh current i_1 goes through 2Ω and $10V$)

$i_c = i_2$ (because only mesh current i_2 goes through 4Ω and $5V$)

$i_b = i_a - i_c = i_1 - i_2$ (two mesh currents i_1 & i_2 go through 6Ω in opposite directions)

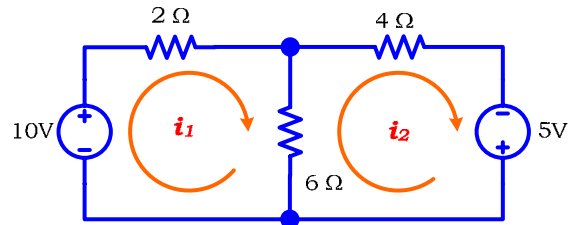


Figure 3

Example 1:

Express the currents through elements (CTE) i_x , i_y , i_z , i_w in terms of mesh currents (MC) i_1 & i_2 .

Solution:

$$i_x = i_1$$

$$i_y = -i_3$$

$$i_z = i_1 - i_2$$

$$i_w = i_3 - i_1$$

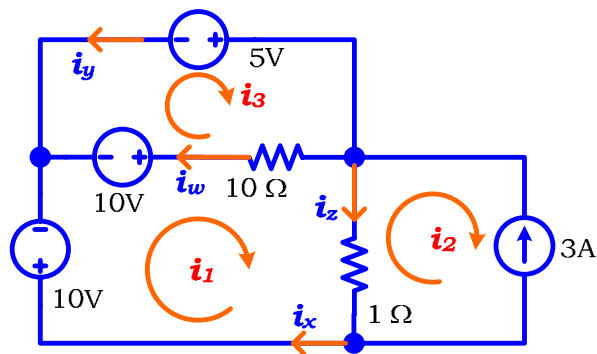


Figure 4

We know all MC \Rightarrow We know all CTE

Number of MC \leq Number of CTE

Mesh Analysis (without Current Sources):

The Mesh Analysis procedure for circuits *without* current sources will be considered first.

We will learn the *basic* Mesh Analysis procedure through a simple example.

Example 2:

Calculate the mesh currents i_1 & i_2 .

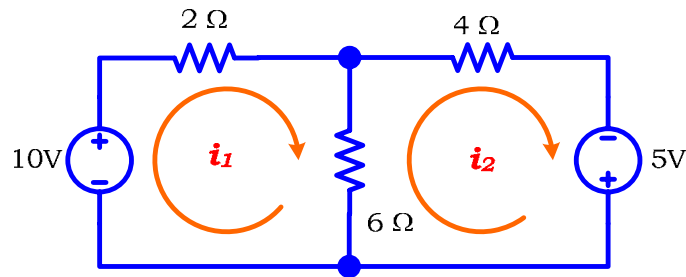


Figure 5

Solution:

Procedure:

1- KVL around mesh 1 $\Rightarrow -10 + V_a + V_b = 0$

2- Ohm's Law $\Rightarrow -10 + 2i_a + 6i_b = 0$

3- KCL $\Rightarrow -10 + 2i_1 + 6(i_1 - i_2) = 0$ [CTE are expressed in terms of MC]

4- Simplify $\Rightarrow 8i_1 - 6i_2 = 10$ (1)

Repeat the same procedure for the remaining meshes:

1- KVL around mesh 2 $\Rightarrow -V_b + V_c - 5 = 0$

2- Ohm's Law $\Rightarrow -6i_b + 4i_c - 5 = 0$

3- KCL $\Rightarrow -6(i_1 - i_2) + 4i_2 - 5 = 0$ [CTE are expressed in terms of MC]

4- Simplify $\Rightarrow -6i_1 + 10i_2 = 5$ (2)

Equations (1) & (2) contain only the *mesh unknowns* i_1 & i_2 .

Solving (1) & (2) $\Rightarrow i_1 = 2.955\text{A}$ & $i_2 = 2.273\text{A}$

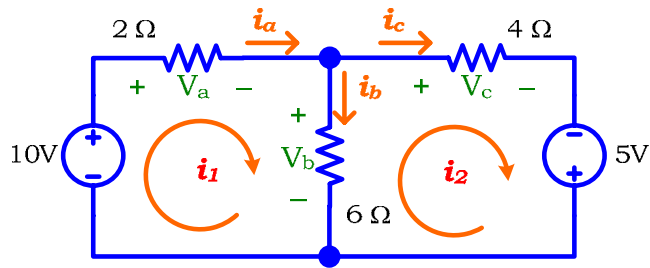


Figure 6

Mesh Analysis procedure: $\text{KVL} \Rightarrow \text{Ohm's Law} \Rightarrow \text{KCL} \equiv \text{VOC}$

Repeat the previous example by combining steps 1 & 2 & 3 into a single step:

Currents through resistors = CTR

Always imagine CTR to be in the same direction as KVL

Express the *imagined* CTR in terms of MC

Mesh 1: KVL & Ohm's Law & KCL $\Rightarrow -10 + 2i_1 + 6(i_1 - i_2) = 0 \Rightarrow 8i_1 - 6i_2 = 10$ (1)

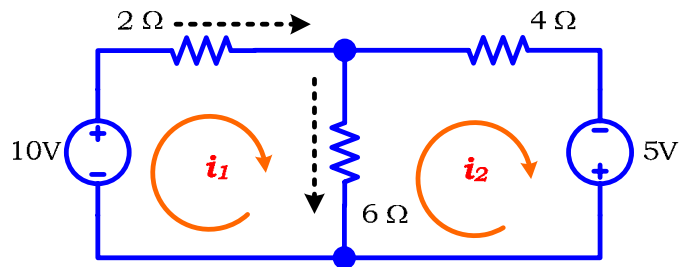


Figure 7

Mesh 2: KVL & Ohm's Law & KCL $\Rightarrow 6(i_2 - i_1) + 4i_2 - 5 = 0 \Rightarrow -6i_1 + 10i_2 = 5$ (2)

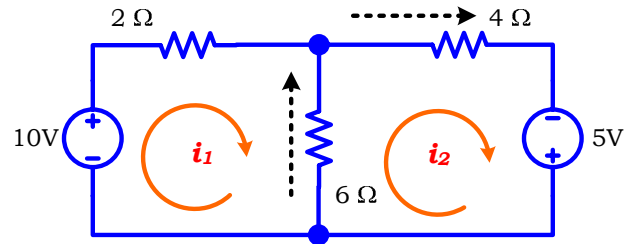


Figure 8

Example 3: Calculate the mesh currents i_1 & i_2 & i_3

Solution:

$$\text{Mesh 1: } \Rightarrow 4i_1 - 8 + 6(i_1 - i_2) = 0 \quad \Rightarrow \quad 10i_1 - 6i_2 = 8 \quad (1)$$

$$\text{Mesh 2: } \Rightarrow 6(i_2 - i_1) + 8(i_2 - i_3) + 12 = 0 \quad \Rightarrow \quad -6i_1 + 14i_2 - 8i_3 = -12 \quad (2)$$

$$\text{Mesh 3: } \Rightarrow 2i_3 + 8(i_3 - i_2) + 8 = 0 \quad \Rightarrow \quad -8i_2 + 10i_3 = -8 \quad (3)$$

$$\text{Solving (1) \& (2) \& (3) } \Rightarrow i_1 = -1.24\text{A} \ \& \ i_2 = -3.40\text{A} \ \& \ i_3 = -3.52\text{A}$$

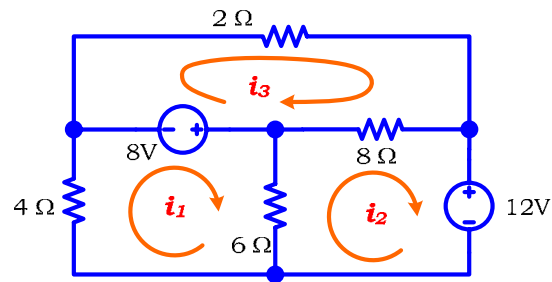


Figure 9