

# EE 204

## Lecture 14


### Mesh Analysis with current sources

**Mesh Analysis (with Current Sources):**

When the circuit contains current sources, the above procedure is modified.

**Example 4:**

Calculate the mesh currents  $i_1$  &  $i_2$  &  $i_3$

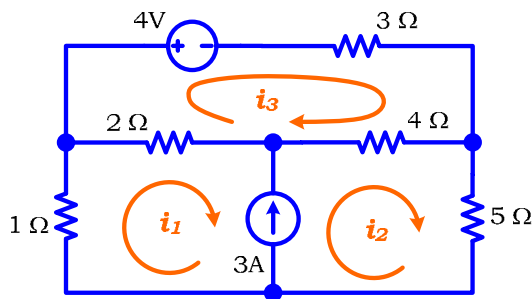

**Figure 10**


Solution:

KVL around mesh 1  $\Rightarrow i_1 + 2(i_1 - i_3) + V_x = 0$  (problem!)

We cannot directly replace  $V_x$  by mesh currents, because Ohm's Law *does not* apply to current sources.

KVL around mesh 2  $\Rightarrow -V_x + 4(i_2 - i_3) + 5i_2 = 0$  (similar problem!)

Mesh 1 & 2 contain a current source (they *share* the 3A source)

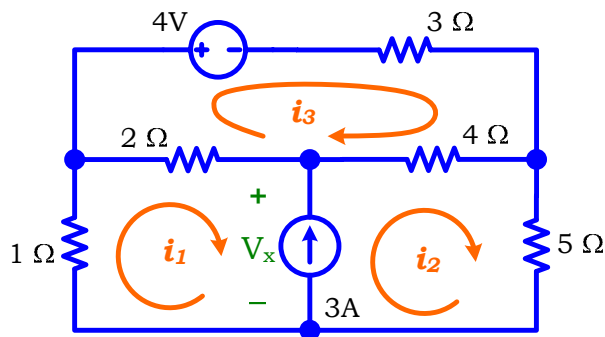

**Figure 11**

What to do in this case?  $\Rightarrow$  Combine mesh 1 & 2  $\Rightarrow$  Super Mesh (SM)

To avoid  $V_x \Rightarrow$  Apply KVL around SM

$\Downarrow$

$$1i_1 + 2(i_1 - i_3) + 4(i_2 - i_3) + 5i_2 = 0$$

$\Downarrow$

$$3i_1 + 11i_2 - 6i_3 = 0 \quad (1)$$

We need one more equation!

Apply KCL  $\Rightarrow$   $i_2 - i_1 = 3 \quad (2)$


Mesh 3 *does not contain a current source*  $\Rightarrow$  no special treatment

KVL around mesh 3  $\Rightarrow$   $4 + 3i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0$

$\Downarrow$

$$-2i_1 - 4i_2 + 9i_3 = -4 \quad (3)$$

Solving (1) & (2) & (3)  $\Rightarrow$   $i_1 = -2.767A$  &  $i_2 = 0.233A$  &  $i_3 = -0.956A$

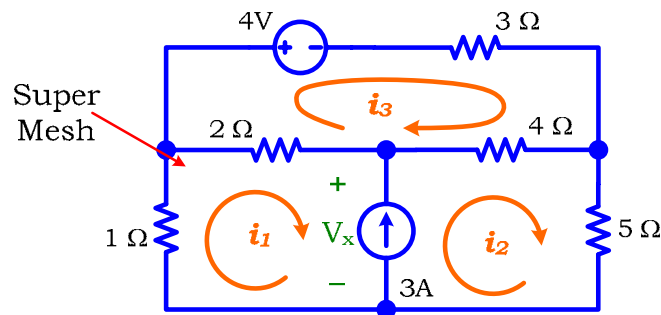

**Figure 12**

Current source *shared* by two meshes

$\Downarrow$


1) Combine the two meshes into a SM

2) Apply KVL around the SM

3) Apply KCL

**Example 5:**

Calculate the mesh currents  $i_1$  &  $i_2$  &  $i_3$

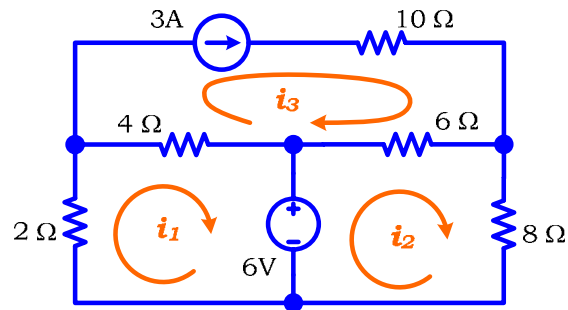

**Figure 13**

Solution:

Mesh 1 & 2 *do not* contain *current* sources  $\Rightarrow$  Just Apply KVL around mesh (1) & (2)

$$\text{KVL around mesh 1} \Rightarrow 2i_1 + 4(i_1 - i_3) + 6 = 0 \Rightarrow 6i_1 - 4i_3 = -6 \quad (1)$$

$$\text{KVL around mesh 2} \Rightarrow -6 + 6(i_2 - i_3) + 8i_2 = 0 \Rightarrow 14i_2 - 6i_3 = 6 \quad (2)$$

Mesh 3 contains 3A current source (*not shared by another mesh*)

$\Downarrow$

*Do not apply KVL* (because KVL involves *voltage* across the *current source*)

$\Downarrow$


Apply KCL Only

$\Downarrow$

$$i_3 = 3 \quad (3)$$

[Note: Since we need *just* one equation from mesh 3, KCL provides it in this case]

$$\text{Solving (1) \& (2) \& (3)} \Rightarrow i_1 = 1.000A \ \& \ i_2 = 1.714A \ \& \ i_3 = 3.000A$$

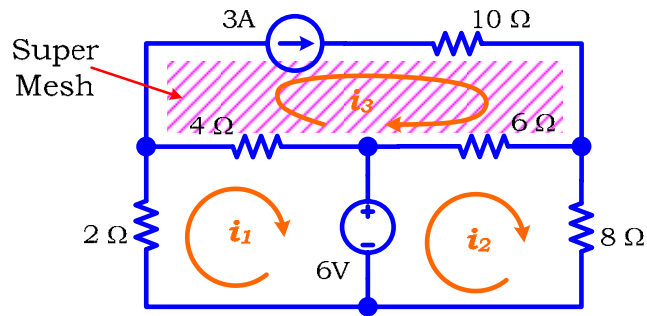

**Figure 14**

Current source in *one mesh only* (not shared)  $\Rightarrow$  No KVL  $\Rightarrow$  Only KCL


### Nodal Vs Mesh Analysis

Which method is more efficient, the nodal or the mesh analysis?

The answer depends on the circuit under consideration. The method that results in the *least* number of *actual* unknowns is generally more efficient.

### Example 4:

Calculate the power absorbed by the  $4\Omega$  resistor.

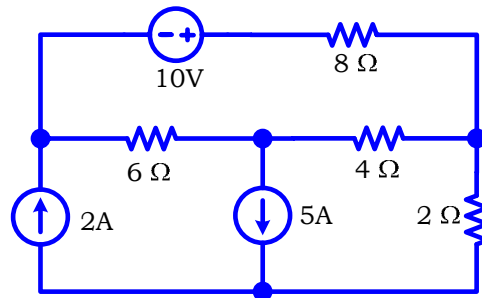


**Figure 7**

Using nodal analysis:

There are 5 essential nodes in the circuit.

Choose the reference node on one side of the 10V source.

$\therefore$  Number of *actual* unknowns is 3 (only  $v_2$  &  $v_3$  &  $v_4$  are unknown, since  $v_1 = 10V$ )

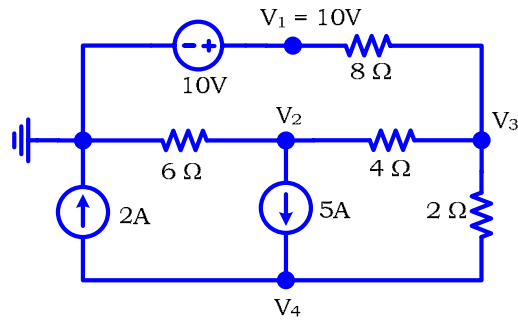

**Figure 8**

Using mesh analysis:


Number of actual unknowns is only 2 (only  $i_2$  &  $i_3$  are unknown, since  $i_1 = 2A$ )

$\therefore$  Use the mesh analysis to solve this problem:

$$\text{KCL} \Rightarrow i_1 - i_2 = 5 \Rightarrow 2 - i_2 = 5 \Rightarrow i_2 = -3A$$

$$\text{KVL around mesh 3} \Rightarrow -10 + 4(i_3 - (-3)) + 6(i_3 - 2) = 0 \Rightarrow i_3 = 1A$$

$$\therefore p_{4\Omega} = 4(i_2 - i_3)^2 = 4(-3 - 1)^2 = 16W$$

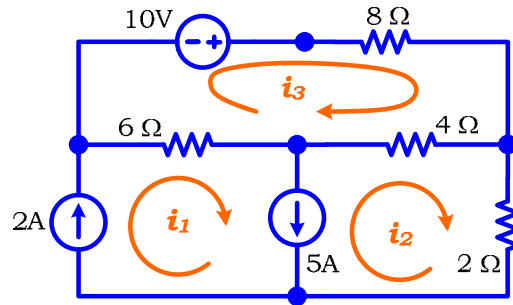

**Figure 9**