

# EE 213 ELECTRIC CIRCUITS II

## Chapter 11 Balanced Three-Phase Circuits

Dr. Hakan Köroğlu



## Recap: Sinusoidal Sources


- A sinusoidal voltage (current) source produces a voltage (current) that varies sinusoidally in time.

$$v(t) = V_m \cos(\omega t + \phi)$$

Amplitude


Frequency  
(radians)

Phase

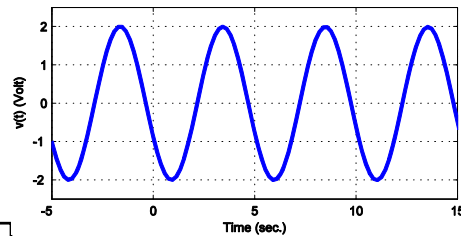
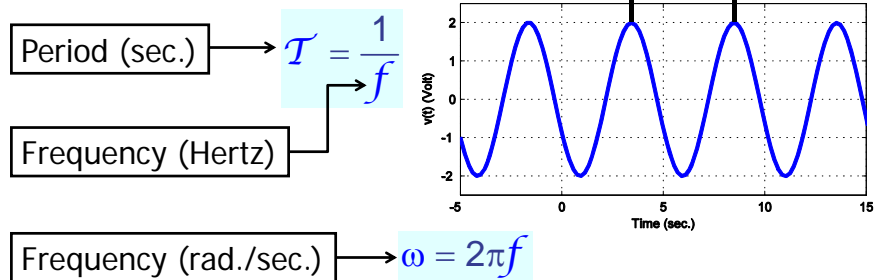
## Recap: Frequency and Period

- A function that repeats itself is called **periodic**. The amount of time required to complete one full cycle is called the **period**.
- The number of cycles per second is called the **frequency**.



3

## Recap: Root-Mean-Square (RMS) Value

- The rms value of a periodic function is defined as the **square-root** of the **mean** value of the **squared** function.

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

- For sinusoidal signal sources, the RMS value can be shown to be

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

4

## Recap: Phasor

- Phasor is a complex number that carries the amplitude and phase information of a sinusoidal function.

$$\mathcal{V} = \mathcal{P}\{\mathcal{V}_m \cos(\omega t + \phi)\} = \mathcal{V}_m e^{j\phi}$$

- The sinusoidal function is obtained from the inverse phasor transform as

$$v(t) = \mathcal{P}^{-1}\{\mathcal{V}\} = \Re\{\mathcal{V}e^{j\omega t}\}$$

5

## Recap: Polar and Rectangular Forms

- Euler Identity shows us how to go from polar form to the rectangular form:

$$e^{j\phi} = \cos(\phi) + j \sin(\phi)$$

- One can then go from rectangular to polar form as

$$\mathcal{V} = x + jy = \mathcal{V}_m e^{j\phi}$$

with

$$\mathcal{V}_m = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1}\left(\frac{y}{x}\right)$$

6

## Recap: Addition and Multiplication

- Multiplication is more convenient in polar form:

$$\underbrace{\mathcal{V}_{m1} e^{j\phi_1}}_{\mathcal{V}_1} \cdot \underbrace{\mathcal{V}_{m2} e^{j\phi_2}}_{\mathcal{V}_2} = \underbrace{\mathcal{V}_{m1} \mathcal{V}_{m2}}_{\mathcal{V}} e^{j(\phi_1 + \phi_2)}$$

- Taking a power is simple in polar form:


$$(\mathcal{V}_m e^{j\phi})^k = \mathcal{V}_m^k e^{jk\phi}$$

- Addition is more convenient in rectangular form:

$$\underbrace{\mathcal{V}_{m1} e^{j\phi_1}}_{\mathcal{V}_1} + \underbrace{\mathcal{V}_{m2} e^{j\phi_2}}_{\mathcal{V}_2} = \mathcal{V}_{m1} \cos(\phi_1) + \mathcal{V}_{m2} \cos(\phi_2) + j(\mathcal{V}_{m1} \sin(\phi_1) + \mathcal{V}_{m2} \sin(\phi_2))$$

7

## Balanced Three-Phase Voltages

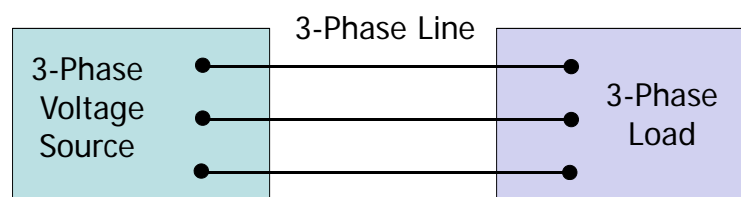


- A set of balanced three-phase voltage consists of three sinusoidal voltages that have identical amplitudes and frequencies, but are out of phase with each other by exactly 120 degrees ( $2\pi/3$  radians).

8
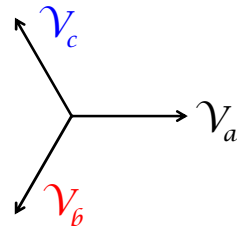
## Positive and Negative Phase Sequences


➤ abc or Positive phase sequence:

$$\begin{aligned} \mathcal{V}_a &= \mathcal{V}_m \\ \mathcal{V}_b &= \mathcal{V}_m e^{-j120^\circ} \\ \mathcal{V}_c &= \mathcal{V}_m e^{+j120^\circ} \end{aligned}$$



➤ acb or Negative phase sequence:


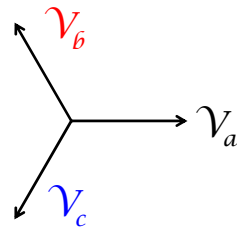
$$\begin{aligned} \mathcal{V}_a &= \mathcal{V}_m \\ \mathcal{V}_b &= \mathcal{V}_m e^{+j120^\circ} \\ \mathcal{V}_c &= \mathcal{V}_m e^{-j120^\circ} \end{aligned}$$



9
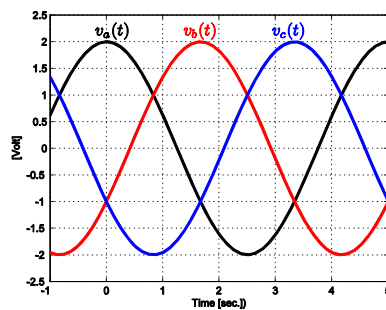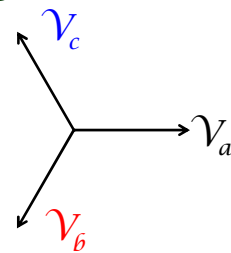
## Positive Phase or abc Sequence



$$\begin{aligned} \mathcal{V}_a &= \mathcal{V}_m \\ \mathcal{V}_b &= \mathcal{V}_m e^{-j120^\circ} \\ \mathcal{V}_c &= \mathcal{V}_m e^{+j120^\circ} \end{aligned}$$



10
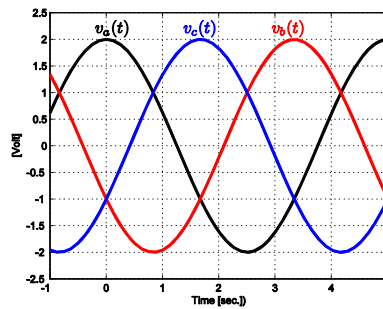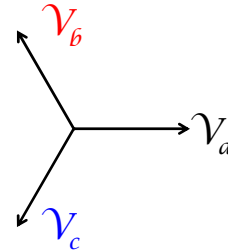
## Negative Phase or acb Sequence

$$\begin{aligned} \mathcal{V}_a &= \mathcal{V}_m \\ \mathcal{V}_b &= \mathcal{V}_m e^{+j120^\circ} \\ \mathcal{V}_c &= \mathcal{V}_m e^{-j120^\circ} \end{aligned}$$



11

## Important Properties

- The sum of balanced three-phase voltages in phasor domain is zero.

$$\mathcal{V}_a + \mathcal{V}_b + \mathcal{V}_c = 0$$

- This is true for the instantaneous voltages as well:


$$v_a(t) + v_b(t) + v_c(t) = 0$$

- If we know the phase sequence (i.e. whether it is positive or negative) and one voltage in the set, then we can determine the entire set.

12

## Three-Phase Voltage Sources


➤ Y-Connected Source:

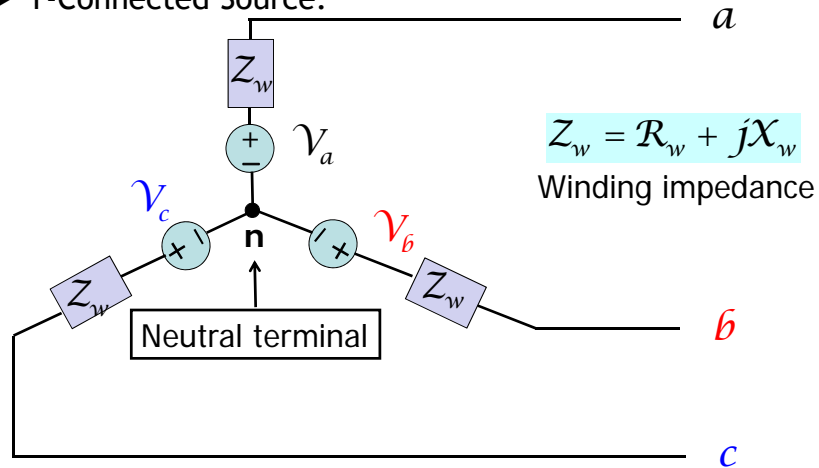

13

## Three-Phase Voltage Sources

➤ Δ-Connected Source:

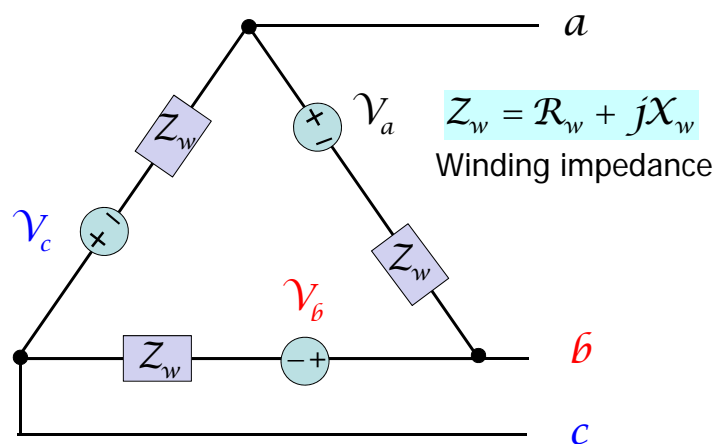

14

## Possible Combinations of Sources & Loads


- Since both source and load can be either Y- or  $\Delta$ -connected, there are four possible combinations:

Source	Load
Y	Y
Y	$\Delta$
$\Delta$	Y
$\Delta$	$\Delta$

- As other combinations can also be reduced to it, we first start with the analysis of the Y-Y combination.

15

## Analysis of the Y-Y Circuit

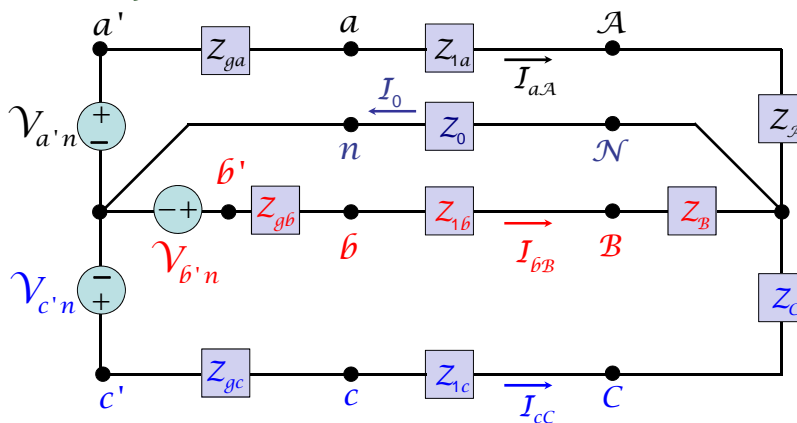

$$\frac{V_N}{Z_0} + \frac{V_N - V_{a'n}}{Z_A + Z_{1a} + Z_{ga}} + \frac{V_N - V_{b'n}}{Z_B + Z_{1b} + Z_{gb}} + \frac{V_N - V_{c'n}}{Z_C + Z_{1c} + Z_{gc}} = 0$$

16



## Conditions for a Balanced 3-Phase Circuit

1. Balanced three-phase voltage sources:

$$\mathcal{V}_{a'n} + \mathcal{V}_{b'n} + \mathcal{V}_{c'n} = 0$$

2. Same impedance in each phase of the voltage source:

$$Z_{ga} = Z_{gb} = Z_{gc}$$

3. Same impedance in each line (or phase) conductor:

$$Z_{1a} = Z_{1b} = Z_{1c}$$

4. Same impedance in each phase of the load:

$$Z_{\mathcal{A}} = Z_{\mathcal{B}} = Z_{\mathcal{C}}$$

17

## Balanced 3-Phase Y-Y Circuit

- For a balanced three-phase Y-Y circuit, we have

$$\mathcal{V}_{\mathcal{N}} \left( \frac{1}{Z_0} + \frac{3}{Z_\phi} \right) = \frac{\mathcal{V}_{a'n} + \mathcal{V}_{b'n} + \mathcal{V}_{c'n}}{Z_\phi} = 0 \quad \Rightarrow \mathcal{V}_{\mathcal{N}} = 0$$

$$\text{where } Z_\phi = Z_{\mathcal{A}} + Z_{1a} + Z_{ga} = Z_{\mathcal{B}} + Z_{1b} + Z_{gb} = Z_{\mathcal{C}} + Z_{1c} + Z_{gc}$$

- The line currents are necessarily balanced:


$$I_{a\mathcal{A}} = \frac{\mathcal{V}_{a'n} - \mathcal{V}_{\mathcal{N}}}{Z_{\mathcal{A}} + Z_{1a} + Z_{ga}} = \frac{\mathcal{V}_{a'n}}{Z_\phi} \quad I_{b\mathcal{B}} = \frac{\mathcal{V}_{b'n} - \mathcal{V}_{\mathcal{N}}}{Z_{\mathcal{B}} + Z_{1b} + Z_{gb}} = \frac{\mathcal{V}_{b'n}}{Z_\phi}$$

$$I_{c\mathcal{C}} = \frac{\mathcal{V}_{c'n} - \mathcal{V}_{\mathcal{N}}}{Z_{\mathcal{C}} + Z_{1c} + Z_{gc}} = \frac{\mathcal{V}_{c'n}}{Z_\phi}$$

18
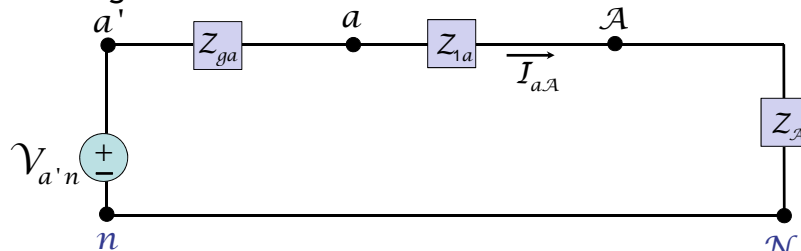
## A Single-Phase Equivalent Circuit

- $V_{\mathcal{N}} = 0 \Rightarrow I_0 = 0$ . Hence, we may either remove the neutral conductor or make a short circuit from  $n$  to  $\mathcal{N}$ .
- Analysis of a single phase is enough, since other phase voltages/currents follow from balancedness.




- **Remark:** The current from  $\mathcal{N}$  to  $n$  in the single-phase circuit is not  $I_0$ ! Recall that  $I_0 = I_{aA} + I_{bB} + I_{cC} = 0$ .

19
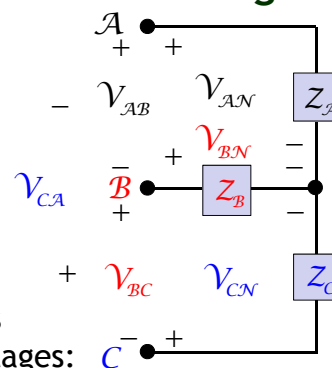
## Line-to-Line and Line-to-Neutral Voltages

- Line-to-line voltages:

$$\begin{aligned} V_{AB} &= V_{AN} - V_{BN} \\ V_{BC} &= V_{BN} - V_{CN} \\ V_{CA} &= V_{CN} - V_{AN} \end{aligned}$$




- Balanced line-to-neutral voltages lead to balanced line-to-line voltages:

$$\begin{aligned} V_{AN} &= V_{\phi} & \Rightarrow & & V_{AB} &= \sqrt{3}V_{\phi} e^{+j30^\circ} \\ V_{BN} &= V_{\phi} e^{-j120^\circ} & & & V_{BC} &= \sqrt{3}V_{\phi} e^{-j90^\circ} \\ V_{CN} &= V_{\phi} e^{+j120^\circ} & & & V_{CA} &= \sqrt{3}V_{\phi} e^{+j150^\circ} \end{aligned}$$

20
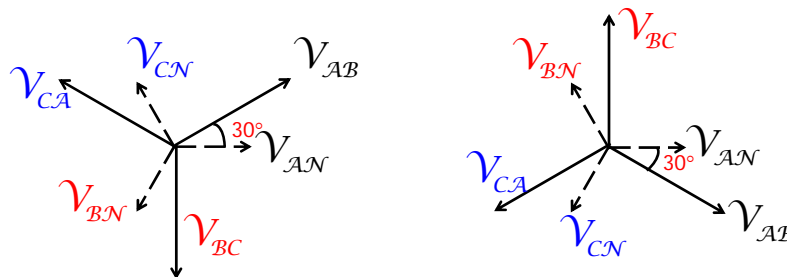
## Balancedness of Line-to-Line Voltages

- Line-to-line voltages form a set of balanced three-phase voltages.
- The magnitude of the line-to-line voltage is  $\sqrt{3}$  times the magnitude of the line-to-neutral voltage.
- Positive- (negative-) phase sequence line-to-line voltages lead (lag) line-to-neutral voltages by  $30^\circ$ .




21

## Some Terminology and Remarks

- **Line voltage:** voltage across any pair of lines
- **Phase voltage:** voltage across a single phase
- **Line current:** current in a single line
- **Phase current:** current in a single phase
- In a Y-connection, line current and phase current are identical.
- In a  $\Delta$ -connection, line voltage and phase voltage are identical.

22

## Recap: $\Delta$ -to-Y Transformations

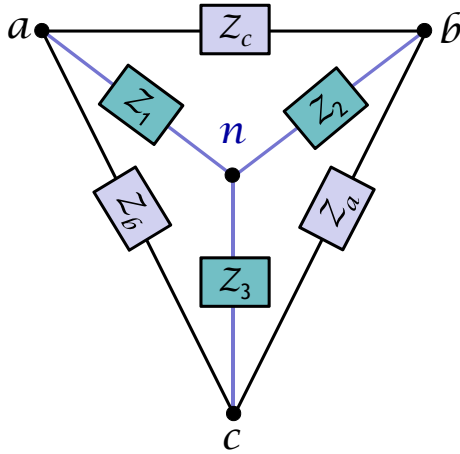

$$\Delta\text{-to-Y: } \begin{aligned} Z_1 &= \frac{Z_b Z_c}{Z_a + Z_b + Z_c} \\ Z_2 &= \frac{Z_c Z_a}{Z_a + Z_b + Z_c} \\ Z_3 &= \frac{Z_a Z_b}{Z_a + Z_b + Z_c} \end{aligned}$$

$$\text{Y-to-}\Delta: \begin{aligned} Z_a &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1} \\ Z_b &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2} \\ Z_c &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3} \end{aligned}$$

$$\text{Equal impedances} \Rightarrow Z_Y = \frac{Z_\Delta}{3}$$

23

## Analysis of the Y- $\Delta$ Circuit

➤ Y-to- $\Delta$  transformation in the load  $\rightarrow$  single-phase equivalent circuit in Slide 19 with  $Z_{\mathcal{A}} = Z_\Delta / 3$ .

➤ Line currents:

$$I_{a\mathcal{A}} = I_{\mathcal{A}B} - I_{\mathcal{C}\mathcal{A}}$$

$$I_{b\mathcal{B}} = I_{\mathcal{B}C} - I_{\mathcal{A}B}$$

$$I_{c\mathcal{C}} = I_{\mathcal{C}\mathcal{A}} - I_{\mathcal{B}C}$$

➤ Balanced phase currents lead to balanced line currents

$$I_{\mathcal{A}B} = I_\phi$$


$$I_{\mathcal{B}C} = I_\phi e^{-j120^\circ}$$

$$I_{\mathcal{C}\mathcal{A}} = I_\phi e^{+j120^\circ}$$

$$\Rightarrow I_{a\mathcal{A}} = \sqrt{3} I_\phi e^{-j30^\circ}$$

$$I_{b\mathcal{B}} = \sqrt{3} I_\phi e^{-j150^\circ}$$

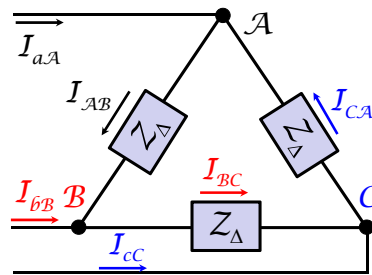
$$I_{c\mathcal{C}} = \sqrt{3} I_\phi e^{+j90^\circ}$$



24
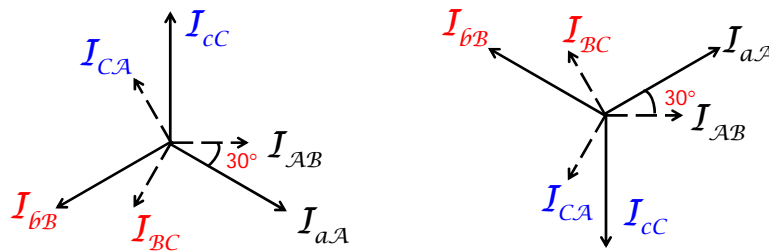
## Balancedness of Line Currents

- Line currents form a set of balanced three-phase currents.
- The magnitude of the line currents is  $\sqrt{3}$  times the magnitude of the phase currents.
- Positive- (negative-) phase sequence line currents lag (lead) the phase currents by  $30^\circ$ .



25

## Recap: Power Calculations

- Complex power:

$$S = \mathcal{V} I^* = |I|^2 Z = \frac{|\mathcal{V}|^2}{Z^*} = P + jQ \quad (\text{VA}) \quad \mathcal{V} = \mathcal{V}_{rms} e^{j\theta_v} \quad Z = R + jX$$

- Average power:  $P = \mathcal{V}_{rms} I_{rms} \cos(\theta_v - \theta_i) \quad (\text{W})$

$$= I_{rms}^2 R = \frac{\mathcal{V}_{rms}^2}{R}$$

- Reactive power:  $Q = \mathcal{V}_{rms} I_{rms} \sin(\theta_v - \theta_i) \quad (\text{VAR})$

$$= I_{rms}^2 X = \frac{\mathcal{V}_{rms}^2}{X}$$

- Apparent power:  $|S| = \sqrt{P^2 + Q^2} \quad (\text{VA})$

- Instantaneous power:  $p(t) = P(1 + \cos 2\omega t) + Q \sin 2\omega t$

26

## Recap: Power Factor and Reactive Factor

### ➤ Power Factor(pf):

$$\text{pf} = \cos(\theta_v - \theta_i)$$

### ➤ Knowing the value of pf is not enough to find $\theta_v - \theta_i$ . Problem is resolved by the following terminology:

❑ **Lagging Power Factor** means current lags voltage  
- hence an inductive load ( $\theta_v - \theta_i > 0$ ).

❑ **Leading Power Factor** means current leads voltage  
- hence a capacitive load ( $\theta_v - \theta_i < 0$ ).

### ➤ Reactive Factor (rf):

$$\text{rf} = \cos(\theta_v - \theta_i)$$

27

## Average Power in a Balanced Y Load

### ➤ With phasors expressed using the rms values:

$$P_A = |V_{AN}| |I_{aA}| \cos(\theta_{vA} - \theta_{iA})$$

$$P_B = |V_{BN}| |I_{bB}| \cos(\theta_{vB} - \theta_{iB})$$


$$P_C = |V_{CN}| |I_{cC}| \cos(\theta_{vC} - \theta_{iC})$$

### ➤ In a balanced 3-phase system:

$$V_\phi = |V_{AN}| = |V_{BN}| = |V_{CN}|$$

$$I_\phi = |I_{aA}| = |I_{bB}| = |I_{cC}|$$
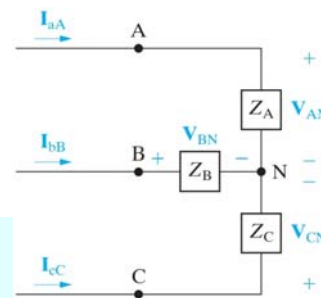
$$\theta_\phi = \theta_{vA} - \theta_{iA} = \theta_{vB} - \theta_{iB} = \theta_{vC} - \theta_{iC}$$



### ➤ Total average power in terms of the rms magnitudes of the line voltage ( $V_L$ ) and line current ( $I_L$ ):

$$P_T = 3 V_\phi I_\phi \cos \theta_\phi = \sqrt{3} V_L I_L \cos \theta_\phi$$

28

## Complex Power in a Balanced Y Load

- With similar derivations for the reactive power:

$$Q_T = 3 V_\phi I_\phi \sin \theta_\phi = \sqrt{3} V_L I_L \sin \theta_\phi$$

- For a balanced load:

$$S_\phi = V_{\mathcal{AN}} I_{a\mathcal{A}}^* = V_{\mathcal{BN}} I_{b\mathcal{B}}^* = V_{\mathcal{CN}} I_{c\mathcal{C}}^* = V_\phi I_\phi^*$$

where  $V_\phi$  and  $I_\phi$  represent, respectively, a voltage and a current taken from the same phase.

- The total complex power is given by:

$$S_T = 3S_\phi = \sqrt{3} V_L I_L e^{j\theta_\phi}$$

29

## Power Calculations in a Balanced $\Delta$ Load

- With phasors expressed using the rms values:

$$P_A = |V_{AB}| |I_{AB}| \cos(\theta_{v_{AB}} - \theta_{i_{AB}})$$

$$P_B = |V_{BC}| |I_{BC}| \cos(\theta_{v_{BC}} - \theta_{i_{BC}})$$

$$P_C = |V_{CA}| |I_{CA}| \cos(\theta_{v_{CA}} - \theta_{i_{CA}})$$

- In a balanced 3-phase system:


$$V_\phi = |V_{AB}| = |V_{BC}| = |V_{CA}|$$

$$I_\phi = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

$$\theta_\phi = \theta_{v_{AB}} - \theta_{i_{AB}} = \theta_{v_{BC}} - \theta_{i_{BC}} = \theta_{v_{CA}} - \theta_{i_{CA}}$$

- Similar calculations lead to:
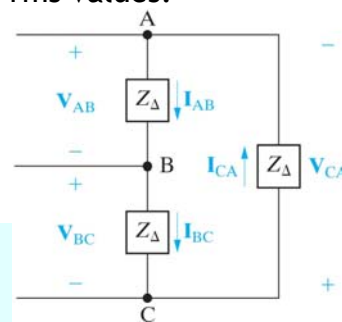
$$S_T = 3S_\phi = \sqrt{3} V_L I_L e^{j\theta_\phi}$$



30

## Instantaneous Power in 3-Phase Circuits

- With  $\mathcal{V}_m$  and  $I_m$  being the maximum amplitudes of the phase voltage and line current, and  $\theta_\phi = \theta_{v_A} - \theta_{i_A}$  :

$$p_A(t) = v_{AN} i_{aA} = \mathcal{V}_m I_m \cos(\omega t) \cos(\omega t - \theta_\phi)$$

$$p_B(t) = v_{BN} i_{bB} = \mathcal{V}_m I_m \cos(\omega t - 120^\circ) \cos(\omega t - \theta_\phi - 120^\circ)$$

$$p_C(t) = v_{CN} i_{cC} = \mathcal{V}_m I_m \cos(\omega t + 120^\circ) \cos(\omega t - \theta_\phi + 120^\circ)$$

- In a balanced three-phase circuit, the total instantaneous power is invariant over time:



$$p_T = p_A + p_B + p_C = 1.5 \mathcal{V}_m I_m \cos \theta_\phi$$

- Hence the torque developed at the shaft of a three-phase motor is constant  $\Rightarrow$  less vibration in machinery powered by 3-phase motors.

31

## Measuring Power in 3-Phase Circuits

Electrodynamometer

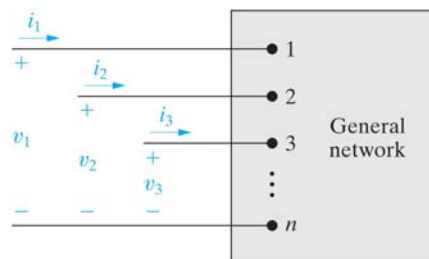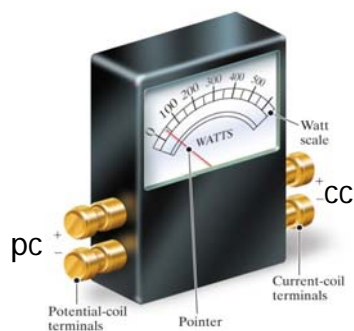

$$\text{Wattmeter Reading} = |\mathcal{V}| |I| \cos \theta$$

$\theta$ : Angle between  $\mathcal{V}$  and  $I$

n-1 wattmeters are needed for a network with n lines.

32



## The Two-Wattmeter Method

$$\begin{aligned} \mathcal{W}_1 &= |\mathcal{V}_{AB}| |I_{aA}| \cos \theta_1 \\ &= \mathcal{V}_L I_L \cos \theta_1 \\ \mathcal{W}_2 &= |\mathcal{V}_{CB}| |I_{cC}| \cos \theta_2 \\ &= \mathcal{V}_L I_L \cos \theta_2 \end{aligned}$$


➤ For an abc sequence:

$$\begin{aligned} \theta_1 &= \theta_\phi + 30^\circ \\ \theta_2 &= \theta_\phi - 30^\circ \end{aligned}$$

$\theta_\phi$ : phase angle between the phase voltage and current

➤ The total power is then given by:
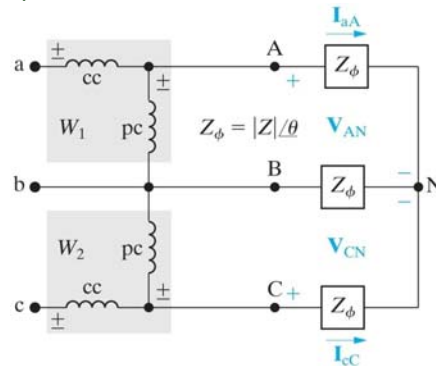
$$\mathcal{P}_T = \mathcal{W}_1 + \mathcal{W}_2 = \sqrt{3} \mathcal{V}_L I_L \cos \theta_\phi$$



33

## HOMEWORK - I

- Download and print the first homework assignment from Blackboard WebCT.
- Try to provide the answers on the printed pages without using extra pages. You can use both sides of the printed pages.
- Homework 1 is due on March 1, Tuesday, at the end of the class.
- Always be ready for a quiz on the due date of a homework or afterwards.


34

## Solution of QUIZ - I: A.1

$$\begin{aligned}
 \cos \mathcal{A} + \cos(\mathcal{A} - 240^\circ) + \cos(\mathcal{A} + 240^\circ) &= \cos \mathcal{A} \\
 &+ \cos(\mathcal{A})\cos 240^\circ + \sin(\mathcal{A})\sin 240^\circ \\
 &+ \cos(\mathcal{A})\cos 240^\circ - \sin(\mathcal{A})\sin 240^\circ \\
 &= \cos \mathcal{A} (1 + 2\cos 240^\circ) = \cos \mathcal{A} (1 + 2\cos(360^\circ - 120^\circ)) \\
 &= \cos \mathcal{A} \left( 1 + \underbrace{2\cos(360^\circ)}_1 \cos(120^\circ) + \underbrace{2\sin(360^\circ)}_0 \sin(120^\circ) \right) \\
 &= \cos \mathcal{A} (1 + 2\cos(90^\circ + 30^\circ)) \\
 &= \cos \mathcal{A} \left( 1 + \underbrace{2\cos(90^\circ)}_0 \cos(30^\circ) - \underbrace{2\sin(90^\circ)}_1 \underbrace{\sin(30^\circ)}_{1/2} \right) \\
 &= 0
 \end{aligned}$$

35

## Solution of QUIZ - I: A.2

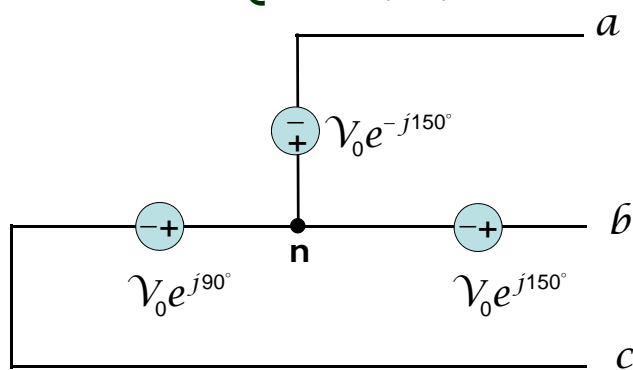

$$\begin{aligned}
 V_a &= -V_0 e^{-j150^\circ} = V_0 e^{j30^\circ} \\
 V_b &= +V_0 e^{j150^\circ} = V_0 e^{j150^\circ} \\
 V_c &= -V_0 e^{j90^\circ} = V_0 e^{-j90^\circ}
 \end{aligned}$$

Balanced 3-phase voltage source with acb (negative) phase sequence

36