

EE 213 ELECTRIC CIRCUITS II

Chapters 6 and 9 Mutual Inductance and Transformers


Dr. Hakan Köroğlu



Magnetically Coupled Circuits

- The circuits studied so far can be considered as **conductively coupled**, since loops affect each other by current conduction.
- When two loops with or without contact affect each other through magnetic fields, they are said to be **magnetically coupled**.
- The **transformer** is a device designed based on the concept of magnetic coupling.
- In preparation for the study of transformers, we will first make a brief recap of **self inductance** and then discuss the concept of **mutual inductance**.

Faraday's Law

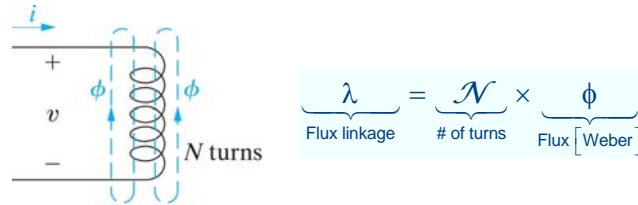

- Consider a coil of \mathcal{N} turns, through which a current i is flowing.
- **Faraday's Law:** The voltage induced in the coil is given by the rate-of-change of the flux linkage:

$$v(t) = \frac{d\lambda(t)}{dt} = \mathcal{N} \frac{d\phi(t)}{dt}$$

3

Self Inductance

- The magnitude of the flux is given by:
 $\phi = \mathcal{P} \times \mathcal{N} \times i$; \mathcal{P} : permeance of the field occupied by the flux
- The **permeance** is flux-dependent for magnetic materials (like iron, nickel, cobalt), whereas it is **constant** for **nonmagnetic** materials.
- When the core material of the coil is nonmagnetic:


$$v(t) = \mathcal{N} \frac{d\phi(t)}{dt} = \underbrace{\mathcal{N}^2 \mathcal{P}}_{\mathcal{L}} \times \frac{di(t)}{dt}$$

- The proportionality constant is the **self-inductance**:

$$\mathcal{L} = \mathcal{N}^2 \mathcal{P}$$

4

Magnetically-Coupled Coils

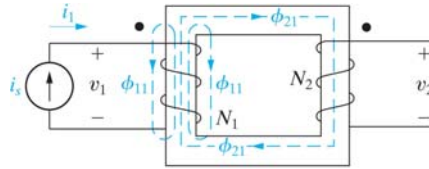

- Now consider two neighboring coils wound on a nonmagnetic core, with a current in the first one:


$$\underbrace{\phi_1}_{\text{total flux}} = \underbrace{\mathcal{P}_{11}\mathcal{N}_1}_{\phi_{11}: \text{flux linking coil-1}} \times i_1 + \underbrace{\mathcal{P}_{21}\mathcal{N}_1}_{\phi_{21}: \text{flux linking coil-2}} \times i_1 = \underbrace{(\mathcal{P}_{11} + \mathcal{P}_{21})}_{\mathcal{P}_1} \mathcal{N}_1 \times i_1$$

- Using Faraday's law, we find:

$$v_1(t) = \mathcal{N}_1 \frac{d\phi_1(t)}{dt} = \underbrace{\mathcal{N}_1^2 \mathcal{P}_1}_{\mathcal{L}_1} \frac{di_1(t)}{dt}; \quad v_2(t) = \mathcal{N}_2 \frac{d\phi_{21}(t)}{dt} = \underbrace{\mathcal{N}_2 \mathcal{N}_1 \mathcal{P}_{21}}_{\mathcal{M}_{21}} \frac{di_1(t)}{dt}$$

5

Mutual Inductance

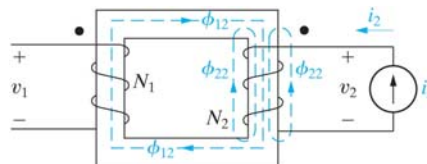

- When the current is fed to the second coil:

$$v_2(t) = \mathcal{N}_2 \frac{d\phi_2(t)}{dt} = \underbrace{\mathcal{N}_2^2 \mathcal{P}_2}_{\mathcal{L}_2} \frac{di_2(t)}{dt}; \quad v_1(t) = \mathcal{N}_1 \frac{d\phi_{12}(t)}{dt} = \underbrace{\mathcal{N}_1 \mathcal{N}_2 \mathcal{P}_{12}}_{\mathcal{M}_{12}} \frac{di_2(t)}{dt}$$

- For nonmagnetic core materials, we have:

$$\mathcal{P}_{12} = \mathcal{P}_{21} \Rightarrow \mathcal{M}_{12} = \mathcal{M}_{21} = \mathcal{M}$$

- \mathcal{L}_1 and \mathcal{L}_2 are the self inductances, whereas \mathcal{M} is the **mutual inductance** between the coils.

6

The Coefficient of Coupling

- Recall the inductance expressions:

$$\mathcal{L}_1 = \mathcal{N}_1^2 \mathcal{P}_1 \quad \text{and} \quad \mathcal{L}_2 = \mathcal{N}_2^2 \mathcal{P}_2 \Rightarrow \mathcal{L}_1 \mathcal{L}_2 = \mathcal{N}_1^2 \mathcal{N}_2^2 \mathcal{P}_1 \mathcal{P}_2$$

- For nonmagnetic core materials, we have:

$$\mathcal{P}_{21} = \mathcal{P}_{12} \quad \mathcal{L}_1 \mathcal{L}_2 = \underbrace{(\mathcal{N}_1 \mathcal{N}_2 \mathcal{P}_{12})^2}_{\mathcal{M}^2} \underbrace{\left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)}_{1/\mathcal{K}}$$


- Coupling is quantified by the **coefficient of coupling**:

$$\mathcal{K} = \sqrt{\left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)}^{-1/2} \in [0, 1]; \quad \mathcal{M} = \mathcal{K} \sqrt{\mathcal{L}_1 \mathcal{L}_2}$$

$\mathcal{K} \in (0.5, 1)$: tightly coupled; $\mathcal{K} \in (0, 0.5)$: loosely coupled

7


Voltage Polarity and the Dot Convention

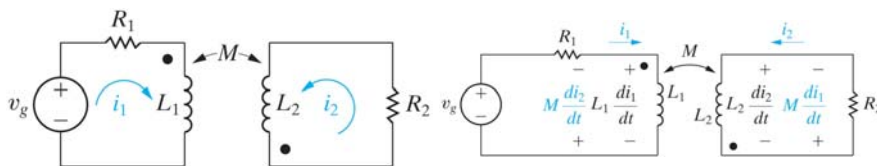

- The polarity of self-induced voltage is identified from the direction of the current.
- The polarity of the mutually-induced voltage is identified based on the dot convention.
- **Dot convention:** When the current enters (leaves) the dotted terminal of a coil, the polarity of the voltage it induces in the other coil is positive (negative) at its dotted terminal.

8

Application of the Dot Convention

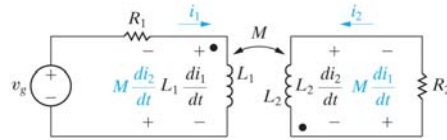


- The easiest way to analyze circuits containing mutual inductance is to use mesh currents.
- KVL is then applied with the addition of the mutually induced voltage with appropriate polarity:

$$v_g = R_1 i_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$0 = R_2 i_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

9


Equivalent Circuit for Mutual Inductance

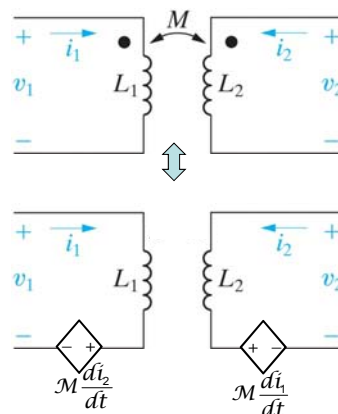

- The dependent source voltages are determined by the derivatives of the currents. The polarities of the sources are identified from the dot convention.

10

Example: Mesh Current Equations

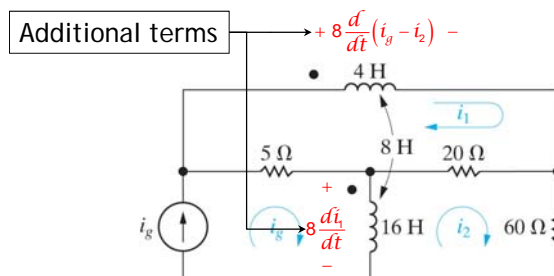


$$i_1 \text{ mesh} : 4 \frac{di_1}{dt} + 8 \frac{d}{dt}(i_g - i_2) + 20(i_1 - i_2) + 5(i_1 - i_g) = 0$$

$$i_2 \text{ mesh} : 20(i_2 - i_1) + 60i_2 + 16 \frac{di_2}{dt}(i_2 - i_g) - 8 \frac{di_1}{dt} = 0$$

11


Procedure for Determining Dot Markings

- Arbitrarily select and mark a terminal, say D, with a dot.
- Assign a current i_D to it.
- Determine the direction of the induced magnetic flux, ϕ_D , based on the right-hand rule.
- Arbitrarily pick a terminal of the second coil, say A, and apply the same steps again.
- If the directions ϕ_A and ϕ_D are the same, then place a dot on A.
- If the directions are opposite, place a dot on the other terminal.

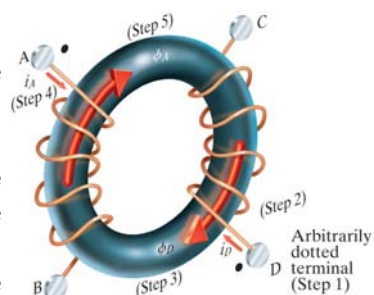

12


Experimental Setup for Dot Marking

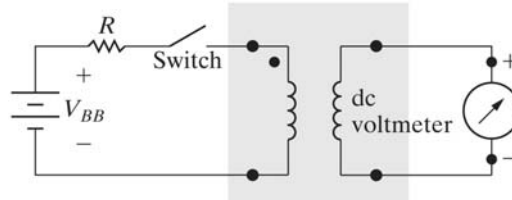

- Put a dot on the terminal to which the resistor is connected.
- Observe the momentary deflection of the DC voltmeter when the switch is closed.
- If it is upscale/downscale, put a dot on the terminal connected to the positive/negative terminal of the voltmeter.

13

Energy Calculations

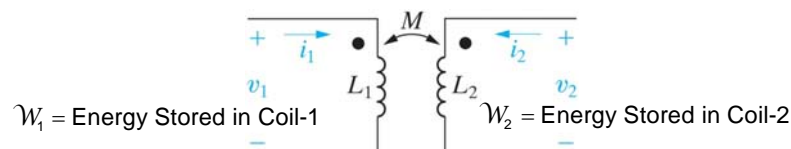

- Assume zero initial energy.
- Increase i_1 from zero to I_1 :

$$W_1^1 = \int_{i_1=0}^{i_1=I_1} i_1 \cdot L_1 \frac{di_1}{dt} dt = \int_0^{I_1} L_1 i_1 di_1 = \frac{1}{2} L_1 I_1^2; \quad W_2^1 = 0$$

- Keep $i_1 = I_1$ constant; increase i_2 from zero to I_2 :

$$W_1^2 = \int_{i_2=0}^{i_2=I_2} I_1 \cdot \mathcal{M}_{12} \frac{di_2}{dt} dt = I_1 I_2 \mathcal{M}_{12}; \quad W_2^2 = \int_{i_2=0}^{i_2=I_2} i_2 \cdot L_2 \frac{di_2}{dt} dt = \frac{1}{2} L_2 I_2^2$$

- Total energy stored in the coils:

$$W = W_1^1 + W_1^2 + W_2^1 + W_2^2 = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + \mathcal{M}_{12} I_1 I_2$$

14

Total Energy Stored in the Coils

- Total energy stored in the coils at time t (with the dot marking not specified) :

$$\mathcal{W}(t) = \frac{1}{2} \mathcal{L}_1 \dot{i}_1^2(t) + \frac{1}{2} \mathcal{L}_2 \dot{i}_2^2(t) \pm \mathcal{M}_{12} \dot{i}_1(t) \dot{i}_2(t)$$

- When the order of the procedure is reversed:

$$\mathcal{W}(t) = \frac{1}{2} \mathcal{L}_1 \dot{i}_1^2(t) + \frac{1}{2} \mathcal{L}_2 \dot{i}_2^2(t) \pm \mathcal{M}_{21} \dot{i}_1(t) \dot{i}_2(t)$$

- For linear coupling media $\mathcal{M}_{12} = \mathcal{M}_{21} = \mathcal{M}$, which means that the total energies stored are the same.
- Determining the sign: If both currents are entering or leaving the dotted terminals, then the sign is positive; otherwise the sign is negative.

15

Positivity of the Total Energy

- Consider finding the i_2 that minimizes \mathcal{W} :

$$\begin{aligned} \mathcal{W}(i_2) &= \frac{1}{2} \mathcal{L}_1 i_1^2 + \frac{1}{2} \mathcal{L}_2 i_2^2 \pm \mathcal{M} i_1 i_2 \\ \Rightarrow \frac{d\mathcal{W}(i_2)}{di_2} &= \mathcal{L}_2 i_2 \pm \mathcal{M} i_1 \quad \text{and} \quad \frac{d^2\mathcal{W}(i_2)}{di_2^2} = \mathcal{L}_2 > 0 \end{aligned}$$

- Equate the first derivative to zero find the minimum:

$$\mathcal{L}_2 i_2^\circ \pm \mathcal{M} i_1 = 0 \Rightarrow i_2^\circ = \mp \frac{\mathcal{M}}{\mathcal{L}_2} i_1 = \mp k \sqrt{\frac{\mathcal{L}_1}{\mathcal{L}_2}} i_1$$

- Since the energy is \geq its minimum value, we have:

$$\mathcal{W}(i_2) \geq \mathcal{W}(i_2^\circ) = \frac{1}{2} \mathcal{L}_1 i_1^2 + \left(\frac{1}{2} \mathcal{L}_2 i_2^\circ \pm \mathcal{M} i_1 \right) i_2^\circ = \frac{1}{2} (1 - k^2) \mathcal{L}_1 i_1^2 \geq 0$$


16

Transformers

- Transformer is a device based on magnetic coupling.
- In communication circuits, transformers are used to match impedances and eliminate DC signals.
- In power circuits, transformers are used to establish AC voltage levels that facilitate the transmission, distribution and consumption of electrical power.
- We will first analyze the steady-state behavior of the **linear transformer**, which is common in communication systems.
- We will then study the **ideal transformer**, which models the ferromagnetic transformer used in power systems.

17


The Linear Transformer

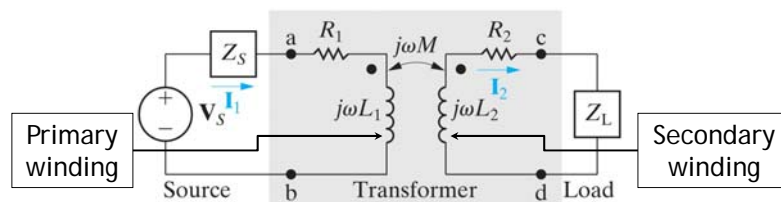

R_1	Resistance of the primary winding
R_2	Resistance of the secondary winding
L_1	Self-inductance of the primary winding
L_2	Self-inductance of the secondary winding
\mathcal{M}	Mutual inductance
\mathcal{V}_s	Source voltage
Z_s	Source impedance
Z_L	Load impedance
I_1	Primary current
I_2	Secondary current

18

Analysis of a Linear Transformer

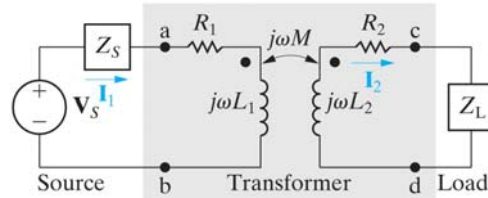

➤ Phasor analysis is adapted easily: $dx/dt \leftrightarrow j\omega \times \mathcal{X}$

$$\underbrace{(Z_s + R_1 + j\omega L_1)}_{Z_{11}} I_1 - j\omega M I_2 = V_s$$

Z_{11} ← Self impedance of the primary


$$\underbrace{(Z_L + R_2 + j\omega L_2)}_Z I_2 - j\omega M I_1 = 0$$

Z ← Self impedance of the secondary

$$\square \quad I_2 = \frac{j\omega M}{Z} I_1 \quad \text{and} \quad I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

19

The Impedance Seen by the Source

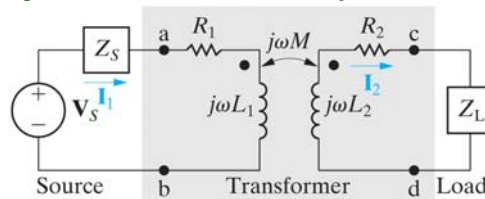

➤ The impedance seen from the nodes a and b is:

$$Z_{ab} = \frac{V_s}{I_1} - Z_s = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

Z_r : Reflected impedance

➤ A key role of the transformer is thus revealed:
Changing the impedance seen by the source:

$$Z_L \rightarrow Z_{ab} = R_1 + j\omega L_1 + Z_r(Z_L)$$

20

The Reflected Impedance

- Impedance of the second coil plus load is transmitted to the primary side via the mutual inductance:

$$Z_r = \frac{\omega^2 \mathcal{M}^2}{\mathcal{R}_2 + j\omega \mathcal{L}_2 + Z_L}$$

- When the load impedance is $Z_L = \mathcal{R}_L + j\mathcal{X}_L$, we have:


$$Z_r = \frac{\omega^2 \mathcal{M}^2}{(\mathcal{R}_2 + \mathcal{R}_L)^2 + (\omega \mathcal{L}_2 + \mathcal{X}_L)^2} [(\mathcal{R}_2 + \mathcal{R}_L) - j(\omega \mathcal{L}_2 + \mathcal{X}_L)]$$

Scaling Factor

- The impedance is thus conjugated and then scaled during the reflection.

21

Example: Linear Transformer Circuit

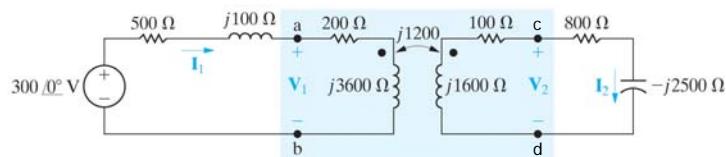


- Scaling factor:
$$= \frac{1200^2}{|800 + 100 + 1600j - 2500j|^2} = \frac{1200^2}{|900 + 900j|^2} = \frac{1200^2}{900^2 + 900^2} = \frac{8}{9}$$
- Reflected impedance:
$$= \frac{8}{9}(900 + 900j) = 800 + 800j \Omega$$
- Impedance seen from a - b:
$$= 200 + 3600j + 800 + 800j = 1000 + 4400j \Omega$$
- Thevenin equivalent seen from c - d:

$$Z_{th} = 100 + 1600j + \frac{1200^2}{700^2 + 3700^2} (700 - 3700j)$$

$$= 171.09 + 1224.26j \Omega$$


$$V_{th} = 1200j \times \frac{300}{500 + 200 + (100 + 3600)j}$$

$$= 95.6 \angle 10.71^\circ \text{ V}$$

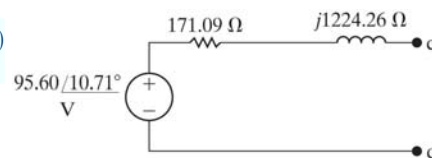

22

The Ideal Transformer

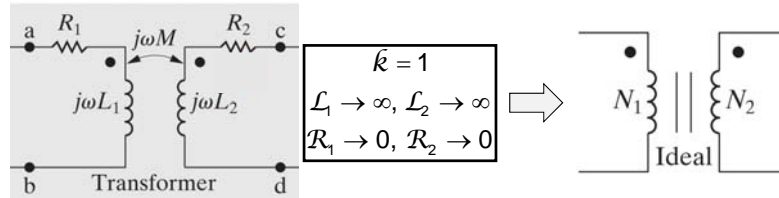


➤ An ideal transformer consists of two magnetically coupled coils having N_1 and N_2 turns respectively, and exhibiting the following three properties:

- ❑ The coefficient of coupling is unity.
- ❑ The self-inductance of each coil is infinite.
- ❑ The coil losses, due to parasitic resistances, are negligible.

23

Analysis of the Limit Values

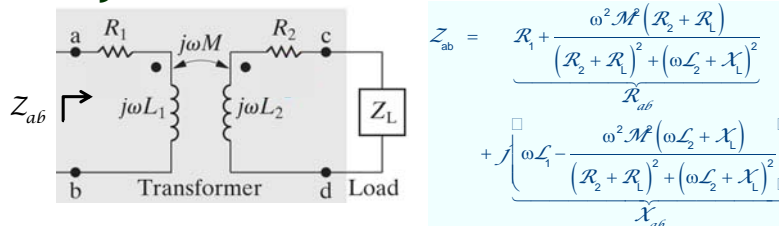

$$Z_{ab} = \mathcal{R}_{ab} + j\mathcal{X}_{ab}$$

$$\mathcal{R}_{ab} = R_1 + \frac{\omega^2 \mathcal{M}^2 (R_2 + \mathcal{R}_L)}{(R_2 + \mathcal{R}_L)^2 + (\omega \mathcal{L}_2 + \mathcal{X}_L)^2}$$

$$\mathcal{X}_{ab} = \omega \mathcal{L}_1 - \frac{\omega^2 \mathcal{M}^2 (\omega \mathcal{L}_2 + \mathcal{X}_L)}{(R_2 + \mathcal{R}_L)^2 + (\omega \mathcal{L}_2 + \mathcal{X}_L)^2}$$

➤ Setting $\mathcal{M}^2 = \mathcal{L}_1 \mathcal{L}_2$ and letting $\mathcal{L}_1 \rightarrow \infty$, $\mathcal{L}_2 \rightarrow \infty$, we find:

$$\mathcal{R}_{ab} = R_1 + \left[\frac{\mathcal{L}_1}{\mathcal{L}_2} \right] \frac{(R_2 + \mathcal{R}_L)}{(R_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2)^2 + (1 + \mathcal{X}_L / (\omega \mathcal{L}_2))^2} \rightarrow R_1 + \left[\frac{\mathcal{L}_1}{\mathcal{L}_2} \right] (R_2 + \mathcal{R}_L)$$


$$\mathcal{X}_{ab} = \left[\frac{\mathcal{L}_1}{\mathcal{L}_2} \right] \frac{(R_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2)^2 + \mathcal{X}_L + \mathcal{X}_L^2 / (\omega \mathcal{L}_2)^2}{(R_2 + \mathcal{R}_L)^2 / (\omega \mathcal{L}_2)^2 + (1 + \mathcal{X}_L / (\omega \mathcal{L}_2))^2} \rightarrow \left[\frac{\mathcal{L}_1}{\mathcal{L}_2} \right] \mathcal{X}_L$$

➤ As $\mathcal{K} \rightarrow 1$, the two permeances \mathcal{L}_1 , \mathcal{L}_2 become equal:

$$\frac{\mathcal{L}_1}{\mathcal{L}_2} = \frac{\mathcal{N}_1^2 \mu_1}{\mathcal{N}_2^2 \mu_2} \rightarrow \left(\frac{\mathcal{N}_1}{\mathcal{N}_2} \right)^2 = a^2; \quad a: \text{turns ratio}$$

24

Ideal Transformer Relations

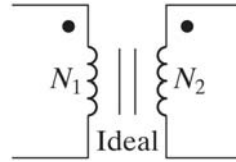

- The voltages of the primary and secondary windings of an ideal transformer are related as:

$$\left| \frac{\mathcal{V}_1}{\mathcal{N}_1} \right| = \left| \frac{\mathcal{V}_2}{\mathcal{N}_2} \right|$$


- The currents of the primary and secondary windings of an ideal transformer are related as:

$$|I_1 \mathcal{N}_1| = |I_2 \mathcal{N}_2|$$

- The polarities are determined via the dot convention.

25

Determining the Voltage-Current Ratios

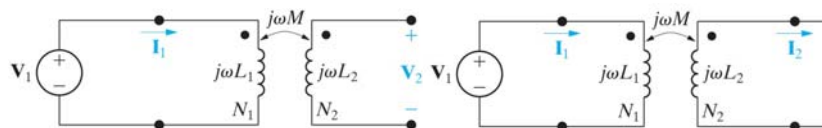

- The voltage ratio is determined using the left circuit:

$$\text{Since } I_2 = 0, \text{ we have } \mathcal{V}_2 = j\omega \mathcal{M} I_1 = \frac{j\omega \mathcal{M}}{j\omega L_1} \mathcal{V}_1.$$

$$\text{With } \mathcal{M} = \sqrt{L_1 L_2}, \text{ it follows that } \frac{\mathcal{V}_1}{\mathcal{V}_2} = \sqrt{\frac{L_1}{L_2}} = \sqrt{\frac{\mathcal{N}_1^2 \mathcal{P}}{\mathcal{N}_2^2 \mathcal{P}}} = \frac{\mathcal{N}_1}{\mathcal{N}_2}.$$


- The current ratio is determined using the right circuit:

$$\text{Since } \mathcal{V}_2 = 0, \text{ we have } j\omega \mathcal{M} I_1 - j\omega L_2 I_2 = 0.$$

$$\text{With } \mathcal{M} = \sqrt{L_1 L_2}, \text{ it follows that } \frac{I_1}{I_2} = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{\mathcal{N}_2^2 \mathcal{P}}{\mathcal{N}_1^2 \mathcal{P}}} = \frac{\mathcal{N}_2}{\mathcal{N}_1}.$$

26


Determining the Polarities

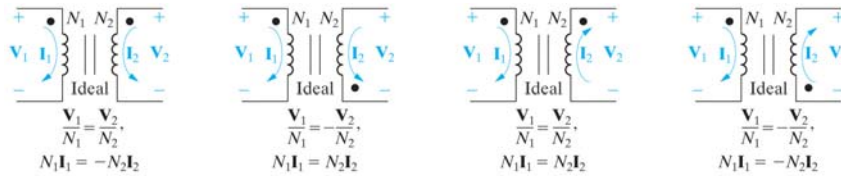

- If the coil voltages are both positive or negative at the dot-marked terminal, use a plus sign in the voltage ratio; otherwise, use a minus sign.
- If the coil currents are both directed into or out of the dot-marked terminal, use a minus sign in the current ratio; otherwise, use a plus sign.

27

Ideal Transformer for Impedance Matching

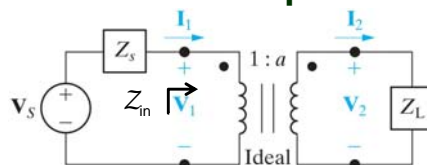

- The ideal transformer relations are:

$$V_1 = \frac{V_2}{a} \quad \text{and} \quad I_1 = aI_2$$


- Then the impedance seen by the practical source is:

$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2} = \frac{1}{a^2} Z_L$$

- The practical version of the ideal transformer is the ferromagnetic core transformer. It is used to match the magnitude of Z_L to the magnitude of Z_s .

28

Example: Ideal Transformer Circuit

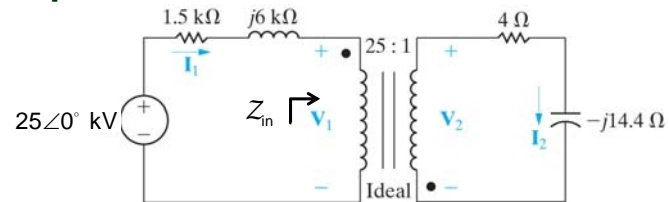

- $Z_{in} = (25)^2 (4 + j14.4) = 2.5 - j9 \text{ k}\Omega$
- $V_1 = \frac{2.5 - j9.0}{4.0 - j3.0} 25 \text{ kV} = 46\,703.85 \angle -37.61^\circ$
- $V_2 = -V_1 / 25 = 1868.15 \angle 142.39^\circ$
- $I_2 = \frac{25 \text{ kV}}{4 - j3} \times 25 = 125 \angle 36.87^\circ$