

King Fahd University of Petroleum & Minerals
Electrical Engineering Department
EE-407; Final Exam.

Prob.1	Prob.2	Prob.3	Prob.4	Prob.5	Total

Answer all the four questions. TIME : 2 hour 30 minutes.

Name:

I.D.

Sec.

Q.1(a) If a 10 GHz wave is propagating through a material with $\mu_r = 11$ and $\sigma = 5.11 \times 10^7$ Mhos/m, find the related

- (i) Skin depth
- (ii) Surface resistance (assume the material is of square shape).


GIVEN: $\mu_0 = 1.2566 \times 10^{-6}$; $\epsilon_0 = 8.84194 \times 10^{-12}$

Q.1(b) The characteristic impedance of a transmission line is $Z_0 = 100 \Omega$. If it is terminated in a load of $Z_L = 100 + j100 \Omega$ and the propagation constant of the line is $0.54 + j3.53$ per meter, calculate (without using the smith chart);


- (i) The transmission coefficient on the line
- (ii) The reflection coefficient at a point 2 meter away from the load.

Q.2 (a) In the figure, all the transmission lines are loss-free and with $\lambda \neq \lambda_0$. If the impedance at junction **AA'** is 75Ω , find the propagation constant (γ).

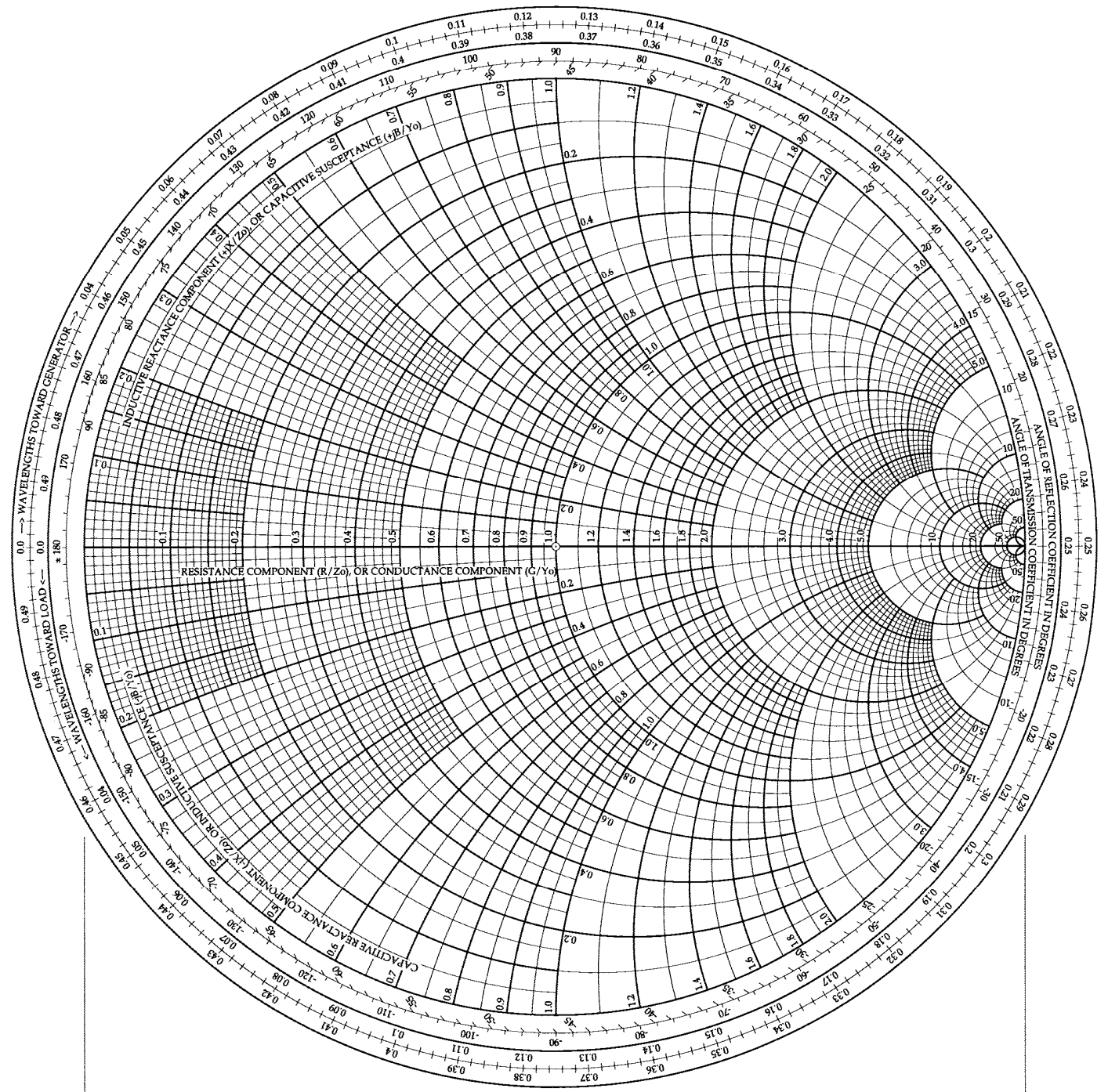Q.2 (b) A load impedance of $Z_L=70\Omega$ has to be matched to a 50Ω line using a parallelly connected shorted-circuited single-stub matching, as illustrated in figure. Use smith-chart to determine the shortest required **length** l_1 and l_2 in fractions (terms) of wavelengths.



RADIALLY SCALED PARAMETERS

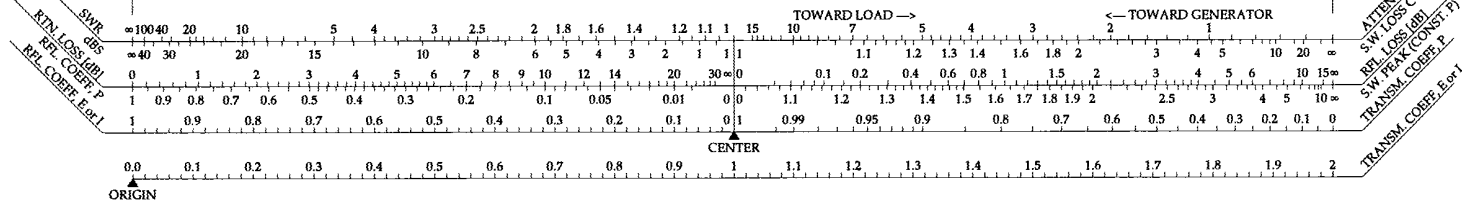

ATTN. LOSS
SWR LOSS COEFF
REFL. LOSS (dB)
SWR REFL. COEFF
TRANSM. COEFF. P or V

Q.3 (a) A microstrip quarter-wavelength-transformer is to match a transistor input with a $50\ \Omega$ microstrip feed line. If the transformer has $w = 0.762\ \text{mm}$, $h = 0.635\ \text{mm}$, $t = 0.035\ \text{mm}$ and $\epsilon_r = 10$. If the circuit is operating at a frequency of **3 GHz**, calculate the

- (i) Effective dielectric-constant of the transformer.
- (ii) The impedance of the transformer.

Q.3(b) The scattering parameter for transistor is given by: $S_{11}=0.65\angle-140^\circ$;
 $S_{21}=2.4\angle50^\circ$; $S_{12}=0.04\angle60^\circ$; $S_{22}=0.70\angle-65^\circ$. The transistor is used in a
common-source amplifier at $f=4$ GHz. The signal source can be represented
by a $10\mu\text{V}$ EMF in series with a 50Ω resistance, and the load is 50Ω . Find

- (i) Determine the stability of the device
- (ii) Calculate the total gain
- (iii) Show how to apply DC biasing of an Microwave transistor

Q.4(a) Briefly describe the difference between Ohmic contact and Schottky contact.

Q.4(b) Using microstrip stepped impedance technology, design a maximally flat low pass filter (that begins with shunt element) with passband of 0 to 3 GHz and an attenuation of 20dB at 5 GHz. Assume $Z_0=50 \Omega$ and for the microstrip $Z_1=15 \Omega$, $Z_h=150 \Omega$, $\epsilon_r=4.2$, $h=0.79$ mm, $t=0$ to find

- (i) Scaled values of the reactive elements and **draw** the circuit.
- (ii) The electrical length of the 1st **two elements** of the filter.