

Date: March 18, 2007

Term: 062

Quiz # 2

SR # _____

ID # _____

Name: _____

Sec # 4

For the circuit shown below, **find** the following:

- The **voltage v** .
- The **power** of the current **source**.
- The **current i_o** .

