

# King Fahd University of Petroleum and Minerals

Electrical Engineering Department

EE 208: Electrical Systems

Instructor: Umar M. Johar


## Home Work # 4

1. The current across a  $0.5H$  inductor is given by:

$$i_s = \begin{cases} 0 & t < -1 \text{ \& } t \geq 1 \\ 1 - t^2 & -1 \leq t < 1 \end{cases}$$

Find:  $i_L(t)$ ,  $p(t)$ ,  $w_L(t)$  and plot them.

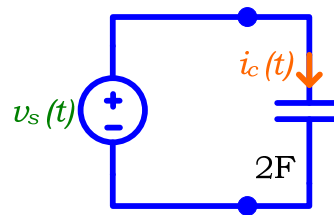
2. For the circuit shown, if the voltage  $v_s(t) = 3e^{-5t}$  [V] for  $t \geq 0$ ,
- find  $i_c(t)$  for  $t \geq 0$ .
  - find the energy stored in the capacitor for  $t \geq 0$ .



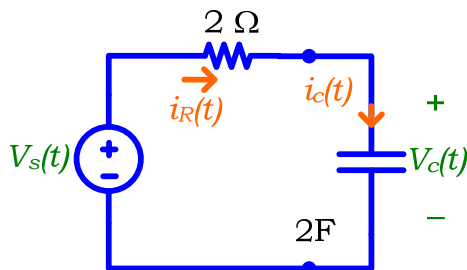
3. The voltage across the capacitor in the circuit below is given by:

$$v_c(t) = \begin{cases} 0 & , \ t \leq 0 \\ 3t & , \ 5 \geq t > 0 \\ -3t + 30 & , \ 5 \leq t < 10 \\ 0 & , \ t > 10 \end{cases}$$


Find:  $i_c(t)$ ,  $v_s(t)$  and  $w_c(t)$



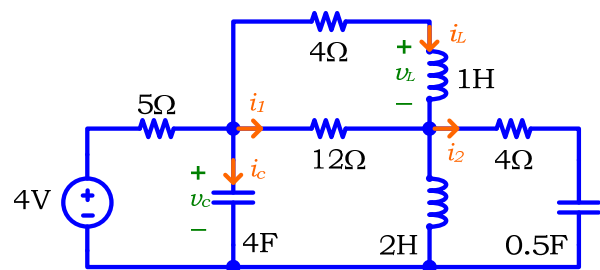4. For the circuit shown, calculate the unknown quantities.



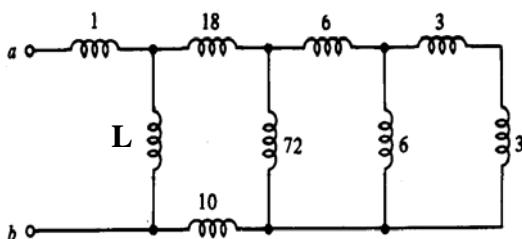5. If the **value of L** is equal to the equivalent inductance at terminals a & b, **find the equivalent inductance.**



6. In the circuit shown below, what **value of R** will make the **energy** stored in the **inductor** and the **capacitor** equal?

