

# King Fahd University of Petroleum and Minerals


Electrical Engineering Department

EE 208: Electrical Systems

*Instructor: Umar M. Johar*


## Home Work # 4

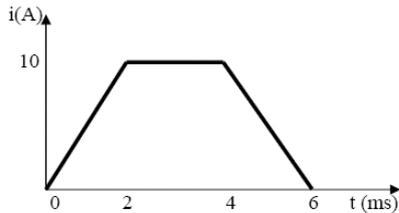1. The current through a 5-mH inductor is shown below. **Determine the voltage** across the inductor at  $t=1, 3,$  and  $5\text{ms}$ .




2. Determine the current through a  $20\text{-}\mu\text{F}$  capacitor, knowing that it has an energy given by  $W(t) = 10\cos^2(377t) \text{ J}$ .

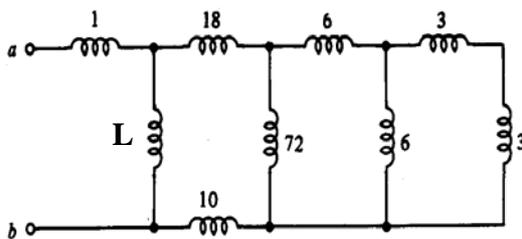3. Find the **value of L**, if the equivalent inductance at terminals a & b is  $6\text{H}$ .



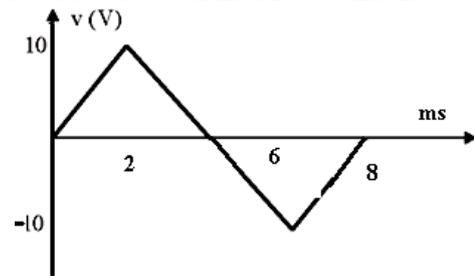
4. The voltage across a  $4\text{-}\mu\text{F}$  capacitor is shown below. **Find its current**.



5. Find the **values of R and C** in the circuit shown below knowing the voltage and the current are given by:

$$v(t) = 56e^{-200t} \text{ V}, t > 0$$

$$i(t) = 8e^{-200t} \text{ mA}, t > 0$$

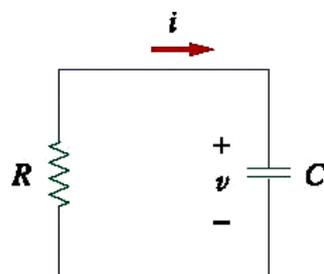

6. Find  $V_s(t)$  knowing that the current through the inductor in the circuit below is given by:

$$i_L = \begin{cases} 0 & t < -1 \text{ \& } t \geq 1 \\ 1 - t^2 & -1 \leq t < 1 \end{cases}$$

