

PROBLEMS

- 16.1** Find the transit time of a pulse through 15 m of RG-59/U coaxial cable.
- 16.2** Describe a convenient method of measuring the characteristic impedance of a coaxial cable by varying its termination conditions.
- 16.3** For each instance cited below, determine whether termination to prevent cable reflections is potentially needed.
- (a) Transmission of 0.5 μ s rise time pulses through 20 m of RG-59/U cable.
 - (b) Transmission of a 10 ns rise time pulse through 10 m of RG-62/U cable.
- 16.4** (a) Fast pulses are to be transmitted from a source with output impedance of 50 Ω to another component with input impedance of 1 k Ω . Choose one of the coaxial cable types listed in Table 16.1, and show the termination conditions required to avoid cable reflections at either end.
- (b) If the output pulse amplitude from the source without any load attached is 5 V, find the amplitude that appears across the input of the second component after the termination required in part (a).
- 16.5** Find the resistance values R_1 and R_2 in the T-attenuator network of Fig. 16.5 if an attenuation factor of 10 is needed while preserving a 50- Ω impedance level.
- 16.6** Prove that the resistance values in the pulse splitter of Fig. 16.6 should be 16.6 Ω in order to distribute a pulse to two 50- Ω loads while maintaining a 50- Ω impedance level.
- 16.7** Pulses from a preamplifier are produced with exponential tails with 50- μ s time constant. What is the minimum spacing between adjacent pulses so that amplitude change due to pile-up is less than 1%?
- 16.8** An input voltage of the form $V(t) = E[1 - \exp(-t/k)]$, where E and k are constants, is supplied to a simple RC integrator circuit. Derive the form of the output voltage.
- 16.9** A differentiator circuit has component values of $C = 500$ pF and $R = 500$ Ω . Find the frequency of a sinusoidal input voltage that will be attenuated by a factor of 2 by the circuit.
- 16.10** A step voltage of 1 V amplitude is applied to the input of a CR-RC differentiator-integrator network with equal time constants. What is the amplitude of the shaped pulse?
- 16.11** Derive Eq. (16.22) for the response of a CR-RC network to a step voltage input by using Eq. (16.12) as the input waveform to the RC stage.
- 16.12** What is the principal advantage of bipolar shaped pulses over monopolar shaped pulses?
- 16.13** What property of the detector is reflected in the rise time of the tail pulse obtained by a large time-constant collection circuit?
- 16.14** Pulses from a detector are shaped to produce monopolar pulses of approximately triangular shape with 10 V amplitude and width of 5 μ s. Find the average value of the baseline shift after these pulses are passed through a capacitor if the pulse rate is 100/s. Repeat for a rate of 50,000/s.
- 16.15** Sketch the result of shaping a rectangular monopolar pulse of 200 ns width by using a shorted stub of RG-59/U of 10-m length.