

### Quiz # 8 Ch.#27 T131-Sec. 7-9-v1

Student ID:..... Student Name:..... Section # .....

Q#1 In the circuit of Figure:  $\varepsilon = 30 \text{ V}$ , and the resistance of each resistor is  $10 \Omega$ . What is the potential difference  $V_A - V_B$ ? A)  $-20 \text{ V}$


$$V_B - i_0 R = V_A \Rightarrow V_A - V_B = -i_0 R$$

For.  $i_0$  calculations

$$\varepsilon - i_0 \left( R + \frac{R}{2} \right) = \varepsilon - i_0 \times \frac{3R}{2} = 0$$

$$i_0 = \frac{2\varepsilon}{3R} = \frac{2 \times 30}{3 \times 10} = 2 \text{ A}$$
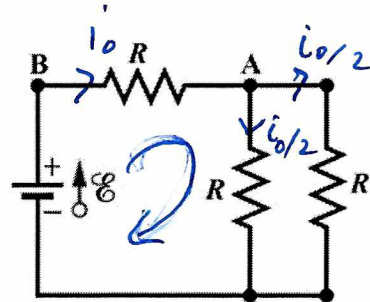
$$V_A - V_B = -i_0 R = -2 \times 10 = -20 \text{ V}$$



4  
4


Q#2 Find the value of  $R_1$  in the circuit of figure (5). (Ans: A)  $6.0 \text{ ohms}$ .

$$i_0 = 2 + 3 = 5 \text{ A}$$

in the loop ①

$$50 - i_0 R_1 - 20 = 0$$
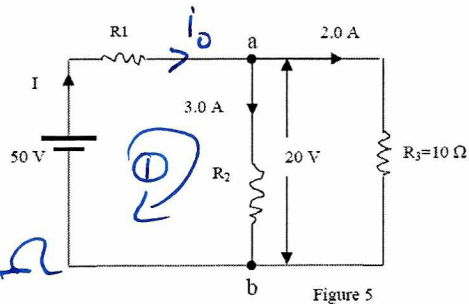
$$R_1 = \frac{20 - 50}{-i_0} = \frac{-30}{-5} = 6 \Omega$$



3  
3

Q#3: A capacitor of  $4 \times 10^{-3} \text{ F}$  capacitance is discharged through a  $4 \text{ k}\Omega$  resistor. How long will it take for the capacitor to lose half its initial stored energy? A)  $5.5 \text{ s}$

$$U(t) = \frac{1}{2} C V(t)^2 = \frac{1}{2} C V_0^2 e^{-\frac{2t}{RC}} = U_0 e^{-\frac{2t}{RC}}$$

$$\frac{U(t)}{U_0} = \frac{1}{2} = e^{-\frac{2t}{RC}} \Rightarrow \ln\left(\frac{1}{2}\right) = -\frac{2t}{RC}$$

$$t = -\frac{RC}{2} \ln\left(\frac{1}{2}\right) = -\frac{4 \times 10^3 \times 4 \times 10^{-3}}{2} \times \ln\left(\frac{1}{2}\right)$$

$$t = -8 \times \ln\left(\frac{1}{2}\right) = 5.55 \text{ s}$$

4  
4

**Quiz # 8 Ch.#27 T131-Sec. 7-9-v2**

Student ID:..... Student Name:..... Section # .....

Q#1 In the circuit shown in figure 1, calculate potential difference  $V_B - V_A$ . The points A, B and C are three junctions. [Take the current  $I = 2.0$  A] (Ans: A) 8.0 V.

$$V_A - 3I + 6 + 2I + 4 = V_B$$

$$V_B - V_A = -3I + 6 + 2I + 4$$

$$= -I + 10$$

$$= -2 + 10 = 8.0 \text{ V}$$

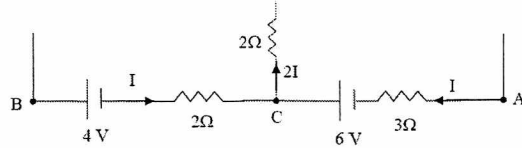


Figure (1)

Q#2: In the circuit shown in figure 4,  $I = 0.65$  A and  $R = 15$  Ohms. What is the value of the emf of the battery? (Ans: A) 39 V

$$\Sigma - 2IR - 2IR = 0$$

$$\Sigma - 4IR = 0$$

$$\Sigma = 4IR$$

$$= 4 \times 0.65 \times 15$$

$$\Sigma = 39 \text{ V}$$

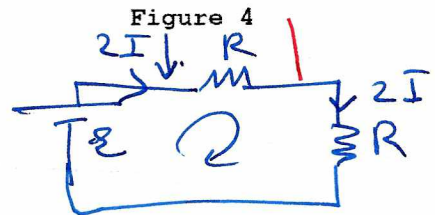
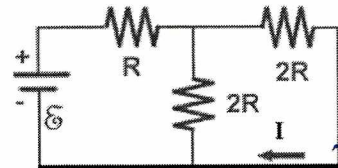


Figure 4

Q#3: Initially, for the circuit shown in Figure 5, the switch S is open and the capacitor is uncharged. The switch S is closed at time  $t = 0$ . At what time will the current be half its initial value? (12.5 s)


$$i(t) = \frac{\Sigma}{R} e^{-t/RC} = i_0 e^{-t/RC}$$

$$\frac{i(t)}{i_0} = e^{-t/RC} \Rightarrow \ln\left(\frac{i(t)}{i_0}\right) = -t/RC$$

$$\ln\left(\frac{1}{2}\right) = -\frac{t}{RC}$$

$$t = -RC \ln\left(\frac{1}{2}\right) = -3 \times 10^5 \times 60 \times 10^{-6} \ln\left(\frac{1}{2}\right)$$
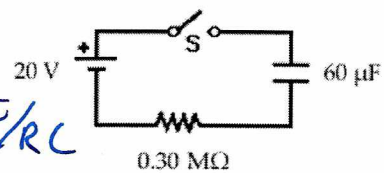
$$t = -18 \ln\left(\frac{1}{2}\right) = 12.47 \text{ s}$$



Quiz # 8 Ch.#27 T131-Sec. 7-9-v3

Student ID:..... Student Name:..... Section # .....

Q#1: Three resistors are connected as shown in figure 3. The potential difference between points A and B is 26 V. How much current flows through the 4-Ohm resistor? A) 2.0 A)

at Junction C  $I = I_2 + I_4$   
 but  $I \times 3 + I \times \frac{2 \times 4}{2+4} = 26$   
 $I(3 + \frac{8}{6}) = 26 \Rightarrow I = \frac{26}{4.33} = 6.0 \text{ A}$

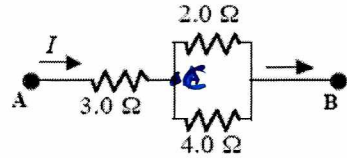


Figure 3

4/4

Then  $I_4 \times 4 = (I - I_4) \times 2$   
 $4I_4 = 2I - 2I_4 \Rightarrow 6I_4 = 2I$   
 $I_4 = \frac{2}{6}I = \frac{2}{6} \times 6 = 2.0 \text{ A}$

Q#2: In the circuit shown in figure 5, what is the current in the 8.00-Ohm resistor? A) 2.25 A to the left

Considering the outer most loop  
 $3 \times 4 - I_8 \times 8 - 5 \times 6 = 0$

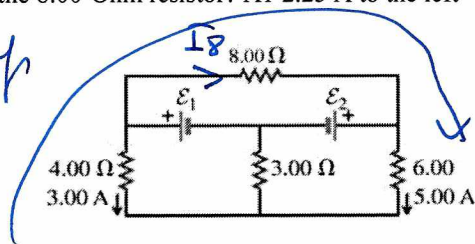


Figure 5

3/3

$8I_8 = 12 - 30 = -18$   
 $I_8 = -\frac{18}{8} = -2.25 \text{ A}$   
 2.25 A to the left.

Q#3 A 5.0 μF capacitor is fully charged by connecting it to a 12-V battery. After disconnecting the battery, it was allowed for capacitor to discharge through a simple RC circuit, with a time constant of 4.0 s. What is the charge on the capacitor after one time constant has elapsed? (Ans: A)  $2.2 \times 10^{-5}$  C)


4/4

$q(t) = q_0 e^{-t/RC} = q_0 e^{-t/\tau} = q_0 e^{-1}$   
 $\frac{q(t)}{q_0} = e^{-1} \Rightarrow q(t) = e^{-1} q_0 = 0.368 \times q_0$   
 $q_0 = C V_0 = 5 \times 10^{-6} \times 12 \text{ C}$   
 $q(t) = 0.368 \times q_0 = 0.368 \times 5 \times 10^{-6} \times 12 = 2.2 \mu\text{C}$   
 $= 2.2 \times 10^{-5} \text{ C}$

**Quiz # 8 Ch.#27 T131-Sec. 7-9-v4**

Student ID:..... Student Name:..... Section # .....

Q1 In the figure shown, the potential difference between point 1 and 2, ( $V_2 - V_1$ ), is -40 V, and the current is equal to 4.0 A, then, the value of the resistance R is : (Ans: 3.0  $\Omega$ .)
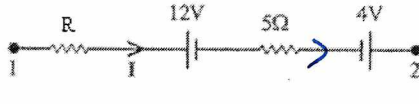
$$V_1 - IR - 12 - 5I + 4 = V_2$$


4  
4

$$-IR = (V_2 - V_1) + 12 + 5I - 4$$

$$IR = -40 + 12 + 5 \times 4 - 4 = 12$$

$$R = \frac{12}{I} = \frac{12}{4} = 3 \Omega$$

Q#2: In Fig. 4,  $I = 0.5$  A and  $R = 12 \Omega$ . What is the value of the emf  $\epsilon$ ? (A) 24 V


$$\Sigma = 2IR - 2IR = 0$$

$$\Sigma - 4IR = 0$$

$$\Sigma = 4 \times 0.5 \times 12$$

$$\Sigma = 24 \text{ V}$$

3  
3

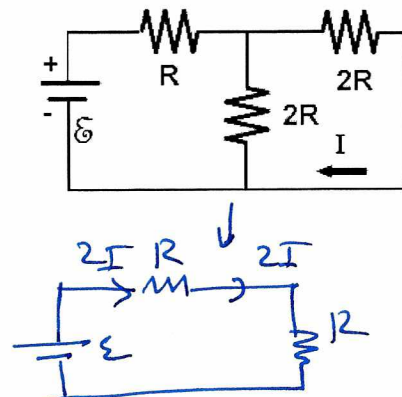

Q3. A capacitor, initially uncharged in a single-loop RC circuit, charged to 85% of its final potential difference in 2.4 s. What is its time constant in seconds? . (Ans: A1 1.3)

$$V(t) = V_0 (1 - e^{-t/RC})$$

$$\frac{V(t)}{V_0} = 1 - e^{-t/RC} \Rightarrow \frac{V(t)}{V_0} - 1 = -e^{-t/RC}$$

$$0.85 - 1 = -0.15 = -e^{-t/RC} = -e^{-t/\tau}$$

$$-0.15 = -e^{-t/\tau}$$

$$\ln(0.15) = -\frac{t}{\tau}$$

$$\tau = \frac{t}{\ln(0.15)} = \frac{-2.4}{\ln(0.15)} = 1.27 \text{ s}$$

4  
4

**Quiz # 8 Ch.#27 T131-Sec. 7-9-v5**

Student ID:..... Student Name:..... Section # .....

Q#1: The potential at point P shown in figure 1 is 20 V. What is the potential at point Q. ( Ans: -18 V.)

$$V_P - 20 - 6I = V_Q$$

$$20 - 20 - 6I = V_Q \Rightarrow V_Q = -6I$$

To calculate I

$$50 - 4I - 20 + 6I = 0$$

$$30 - 10I = 0 \Rightarrow I = 3A$$

$$V_Q = -6I = -6 \times 3 = -18V$$

4/4

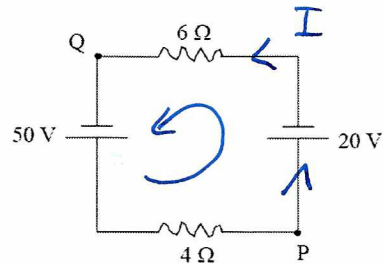


Figure 1

Q#2: In Figure 2,  $R_1 = R_2 = R_3 = 5 \Omega$ . What is the value of the emf of the second battery  $\epsilon_2$ . (Ans: 5 V.)

$$-\epsilon_2 - 0.5 \times 5 + 1.5 \times 5 = 0$$

$$-\epsilon_2 - 2.5 + 7.5 = 0$$

$$\epsilon_2 = 5V$$

3/3

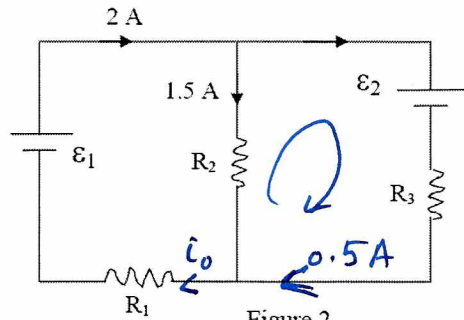


Figure 2

Q#3: An uncharged capacitor is connected as in the circuit shown. When the switch is closed, the charge on the capacitor reaches half its maximum value in 20 ms. If  $R=500 \Omega$  and the voltage of the battery is 10 V, then the capacitance of the capacitor is:


$$q(t) = q_0(1 - e^{-t/RC})$$

$$\frac{q(t)}{q_0} - 1 = -e^{-t/RC}$$

$$0.5 - 1 = -0.5 = e^{-t/RC}$$

$$\ln(0.5) = -t/RC$$

4/4

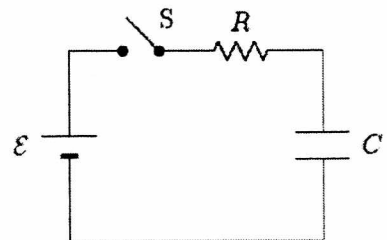


$$C = \frac{-t}{R \ln(0.5)} = \frac{-20 \times 10^{-3}}{500 \times \ln(0.5)} = 57.7 \mu F$$

### Quiz # 8 Ch.#27 T131-Sec. 7-9-v6

Student ID:..... Student Name:..... Section # .....

If  $Q = 400 \mu\text{C}$  and the potential difference  $V_A - V_B = -30 \text{ V}$  in the circuit segment shown in Fig. 3, what is the current in the resistor R? (Ans) 1.0 mA counterclockwise
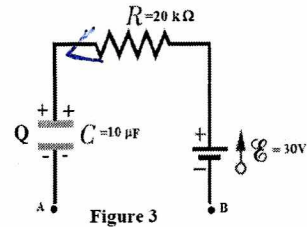
$$\begin{aligned}
 V_A + \frac{Q}{C} + iR - 30 &= V_B \\
 V_A - V_B + \frac{Q}{C} + iR - 30 &= 0 \\
 -30 + \frac{400 \times 10^{-6}}{10 \times 10^{-6}} + i \times 20 \times 10^{-3} - 30 &= 0 \\
 -60 + 40 + 20 \times 10^{-3} i &= 0 \\
 -20 + 20 \times 10^{-3} i &= 0 \\
 -1 + 10^{-3} i &= 0 \\
 i &= +10^{-3} \text{ A}
 \end{aligned}$$



Q#2 In the following figure, find the current in  $3 \Omega$  resistor and the resistance R for the given currents. A) 8 A,  $9 \Omega$

in the outermost loop, ~~starting~~  
from C junction


$$3 + 5 = i_3 \Rightarrow i_3 = 8 \text{ A}$$

going around outermost loop  
starting at C

$$3 \times 4 + 2R + 5 \times 6 = 0$$

$$12 + 2R + 30 = 0$$

$$R = \frac{-18}{-2} = 9 \Omega$$

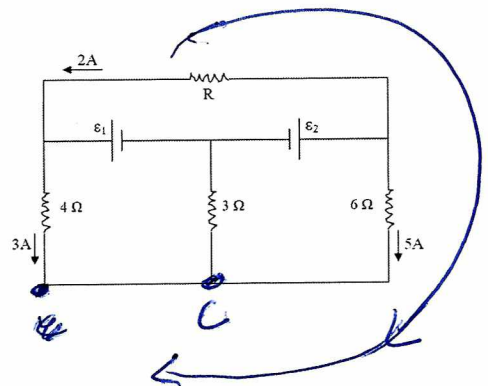

Q#3: A capacitor of capacitance  $5.0 \times 10^{-6} \text{ F}$  is discharging through a  $4.0 \text{ M}\Omega$  resistor. At what time will the energy stored in the capacitor be half of its initial value? (Ans: 7 s)

$$U(t) = \frac{1}{2} C V(t)^2 = \frac{1}{2} C V_0^2 e^{-2t/RC} = U_0 e^{-2t/RC}$$

$$\frac{U(t)}{U_0} = \frac{1}{2} = e^{-2t/RC}$$

$$\ln\left(\frac{U(t)}{U_0}\right) = \ln\left(\frac{1}{2}\right) = -\frac{2t}{RC}$$

$$t = -\frac{RC}{2} \ln\left(\frac{1}{2}\right) = -\frac{4 \times 10^6 \times 5 \times 10^{-6}}{2} \ln\left(\frac{1}{2}\right) = 6.93 \text{ s}$$

Quiz # 8 Ch.#27 T131-Sec. 7-9-v7

Student ID:..... Student Name:..... Section # .....


Q#1: Two ideal emf sources along with two resistors are connected as shown in the following figure. If the potential at A is 150 V, what would be the potential at point B? A) - 5 V

$V_A - 80 - 5I = V_B$   
 For calculation of I, starting at C

$-3i - 80 - 5i + 200 = 0$   
 $-8i + 120 = 0$   
 $i = \frac{-120}{-8} = 15 \text{ A}$

Then

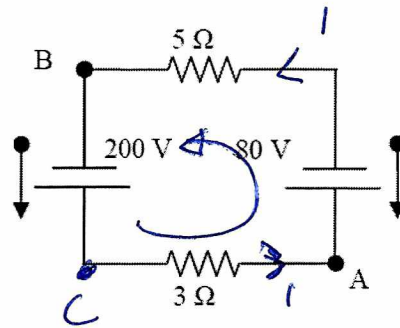$V_A - 80 - 5I = V_B$   
 $150 - 80 - 5 \times 15 = V_B \Rightarrow V_B = 150 - 75 = -75 \text{ V}$




Q#2: A single loop circuit contains two external resistors and two emf sources as shown in the figure. Assume the emf sources are ideal, what is the power dissipation across resistor R1. A) 0.9 W

$P_{R_1} = i^2 R$

to calculate i

$12 - 8i - 6 - 10i = 0$   
 $6 - 18i = 0$   
 $i = \frac{6}{18} = \frac{1}{3} \text{ A}$

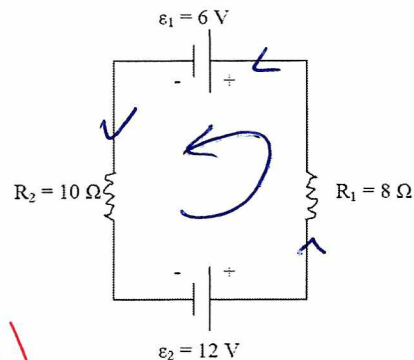$P_{R_1} = i^2 R = \left(\frac{1}{3}\right)^2 \times 8 = \frac{8}{9} \text{ W}$



Q#3: A 1.0 μF capacitor with an initial stored energy of 0.50 J is discharged through a 1.0 M Ω resistor. Find the current through the resistor when the discharge starts. A) 1.0 mA

$C = 1.0 \mu\text{F}$ ,  $U = \frac{1}{2} C V_0^2 \Rightarrow V_0 = \sqrt{\frac{2U}{C}} = \sqrt{\frac{2 \times 0.5}{10^{-6}}}$

$i_0 = \frac{V_0}{R} = \frac{1000}{10^6} = 10^{-3} \text{ A}$

$V_0 = 1000 \text{ V}$

**Quiz # 8 Ch.#27 T131-Sec. 7-9-v8**

Student ID:..... Student Name:..... Section # .....

Q#1: Four resistors are connected as shown in the figure. What is the current through  $R_1$ , when a potential difference of 30.0 Volts is applied between points a and b? (Ans: A) 1.75 A


4/4

$$V_a - i_0 R' = V_b$$

$$V_a - V_b = i_0 R'$$

$$i_0 = \frac{V_a - V_b}{R'}$$

$$i_0 = \frac{30}{17.11} = 1.75 A$$

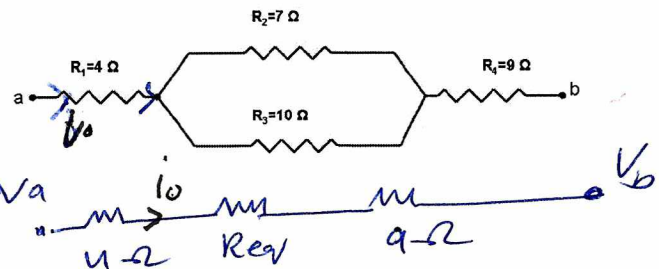

Equivalent circuit diagram showing a single resistor  $R'$  between points  $V_a$  and  $V_b$  with current  $i_0$ .

$$R' = 4 + \frac{7 \times 10}{7 + 10} + 9 = 4 + \frac{70}{17} + 9 = 17.11 \Omega$$

Q2 Three resistors and two batteries are connected as shown in the circuit diagram below. What is the potential difference,  $V_a - V_b$ ? A) 15 V

4/4

$$V_a - 16i_0 - 18i' = V_b$$

in loop ①

$$-16i_0 + 18 - 16i_0 - 12 = 0 \Rightarrow -32i_0 + 6 = 0$$


$$i_0 = \frac{6}{32} = 0.188 A$$

in loop ②

$$12 - 18i' = 0 \Rightarrow i' = \frac{12}{18} = 0.67 A$$

$$V_a - 16 \times 0.188 - 18 \times 0.67 = V_b$$
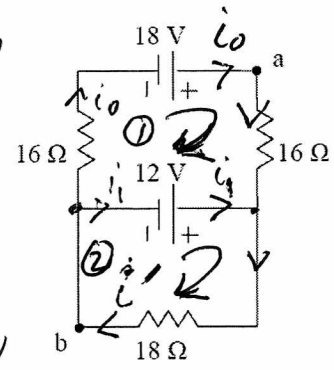
$$V_a - V_b = 16 \times 0.188 + 18 \times 0.67 = 15.06 V$$



Q#3 Consider a series RC circuit as shown in the following circuit, where  $R = 1.0 \times 10^6 \Omega$ ,  $C = 5.0 \mu F$  and  $\epsilon = 30 V$ . If the switch is closed at  $t = 0$ , what is the current in resistance  $R$  at time 10 s after the switch is closed? (Ans;  $4.1 \times 10^{-6} A$ )


3/3

$$i(t) = \frac{\epsilon}{R} \times e^{-t/RC}$$

$$= \frac{30}{10^6} \times e^{-\frac{10}{(10^6 \times 5 \times 10^{-6})}}$$

$$= \frac{30}{10^6} \times e^{-2}$$
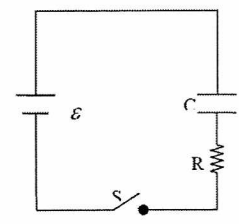
$$i(t) = 30 \times 10^{-6} \times e^{-2} = 30 \times 10^{-6} \times 0.135 = 4.1 \times 10^{-6} A$$





### Quiz # 8 Ch.#27 T131-Sec. 7-9-v9

Student ID:..... Student Name:..... Section # .....


Q1: If  $V_a - V_b = 3.2$  V, what is  $V_d - V_c$ ?

$$-i_4 = \frac{V_a - V_b}{R}; i_4 = \frac{V_b - V_a}{R} = \frac{-3.2}{2} = -1.6 \text{ A}$$

$$V_c - i_4(4+2) = V_d$$

$$V_d - V_c = -i_4 \times 6 = -1.6 \times 6$$

$$V_d - V_c = -9.6 \text{ V}$$

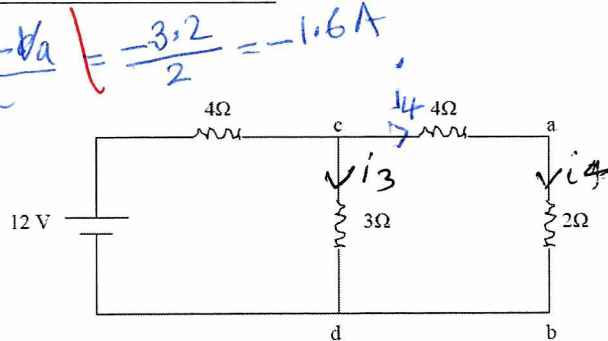

Q#2: In the circuit shown in Figure 6,  $\epsilon_1 = 6.00$  V,  $\epsilon_2 = 12.0$  V,  $R_1 = 200 \Omega$ , and  $R_2 = 100 \Omega$ . What is the power supplied by  $\epsilon_1$ ? (Consider the two emf to be ideal).

$$P_{\epsilon_2} = i_2 \epsilon_1$$

in loop ②

$$i_1 R_1 - i_2 R_2 + 6 = 0$$

in loop ①

$$i_1 R_1 - 12 = 0$$

$$i_1 = \frac{12}{R_1} = \frac{12}{200} = 0.06 \text{ A}$$

$$\text{Then } i_1 R_1 - i_2 R_2 + 6 = 0$$

$$i_2 = \frac{6 - i_1 R_1}{R_2} = \frac{6 - 0.06 \times 200}{100} = 0.18 \text{ A}$$

$$P_{\epsilon_2} = i_2 \epsilon_1 = 0.18 \times 6 = 1.08 \text{ W}$$

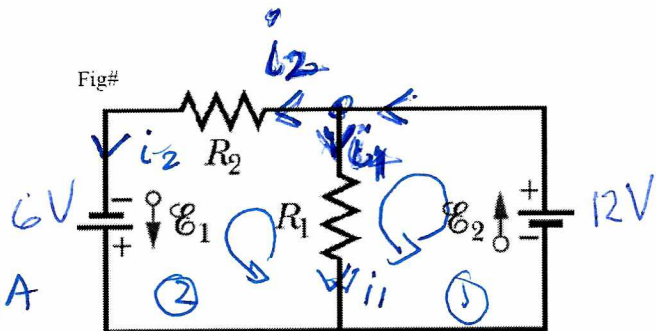


Figure 6

Q#3: A capacitor of capacitance  $C$  takes 2 s to reach 63 % of its maximum charge when connected in series to a resistance  $R$  and a battery of emf  $\epsilon$ . How long does it take for this capacitor to reach 95 % of its maximum charge (from zero initial charge)?

$$q(t) = q_0 (1 - e^{-t/RC}) \Rightarrow \frac{q(t)}{q_0} - 1 = 0.63 - 1 = -e^{-t/RC}$$

$$-0.37 = -e^{-t/RC} \Rightarrow \ln(0.37) = -t/RC$$

$$\text{Since } \frac{q(t_2)}{q_0} - 1 = 0.95 - 1 = -0.05 = -e^{-t_2/RC}$$

$$\ln(0.05) = -\frac{t_2}{RC} \quad \text{Then } \frac{\ln(0.05)}{\ln(0.37)} = \frac{t_2/RC}{t_1/RC} = \frac{t_2}{t_1}$$

$$t_2 = t_1 \frac{\ln(0.05)}{\ln(0.37)} = 2 \times \frac{\ln(0.05)}{\ln(0.37)} = 6.05$$

**Quiz # 8 Ch.#27 T131-Sec. 7-9-v10**

Student ID:..... Student Name:..... Section # .....

Q#1 The figure shows two resistors, each of the resistance  $R$ , connected to two ideal batteries of emf  $\epsilon_1$  and  $\epsilon_2$  ( $\epsilon_1 > \epsilon_2$ ). The potential difference  $V_a - V_b$  is equal to  $\epsilon_1/5$ . What is the ratio  $\epsilon_2/\epsilon_1$ ? (Ans: A)  $3/5$


$V_a - iR = V_b$   
 $iR = V_a - V_b = \epsilon_1/5$   
 $i = \frac{\epsilon_1}{5R}$

in the loop

$\epsilon_1 - iR - iR - \epsilon_2 = 0$   
 $\epsilon_1 - 2iR = \epsilon_2$

$\frac{\epsilon_2}{\epsilon_1} = 1 - \frac{2iR}{\epsilon_1} = 1 - \frac{2R}{\epsilon_1} \times \frac{\epsilon_1}{5R} = 1 - \frac{2}{5} = \frac{3}{5}$

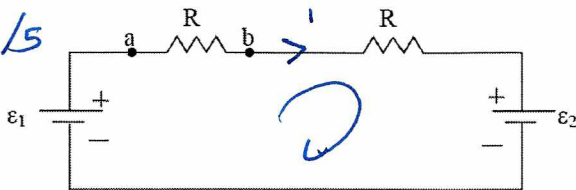$\frac{\epsilon_2}{\epsilon_1} = \frac{3}{5}$



Q#2 In Fig 3, what is the potential difference  $V_a - V_b$ ?


$V_a - i_1 \times 2 - i_2 \times 1 = V_b$   
 $V_a - V_b = i_2(2+1) = 3i_2$

left

$V_a - i_2 \times 2 - i_2 \times 1 - i_2 \times 2 = V_D$   
 $V_a - V_D = 2i_2 + i_2 + 2i_2 = 5i_2$   
 but  $V_a - V_D = 20V$   
 $V_a - V_D = 20 = 5i_2$   
 $i_2 = \frac{20}{5} = 4A$

then

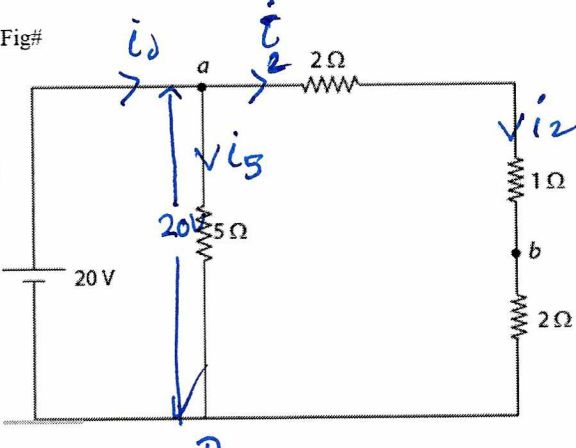$V_a - V_b = 3 \times i_2 = 3 \times 4 = 12V$



Q#3: A capacitor of capacitance  $C$  is discharging through a resistor of resistance  $R$ . In terms of  $RC$ , when will the energy stored in the capacitor reduces to one fifth of its initial value? (Ans: A)  $0.80 RC$

$U(t) = \frac{1}{2} C V^2(t) = \frac{1}{2} C V_0^2 e^{-2t/RC} = U_0 e^{-\frac{2t}{RC}}$

$\frac{U(t)}{U_0} = e^{-2t/RC}$   
 $\frac{1}{5} = e^{-2t/RC} \Rightarrow \ln\left(\frac{1}{5}\right) = -\frac{2t}{RC}$   
 $t = -\frac{RC}{2} \ln\left(\frac{1}{5}\right) = 0.805 \times RC$