

**KING FHAD UNIVERSITY OF PETROLEUM & MINERALS  
DEPARTMENT OF PHYSICS**

**PHYSICS 102 (992)  
SOLUTIONS (CHAPTER 26)**

Q.1 A spherical drop of mercury of radius  $R$  has a capacitance given by  $C = 4\pi\epsilon_0 R$ . If two such drops combine to form a single larger drop what is its capacitance?

$$C_0 = 4\pi\epsilon_0 R$$

$$2 \left( \frac{4}{3}\pi R^3 \right) = \frac{4}{3}\pi R'^3 \Rightarrow R' = 2^{1/3} R$$

$$C = 4\pi\epsilon_0 (2^{1/3} R) \quad (2^{1/3} = 1.26)$$
$$= 1.26 (4\pi\epsilon_0 R)$$

$$C = 1.26 C_0$$

Q.2 Each of the uncharged capacitors in Figure 26.2 has a capacitance of  $25.0 \mu\text{F}$ . A potential difference of  $4200 \text{ V}$  is established when the switch is closed. How many coulombs of charge then pass through meter A?

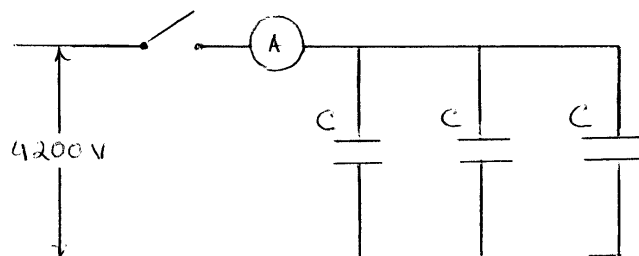


FIGURE 26.2

$$Q = 3CV = 3(25 \mu\text{F})(4200 \text{ V}) = 0.315 \text{ Coulomb}$$

$$Q = 315 \text{ mC}$$

Q.3 In Figure 26.3, capacitors  $C_1 = 1.0 \mu\text{F}$  and  $C_2 = 3.0 \mu\text{F}$  are charged to a potential difference of  $V = 100 \text{ V}$  but with opposite polarity as shown. Switches  $S_1$  and  $S_2$  are now closed. (a) What is now the potential difference between points a and b? What are now the charges on (b)  $C_1$  and (c)  $C_2$ ?

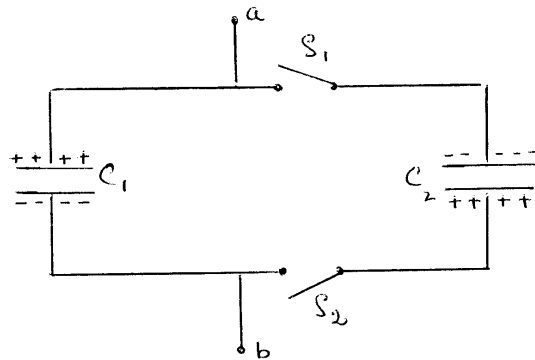


FIGURE 26-3

$$C_1 = 1.0 \mu\text{F}, C_2 = 3.0 \mu\text{F}, V = 100 \text{ volts}$$

$$(a) \quad q_1 = C_1 V = -100 \mu\text{C}, \quad q_2 = C_2 V = 300 \mu\text{C}$$

$$q_1' + q_2' = 300 - 100 = 200 \mu\text{C}$$

$$C_1 V + C_2 V = 200$$

$$1V + 3V = 200 \Rightarrow V = 50 \text{ volts}$$

$$(b) \quad q_1' = C_1 V = 50 \mu\text{C}$$

$$q_2' = C_2 V = 150 \mu\text{C}$$

Q.4 In the Figure 26.4, battery B supplies 12V. (a) Find the charge on each capacitor first when only switch  $S_1$  is closed and (b) later when switch  $S_2$  is closed. Take  $C_1 = 1.0 \mu\text{F}$ ,  $C_2 = 2.0 \mu\text{F}$ ,  $C_3 = 3.0 \mu\text{F}$  and  $C_4 = 4.0 \mu\text{F}$ .

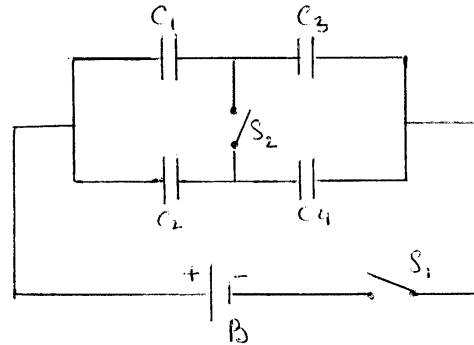


FIGURE 26.4

$$\mathcal{E} = 12 \text{ volts}, \quad C_1 = 1.0 \mu\text{F}, \quad C_2 = 2.0 \mu\text{F}, \quad C_3 = 3.0 \mu\text{F}, \\ C_4 = 4.0 \mu\text{F}.$$


(a) on  $C_1$  &  $S_1$  closed

$$12 = \frac{q}{C_1} + \frac{q}{C_3} = \frac{q}{1} + \frac{q}{3}, \quad 4q = 36 \Rightarrow q = 9 \mu\text{C}$$

$$12 = \frac{q}{C_2} + \frac{q}{C_4} = \frac{q}{2} + \frac{q}{4}, \quad 3q = 48 \Rightarrow q = 16 \mu\text{C}$$

$$\boxed{q_1 = q_3 = 9 \mu\text{C}}$$

$$\boxed{q_2 = q_4 = 16 \mu\text{C}}$$

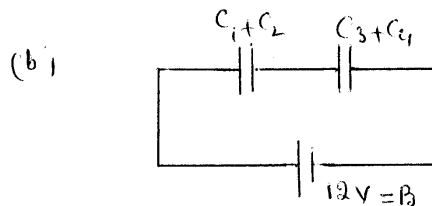

$$\frac{q}{C_1+C_2} + \frac{q}{C_3+C_4} = 12 \Rightarrow \frac{q}{3} + \frac{q}{7} = 12 \Rightarrow 7q+3q = 252$$

$$\boxed{q = 25.2 \mu\text{C}}$$

$$V_1 = \frac{25.2}{3} = 8.4 \text{ volts}, \quad V_2 = \frac{25.2}{7} = 3.6 \text{ volts}.$$

$$q_1 = (C_1)(8.4) = \boxed{8.4 \mu\text{C}}$$

$$q_2 = (C_2)(8.4) = \boxed{16.8 \mu\text{C}}$$

$$q_3 = (C_3)(3.6) = \boxed{10.8 \mu\text{C}}$$

$$q_4 = (C_4)(3.6) = \boxed{14.4 \mu\text{C}}$$

Q.5 A certain substance has a dielectric constant of 2.8 and a dielectric strength of 18 MV/m. If it is used as the dielectric material in parallel-plate capacitor, what minimum area should the plates of the capacitor have to obtain a capacitance of  $7.0 \times 10^{-8} \mu\text{F}$  and to ensure that the capacitor will be able to withstand a potential difference of 4.0 kV?

$$k = 2.8, \text{ dielectric strength, } E_{\text{max}} = 18 \text{ MV/m}$$

$$V_{\text{max}} = 4.0 \text{ kV}, \quad d = \frac{V}{E} = \frac{4 \times 10^3}{10 \times 10^6} = 2.2 \times 10^{-4} \text{ m or } 0.22 \text{ mm.}$$

$$C = k \epsilon_0 \frac{A}{d}$$

$$7 \times 10^{-8} = k \epsilon_0 \frac{A}{d}$$

$$A = \frac{(7 \times 10^{-8}) \times (2.2 \times 10^{-4})}{(2.8)(8.85 \times 10^{-12})} = 0.63 \text{ m}^2$$

$$\boxed{A = 0.63 \text{ m}^2}$$