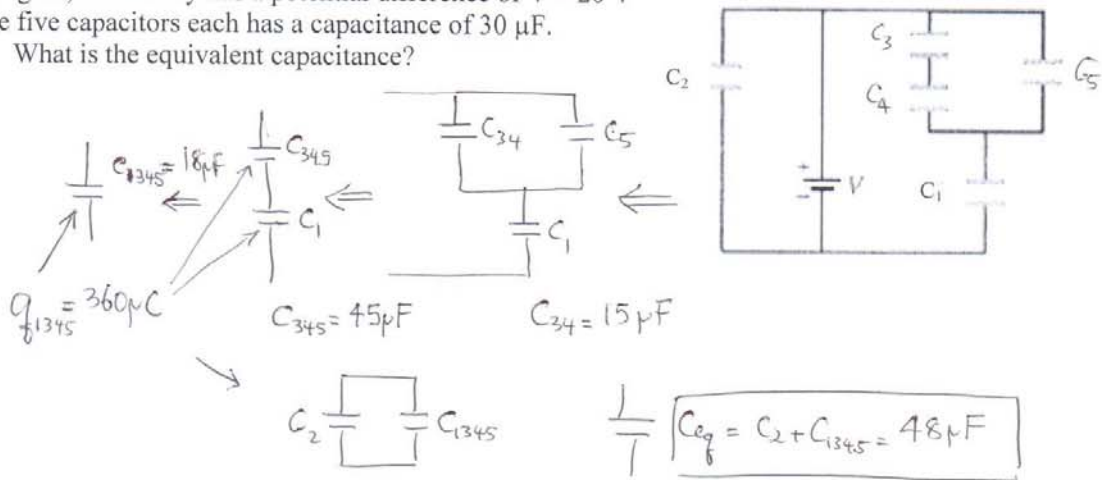


Physics 102Rec  
 Quiz #10  
 Chapter 25

Name: Key Id#: \_\_\_\_\_ Sect#: \_\_\_\_\_

In the figure, the battery has a potential difference of  $V = 20\text{ V}$  and the five capacitors each has a capacitance of  $30\ \mu\text{F}$ .

(a) What is the equivalent capacitance?



(b) What is the voltage across capacitor  $C_1$ ?

$$q_1 = q_{1345} = 360\ \mu\text{C}$$

$$V_1 = \frac{q_1}{C_1} = \frac{360\ \mu\text{C}}{30\ \mu\text{F}} = 12\ \text{V}$$

(c) What is the charge on capacitor  $C_2$ ?

$$q_2 = C_2 V = 30\ \mu\text{F} \times 20\ \text{V} = 600\ \mu\text{C}$$

Physics 102Rec  
 Quiz #10  
 Chapter 25

Name: \_\_\_\_\_




Key

Id#: \_\_\_\_\_

Sect#: \_\_\_\_\_

The figure shows a combination of four capacitors  $C_1 = C_3 = 8.0 \mu\text{F}$  and  $C_2 = C_4 = 6.0 \mu\text{F}$  connected to a 12-V battery.

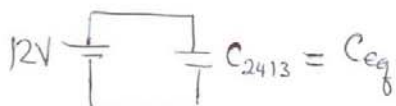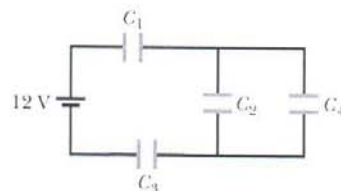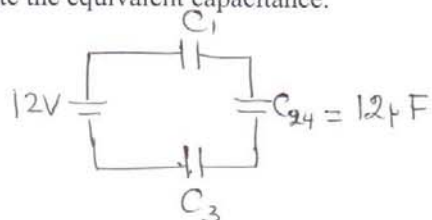(a) Calculate the equivalent capacitance.



$$\frac{1}{C_{2413}} = \frac{1}{C_{24}} + \frac{1}{C_3} + \frac{1}{C_1} = \frac{1}{12} + \frac{1}{8} + \frac{1}{8} \Rightarrow \boxed{C_{2413} = 3 \mu\text{F}}$$

(b) Calculate the voltage across capacitor C2.

$$q_{eq} = C_{eq} \cdot V = 36 \mu\text{C}$$

$$q_{24} = 36 \mu\text{C} \Rightarrow V_{24} = V_2 = \frac{q_{24}}{C_{24}} = \frac{36 \mu\text{C}}{12 \mu\text{F}} = \boxed{3\text{V}}$$

(c) Calculate the voltage across capacitor C1.

$$q_1 = q_{eq} = 36 \mu\text{C}$$

$$V_1 = \frac{q_1}{C_1} = \frac{36 \mu\text{C}}{8 \mu\text{F}} = \boxed{4.5\text{V}}$$

Physics 102Rec  
Quiz #10  
Chapter 25

Name:

Key

Id#:

Sect#:

- (a) A 20-V battery is connected to a series of  $N$  capacitors, each of capacitance  $4.0 \mu\text{F}$ . If the total energy stored in the capacitors is  $50 \mu\text{J}$ , what is  $N$ ?

$$U_{\text{Total}} = \frac{1}{2} C_{\text{eq}} V^2$$

$$= \frac{1}{2} \frac{C_1}{n} V^2$$

$$n = \frac{C_1 V^2}{2 U_{\text{Total}}} = \frac{4 \times 10^{-6} \times (20)^2}{2 \times (50 \times 10^{-6})}$$

$$\boxed{n = 16}$$

- (b) A 100-V battery is connected to  $N$  capacitors connected in parallel, each of capacitance  $4.0 \mu\text{F}$ . If the total charge of  $1.0 \text{ C}$  is stored on the capacitors, what is  $N$ ?

$$q_{\text{net}} = n q_1 = n C_1 V$$

$$n = \frac{q_{\text{net}}}{C_1 V} = \frac{1}{4 \times 10^{-6} \times 100} = 2500$$

$$\boxed{n = 2500}$$