

31.4 $f = 200 \text{ kHz}$

$t = 0$ Q_{max}

a) See Fig. 31.1

Earliest time is $t = T = \frac{1}{f} = \frac{1}{200 \times 10^3} = \underline{\underline{5 \mu\text{s}}}$

b) See Fig. 31.1


Earliest time is $t = \frac{T}{2} = \underline{\underline{2.5 \mu\text{s}}}$

c) See Fig. 31.1

Earliest time is $t = \frac{T}{4} = \underline{\underline{1.25 \mu\text{s}}}$

31.17 LC circuit

$C = 64 \mu\text{F}$

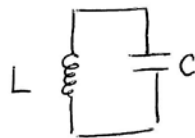

$i(t) = 1.6 \sin(2500t + 0.68)$

$i(t) = I_{\text{max}} \sin(\omega t + \phi)$

See Fig. 31.1

a) i is max when $\sin(\omega t + \phi) = 1 \Rightarrow \omega t + \phi = \frac{\pi}{2}$

$\Rightarrow 2500t + 0.68 = \frac{\pi}{2} \Rightarrow \underline{\underline{t = 3.56 \times 10^{-4} \text{ s}}}$

b) $\omega = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{\omega^2 C} = \frac{1}{(2500)^2 \times (64 \times 10^{-6})} = \underline{\underline{2.5 \times 10^{-3} \text{ H}}}$

c) $U_{\text{total}} = \frac{1}{2} L I_{\text{max}}^2 = \frac{1}{2} (2.5 \times 10^{-3}) (1.6)^2 = \underline{\underline{3.2 \times 10^{-3} \text{ J}}}$

31.20

$I_{\text{max}} = 7.5 \text{ mA}$

$V_{\text{max}} = 250 \text{ mV}$

$C = 220 \text{ nF}$

a) $T = \frac{2\pi}{\omega}$

$I_{\text{max}} = \omega Q$ } $\Rightarrow \frac{I_{\text{max}}}{V_{\text{max}}} = \frac{\omega Q}{\frac{Q}{C}} = \omega C$

$V_{\text{max}} = \frac{Q}{C}$ } $\Rightarrow \omega = \frac{I_{\text{max}}}{C V_{\text{max}}} = \frac{7.5 \times 10^{-3}}{250 \times 10^{-3} \times 220 \times 10^{-9}}$

$$\omega = 1.3636 \times 10^5 \text{ rad/s} \Rightarrow T = \frac{2\pi}{1.3636 \times 10^5} = 4.6 \times 10^{-5} \text{ s}$$

$$b) U_{E_{\max}} = \frac{1}{2} C V_{\max}^2 = \frac{1}{2} (220 \times 10^{-9}) (250 \times 10^{-3})^2 = \underline{\underline{6.88 \times 10^{-9} \text{ J}}} = \underline{\underline{46 \text{ pJ}}}$$

$$U_E = \frac{Q^2}{2C} \Rightarrow Q = \sqrt{2CU_E} =$$

$$c) U_{B_{\max}} = \frac{1}{2} L I^2 = U_{E_{\max}} = \underline{\underline{6.88 \times 10^{-9} \text{ J}}}$$

$$d) \left(\frac{di}{dt} \right)_{\max} = ?$$

$$i = -Q\omega \sin(\omega t + \phi) = -I \sin(\omega t + \phi)$$

$$\frac{di}{dt} = - \underbrace{Q\omega^2}_{\left(\frac{dI}{dt} \right)_{\max}} \cos(\omega t + \phi)$$

$$\left(\frac{di}{dt} \right)_{\max} = Q\omega^2 = \sqrt{2CU_{E_{\max}}} \omega^2 = 1023 \text{ A/sec}$$

$$e) U_B = \frac{1}{2} L i^2$$

$$\frac{dU_B}{dt} = L i \frac{di}{dt} = L I^2 \omega \sin \omega t \cos \omega t = \frac{1}{2} L I^2 \omega \sin 2\omega t \quad \left\{ L I \omega = V \right.$$

$$\left(\frac{dU_B}{dt} \right)_{\max} = \frac{1}{2} L I^2 \omega = \frac{1}{2} (7.5 \times 10^{-3}) (250 \times 10^{-3}) = 0.938 \times 10^{-3} \text{ W}$$

$$= \frac{1}{2} \underbrace{(L I \omega)}_V$$

31.24

$$q = Q e^{-\frac{R}{2L}t} \cos(\omega t + \phi) = q_{\max} \cos(\omega t + \phi)$$

$$t \rightarrow 0 \quad q = Q \Rightarrow \phi = 0$$

$$q_{\max} = Q e^{-\frac{R}{2L}t}$$

$$U = \frac{1}{2} \frac{Q^2}{C} \Rightarrow \frac{1}{2} \left(\frac{1}{2} \frac{Q^2}{2C} \right) = \frac{q_{\max}^2}{2C} = \frac{Q^2 \cdot e^{-\frac{R}{L}t}}{2C}$$

$$\frac{1}{2} = e^{-\frac{R}{L}t} \quad \ln\left(\frac{1}{2}\right) = -\frac{R}{L}t$$


$$t = \frac{L}{R} \ln 2 = 0.693 \frac{L}{R}$$

$$\boxed{t = 0.693 \frac{L}{R}}$$

31.32

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t \quad \mathcal{E}_m = 25V \quad \omega_d = 377 \text{ rad/s}$$

$$C = 4.15 \mu\text{F}$$

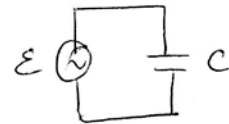

$$a) \quad i = \frac{dq}{dt} \quad \text{and } q = C\mathcal{E} \\ = C \mathcal{E}_m \sin \omega_d t$$

$$i = (\omega_d C \mathcal{E}_m) \cos \omega_d t = I_m \cos \omega_d t$$

$$I_m = \mathcal{E}_m C \omega_d = 25 \times (4.15 \times 10^{-6}) (377) = \underline{\underline{3.91 \times 10^{-2} \text{ A}}}$$

$$b) \quad \text{when } i = I_m \Rightarrow \cos \omega_d t = 1 \Rightarrow \sin \omega_d t = 0$$

$$\Rightarrow \mathcal{E} = 0 \quad \text{and } q = 0$$


$$c) \quad \mathcal{E} = -\frac{\mathcal{E}_m}{2} = \mathcal{E}_m \sin \omega_d t \Rightarrow \sin \omega_d t = -\frac{1}{2} \\ \omega_d t = -\frac{\pi}{2}$$

31.34

$$\Sigma = \Sigma_m \sin \omega_d t$$

$$\Sigma_m = 25 \text{ V} \quad \omega_d = 377 \text{ rad/s} \quad L = 12.7 \text{ H}$$
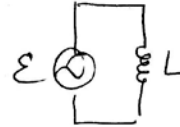
$$a) I_m = \frac{\Sigma_m}{X_L} = \frac{\Sigma_m}{\omega_d L} = 5.22 \times 10^{-3} \text{ A}$$



$$b) L \frac{di}{dt} = \Sigma \Rightarrow \frac{di}{dt} = \frac{\Sigma}{L} \quad i = \int \frac{\Sigma}{L} dt$$

$$i = - \frac{\Sigma_m}{L \omega_d} \cos(\omega_d t)$$

$$i = \frac{\Sigma_m}{L \omega_d} \sin(\omega_d t - 90^\circ) = I_m \sin(\omega_d t - 90^\circ)$$

$$I_m = \frac{\Sigma_m}{L \omega_d} = 5.22 \times 10^{-3} \text{ A}$$

$$b) i = I_m \Rightarrow \sin(\omega_d t - 90^\circ) = 1$$

$$\Rightarrow \omega_d t - \frac{\pi}{2} = \frac{\pi}{2} \Rightarrow \omega_d t = \pi$$

$$\Sigma = \Sigma_m \sin(\omega_d t) = \Sigma_m \sin \pi = 0$$

32.36 driven RLC circuit

$$I_s = 4 \text{ A} \quad L = 200 \mu\text{H} \quad \mathcal{E}_m = 8 \text{ V}$$

$$b) \quad I_s = \frac{\mathcal{E}_m}{R} \Rightarrow R = \frac{\mathcal{E}_m}{I_s} = \frac{8}{4} = \underline{\underline{2 \Omega}}$$

$$a) \quad \omega_r = \frac{1}{\sqrt{LC}} \quad \text{at the resonance}$$

$$\omega_r = 25000 \text{ rad/s} \quad C = \frac{1}{L \omega_r^2}$$


$$C = \frac{1}{200 \times 10^{-6} \times (25000)^2} = \underline{\underline{8 \mu\text{F}}}$$

32.39

$$R = 200 \Omega \quad C = 70 \mu\text{F}$$

$$L = 230 \text{ mH} \quad f_d = 60 \text{ Hz}$$

$$\mathcal{E}_m = 36 \text{ V}$$

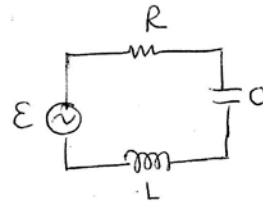

$$a) \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega_d L = 86.7 \Omega$$

$$X_C = \frac{1}{\omega_d C} = 37.9 \Omega$$

$$Z = \sqrt{(200)^2 + (86.7 - 37.9)^2} = \underline{\underline{205.9 \Omega}}$$

$X_L > X_C$ more inductive

$$b) \quad \tan \phi = \frac{X_L - X_C}{R} = 0.244 \Rightarrow \phi = \cancel{\neq} 0.239 \text{ rad}$$


$$= \cancel{\neq} 13.7^\circ$$

more inductive $\phi = \underline{\underline{+13.7^\circ}}$

$$c) \quad I = \frac{\mathcal{E}_m}{Z} = \frac{36}{205.9} = \underline{\underline{0.175 \text{ A}}}$$

$$P_E = (1.93)(45) \sin(3000 \times 0.442 \times 10^{-3}) \sin(3000 \times 0.442 \times 10^{-3} - 46.5^\circ)$$
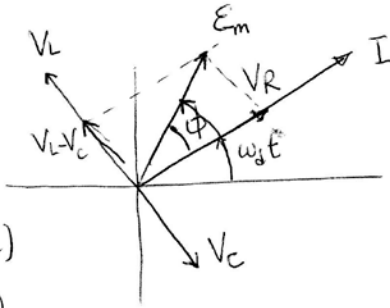
$$\underline{\underline{P_E = 41.6 \text{ W}}}$$



$$\begin{aligned} b) \quad v_c &= V_c \sin(\omega_d t - \phi - \frac{\pi}{2}) \\ &= \frac{I X_c \sin(\omega_d t - \phi - \pi/2)}{\omega_d C} \\ &= -\frac{I}{\omega_d C} \cos(\omega_d t - \phi) \end{aligned}$$

$$P_c = \frac{d}{dt} \left(\frac{q^2}{2C} \right) = \left(\frac{q}{C} \right) \frac{dq}{dt} = v_c i_c$$

$$= -\frac{I}{\omega_d C} \cos(\omega_d t - \phi) I \sin(\omega_d t - \phi)$$

$$P_c = -\frac{I^2}{2\omega_d C} \sin[2(\omega_d t - \phi)]$$

$$\text{at } t = 0.442 \text{ ms} \quad P_c = -\frac{(1.93)^2}{2 \times (3000)(31.2 \times 10^{-6})} \sin\left[2(3000 \times 0.442 \times 10^{-3} - 0.81)\right]$$

$$= \underline{\underline{-17.1 \text{ W}}}$$

$$c) \quad P_L = \frac{d}{dt} \left(\frac{1}{2} L i^2 \right) = L i \frac{di}{dt}$$


$$i = I \sin(\omega_d t - \phi)$$

$$\frac{di}{dt} = I \omega_d \cos(\omega_d t - \phi)$$

$$P_L = L I^2 \omega_d \sin(\omega_d t - \phi) \cos(\omega_d t - \phi)$$

$$= \frac{1}{2} L I^2 \omega_d \sin[2(\omega_d t - \phi)]$$
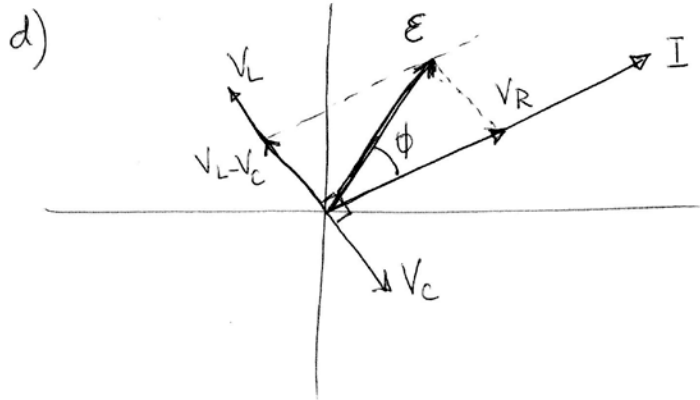
$$= \frac{1}{2} (9.2 \times 10^{-3}) (1.93)^2 (3000) \sin\left[2(3000 \times 0.442 \times 10^{-3} - 0.81)\right]$$



31.42

$$E = 6 \text{ V} \quad \phi = 30^\circ \quad \text{more inductive}$$

According to previous figure

$$\sin \phi = \frac{V_L - V_C}{E} \Rightarrow V_L - V_C = E \sin \phi$$

$$V_L - V_C = 6 \sin 30^\circ = 3 \text{ V}$$

$$\text{when } V_C = 5 \text{ V} \Rightarrow V_L = V_C + 3 = \underline{\underline{8 \text{ V}}}$$

31.58

RLC circuit

$$R = 16 \Omega \quad C = 31.2 \mu\text{F} \quad L = 9.2 \text{ mH}$$

$$E = E_m \sin \omega_d t \quad E_m = 45 \text{ V} \quad \omega_d = 3000 \text{ rad/s}$$

$$a) P_E = i(t) E(t) = I E_m \sin \omega_d t \sin(\omega_d t - \phi)$$

Calculate I and ϕ

$$I = \frac{E_m}{Z} \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(16)^2 + (27.6 - 10.7)^2}$$

$$= 23.3 \Omega$$

$$I = \frac{45}{23.3} = \underline{\underline{1.93 \text{ A}}}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = 0.81 \text{ rad} = 46.5^\circ$$

$$P_L = \underline{\underline{44.1 \text{ W}}}$$

$$\begin{aligned} \text{d) } P_R &= i^2 R = I^2 R \sin^2(\omega_d t - \phi) \\ &= (1.93)^2 \times (16) \sin^2(3000 \times 0.442 \times 10^{-2} - 0.81) \\ &= \underline{\underline{14.5 \text{ W}}} \end{aligned}$$

$$P_L + P_C + P_R \stackrel{?}{=} P_E$$

$$44.1 - 17.1 + 14.5 = 41.5 \text{ W} = P_E \quad !!!$$

31.63

$$N_p = 500$$

$$V_p = 120 \text{ V}$$

This is a step down transformer.

$$N_s = 10$$

$$V_s = ?$$

$$\text{a) } \frac{V_s}{V_p} = \frac{N_s}{N_p} \Rightarrow V_s = V_p \frac{N_s}{N_p} = 120 \times \frac{10}{500} = \underline{\underline{2.4 \text{ V}}}$$

$$\text{b) } I_s = \frac{V_s}{R} = \frac{2.4}{15} = \underline{\underline{0.16 \text{ A}}}$$

$$\frac{I_s}{I_p} = \frac{N_p}{N_s} \Rightarrow I_p = I_s \frac{N_p}{N_s} = \underline{\underline{3.2 \times 10^{-3} \text{ A}}}$$