

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
PHYSICS DEPARTMENT
PHYS 201- Term 112
QUIZ #1 - CHAPTER 31

Name: Key ID#: _____

A coil with inductance $L = 1.0 \text{ H}$ and a resistance $R = 10 \Omega$ is suddenly connected to an ideal battery with $\mathcal{E} = 200 \text{ V}$. At $t = 0.5 \text{ s}$ after the connection is made, what is the **rate** at which

- (a) Energy is being stored in the magnetic field
- (b) Thermal energy is appearing in the resistance
- (c) Energy is being delivered by the battery

$$a) i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L}) \quad \tau_L = \frac{L}{R} = \frac{1}{10} = 0.1 \text{ s}$$

$$P_L = \frac{dU_B}{dt} = \frac{d}{dt} \left(\frac{1}{2} L i^2 \right) = L i \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{\mathcal{E}}{R\tau_L} e^{-t/\tau_L} = \frac{\mathcal{E}}{L} e^{-t/\tau_L}$$

$$P_L = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L}) (e^{-t/\tau_L}) = \frac{(200)^2}{10} (1 - e^{-\frac{0.5}{0.1}}) (e^{-\frac{0.5}{0.1}})$$
$$= \underline{26.8 \text{ W}}$$

$$b) P_R = i^2 R = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L})^2 = \frac{(200)^2}{10} (1 - e^{-\frac{0.5}{0.1}})^2$$
$$= \underline{3946.3 \text{ W}}$$

$$c) P_{\mathcal{E}} = i \mathcal{E} = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L}) = \frac{(200)^2}{10} (1 - e^{-\frac{0.5}{0.1}})$$
$$= \underline{3973 \text{ W}}$$

Note $P_{\mathcal{E}} \approx P_R + P_L$