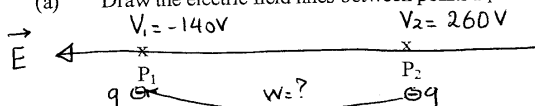


Physics 102Rec
Quiz #7
Chapters 25 & 26

Name: Key Id#: _____ Sect#: _____

1. Consider two points in an electric field. The potential at point P_1 is $V_1 = -140$ V, and the potential at point P_2 is $V_2 = 260$ V.

(a) Draw the electric field lines between points P_1 and P_2 .



- (b) How much work is required in moving a charge $q = -12$ μ C from point P_2 to point P_1 .


$$W = \Delta U = q \Delta V = (-12 \times 10^{-6}) (V_1 - V_2) \\ = (-12 \times 10^{-6}) (-140 - 260) = 4.8 \times 10^{-3} \text{ J}$$

$W > 0 \Rightarrow$ It is done by an external agent.

2. In the figure, the battery has a potential difference of 50 V and the five capacitors each having a capacitance of 5 μ F.

(a) What is the energy stored in the capacitor C_5 ?

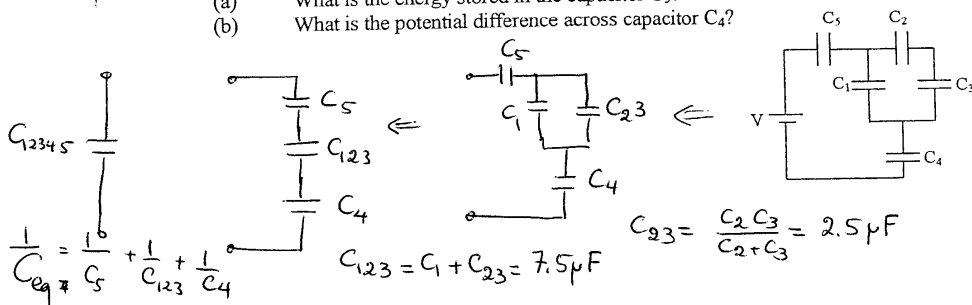(b) What is the potential difference across capacitor C_4 ?



$$\frac{1}{C_{eq}} = \frac{1}{C_5} + \frac{1}{C_{123}} + \frac{1}{C_4}$$

$$C_{123} = C_1 + C_2 + C_3 = 7.5 \mu F$$

$$C_{23} = \frac{C_2 C_3}{C_2 + C_3} = 2.5 \mu F$$

$$C_{eq} = 1.88 \mu F$$

$$\Rightarrow q_{eq} = C_{eq} V = 1.88 \mu F \times 50 V = 93.75 \mu C$$

$$\Rightarrow q_5 = q_{123} = q_4 = 93.75 \mu C$$

$$\Rightarrow U_5 = \frac{1}{2} \frac{q_5^2}{C_5} = \frac{1}{2} \frac{(93.75 \times 10^{-6})^2}{5 \times 10^{-6}} = 8.8 \times 10^{-4} \text{ J}$$

$$V_4 = \frac{q_4}{C_4} = \frac{93.75 \times 10^{-6}}{5 \times 10^{-6}} = 18.75 \text{ V}$$