

Physics 102-Rec
Quiz # 7
Chapter 28

Date: 12 May 2002





Name: Key

Id:

Sect:

Consider the circuit shown in the figure. Calculate:

- (a) The equivalent resistor.

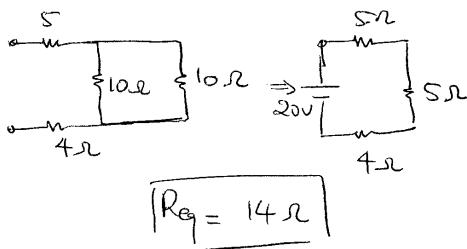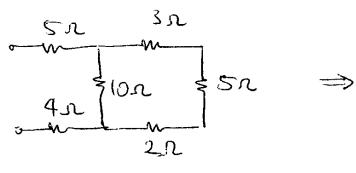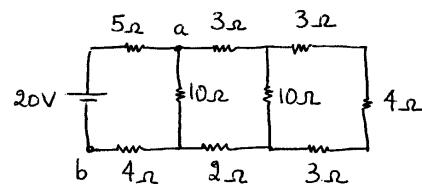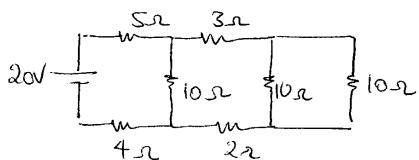

- (b) The current in the 4Ω resistor.

$$20V = 14I \Rightarrow I = \frac{20}{14} = 1.4A$$

$$\boxed{I_{4\Omega} = 1.4 A}$$

- (c) The potential difference $V_b - V_a$.

$$V_b - V_a = +5I - 20 = +5 \times 1.4 - 20 = \boxed{-13 V}$$