
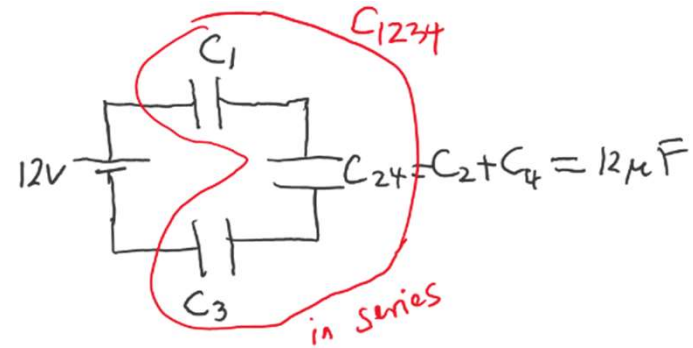
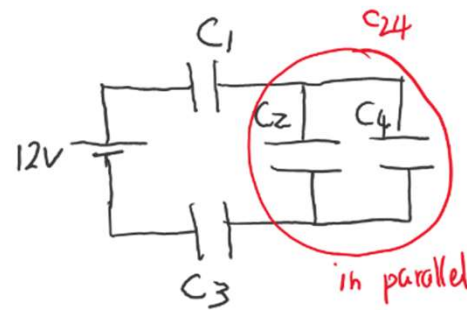


Q1

M2-112-17

The figure shows a combination of four capacitors $C_1 = C_3 = 8.0 \mu\text{F}$ and $C_2 = C_4 = 6.0 \mu\text{F}$ connected to a 12-V battery. Calculate the charge on capacitor C_1 .

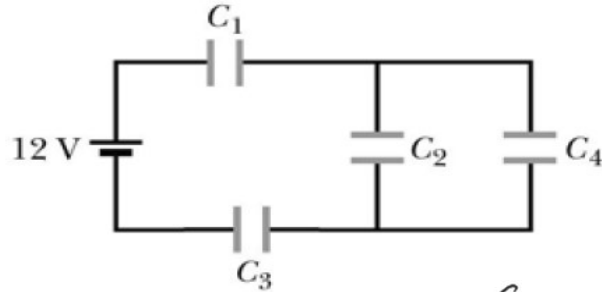- A) $36 \mu\text{C}$
- B) $18 \mu\text{C}$
- C) $12 \mu\text{C}$
- D) $24 \mu\text{C}$
- E) $30 \mu\text{C}$



$$12\text{V} \text{ --- } C_{1234} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_3} + \frac{1}{C_{24}}} = \frac{1}{\frac{1}{8} + \frac{1}{8} + \frac{1}{12}} \mu\text{F} = 3 \mu\text{F}$$

$$\Rightarrow q_{1234} = C_{1234}V = 36 \mu\text{C}$$

The charge on C_1 is the same as that on C_{1234}



$$\Rightarrow q_1 = 36 \mu\text{C}$$

Q2

M2-122-18

Consider the circuit of identical capacitors shown in the figure. A potential difference of $2.0 \times 10^2 \text{ V}$ is applied by the battery V . Calculate the energy stored in the system if the capacitance of each capacitor is $50 \mu\text{F}$.

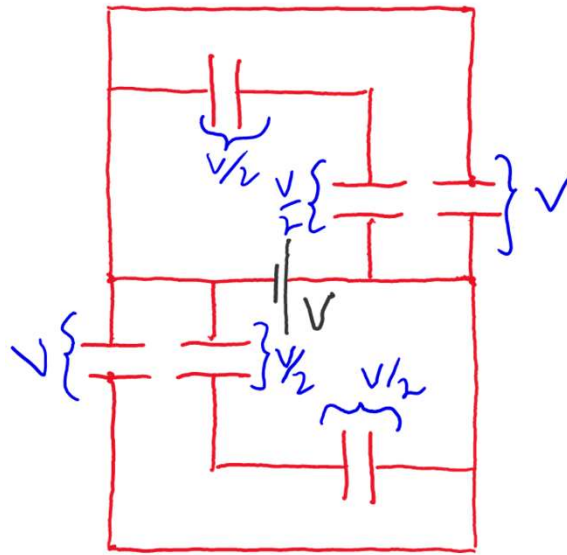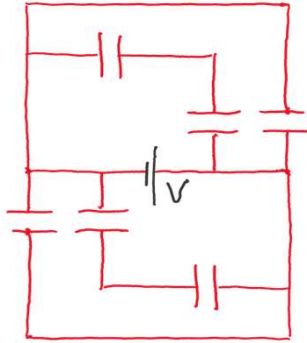- A) 3.0 J
- B) 4.0 J
- C) 6.0 J
- D) 1.0 J
- E) 7.0 J



The electric potential across 4 capacitors is $\frac{V}{2}$ and across 2 capacitors is V .

$$U = 4 \left[\frac{1}{2} C \left(\frac{V}{2} \right)^2 \right] + 2 \left[\frac{1}{2} C V^2 \right]$$

$$U = \frac{3}{2} C V^2 = \frac{3}{2} (50 \times 10^{-6}) (200)^2$$

$$U = 3.0 \text{ J}$$

Q3

M2-142-16

An air-filled parallel plate capacitor has a capacitance of $5.0 \mu\text{F}$ and a plate area of 60 cm^2 . What is the energy density stored, in J/m^3 , between the plates if the potential difference across them is 8.0 V ?

- A) 2.5×10^6
- B) 5.0×10^5
- C) 1.2×10^6
- D) 1.6×10^6
- E) 8.9×10^5

$$U = \frac{1}{2} CV^2$$

$$\text{Volume} = Ad = \frac{\epsilon_0 A^2}{C}$$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow d = \frac{\epsilon_0 A}{C}$$

$$u = \frac{U}{\text{Volume}} = \frac{\frac{1}{2} CV^2}{\frac{\epsilon_0 A^2}{C}} = \frac{1}{2} \frac{(5.0 \times 10^{-6})^2 (8)^2}{8.85 \times 10^{-12} (60 \times 10^{-4})^2}$$




$$u = 2.5 \times 10^6 \frac{\text{J}}{\text{m}^3}$$

Q4

M2-142-15

The figure shows 6 identical capacitors, each with a capacitance of $1.0 \mu\text{F}$. Find the equivalent capacitance C_{eq} between points A and B.

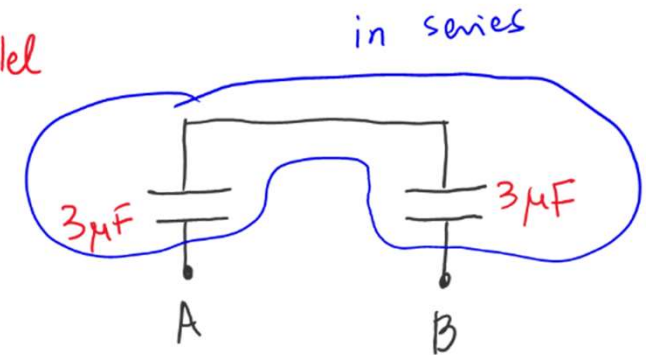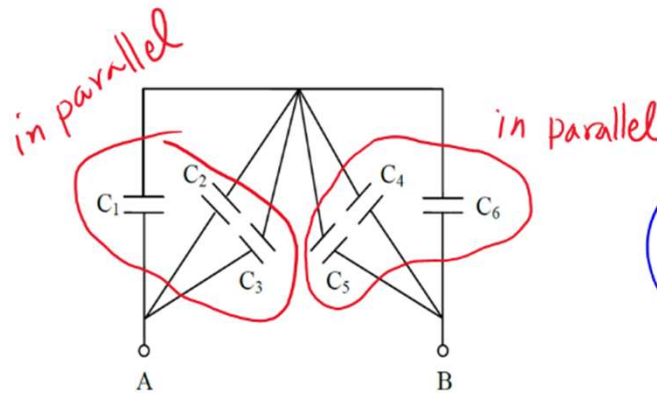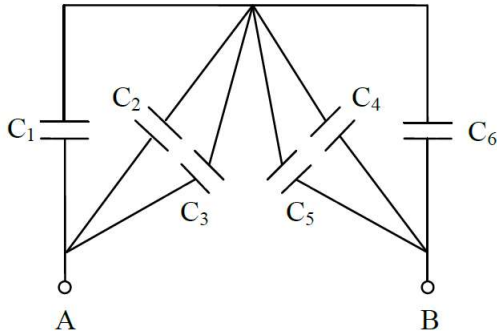- A) $1.5 \mu\text{F}$
- B) $4.0 \mu\text{F}$
- C) $3.0 \mu\text{F}$
- D) $2.5 \mu\text{F}$
- E) $9.0 \mu\text{F}$



$$C_{\text{eq}} = \frac{1}{\frac{1}{3} + \frac{1}{3}} \mu\text{F} = 1.5 \mu\text{F}$$

A final simplified circuit diagram showing a single capacitor labeled $1.5 \mu\text{F}$ connected between terminals A and B.

Q5

M2-112-20

A 2.0-nF parallel plate capacitor is charged using a 12-V battery. The battery is removed and a dielectric of dielectric constant $\kappa = 3.5$ is inserted, filling completely the space between the plates of the capacitor. What is the energy stored in the capacitor after inserting the dielectric?

- A) $4.1 \times 10^{-8} \text{ J}$
- B) $5.0 \times 10^{-5} \text{ J}$
- C) $1.4 \times 10^{-7} \text{ J}$
- D) $2.4 \times 10^{-8} \text{ J}$
- E) $1.0 \times 10^{-6} \text{ J}$

$$q = CV = 2 \times 10^{-9} \times 12 = 24 \text{ nC}$$

When the battery is removed, the charge on the capacitor does not change


$$U = \frac{q^2}{2 \kappa C} = \frac{(24 \times 10^{-9})^2}{2(3.5) 2 \times 10^{-9}} = 4.1 \times 10^{-8} \text{ J}$$

Q6

M2-142-14

Two capacitors, C_1 and, C_2 are connected in series to a 40 V power supply. If the capacitance $C_1 = 35 \text{ nF}$, and of $C_2 = 85 \text{ nF}$, find the voltage across C_1 .

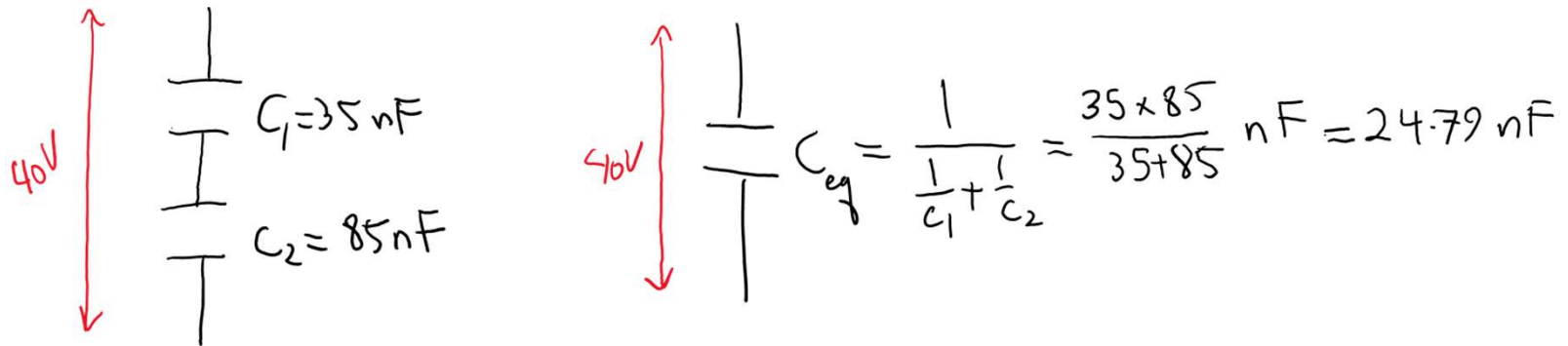- A) 28 V
- B) 12 V
- C) 16 V
- D) 40 V
- E) 24 V



The charge on C_{eq} is the same as the charge on C_1 .

$$q = C V = 24.79 \times 10^{-9} \times 40 = 991.7 \text{ nC}$$

$$\text{The voltage across } C_1 \text{ is } V_1 = \frac{q_1}{C_1} = \frac{q}{C_1} = \frac{991.7}{35} = 28.3 \text{ V}$$