

Q1

F-112-15

In the circuit, the current $I_1 = 3.0$ A. What is the value of current I_3 ?


- A) 5.0 A
- B) 1.0 A
- C) 13 A
- D) 7.0 A
- E) 6.0 A

$$12 - 6I_1 + 3I_2 = 0$$

$$12 - 6(3) + 3I_2 = 0$$

$$\Rightarrow I_2 = \frac{-12 + 18}{3} = 2 \text{ A}$$
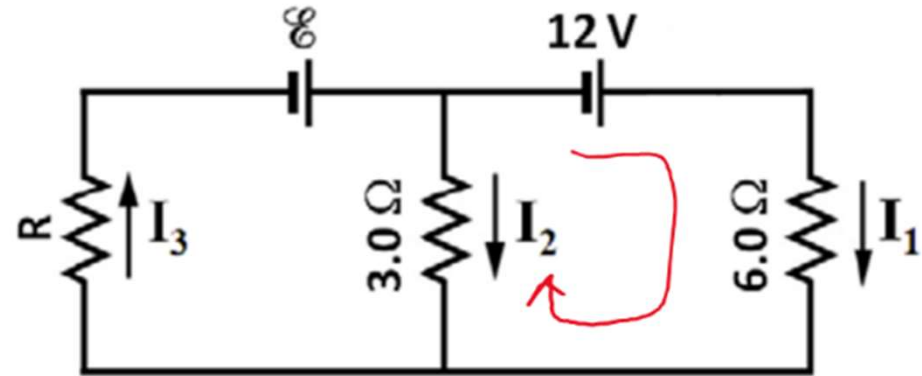
$$I_3 = I_1 + I_2 = 2 \text{ A} + 3 \text{ A} = 5 \text{ A}$$




Q2

F-122-15

What are the resistance R and the emf ε of the battery in the figure.

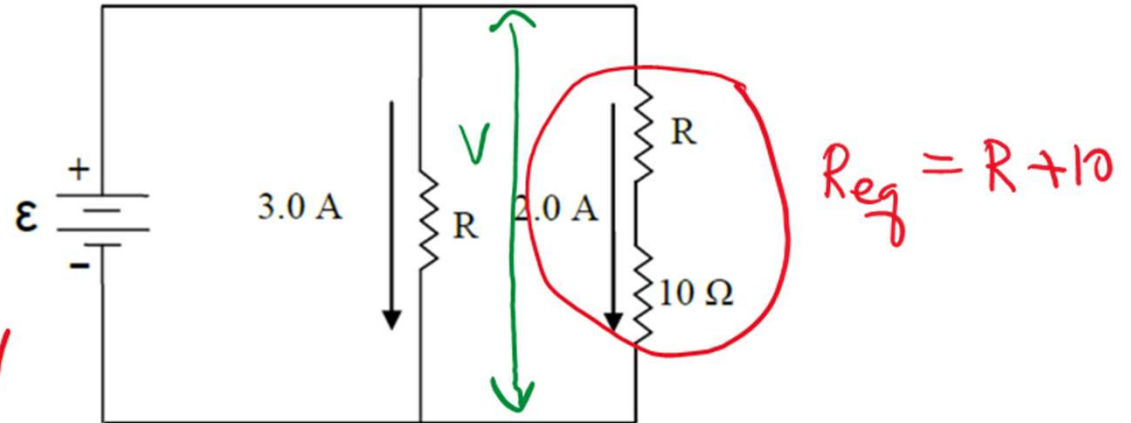- A) $R = 20 \Omega$, $\varepsilon = 60 \text{ V}$
- B) $R = 10 \Omega$, $\varepsilon = 60 \text{ V}$
- C) $R = 10 \Omega$, $\varepsilon = 30 \text{ V}$
- D) $R = 20 \Omega$, $\varepsilon = 50 \text{ V}$
- E) $R = 15 \Omega$, $\varepsilon = 45 \text{ V}$

$$\begin{aligned}\varepsilon &= V = 3R = 2R_{\text{eq}} \\ \Rightarrow 3R &= 2(R+10) \\ R &= 20 \Omega \\ \Rightarrow \varepsilon &= 3(20) = 60 \text{ V}\end{aligned}$$





Q3

F-132-02

The current in the 12-Ω resistor shown in the circuit of the figure is:

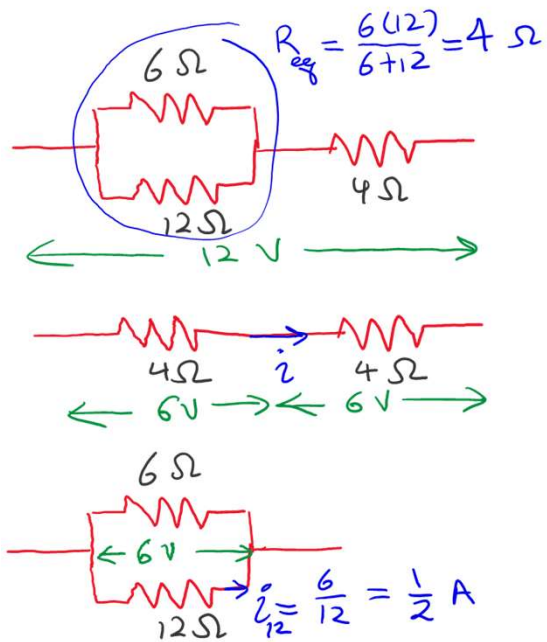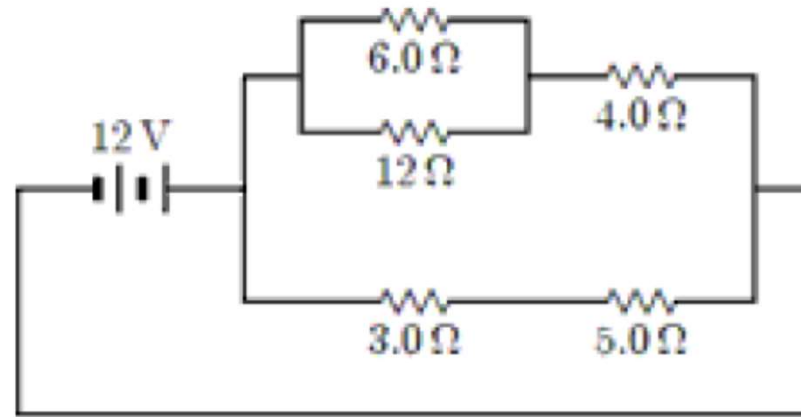- A) 0.50 A
- B) 1.5 A
- C) 2.5 A
- D) 2.0 A
- E) 0.30 A



$$i = \frac{12}{4+4} = \frac{12}{8} = \frac{3}{2} \text{ A}$$

Q4

F-142-12

In the figure, find the resistance R,

- A) 12.9 Ω
- B) 10.0 Ω
- C) 16.2 Ω
- D) 14.3 Ω
- E) 18.8 Ω


$$V = I_c R_1 = I_b (R + R_2)$$

$$(I_a - I_b) R_1 = I_b (R + R_2)$$

$$R = \frac{I_a R_1 - I_b R_1 - I_b R_2}{I_b}$$

$$R = \frac{I_a}{I_b} R_1 - R_1 - R_2 = \left(\frac{I_a}{I_b} - 1 \right) R_1 - R_2$$
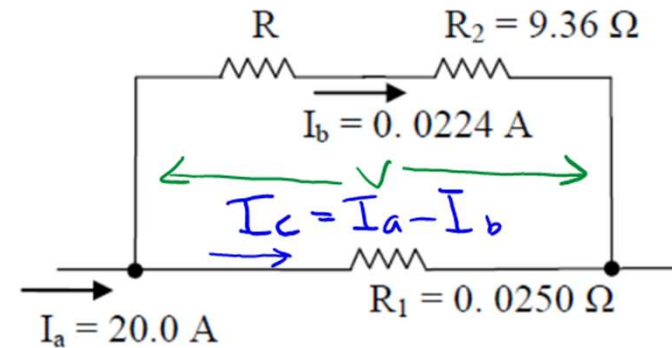
$$R = \left(\frac{20}{0.0224} - 1 \right) 0.025 - 9.36 = 12.9 \Omega$$



Q5

F2-122-16

A $1.0 \mu\text{F}$ capacitor with an initial stored energy of 0.50 J is discharged through $1.0 \text{ M}\Omega$ resistor. Find the charge on the capacitor at $t = 0.40 \text{ s}$.

- A) $6.7 \times 10^{-4} \text{ C}$
- B) $3.7 \times 10^{-4} \text{ C}$
- C) $1.3 \times 10^{-4} \text{ C}$
- D) $9.4 \times 10^{-4} \text{ C}$
- E) $7.3 \times 10^{-4} \text{ C}$

initial stored energy $U_0 = \frac{q_0^2}{2C} = 0.5 \text{ J}$


$$\Rightarrow q_0 = \sqrt{U_0(2C)} \Rightarrow q_0 = \sqrt{(0.5)(2)(1 \times 10^{-6})}$$
$$\Rightarrow q_0 = 1 \times 10^{-3} \text{ C}$$
$$q(t) = q_0 e^{-t/RC}$$
$$q(t=0.4\text{s}) = 1 \times 10^{-3} e^{-0.4 / (1 \times 10^{-6} \times 1 \times 10^6)} \text{ C}$$
$$= 10^{-3} e^{-0.4} = 6.7 \times 10^{-4} \text{ C}$$

Q6

F-112-16

A capacitor of capacitance C is connected to a 12-V battery, as shown in the figure. First, switch S_2 was open, and switch S_1 was closed until the capacitor is fully charged. Then, S_1 is open and S_2 is closed. If the voltage across the capacitor decays and reaches 6.0 V after 0.10 s, the capacitance C is equal to

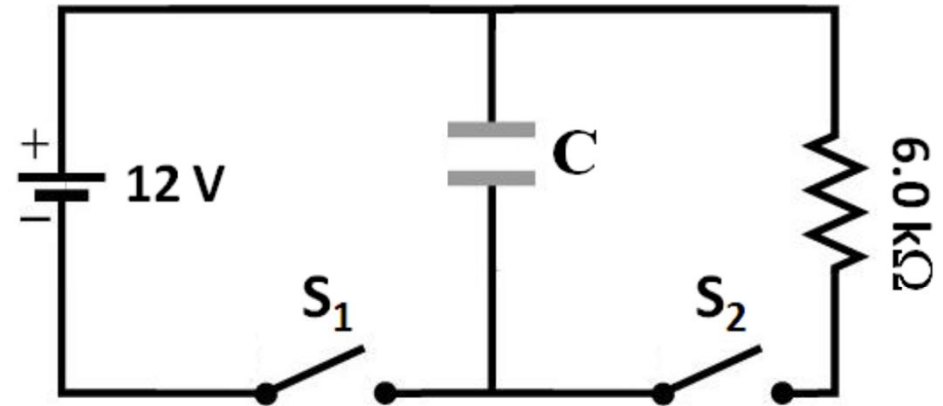- A) 24 μF
- B) 11 μF
- C) 14 μF
- D) 140 μF
- E) 47 μF



$$q_0 = C(12)$$

$$q(t) = q_0 e^{-t/RC}$$

$$V(t) = \frac{q(t)}{C} = \frac{q_0}{C} e^{-t/RC}$$

$$V(t) = \frac{q(12)}{C} e^{-t/RC} \Rightarrow 6 = 12 e^{-0.1/RC}$$

$$\ln \frac{6}{12} = \ln e^{-0.1/RC} \Rightarrow \ln 2 = \frac{0.1}{RC} \Rightarrow C = \frac{0.1}{R \ln 2}$$

$$\Rightarrow C = \frac{0.1}{(6 \times 10^3) \ln 2} = 24 \mu\text{F}$$