

Recitation 10

•1 The two metal objects in Fig. 25-24 have net charges of $+70 \text{ pC}$ and -70 pC , which result in a 20 V potential difference between them.

(a) What is the capacitance of the system? (b) If the charges are changed to $+200 \text{ pC}$ and -200 pC , what does the capacitance become? (c) What does the potential difference become?



Fig. 25-24 Problem 1.

a)

$$C = \frac{q}{V} = \frac{70 \text{ pC}}{20 \text{ V}} = 3.5 \text{ pF.}$$

b) Same.

c)

$$V_2 = \frac{q_2}{C} = \frac{200 \text{ pC}}{3.5 \text{ pF}} = 57 \text{ V.}$$

••13 **SSM** **ILW** A 100 pF capacitor is charged to a potential difference of 50 V, and the charging battery is disconnected. The capacitor is then connected in parallel with a second (initially uncharged) capacitor. If the potential difference across the first capacitor drops to 35 V, what is the capacitance of this second capacitor?

$$q_1 + q_2 = q = C_1 V.$$

$$V_1 = V_2 = V'.$$

$$q_1 = C_1 V'.$$

$$q_2 = C_1 V - q_1 = C_1 V - C_1 V' = C_1 (V - V')$$

$$C_2 = \frac{q_2}{V'} = C_1 \frac{V - V'}{V'} = (100 \text{ pF}) \frac{50 \text{ V} - 35 \text{ V}}{35 \text{ V}} = 43 \text{ pF}.$$

••21 **SSM** **WWW** In Fig. 25-36, the capacitances are $C_1 = 1.0 \mu\text{F}$ and $C_2 = 3.0 \mu\text{F}$, and both capacitors are charged to a potential difference of $V = 100 \text{ V}$ but with opposite polarity as shown. Switches S_1 and S_2 are now closed. (a) What is now the potential difference between points a and b ? What now is the charge on capacitor (b) 1 and (c) 2?

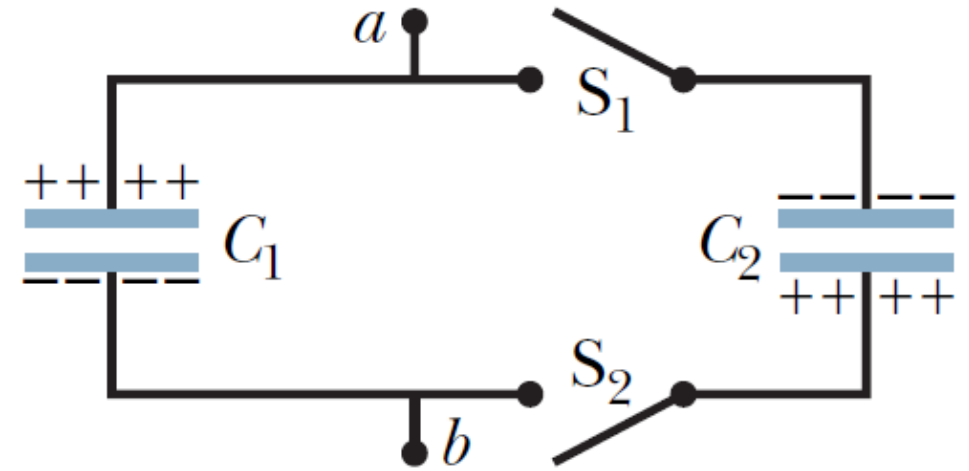


Fig. 25-36 Problem 21.

a)

$$q = q_2 - q_1 = (C_2 - C_1)V$$

$$V' = \frac{q}{C_{\text{eq}}} = \frac{C_2 - C_1}{C_2 + C_1} V = \frac{3.0 \mu\text{F} - 1.0 \mu\text{F}}{3.0 \mu\text{F} + 1.0 \mu\text{F}} (100 \text{ V}) = 50 \text{ V}.$$

b)

$$q_1 = C_1 V' = (1.0 \mu\text{F})(50 \text{ V}) = 50 \mu\text{F}.$$

c)

$$q_2 = C_2 V' = (3.0 \mu\text{F})(50 \text{ V}) = 150 \mu\text{F}.$$

••37 **SSM** **ILW** **WWW** The parallel plates in a capacitor, with a plate area of 8.50 cm^2 and an air-filled separation of 3.00 mm , are charged by a 6.00 V battery. They are then disconnected from the battery and pulled apart (without discharge) to a separation of 8.00 mm . Neglecting fringing, find (a) the potential difference between the plates, (b) the initial stored energy, (c) the final stored energy, and (d) the work required to separate the plates.

a)

$$V_2 = E d_2 = \frac{V_1}{d_1} d_2 = \frac{6.00 \text{ V}}{3.00 \text{ mm}} (8.00 \text{ mm}) = 16.0 \text{ V.}$$

b)

$$C_1 = \epsilon_0 \frac{A}{d_1} = (8.85 \text{ pF}) \frac{8.50 \times 10^{-4} \text{ m}^2}{3.00 \times 10^{-3} \text{ m}} = 2.51 \text{ pF.}$$

$$U_1 = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (2.51 \text{ pF})(6.00 \text{ V})^2 = 45.1 \text{ pJ.}$$

c)

$$U_2 = U_1 \frac{d_2}{d_1} = 45.1 \text{ pJ} \frac{8.00 \text{ mm}}{3.00 \text{ mm}} = 120 \text{ pJ.}$$

d)

$$W = U_2 - U_1 = 75.2 \text{ pJ.}$$

••54 Two parallel plates of area 100 cm^2 are given charges of equal magnitudes $8.9 \times 10^{-7} \text{ C}$ but opposite signs. The electric field within the dielectric material filling the space between the plates is $1.4 \times 10^6 \text{ V/m}$. (a) Calculate the dielectric constant of the material. (b) Determine the magnitude of the charge induced on each dielectric surface.

a)

$$E_0 = \frac{V}{d} = \frac{q}{Cd} = \frac{q}{(\epsilon_0 A/d)d} = \frac{q}{\epsilon_0 A} = \frac{8.9 \times 10^{-7} \text{ C}}{(8.85 \text{ pF})(100 \times 10^{-4} \text{ m}^2)}$$
$$= 1.0 \times 10^7 \frac{\text{V}}{\text{m}}.$$

$$\kappa = \frac{E_0}{E} = \frac{1.0 \times 10^7 \text{ V/m}}{1.4 \times 10^6 \text{ V/m}} = 7.2.$$


b)


$$q - q' = \frac{q}{\kappa}$$


or


$$q' = (1 - 1/\kappa)q = (1 - 1/7.2)(8.9 \times 10^{-7} \text{ C}) = 7.7 \times 10^{-7} \text{ C}.$$

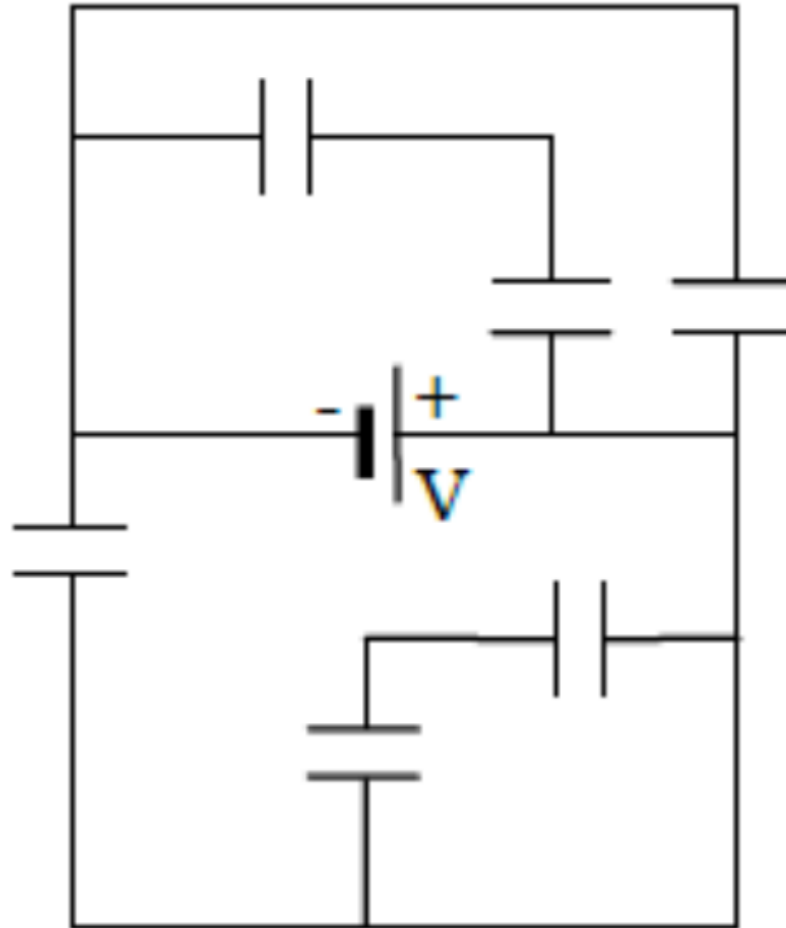
Δ□58. Consider the circuit of identical capacitors shown in figure 28. A potential difference of $2.0 \times 10^2 \text{ V}$ is applied by the battery V . Calculate the energy stored in the system if the capacitance of each capacitor is $50 \mu\text{F}$.
 (Ans: 2.5 J)




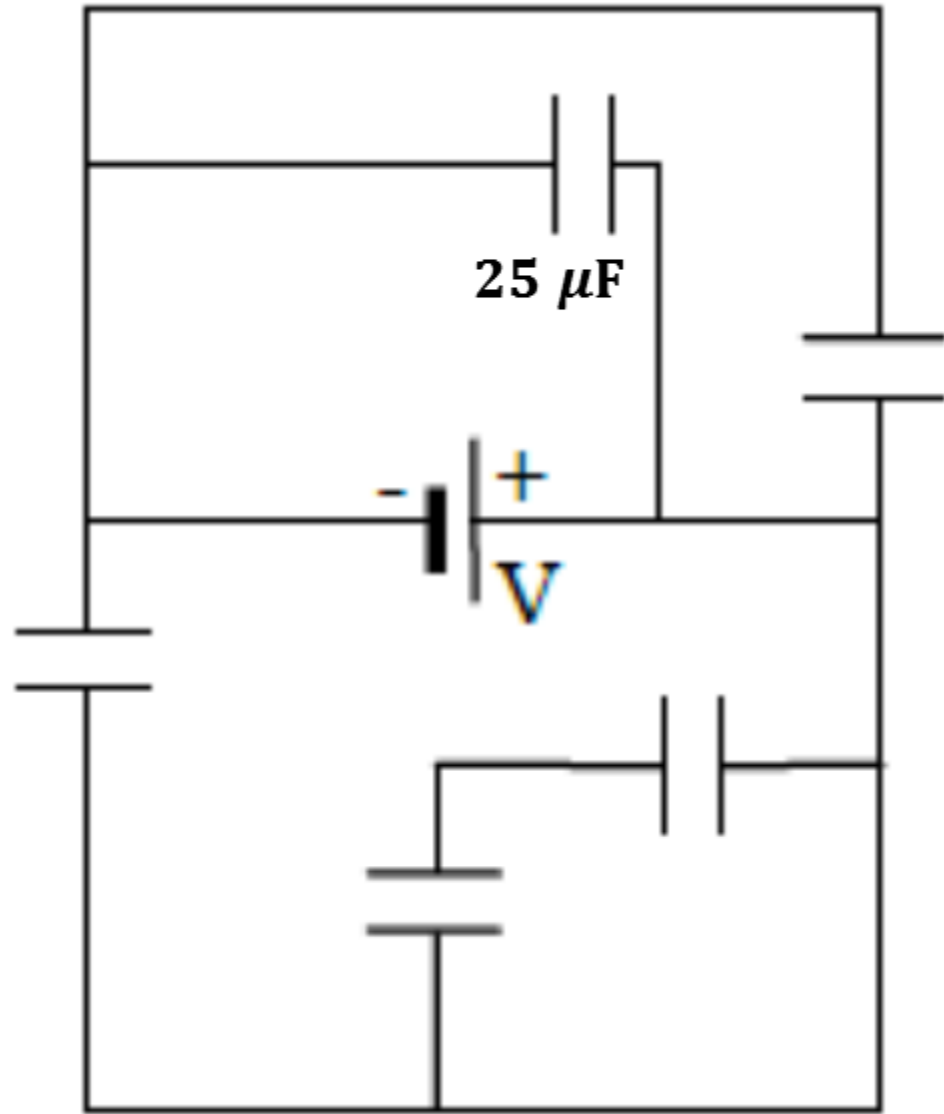


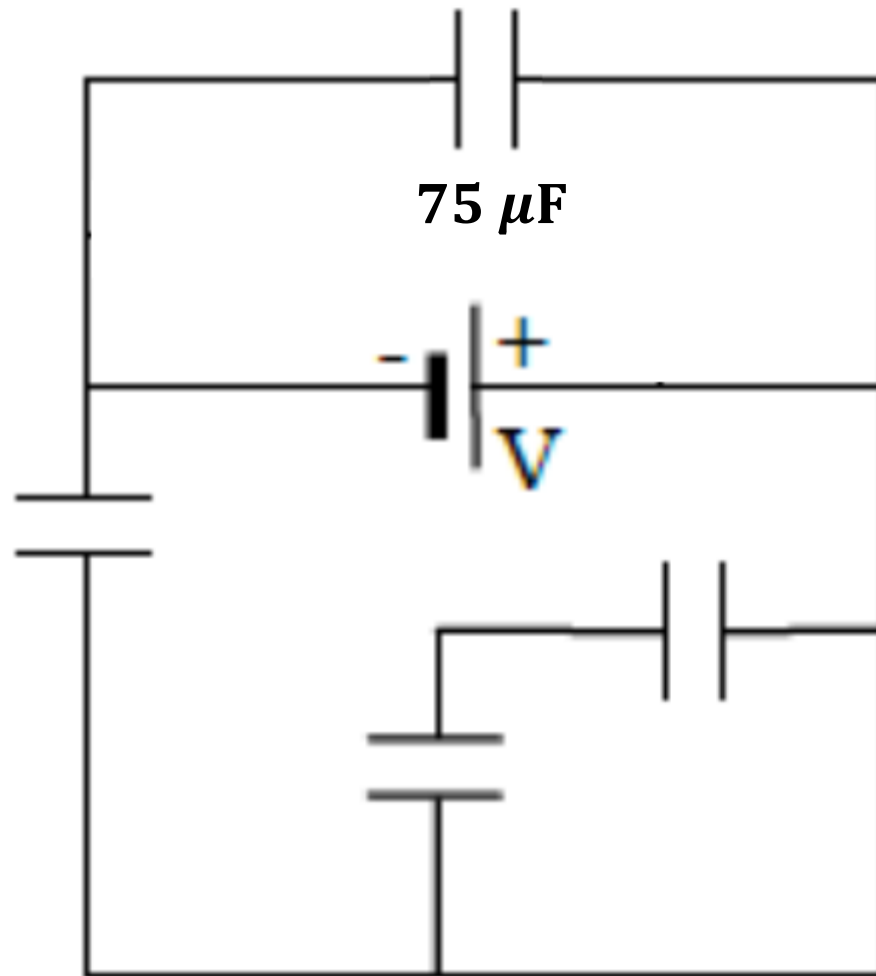

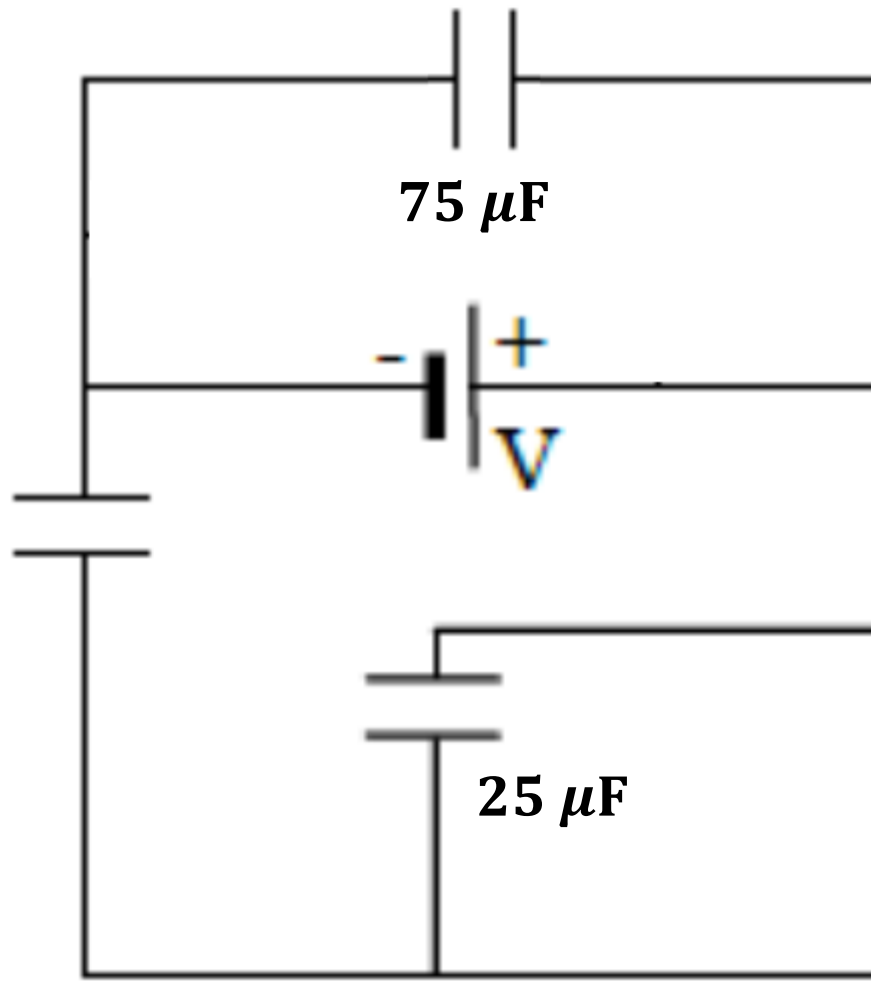

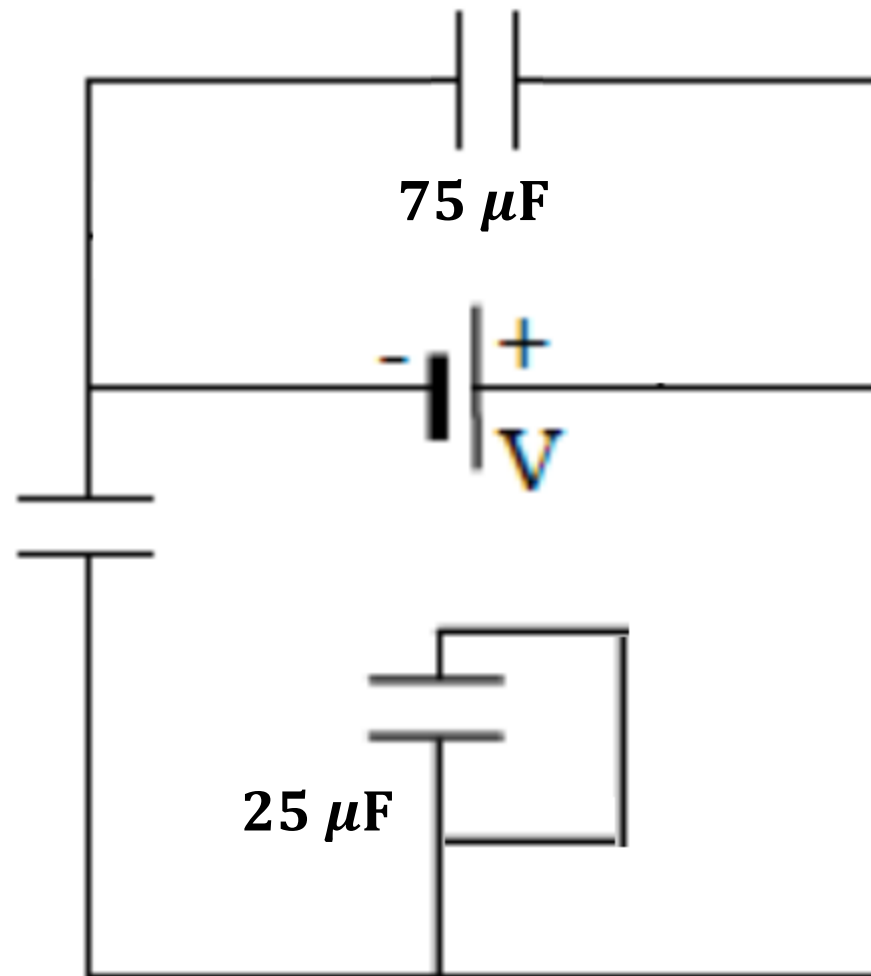

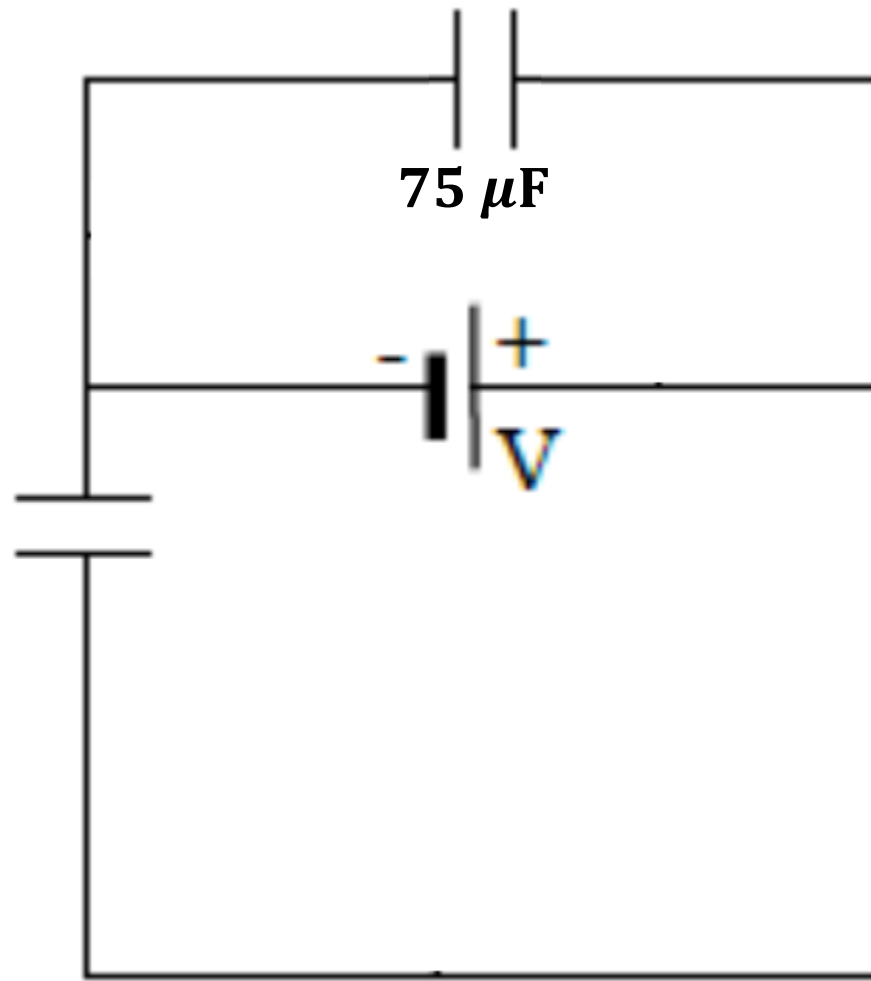

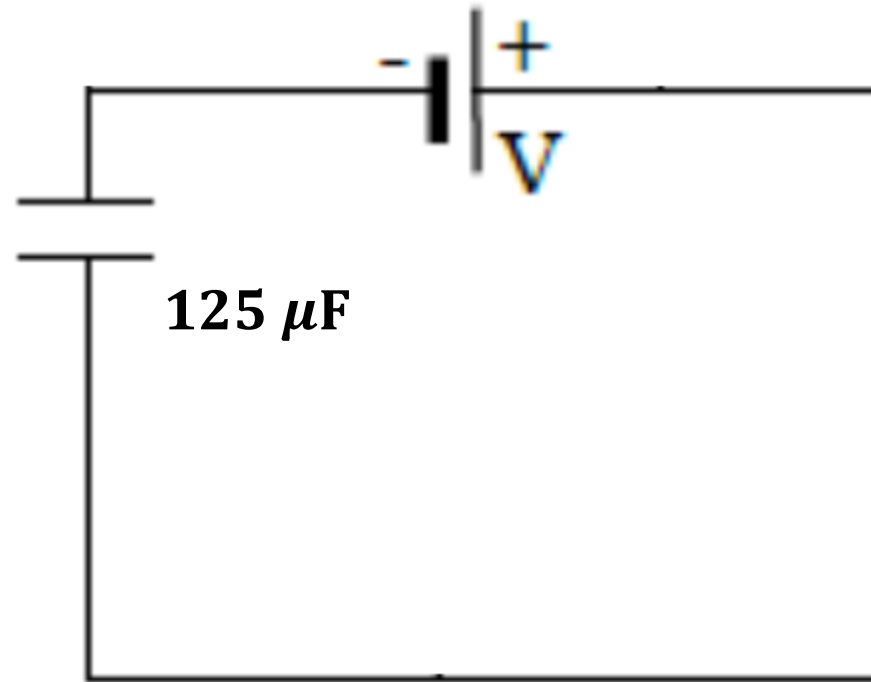

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (125 \mu\text{F})(200)^2 = 2.5 \text{ J}$$