

COE 202, Term 162

Digital Logic Design


Assignment# 3 Solution

Due date: Thursday, April 27

- Q.1.** It is required to design a circuit that receives two **4-bit** signed numbers in 2's complement representation $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$ and produces a **6-bit output** $C = C_5C_4C_3C_2C_1C_0$. The circuit implements the following functions based on the values of the two selection inputs: S1 and S0.

S1 S0	Function
0 0	$C = A + B$
0 1	$C = A - B$
1 0	$C = 2A + 1$
1 1	$C = 2A - 1$

 - (i) Show the block diagram design of your circuit using MSI components like Adder, Multiplexor, as needed. Use only one adder in your solution.



- (ii) Model your design in Verilog by modeling each component separately i.e. adder, MUX, etc. and then instantiating these components to model your circuit.

```

module adder #(parameter width = 6)
(output cout, output [width-1:0] sum,
input [width-1:0] a, b, input cin);
    assign {cout, sum} = a + b + cin;
endmodule

module mux2x1 #(parameter width = 6)
(output [width-1:0] c,
input [width-1:0] a, b, input select);
    assign c = (select ? a : b);
endmodule

module mux4x1 #(parameter width = 6)
(output reg [width-1:0] y,
input [width-1:0] a, b, c, d, input s1, s0);
always @ (a, b, c, d, s1, s0) begin
case ({s1, s0})
    2'b 00 : y = d;
    2'b 01 : y = c;
    2'b 10 : y = b;
    2'b 11 : y = a;
endcase
end
endmodule

module ALU
(output cout, output [5:0] c,
input [3:0] a, b, input s1, s0);

wire [5:0] T1, T2;

mux2x1 M1 (T1, {a[3], a, 1'b0}, {a[3],a[3],a}, s1);
mux4x1 M2 (T2, 6'b111110, 6'b1, ~{b[3],b[3],b}, {b[3],b[3],b}, s1, s0);
adder M3 (cout, c, T1, T2, s0);

endmodule

```

- (iii) Write a Verilog test bench to test your design and verify its correctness by simulation. Show snapshots of your simulation to demonstrate its correctness. For each function, test at least 2 input combinations of your choice to demonstrate correct functionality.

```

module ALU_Test();

reg [3:0] A, B;
reg s1, s0;
wire Cout;
wire [5:0] C;

ALU M1 (Cout, C, A, B, s1, s0);

initial begin
s1=0; s0=0; A=4'b0101; B=4'b0111;
#100 A=4'b0100; B=4'b1111;
#100 A=4'b0111; B=4'b0111;
#100 A=4'b1000; B=4'b1000;
#100 s1=0; s0=1; A=4'b0110; B=4'b0011;
#100 A=4'b1110; B=4'b1111;
#100 A=4'b1000; B=4'b0111;
#100 s1=1; s0=0; A=4'b0010;
#100 A=4'b1111;
#100 A=4'b0111;
#100 A=4'b1000;
#100 s1=1; s0=1; A=4'b0111;
#100 A=4'b1111;
#100 A=4'b1000;
end
endmodule

```

The test bench has been simulated and can be seen from the simulation waveform given below, the ALU is functioning correctly.

