

# King Fahd University of Petroleum & Minerals Computer Engineering Dept

---

**COE 202 – Fundamentals of Computer  
Engineering**

**Term 081**

**Dr. Ashraf S. Hasan Mahmoud**

**Rm 22-148-3**

**Ext. 1724**

**Email: [ashraf@kfupm.edu.sa](mailto:ashraf@kfupm.edu.sa)**

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

1

## Counter

---

- **Counter:** A register (sequential circuit) that goes through a pre-determined sequence of states upon the application of input (clock or other source) pulses
- **Binary Counter:** The sequence of the states follows the binary number sequence (e.g. 000 → 001 → 010 → 011 → etc.)
  - n-bit binary counter requires n flip-flops – counts from 0 to  $2^n - 1$
- Two Types of Counters:
  1. Ripple counter:
    - Flip-flop output transition serves as source for triggering the other flip-flops
  2. Synchronous counter: the clock input of all flip-flops receive the common clock signal

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

2

# Binary Counter

## Counting Sequence for Binary Number



No	Upward Counting Sequence				No	Downward Counting Sequence			
	Q3	Q2	Q1	Q0		Q3	Q2	Q1	Q0
0	0	0	0	0	15	1	1	1	1
1	0	0	0	1	14	1	1	1	0
2	0	0	1	0	13	1	1	0	1
3	0	0	1	1	12	1	1	0	0
4	0	1	0	0	11	1	0	1	1
5	0	1	0	1	10	1	0	1	0
6	0	1	1	0	9	1	0	0	1
7	0	1	1	1	8	1	0	0	0
8	1	0	0	0	7	0	1	1	1
9	1	0	0	1	6	0	1	1	0
10	1	0	1	0	5	0	1	0	1
11	1	0	1	1	4	0	1	0	0
12	1	1	0	0	3	0	0	1	1
13	1	1	0	1	2	0	0	1	0
14	1	1	1	0	1	0	0	0	1
15	1	1	1	1	0	0	0	0	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

3

# 4-bit Ripple Counter

 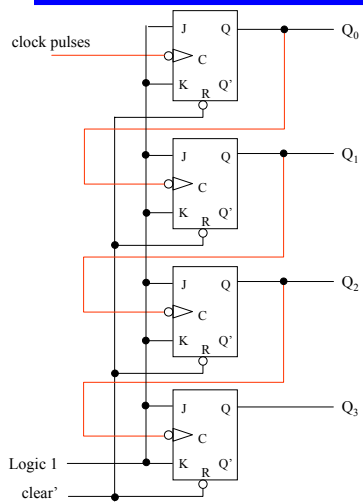

How to modify this circuit to count downwards:  
 1. Use Q' as input to C  
 2. Use +ve edge triggered f/f

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

4

## **Ripple Counter**

---

- Advantages:
  - Simple hardware
- Disadvantages:
  - Asynchronous – delay dependent
- Good for low power circuits

## **Synchronous Binary Counter**

---

- Clock pulses are applied to the inputs of all of the flip-flops.
- Design of binary counters
  - Same as we learned in Chapter 4!

## Example: 4-bit Binary Counter

State Table and Flip-Flops Inputs for Binary Counter

Present State				Next State				Flip-flops inputs							
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>Q3</sub>	K <sub>Q3</sub>	J <sub>Q2</sub>	K <sub>Q1</sub>	J <sub>Q1</sub>	K <sub>Q1</sub>	J <sub>Q0</sub>	K <sub>Q0</sub>
0	0	0	0	0	0	0	1	0	X	0	X	0	X	0	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

7

## Example: 4-bit Binary Counter – cont'd

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	0	0	0	0
01	00	0	0	1	0
11	00	x	x	x	x
10	00	x	x	x	x

$$J_{Q3} = Q_0Q_1Q_2$$

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	0	0	1	0
01	00	x	x	x	x
11	00	x	x	x	x
10	00	0	0	1	0

$$J_{Q2} = Q_0Q_1$$

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	0	1	x	x
01	00	0	1	x	x
11	00	0	1	x	x
10	00	0	1	x	x

$$J_{Q1} = Q_0$$

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	x	x	x	x
01	00	x	x	x	x
11	00	0	0	1	0
10	00	0	0	0	0

$$K_{Q3} = Q_0Q_1Q_2$$

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	x	x	x	x
01	00	0	0	1	0
11	00	0	0	1	0
10	00	x	x	x	x

$$K_{Q2} = Q_0Q_1$$

Q <sub>3</sub> Q <sub>2</sub>	Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
00	00	x	x	1	0
01	00	x	x	1	0
11	00	x	x	1	0
10	00	x	x	1	0

$$K_{Q1} = Q_0$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

8

## Example: 4-bit Binary Counter – Implementation

$Q_3Q_2$	$Q_1Q_0$	00	01	11	10
00		1	x	x	1
01		1	x	x	1
11		1	x	x	1
10		1	x	x	1

$$J_{Q_0} = 1$$

$Q_3Q_2$	$Q_1Q_0$	00	01	11	10
00		x	1	1	x
01		x	1	1	x
11		x	1	1	x
10		x	1	1	x

$$K_{Q_0} = 1$$

$$J_{Q_3} = Q_0Q_1Q_2$$

$$K_{Q_3} = Q_0Q_1Q_2$$

$$J_{Q_2} = Q_0Q_1$$

$$K_{Q_2} = Q_0Q_1$$

$$J_{Q_1} = Q_0$$

$$K_{Q_1} = Q_0$$

$$J_{Q_0} = 1$$

$$K_{Q_0} = 1$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

9

## Example: 4-bit Binary Counter – Implementation - continued

- Sometimes it is desirable to control the counter operation by added a count enable signal: En
  - When En = 1 → counter counts
  - When En = 0 → counter holds state (stops counting)
- Hence the new input equations are:

$$J_{Q_3} = Q_0Q_1Q_2En, \quad K_{Q_3} = Q_0Q_1Q_2En$$

$$J_{Q_2} = Q_0Q_1En, \quad K_{Q_2} = Q_0Q_1En$$

$$J_{Q_1} = Q_0En, \quad K_{Q_1} = Q_0En$$


$$J_{Q_0} = En, \quad K_{Q_0} = En$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

10
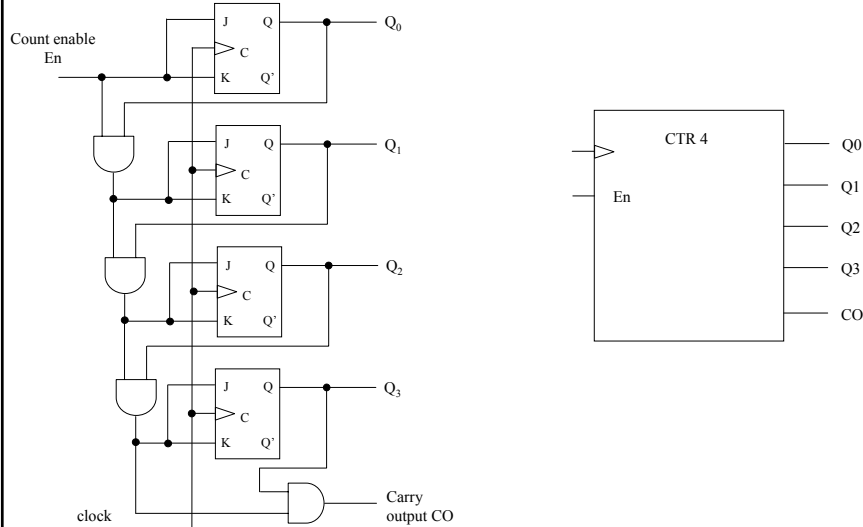
## Example: 4-bit Binary Counter – Circuit



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

11

## Notes on Binary Synchronous Counter

- When  $En = 0 \rightarrow J = K = 0 \rightarrow$  flip-flop holds state
- For general  $n$ -bit binary synchronous counter the input equation for the  $i$ th  $JK$  flip-flop is:

$$J_{Q_i} = K_{Q_i} = Q_0 Q_1 Q_2 \dots Q_{i-1} Q_i En$$

- The CO output can be used to extend the counter to more stages (How?)

If we use a -ve edge triggered clock, will this circuit count downwards?

Draw the state diagram for this counter?

- Binary synchronous counters are MOST efficiently constructed with complementing  $T$  or  $JK$  flip-flops – but can be designed with  $D$  flip-flops

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

12

## Problem: 4-bit Binary Counter with D flip-flops

**Problem:** Design a 4-bit binary synchronous counter with counter enable (En) signal

**Solution:**

### State Table and Flip-Flop inputs for Binary Counter

Present State				Next State				Flip-flops inputs			
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	D <sub>03</sub>	D <sub>02</sub>	D <sub>01</sub>	D <sub>00</sub>
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	0
1	0	0	0	1	0	0	1	1	0	0	1
1	0	0	1	1	0	1	0	1	0	1	0
1	0	1	0	1	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1	1	0	0
1	1	0	0	1	1	0	1	1	1	0	1
1	1	0	1	1	1	1	0	1	1	1	0
1	1	1	0	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0	0	0	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

13

## Problem: 4-bit Binary Counter with D flip-flops – cont'd

- The flip-flops input equations are given by:

Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
Q <sub>3</sub> Q <sub>2</sub>				
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	0	0	1

$$D_{Q0} = Q_0' = Q_0 \oplus 1$$

Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
Q <sub>3</sub> Q <sub>2</sub>				
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$D_{Q1} = Q_0 Q_1' + Q_0' Q_1 = Q_1 \oplus Q_0$$

Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
Q <sub>3</sub> Q <sub>2</sub>				
00	0	0	1	0
01	1	1	0	1
11	1	1	0	1
10	0	0	1	0

$$D_{Q2} = Q_0 Q_1 Q_2' + Q_1' Q_2 + Q_0' Q_2 = Q_2 \oplus (Q_0 Q_1)$$

Q <sub>1</sub> Q <sub>0</sub>	00	01	11	10
Q <sub>3</sub> Q <sub>2</sub>				
00	0	0	0	0
01	0	0	1	0
11	1	1	0	1
10	1	1	1	1

$$D_{Q3} = Q_0 Q_1 Q_2 Q_3' + Q_2' Q_3 + Q_1' Q_3 + Q_0' Q_3 = Q_3 \oplus (Q_2 Q_1 Q_0)$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

14

## Problem: 4-bit Binary Counter with D flip-flops – cont'd


- Rewriting the input equations and using the count enable signal En:

$$D_{Q_0} = Q_0' = Q_0 \oplus 1$$

$$D_{Q_1} = Q_0 Q_1' + Q_0' Q_1 = Q_1 \oplus Q_0$$

$$D_{Q_2} = Q_0 Q_1 Q_2' + Q_1' Q_2 + Q_0' Q_2 = Q_2 \oplus (Q_0 Q_1)$$
 
$$D_{Q_3} = Q_0 Q_1 Q_2 Q_3' + Q_2' Q_3 + Q_1' Q_3 + Q_0' Q_3 = Q_3 \oplus (Q_2 Q_1 Q_0)$$



Note: when En = 0, the Qi is input to DQi → i.e flip-flop holds state

$$D_{Q_0} = Q_0 \oplus En = Q_0' \text{ if } En = 1 \\ = Q_0 \text{ if } En = 0$$

$$D_{Q_1} = Q_1 \oplus (Q_0 En) = Q_0 Q_1' + Q_0' Q_1 \text{ if } En = 1 \\ = Q_1 \text{ if } En = 0$$

$$D_{Q_2} = Q_2 \oplus (Q_0 Q_1 En) = Q_0 Q_1 Q_2' + Q_1' Q_2 + Q_0' Q_2 \text{ if } En = 1 \\ = Q_2 \text{ if } En = 0$$

$$D_{Q_3} = Q_3 \oplus (Q_2 Q_1 Q_0 En) = Q_0 Q_1 Q_2 Q_3' + Q_2' Q_3 + Q_1' Q_3 + Q_0' Q_3 \text{ if } En = 1 \\ = Q_3 \text{ if } En = 0$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud


15

## Problem: 4-bit Binary Counter with D flip-flops – Circuit Diagram

- Notes:

- For a general n-bit counter, the  $i^{\text{th}}$  D flip-flop input equation is given by:
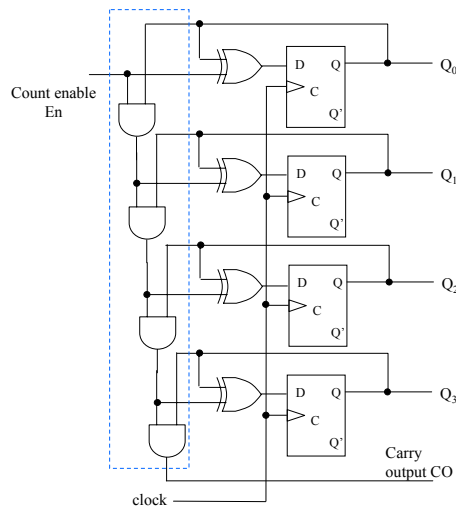
$$D_{Q_i} = Q_i \oplus (Q_0 Q_1 \dots Q_{i-1} En)$$



1/11/2009


Dr. Ashraf S. Hasan Mahmoud

16


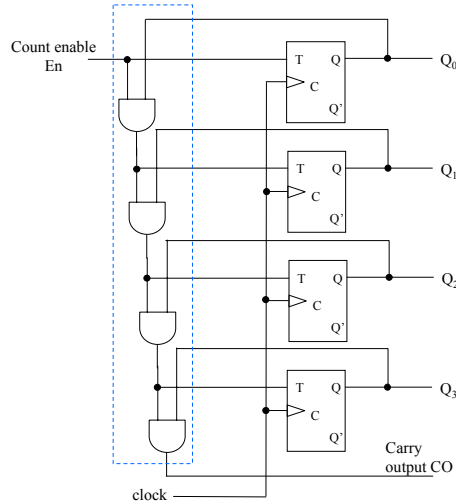
## Exercise: 4-bit Binary Counter with T flip-flops

- 👉 **Problem:** Verify that the circuit shown in Figure is a 4-bit synchronous binary counter  
 (Hint: Draw the timing diagram)




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

17
 
## What is the Use of the CO signal? Design of 8-bit Binary Counter

- Using 4-bit counters with carry out signal one can construct larger counters by using the carry out signal from one stage as the enable signal of the next
- Figure shows 2 4-bit binary counters connected in series to form an 8-bit binary counter
- Exercise:** Draw the timing diagram showing clock, Q0, Q1, Q2, Q3, CO1, Q4, Q5, Q6, Q7, and CO2



1/11/2009


Dr. Ashraf S. Hasan Mahmoud

18
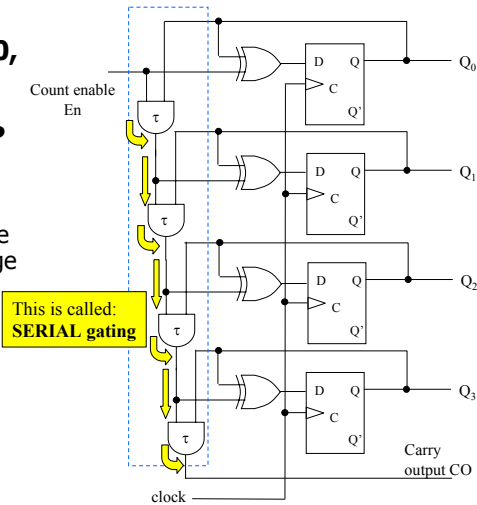
## Serial and Parallel Counters

- **When counter changes state from 1111 to 0000, how many AND gate delays there will be before CO is generated?**

- **Answer:** FOUR. Because stage 1 requires one AND gate delay to know the state change in  $Q_0$ ; stage 2 requires one additional AND gate delay to know the state change in  $Q_1$ ; stage 3 requires one additional AND gate delay to know the state change in  $Q_2$ ; and to generate CO, one more AND gate delay is required.




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

SERIAL counter

19

## Timing Diagram for Serial Gating

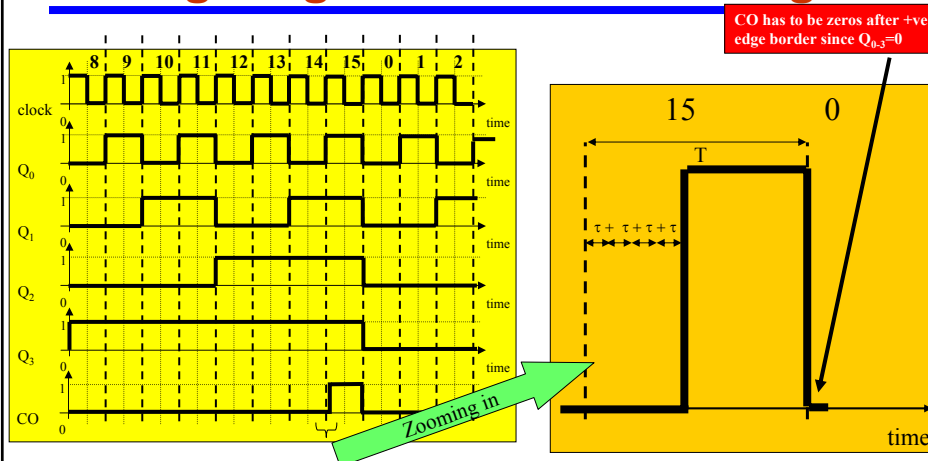

What happens if  $4\tau$  is greater than  $T$ ?

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

20

## Why Serial Gating is Bad?

- Delay taken when CO signal is generated – if this CO signal is used to drive another counter (refer to 8-bit counter construction) → cumulative delay may exceed clock pulse (or cumulative delay limits speed of counting – clock frequency)
- Not good for design of fast counters
- **Solution:** Use parallel gating!

This problem is similar to the delay problem we faced with the ripple carry adder. The parallel gating is analogous to the carry lookahead adder idea where the required signals are Generated without propagating the f/f status from Q0 to Q1 to Q2 to Q3


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

21
 
## Parallel Gating

- For the D flip-flop synchronous binary counter, the equations for parallel gating can be taken directly from the AND terms in the flip-flop input equations on slide 15



parallel counter: ONE AND gate delay ( $\tau$ ) is required to generate CO


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

22
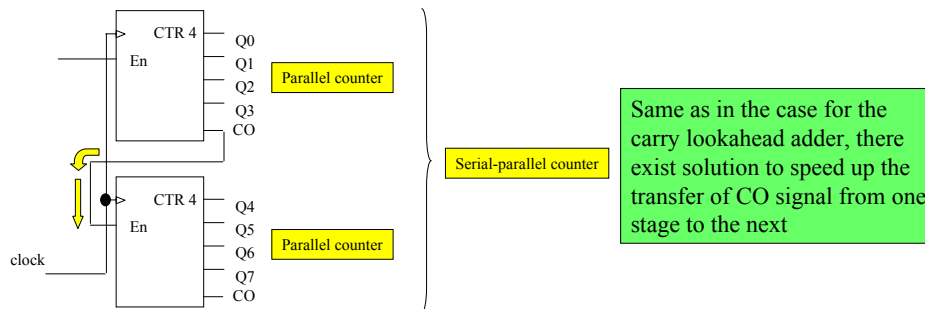
## Serial-Parallel Counter

- Each stage (4-bit counter) is constructed using parallel gating
- Stages are connected in series by using the CO output of one stage as the counter enable input of the next state



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

23

## Problem: Parallel Counter Design – Maximum Frequency

**Problem:** A 64-bit synchronous parallel counter is to be designed


- (a) Draw the logic diagram of a 64-bit parallel counter using 8-bit parallel counter blocks and two levels of parallel gating connections between the blocks. In these blocks CO is not driven by En

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

24

## Problem: Solution

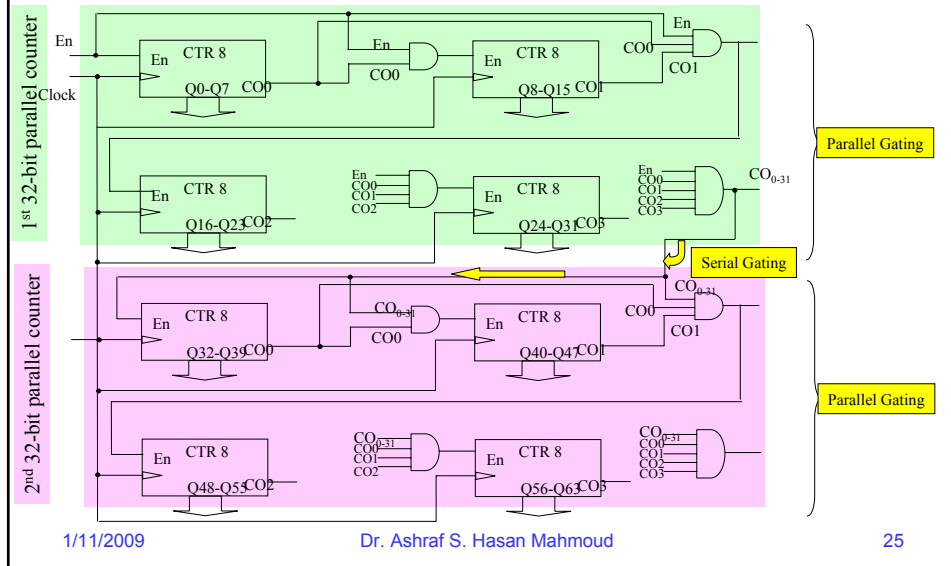

## Problem: Solution – cont'd

- Notes:
  - Each of the CTR 8 blocks is a parallel counter (i.e. it uses parallel gating)
  - The 32-bit counter resulting from connecting the first (or second) 4 8-bit block counters is also a parallel counter since it uses parallel gating to generate the CO signals
  - The 2 32-bit counters are serially connected to form the required 64-bit counter



• Would it be possible to use only parallel gating to obtain the 64-bit counter? What would be the maximum fan in for the used AND gates in this case?

## Synchronous Binary Down-Counter

- **Problem:** Design a 4-bit synchronous  $T$  flip-flop down-counter.
- **Solution:** (show that the previous circuits work as a down-counter if we use  $Q'$  instead of  $Q$  in the input equations; i.e. the as input to the AND gates – This applies to the  $JK$  flip-flop counter on slide 11, the  $D$  flip-flop counter on slide 16 and the  $T$  flip-flop counter on slide 17)

1/11/2009

Dr. Ashraf S. Hasan Mahmoud


27

Refer to problem solved in the previous package – same problem but using JK F/Fs

## Up-Down Binary Counter

- **Problem:** Design a synchronous up-down  $T$  flip-flop 2-bit binary counter with a select input line  $S$  and a count enable  $En$  input. When  $S = 0$ , the counter counts down; and when  $S = 1$ , the counter counts up. When  $En = 1$ , the counter is in normal up- or down- counting; and  $En = 0$  for disabling both counts.
- **Solution:** Required mode of operation:

Functional Table:

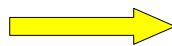


Inputs		Operation
En	S	
0	x	Hold status
1	0	Count Down
1	1	Count Up

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

28
 
## State Diagram/Table for 2-bit Up-Down Binary Counter



Arc Label: EnS

T Flip-Flop		
Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

No	Present State		Inputs		Next State			T flip-flops	
	Q1	Q0	En	S	No	Q1	Q0	T <sub>Q1</sub>	T <sub>Q0</sub>
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0
0	0	0	1	0	3	1	1	1	1
0	0	0	1	1	1	0	1	0	1
1	0	1	0	0	1	0	1	0	0
1	0	1	0	1	1	0	1	0	0
1	0	1	1	0	0	0	0	0	1
1	0	1	1	1	2	1	0	1	1
2	1	0	0	0	2	1	0	0	0
2	1	0	0	1	2	1	0	0	0
2	1	0	1	0	1	0	1	1	1
2	1	0	1	1	3	1	1	0	1
3	1	1	0	0	3	1	1	0	0
3	1	1	0	1	3	1	1	0	0
3	1	1	1	0	2	1	0	0	1
3	1	1	1	1	0	0	0	1	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

29

## Input Equations for 2-bit Up-Down Binary Counter

EnS	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	0	0	1	0
10	0	0	0	1

$$T_{Q1} = Q_0 \text{EnS} + Q_0' \text{EnS}'$$

EnS	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$T_{Q0} = \text{En}$$

- The carry out signals:

- $\text{CO}_{\text{up}}$  and  $\text{CO}_{\text{down}}$

$\text{CO}_{\text{up}} = Q_0 Q_1 \text{EnS} \rightarrow$  counter reached 11 and it is counting up

$\text{CO}_{\text{down}} = Q_0' Q_1' \text{EnS}' \rightarrow$  counter reached 00 and it is counting down

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

30


## Circuit for 2-bit Up-Down Binary Counter

$$T_{Q1} = Q_0 En S + Q_0' En S'$$

$$T_{Q0} = En$$

$$CO_{up} = Q_0 Q_1 En S$$

$$CO_{down} = Q_0' Q_1' En S'$$

 

The F/Fs can be +ve or -ve edge triggered  
 This would NOT affect the equations or the implementation  
 It would, however, effect when the F/Fs can change state  
 – see the timing diagram on next slide


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

31

## Circuit for 2-bit Up-Down Binary Counter – Timing Diagrams

Assume  $En = 1$   
 -ve edge trig F/Fs

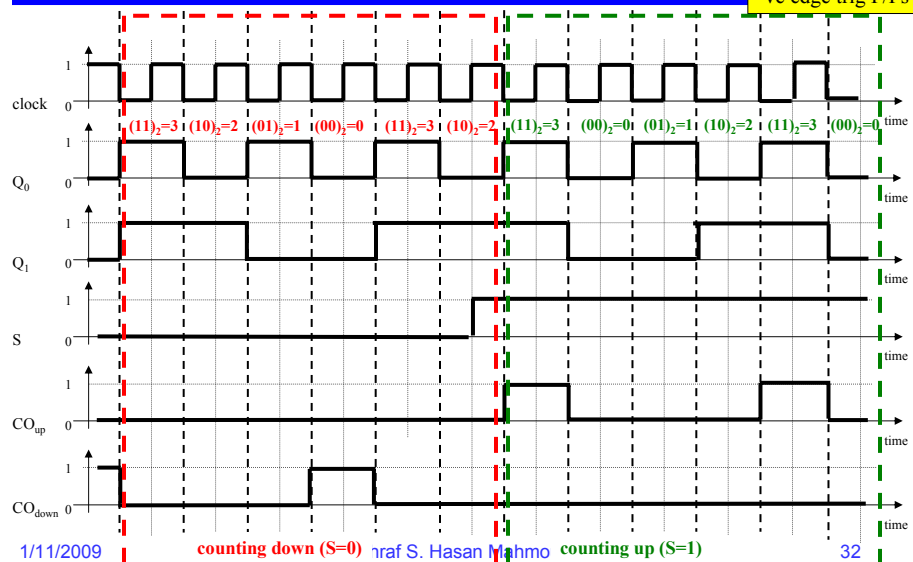



## 4-bit Up-Down Binary Counter

- You can show that input equations for 4-bit up-down binary counter are given by (compare to 2-bit case):

$$TQ_0 = E_n$$

$$TQ_1 = Q_0.S.E_n + Q_0'.S'.E_n$$

$$TQ_2 = Q_1.Q_0.S.E_n + Q_1'.Q_0'.S'.E_n$$

$$TQ_3 = Q_2.Q_1.Q_0.S.E_n + Q_2'.Q_1'.Q_0'.S'.E_n$$


$$CO_{up} = Q_0.Q_1.Q_2.Q_3.S.E_n$$

$$CO_{down} = Q_0'.Q_1'.Q_2'.Q_3'.S'.E_n$$

## Binary Counter with Parallel Load

- **Counter with parallel load:** capability for transferring an initial binary number into the counter prior to the count operation

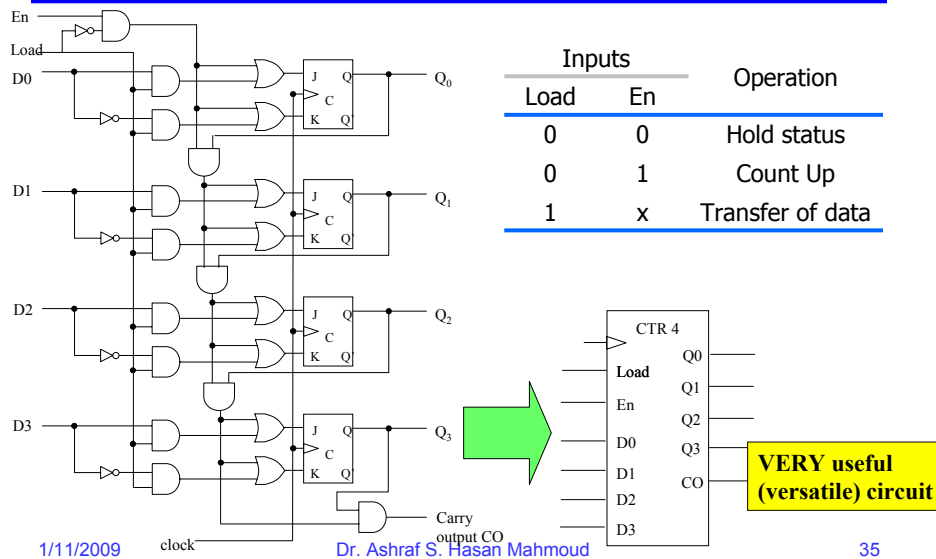
## Binary Counter with Parallel Load - Circuit


 
## BCD Counter

- **BCD Counter:**  
0000 → 0001 → 0010 → ... → 1000 → 1001 → 0000 → 0010 → ...
- We can use the use binary counter with load (previous slide) as follows:

Note: When  $Q_3Q_2Q_1Q_0 = 1001$ , the load signal is equal to 1 and the counter loads 0000 and starts counting again



## Other Counters

---

- **Divide-by-N counter OR Modulo-N counter:** A counter that goes through a repeated sequence of N state
- This is the general definition of the counter
- The 4-bit Binary counter → divide-by-16 counter or modulo-16 counter (because we have 16 states)

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

37

## BCD Counter - Revisited

---

- **Problem:** Design a BCD counter (without  $E_n$ ) using  $T$  flip-flops with an output signal that can be used to extend the counter
- **Solution:**
  - Let's design one state (4-bit BCD which counts  $0000 \rightarrow 0001 \rightarrow \dots \rightarrow 1000 \rightarrow 1001 \rightarrow 0000 \rightarrow \dots$ )
  - Use the output 1001 to generate the carry out signal

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

38

## BCD Counter – State Table

7 Flip-Flop			Present State				Next State				Output	Flip-flops inputs			
Q(t)	Q(t+1)	T	Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>8</sub>	Q <sub>4</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Y	T <sub>Q8</sub>	T <sub>Q4</sub>	T <sub>Q2</sub>	T <sub>Q1</sub>
0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1
0	1	1	0	0	0	1	0	0	1	0	0	0	0	1	1
1	0	1	0	0	1	0	0	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	1	0	0	0	0	1	1	1	1
0	0	0	0	1	0	0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	1	1	0	0	0	0	1	1
0	0	1	0	0	1	0	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	1	1	0	0	0	0	1	1
0	0	0	1	0	0	0	1	0	0	0	0	1	1	1	1
0	1	0	1	0	1	0	1	0	1	0	0	0	0	1	1
0	1	1	0	1	0	1	1	1	1	0	0	0	0	1	1
1	0	0	0	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	1	0	0	0	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

39

## BCD Counter – Input Equation

Q <sub>2</sub> Q <sub>1</sub>	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	x	x	x
10	1	1	x	x

$T_{Q1} = 1$

Q <sub>2</sub> Q <sub>1</sub>	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	x	x	x	x
10	0	0	x	x

$T_{Q2} = Q_1 Q_8'$

Q <sub>2</sub> Q <sub>1</sub>	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	x	x	x	x
10	0	0	x	x

$T_{Q4} = Q_1 Q_2$

Q <sub>2</sub> Q <sub>1</sub>	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	0	1	x	x

$T_{Q8} = Q_1 Q_8 + Q_1 Q_2 Q_4$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

40

## BCD Counter – Input Equation


$$T_{Q1} = 1$$

$$T_{Q2} = Q_1 Q_8'$$

$$T_{Q4} = Q_1 Q_2$$

$$T_{Q8} = Q_1 Q_8 + Q_1 Q_2 Q_4$$

$$Y = Q_8 Q_1$$

 

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

41

## Decimal Numbers Counters

- Synchronous BCD counters (same as the one built in previous slide) can be cascaded to form counters for decimal numbers of any length



- **Exercise 1:** Using the logic diagram of previous slide, design a counter which counts from 0 till 99 and then repeats



- **Exercise 2:** Given synchronous BCD counter with parallel load blocks (on slide 31) and perhaps using other logic gates design a stop watch that times up to one minute
  - What should be the frequency of the driving clock signal?

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

42

## Arbitrary Count Sequence

- **Problem:** Design a counter that has a repeated sequence of 6 states, as listed in table. In this sequence, flip-flops B and C repeat the binary count 00, 01, 10, while flip-flop A alternates between 0 and 1 every three counts.
- **Solution:**

Present State			Next State		
A	B	C	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

43

## Arbitrary Count Sequence – State Table

- Assuming *JK* flip-flops

Present State			Next State			Flip-flop Inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	x	1	0	x

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

44

## Arbitrary Count Sequence – Input Equations

BC	00	01	11	10
A				
0	0	0	x	1
1	x	x	x	x

BC	00	01	11	10
A				
0	x	x	x	x
1	0	0	x	1

JA = B  
KA = B

BC	00	01	11	10
A				
0	0	1	x	x
1	0	1	x	x

JB = C  
KB = 1

BC	00	01	11	10
A				
0	1	x	x	0
1	1	x	x	0



JC = B'  
KC = 1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

45
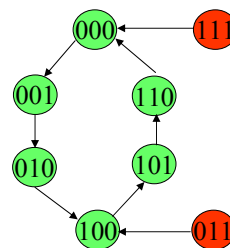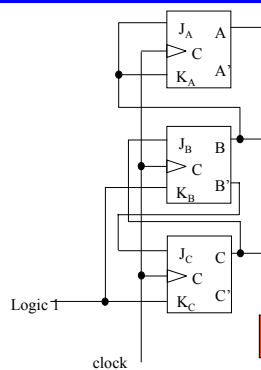
## Arbitrary Count Sequence – Circuit and Unused States



1) What if the counter “finds itself” in state 111 or state 011? Will the counter be able to proceed (count) normally afterward? How?

2) Is this circuit safe or reliable?


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

46

## Problem:

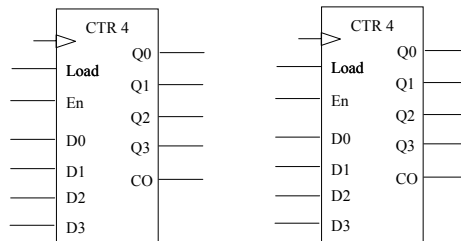- **Problem:** Using the two binary counters shown in figure and logic gates, construct a *binary* counter that counts from 9 through *binary* 69. Add an additional input to the counter that initializes it synchronously to 9 when the INIT is 1



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

47

## Problem: Solution

- **Solution:**

The key word in the problem statement is "*BINARY*"  
Hence the designed counter should count in binary from binary 9 through binary 69 and then back to binary 9 and so on

Binary 9 → 0000 1001

Binary 69 → 0100 0101

Hence it is obvious that the two counters providing 8 Qs are enough to represent 69

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

48



## Problem 5-23: Solution-cont'd

- **Solution:**

- The counting sequence is as shown in table
- Note that:
  - The we can assign first bit counter to count  $Q_3Q_2Q_1Q_0$  while the second is assigned  $Q_7Q_6Q_5Q_4$
  - Note that second counter increments count only if  $Q_3Q_2Q_1Q_0$  is equal to 1111; i.e the CO signal first counter is 1
  - During count – first counter counts normally from 01001 all the way to 1111 and back to 0000, 0001, etc except when binary 69 is reached – 1001 is reloaded again
  - During count – second counter counts normally from 0000 all the way to 0100 and then it restarts from 0000 again.


No	Binary
	$Q_7Q_6Q_5Q_4$ $Q_3Q_2Q_1Q_0$
9	0000 1001
10	0000 1010
11	0000 1011
12	0000 1100
.	.
15	0000 1111
16	0001 0000
17	0001 0001
18	0001 0010
19	0001 0011
20	0001 0100
21	0001 0101
.	.
68	0100 0100
69	0100 0101
9	0000 1001
10	0000 1010
.	.

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

49

## Problem: Solution-cont'd

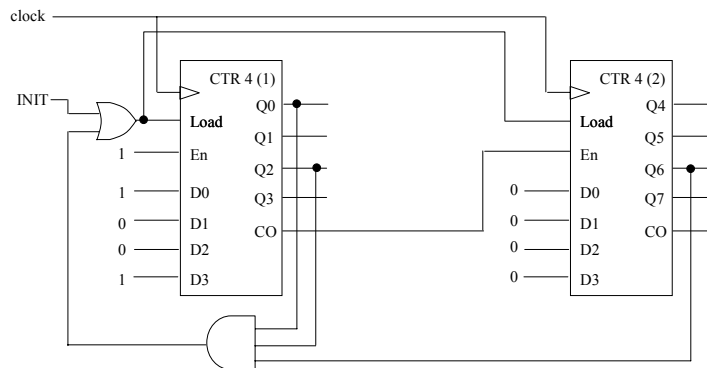


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

50

## Exercise: BCD Counter

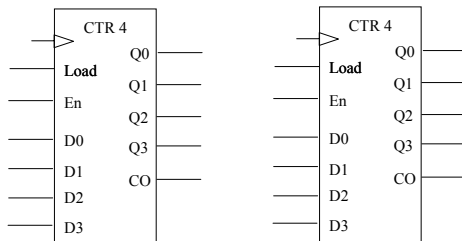- Problem:** Using the two binary counters shown in figure and logic gates, construct a *BCD* counter that counts from 9 through *BCD* 69. Add an additional input to the counter that initializes it synchronously to 9 when the INIT is 1



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

51

## Exercise: BCD Counter – cont'd

### Solution:

- The key word in the problem statement is "*BCD*"
- The counting sequence is as shown in table:
  - Counter 1 ( $Q_3Q_2Q_1Q_0$ ) counts 9, 0, 1, 2, ..., 9, 0 and so on
  - Counter 1 increments every clock cycle
  - Counter 2 ( $Q_7Q_6Q_5Q_4$ ) counts 0, 1, 2, 3, 4, 5, 6, 0, 1, and so on
  - Counter 2 increments every time counter 1 reaches 1001
  - Counter 1 loads
    - 0000 when 9 is reached; OR
    - 1001 if INIT is 1 or 69 is reached
  - Counter 2 loads 0000 when 69 is reached or when INIT is 1


No	Binary $Q_7Q_6Q_5Q_4 Q_3Q_2Q_1Q_0$
9	0000 1001
10	0001 0000
11	0001 0001
12	0001 0010
.	.
15	0001 0101
16	0001 0110
17	0001 0111
18	0001 1000
19	0001 1001
20	0010 0000
21	0010 0001
.	.
68	0110 1000
69	0110 1001
9	0000 1001
10	0001 0000
.	.

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

52

## Exercise: BCD Counter – cont'd

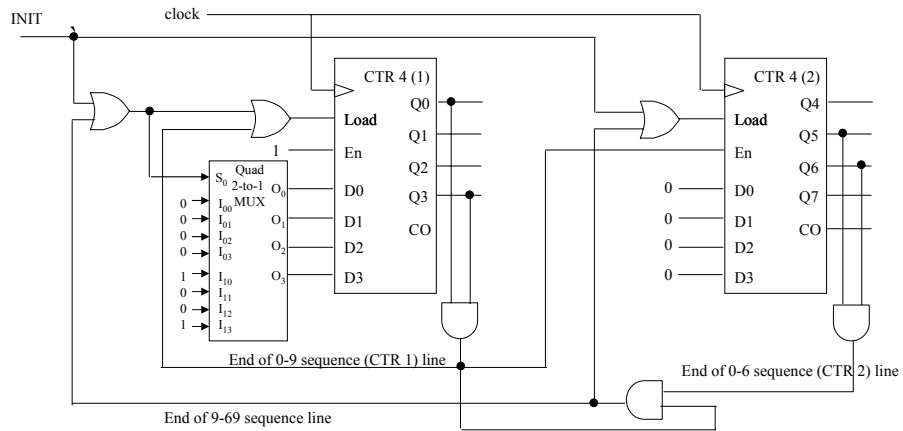


The circuit can be built without using the MUX as shown in next slide

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

53

## Exercise: BCD Counter – cont'd

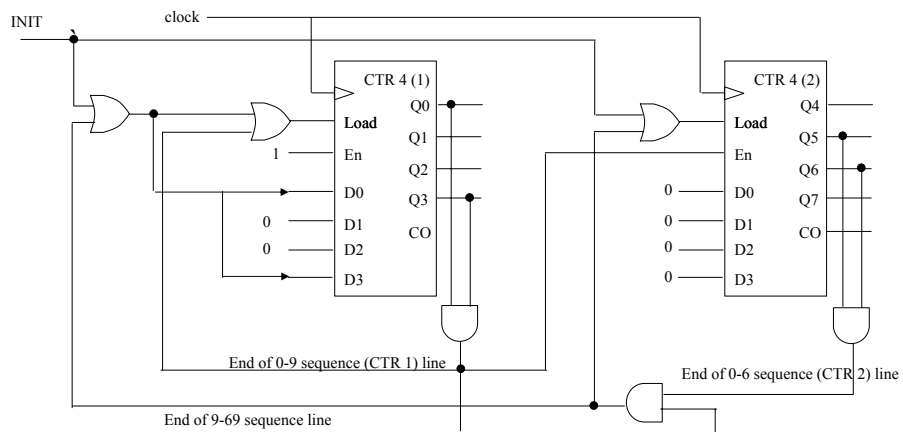


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

54

## Problem:

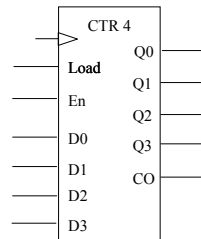- **Problem:** Using the binary counter shown in figure and logic gates, construct a *binary* counter that counts from 3 through *binary* 12.




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

55

## Problem:

- **Solution:**

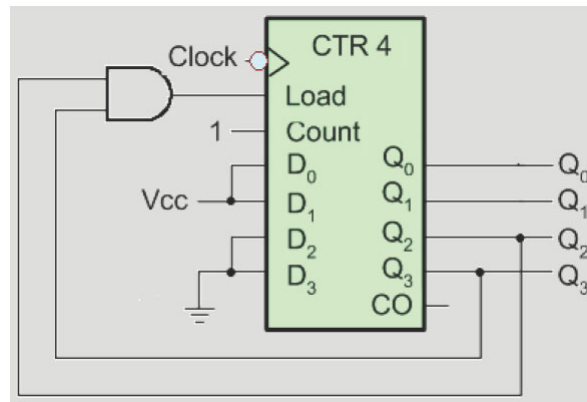

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

56

## **Problem:**

---

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

57