

EE 200: Digital Logic Circuit Design

Dr Radwan E Abdel-Aal, COE

Unit 3 Combinational Logic

- Introduction to **Analysis & Design** with Examples
- **Arithmetic Functions and Circuits**
- **MSI Functional Blocks: Decoders, Encoders, etc.**

© 2004 Pearson Education, Inc.

[Terms of Use](#)

(Hyperlinks are active in View Show mode)

Unit 3: Combinational Logic (CL) Design Contents

1. Procedures for **Analysis** and **Design of CL circuits**.
Example: BCD to Excess-3 Code Converter
2. Iterative Arithmetic Circuits: Half & Full adders, Ripple Carry Adder, Carry Look-ahead adder
3. CL MSI Functional Blocks: Decoders, Demultiplexrs, Encoders, Multiplexers, in addition to adders/subtractors, **Decimal Adder**, **Magnitude comparator**
4. Implementing combinational functions using: Decoders and Multiplexers


Combinational Logic Circuits

- A combinational logic circuit that has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs*Performs n logic functions, each mapping the 2^m input combinations to an output*
- Outputs are determined **only** by the **present** inputs

(appearing after some delay) **Effect of Previous inputs is NOT "remembered"**

- No feedback paths
- No memory elements

Each Output = F (the m inputs)

 

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

m Boolean Inputs n Boolean Outputs 3

CL Circuit **Analysis** Procedure:

Analysis:

Given:

a **CL Circuit*** (logic diagram),

Determine:

the **logic function** implemented by the circuit


We can describe such a logic function by:

- A set of Boolean Equations, or
- A truth table, or
- A word description

***Ensure circuit is combinational: It should not have O/P to I/P feedback through storage elements**


4-Step Procedure to get O/P Function:

1. Label the outputs of gates that are functions of only the circuit inputs and obtain the Boolean function of each output
2. Label the outputs of gates that are functions of the inputs and the outputs of gates in step 1, and obtain the Boolean function of each output
3. Repeat 2 until you obtain the final output of the circuit
4. Use direct substitution to determine each output as a function of the external circuit inputs, e.g. as a SOP

 

Chapter 3 - Part 1 5


O/P Function: Example

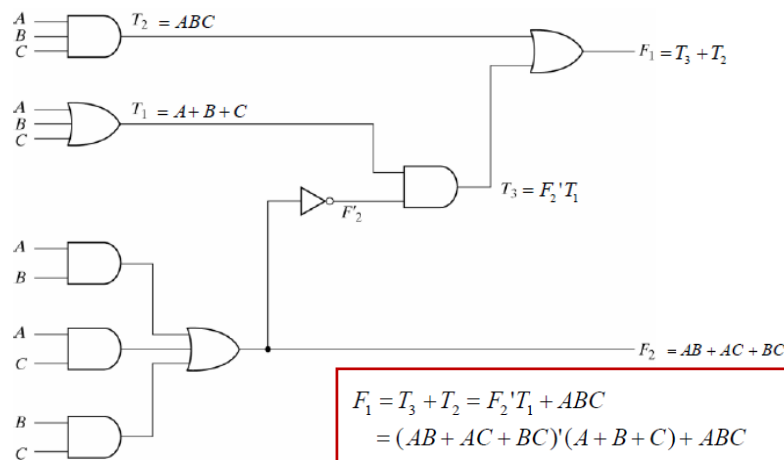

$$\begin{aligned}
 F_1 &= T_3 + T_2 = F_2' T_1 + ABC \\
 &= (AB + AC + BC)'(A + B + C) + ABC \\
 &= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\
 &= (A' + B' C')(AB' + AC' + BC' + B' C) + ABC \\
 &= A' BC' + A' B' C + AB' C' + ABC
 \end{aligned}$$

$$F_2 = AB + AC + BC$$

Truth Table: Example

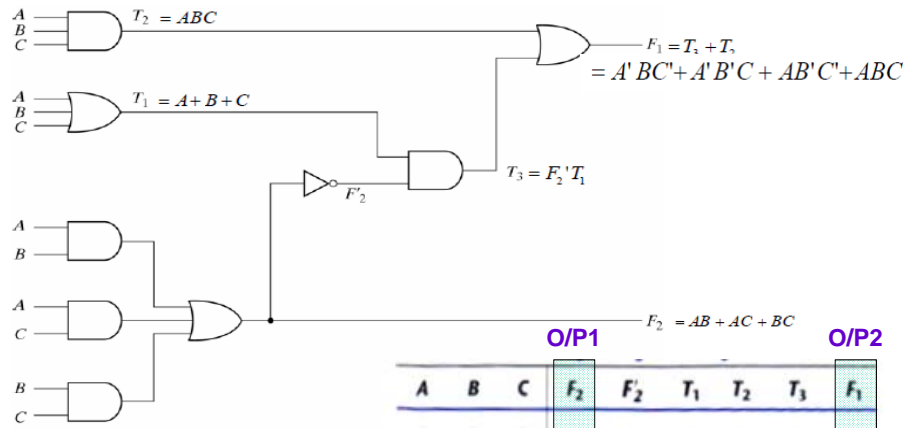

Truth Table: 2 Ways:

1. Step by step- T1, T2 etc.
2. Get eqn. of the final output and plot it on the table

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

			O/P1				O/P2	
A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

CL Design Procedure: 5 Steps

Given:

A specification of required **functionality** (as a Word description, Truth table, Boolean Equations),

Determine:

The **logic diagram** for an **optimal** circuit that provides the functionality


1. From the Specification given, determine the number of **inputs**, number of **outputs** and **label** them
2. Work out the **truth table** specification for **each** output (if not given)
3. Obtain an **optimized*** logic expression for each outputs (using K-maps etc.). **Global optimization** if multiple outputs
4. Get **logic diagram** and **truth table of circuit used and verify** that it fulfills the required specification – manually or using a simulator
4. Implement with a universal gate if required

*Note: In practice, other physical parameters need also to be optimized and verified, e.g. propagation delay, area on the chip, power consumption, etc.

Design Example: BCD to Excess 3 Code Converter

Specifications

 - The circuit should convert a BCD input code (decimal digits 0-9) to the corresponding Excess-3 code
- Inputs:** BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Outputs:** Excess-3 code words for digits 0 through 9: 4-bit patterns obtained by adding 3 (binary 0011) to each BCD code input
- Utilize Don't cares!



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

9

Design Example: BCD to Excess 3 Code Converter

1, 2: Formulation

- How many outputs we need? Name them**
- **The Truth Table**
- I/P Variables**
 - **BCD:**
A, B, C, D
- O/P Variables**
 - **Excess-3**
W, X, Y, Z
- Don't Cares**
 - BCD codes 1010 to 1111

Index	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
..				X	X	X	X
15	1	1	1	1	X	X	X	X

FIGURE 1-10

Design Example 1: BCD to Excess 3 Code Converter

3. Logic Optimization

2-level using
K-maps

$$W = A + BC + BD$$





$$X = \bar{B}C + \bar{B}D + \bar{B}\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

Standard SOP 2-level Form
(Directly from the K-maps)

Optimized each O/P separately

    

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 11

Design Example 2: BCD to Excess 3 Code Converter

3. Contd. Global Logic Optimization

b. Further optimization through **multi-level**, from:

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + \bar{B}\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

For circuits having
Multiple Outputs (here 4)

• By taking common factors:

$$\text{Let } T_1 = C + D$$

$$W = A + BT_1$$

$$X = \bar{B}T_1 + \bar{B}\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

Simpler but non-standard Form

(no longer SOP,

i.e. > 2 logic levels-

(multi-level logic)


→ Now (C+D) is generated only once
and used by the 2 outputs W, X!

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 12

Design Example 2: BCD to Excess 3 Code Converter
 
$$\begin{aligned} \text{Let } T_1 &= C + D \\ W &= \bar{A} + BT_1 \\ X &= \bar{B}T_1 + B\bar{C}\bar{D} \\ Y &= CD + \bar{C}\bar{D} \\ Z &= \bar{D} \end{aligned}$$



Multilevel (non-standard) implementation
Optimizes the logic but can increase propagation delay

Design Example 1: BCD to Excess 3 Code Converter


4. **Verification**- Get the truth table of the actual circuit implemented (analysis) and show it satisfies the specified truth table:

Input BCD A B C D	Output Excess-3 WXYZ
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

Arithmetic Combinational Circuits: Iterative Cells (Repeated - in space or time)

- Practical Arithmetic Functions:
 - Operate on binary **bit vectors** (e.g. a 32-bit adder adds two 32-bit numbers and produces a 32-bit sum)
 - Use same basic sub-function for each **bit** position
- Designing circuits that handle the I/P vectors directly can be very difficult (large # of inputs & outputs! → large K-maps, Huge truth tables!)
- Solution: Design functional block for sub-function (e.g. for a bit) and **repeat it** (iterate it, reuse it) to obtain a functional block for the overall operation
- Cell** = sub-function block
- Iterative array** = An array of interconnected such **cells**

 Block Diagram of a 1-D Iterative Array Adder/Subtractor for two n-bit integers: $C=A\pm B$



- Example: n = 32: Direct Implementation**
 - Number of inputs = ? (K-map size)
 - Truth table rows = ?
 - Equations in up to ? input variables
 - Equations with a huge number of literals
 - Flat Design: impractical!**
- Iterative array takes advantage of **regularity** to make designs more feasible


Functional Blocks: Addition

- Binary addition is used frequently in computers
- “Adder” Design:
- 1-bit adder cell (i.e. does the addition for 1 digit)
 - *Half-Adder* (HA), a 2-input bit-wise addition functional block
 - *Full-Adder* (FA), a 3-input bit-wise addition functional block
- For an **n-bit iterative adder**: Combine **n** 1-bit FA adder cells together- Two ways:
 - *Ripple Carry Adder* (RCA): Carry ripples through the adder from LSB to MSB → slows down the addition operation
 - *Carry-Look-Ahead Adder* (CLA), Speeds up addition by letting each bit stage generate its carry input from scratch (i.e. from the input numbers **directly**) to avoid waiting for the carry to ripple through all previous stages

Chapter 3 - Part 1 17

The Functional Blocks: Half-Adder (HA)

 - A **2-input (no carry input)**, 1-bit wide binary adder that performs the following computations:



X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
C S	0 0	0 1	0 1	1 0

- A half adder adds two bits, giving two outputs: S & C
- The result is expressed as a sum bit S and a carry bit C
- The half adder can be specified by the truth table ⇒


I/Ps		O/Ps	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Applications:
 - Use as the 1st stage of n-bit adder (no carry I/P)
 - Use two HAs to make a full adder (FA)- **see later**

Chapter 3 - Part 1 18

Logic Simplification: Half-Adder (HA)

- The K-maps for S, C are:


 


X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- By inspection:

$$S = X \bar{Y} + \bar{X} Y \quad C = X Y$$

$$C = X Y$$

  

19

Functional Block: Full-Adder


- A full adder is similar to a half adder, but **includes a carry-in bit from the lower stage**. Like the half-adder, it computes a sum bit, S and a carry bit, C.

- For a carry-in (Z) of 0, it is the same as the half-adder:

Z	0	0	0	0
X	0	0	1	1
	<u>+ Y</u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>
	C S	0 0	0 1	0 1
				1 0

- For a carry-in (Z) of 1:

Z	1	1	1	1
X	0	0	1	1
	<u>+ Y</u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>
	C S	0 1	1 0	1 0
				1 1


 


Chapter 3 - Part 1 20

Logic Optimization: Full-Adder

- Full-Adder Truth Table:
- Full-Adder K-Maps:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

$$S = X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z + XYZ$$

$$S = X \oplus Y \oplus Z$$


The Odd function

$$C = XY + X\bar{Y}Z + \bar{X}YZ$$

$$= XY + Z(X\bar{Y} + \bar{X}Y)$$

$$C = XY + Z(X \oplus Y)$$


Generated Carry Propagated Carry

 

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 21

 
Full-Adder (FA): Implementation Using two Half-Adders (HAs) + OR Gate



Half-Adder

$$Sh = X \oplus Y$$

$$Ch = X Y$$

 

Full-Adder



$$S = X \oplus Y \oplus Z$$

$$= Sh \oplus Z$$

$$C = XY + (X \oplus Y) \cdot Z$$

$$= Ch + Sh \cdot Z$$

Generated Carry Propagated Carry

  

22


Worst Case (Critical Path) Propagation Delay for a FA Stage

Assume:

XOR: 3 standard gate delays

OR: 1 standard gate delay, AND: 1 standard gate delay

critical delay path for the FA

 

Path from input (X,Y,Z) to S is the critical path (largest delay to output)
Hence propagation delay is 6 standard gate delays

If this gate delay is 5 ns → FA propagation delay = 6 x 5 = 30 ns.

- How many additions per sec??

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 23

4-bit binary adder block using 4 FA stages

1. The ripple carry approach (simple but slow)

- Mimics what we do when adding multiple bits with paper and pencil

- Carry output from FA stage i is fed as carry input to FA stage $(i+1)$

$$\begin{array}{r} < < < < \\ 1011 \\ +0011 \\ \hline 1110 \end{array}$$


Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 24

4-bit Ripple-Carry Binary Adder

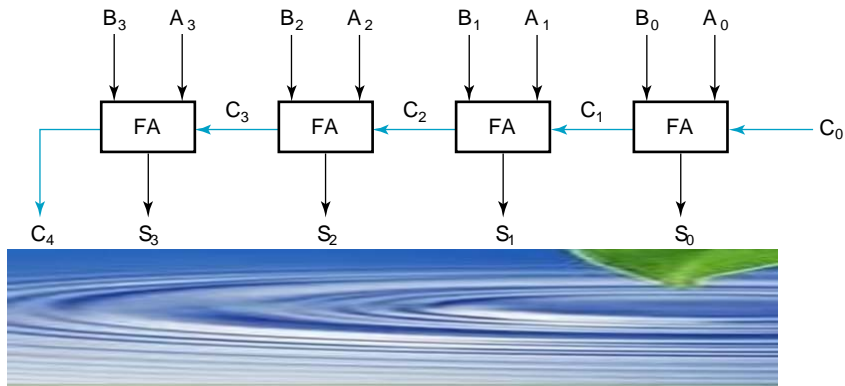- Four-bit Ripple Carry Adder made from four 1-bit Full Adder cells:




Problem: Carry has to ripple through till the end stage for the final result to appear
 → Slow addition speed for large number of stages (bits) n

© 2004 Pearson Education, Inc.

23

4-bit Ripple-Carry Binary Adder Propagation Delay Analysis

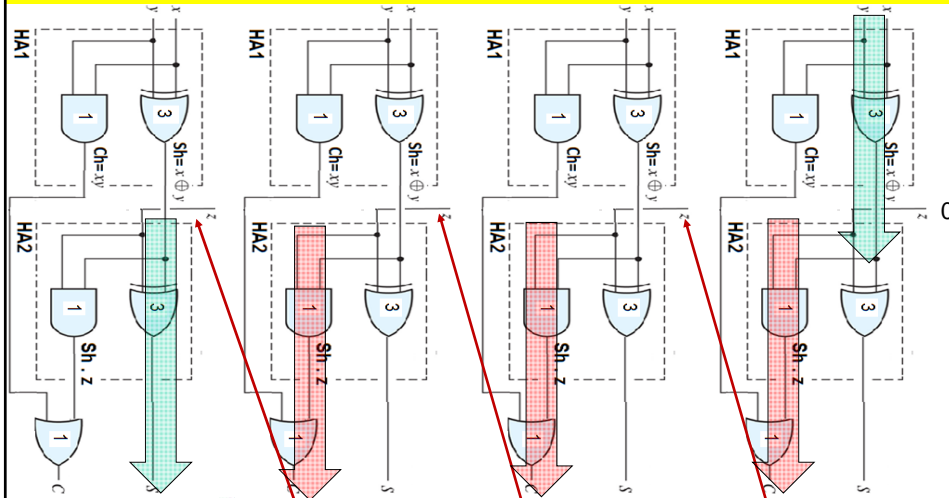Total Worst Case Delay = $3 + 2 + 2 + 2 + 3 = 12$ gate delays = $6 + (n-1) \cdot 2$, $n = 4$ stages




Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.

26

Full-Adder Alternative Formulation

Carry: Generated or Propagated

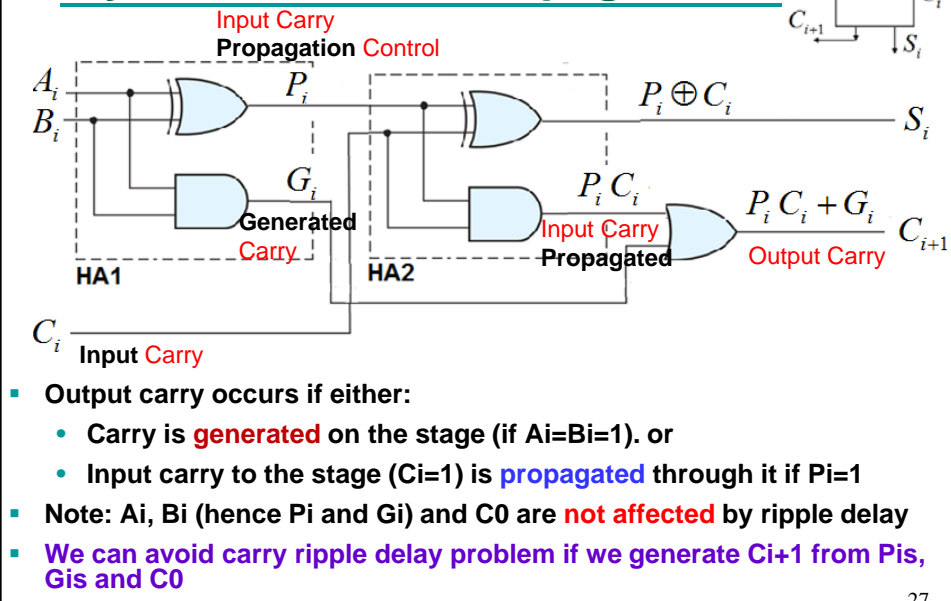

Carry Lookahead Binary Adder

Speed up at the expense of more complex hardware

- C_{i+1} outputs by all stages are derived **in parallel** with a set of equations using A, B, C_0 inputs only
- Beginning at cell 0 with carry in C_0 :

Note: All P_i, G_i are functions of (A_i, B_i) Only!

Carry does not ripple anymore!
All 4 carry outputs can be generated **in one go** from: C_0 and the two input numbers to be added (A, B)

$$\checkmark C_1 = G_0 + P_0 C_0 \quad (\text{No change})$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0)$$

$$\checkmark C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

2-Level logic (Only 2 gate delays)

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2(G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$\checkmark C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


$$\checkmark C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

No Rippling


Carry generated within the 4-bit block

Carry Propagated through the 4-bit block

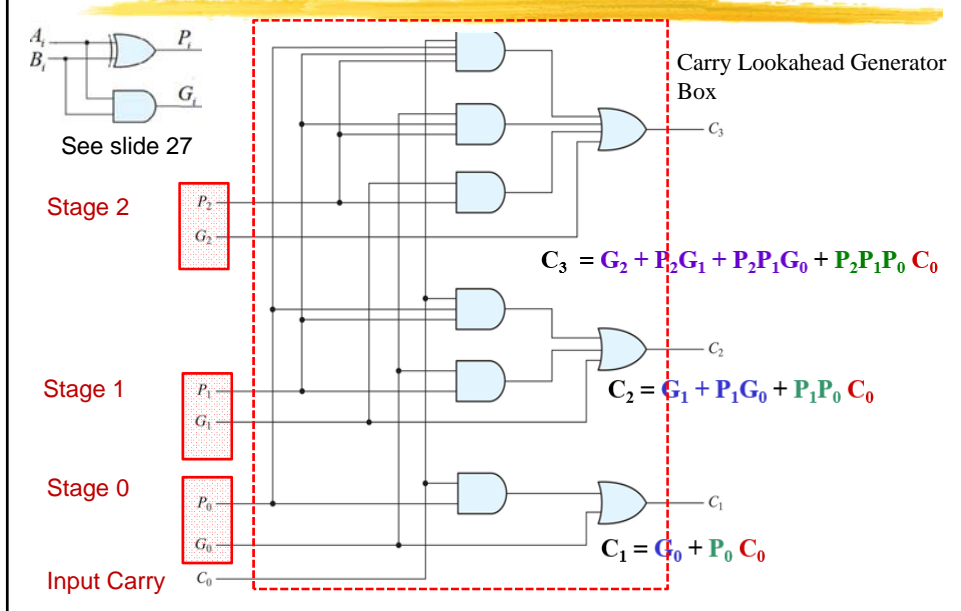
Carry Lookahead Generator Box (for 4-bit adder) C1 to C4 are generated - Only C1-C3 shown




4-bit Carry Lookahead Adder: A+B = C4 S

 

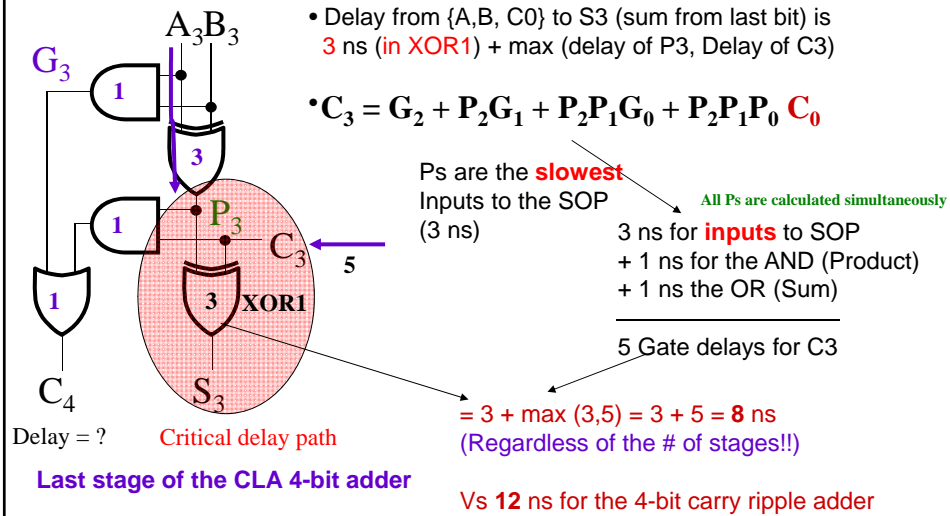
Delay reduction for the 4-bit Carry Lookahead adder: Consider last stage



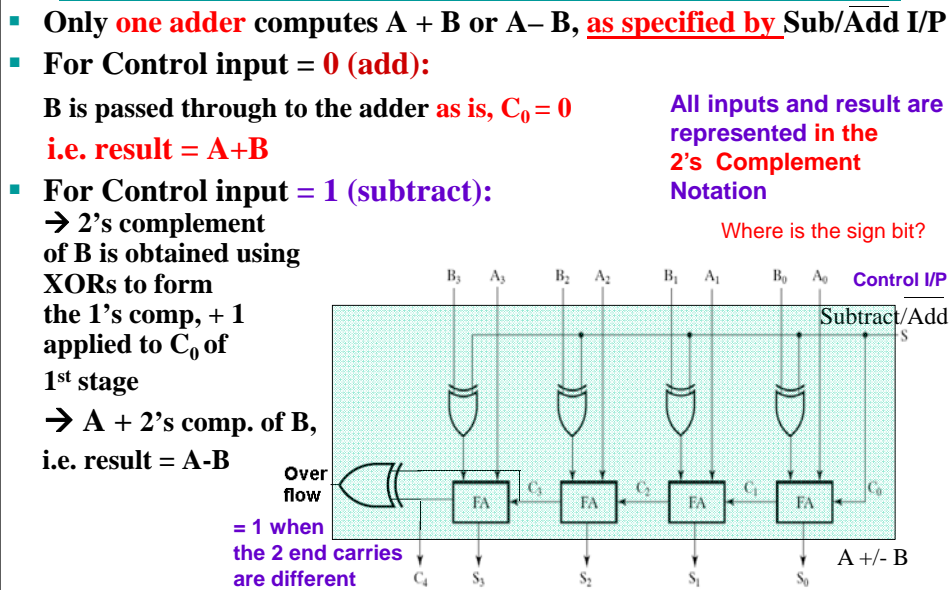Adder/Subtractor Combined Hardware In Signed 2's Complement Notation



BCD Decimal Adder

 

A circuit that adds **two** decimal digits (0-9) (in **BCD**) with a possible **carry input** and gives the sum as a **BCD** + a **carry out**

9 inputs, 5 outputs

$$\begin{array}{r}
 \overset{\leftarrow 0}{6} \\
 + 2 \\
 \hline
 8 \text{ (<9)} \\
 \text{0 8} \\
 \text{carry}
 \end{array}
 \qquad
 \begin{array}{r}
 \overset{\leftarrow 1}{7} \\
 + 4 \\
 \hline
 12 \text{ (>9)} \\
 \text{1 2} \\
 \text{carry}
 \end{array}
 \qquad
 \begin{array}{r}
 \overset{\leftarrow 0}{9} \\
 + 9 \\
 \hline
 18 \text{ (>9)} \\
 \text{1 8} \\
 \text{carry}
 \end{array}$$

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Using a standard 4-bit binary adder - What changes are needed?

- ⌘ For sums ≤ 1001 binary and BCD are identical- No correction
- ⌘ For sums ≥ 1010 , we should subtract 10_{10} and **send a carry to next BCD stage**
- ⌘ Instead of subtracting 10_{10} , we **add** its 2's complement which is 0110
- ⌘ Use the binary adder o/p/s to determine if correction is needed

Binary Adder Performance					Required BCD Performance					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	sum
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	0	1	0	4
0	0	1	0	1	0	0	0	1	0	5
0	0	1	1	0	0	0	0	1	1	6
0	0	1	1	1	0	0	0	1	1	7
0	1	0	0	0	0	0	1	0	0	8
0	1	0	0	1	0	0	1	0	0	9
0	1	0	1	0	0	1	0	0	0	10
0	1	0	1	1	0	1	0	0	1	11
0	1	1	0	0	0	1	0	0	1	12
0	1	1	0	1	0	1	0	0	1	13
0	1	1	1	0	0	1	0	1	0	14
0	1	1	1	1	0	1	0	1	0	15
1	0	0	0	0	1	1	0	1	1	16
1	0	0	0	1	1	1	0	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

Binary Carry

Identical- No Change

Corrections Needed

BCD Carry For sum ≥ 10 Subtract 10 (add 6) and set Carry

BCD decimal adder

Numbers that need correction (add 6) are:

K	Z ₈	Z ₄	Z ₂	Z ₁	
0	1	0	1	0	(10)
0	1	0	1	1	(11)
0	1	1	0	0	(12)
0	1	1	0	1	(13)
0	1	1	1	0	(14)
0	1	1	1	1	(15)
1	0	0	0	0	(16)
1	0	0	0	1	(17)
1	0	0	1	0	(18)
1	0	0	1	1	(19)

$$C = K + Z_8Z_4 + Z_8Z_2$$

BCD Carry = 0 → Add 0
 = 1 → Add 6

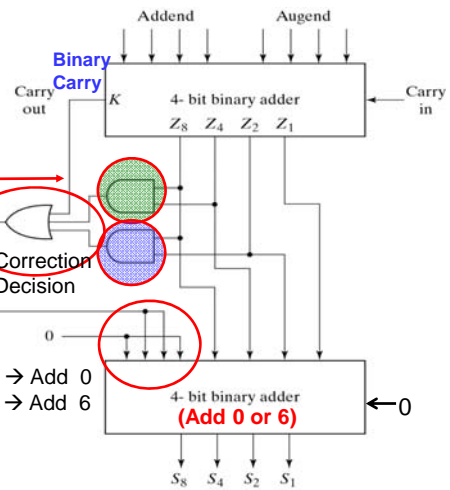


Fig. 4-14 Block Diagram of a BCD Adder

35

Binary Multiplier

- ⌘ Binary multiplication is done in the same way as decimal multiplication.
- ⌘ Multiplicand is multiplied by each bit of the multiplier. Shift results 1-bit for each bit of multiplier. Add.

Multiplicand	1011	11
Multiplier	<u>x 101</u>	5
Partial Products	1011	
	0000 -	
	<u>1011 - -</u>	
Product	110111	55

36

Binary Multiplier: 2-bit x 2-bit

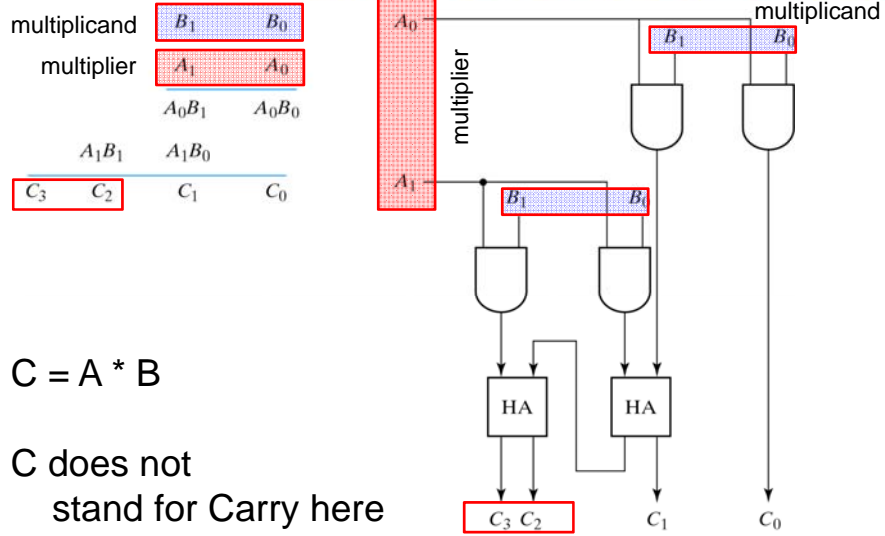


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

37

4-bit by 3-bit Binary Multiplier


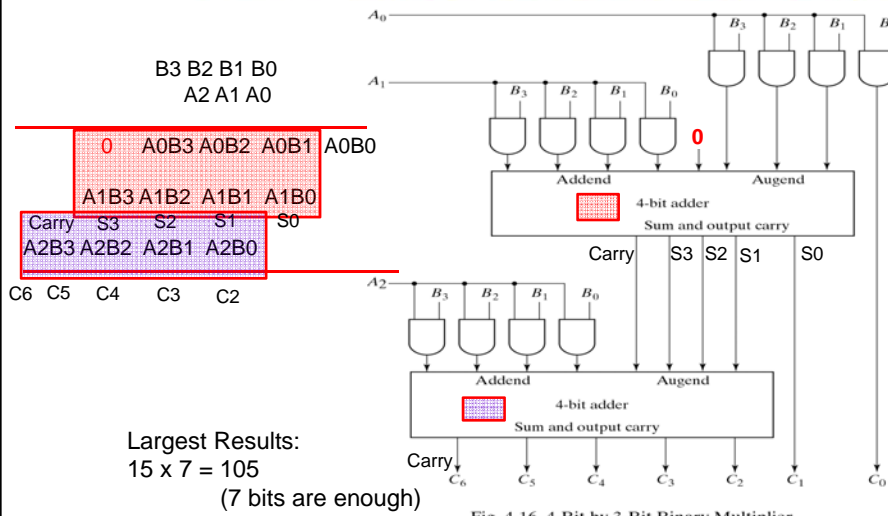


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

38

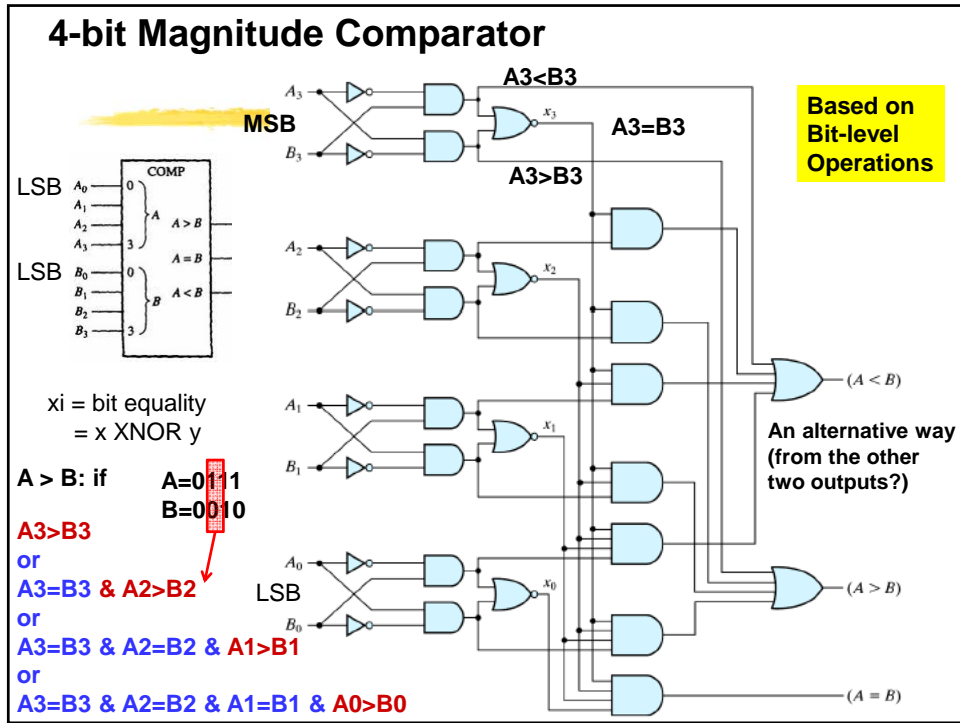


- ### 4-bit Magnitude Comparator
- ◆ The comparison of two numbers
 - outputs: $A > B$, $A = B$, $A < B$
 - ◆ Design Approaches
 - the truth table **for an n-bit comparator**
 - ◆ 2^{2n} entries - too cumbersome for large n
 - use inherent regularity of the problem
 - ◆ reduce design efforts (**Bit-level Operations**)
 - ◆ reduce human errors
 - ◆ Algorithm -> logic
 - $A = A_3A_2A_1A_0$; $B = B_3B_2B_1B_0$
 - $A = B$ if $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = B_0$
 - ◆ equality: $x_i = A_iB_i + A_i'B_i'$
 - ◆ $(A = B) = x_3x_2x_1x_0$
 - $(A > B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
 - $(A < B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
- 40

Other Combinational Logic Functions

- **Functions** & **Functional Blocks** that implement them
 - **Enabling**
 - **Encoding, Encoding with Priority in mind**
 - **Decoding, Demultiplexing (Data routing)**
 - **Multiplexing (Data selecting)**
- Implementing **any** combinational function using:
 - **Decoders & OR gates**
 - **Multiplexers (with inverters if needed)**
- **MSI Functional Block Applications**

Functions and Functional Blocks

 - We consider here functions that are useful in designing and building other (**higher-level**) combinational and sequential circuits



- Such functions may exist as *functional blocks*
 - In the past, many such blocks were implemented as **discrete** integrated circuits (ICs): SSI (small scale integration), MSI, and LSI **e.g. the 7483 is a 4-bit CLA adder, 74157 is a 4-bit Multiplexer**
 - Today, they are often available as components in a **design library** for use within larger VLSI circuits

2

1. Enabling Function


- **Enable:** Allow an input signal to pass through to an output
- **Disable:** block an input signal from passing through to an output, replacing it with a fixed state. This could be HiZ, 1, 0, depending on the gate used)




- Later we use the enable function to implement decoders and multiplexers

- Two Examples: EN = 1 → Enable, EN = 0 → Disable

- When I/P disabled, output = 0

 


- When I/P disabled, output = 1

 


Encoding & Decoding

$m = 2^n$
For full
Decoders/Encoders

 Encoder: For each unique activated input line, Generate the corresponding code



 
Decoder: For each input code, Activate the unique corresponding output line



Encoder is the opposite of Decoder

Will start with Decoding


2. Decoding

 

- A decoder converts an n -bit **input code** to a unique state on m **outputs** where $2 \leq m \leq 2^n$ (with $m = 2^n$ we call it a **Full Decoder**)
- For each valid input code, **only one unique output line is activated**
- **Decoder** functional blocks:
 - Are called n -to- m line decoders, where $m \leq 2^n$, and
 - Generate 2^n (or fewer) **minterms** from the n input variables

Decoder Design: 3-to-8 Example

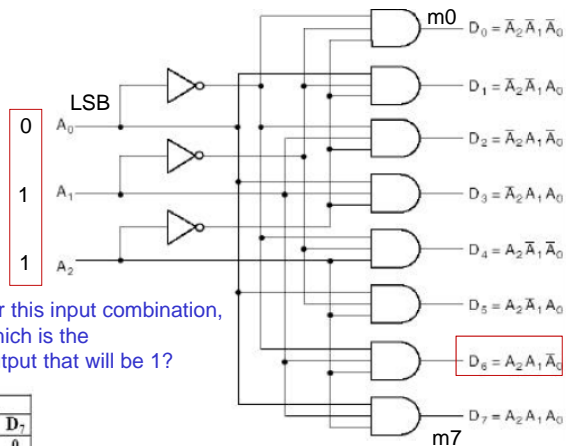Direct Approach: Generate All Minterms of the code I/Ps



Function Table

Notice that each output line is the **minterm** corresponding to the input code, e.g. D_5 is m_5


For this input combination, Which is the Output that will be 1?

Dec. Code	Inputs			Outputs							
	A_2	A_1	A_0	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
2	0	1	0	0	0	1	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	0
4	1	0	0	0	0	0	0	1	0	0	0
5	1	0	1	0	0	0	0	0	1	0	0
6	1	1	0	0	0	0	0	0	0	1	0
7	1	1	1	0	0	0	0	0	0	0	1

3-to-8 Line decoder

Hierarchical Decoder Design (Decoder Expansion) Using simpler decoders to build more complex ones

 - 1-to-2-Line Decoder
1 to 2^1 - **The simplest Decoder**




- 2-to-4-Line Decoder

MSB ←

A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoder Expansion

- Note that the 2-4-line made up of 2 1-to-2-line decoders and 4 AND gates.

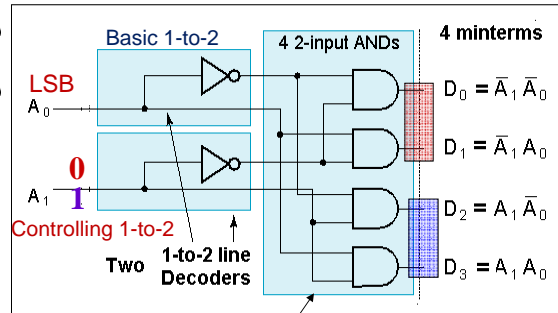

One 2-to-4-Line decoder

Enabling/Disabling Block of ANDs

For the 2-to-4: Logically, we get same Circuit of the formal design (the 4 minterms!)

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

We better design each decoder to have its own enable input!

n-to-m Decoder with Enable (EN)

- Use the EN input to open/close the **minterm-forming** gates
- See truth table below for function
 - Note use of X's to denote both 0 and 1 **at the inputs**
 - Combination containing two X's represent four input binary combinations

2-to-4 with Enable:

Disabled decoder has all outputs = 0

→ Allows simple expansion e.g. to 3-to-8


→ Also, will use to make a demultiplexer (see later)

	EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
Decoder is disabled	0	X	X	0	0	0	0
Decoder Enabled: Normal Operation	1	0	0	1	0	0	0
	1	0	1	0	1	0	0
	1	1	0	0	0	1	0
	1	1	1	0	0	0	1

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

(a)

2-to-4 with Enable

 


4 minterm-forming & Enabling gates

Decoder Expansion

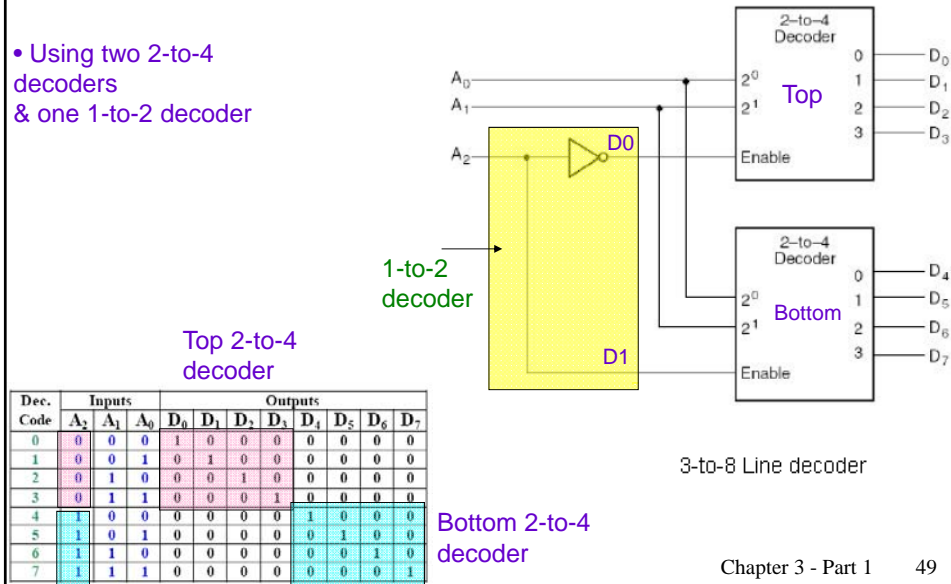Example: 3-to-8 from two (2-to-4 with EN)

- Using two 2-to-4 decoders & one 1-to-2 decoder




2-to-4 Decoder With Enable

Polarities for E and O/Ps can be reversed

Note: Here polarity of the Enable I/P and the decoder outputs is reversed....

 NAND Gates (not ANDs):
→ Selected Decoder O/P = 0 (not 1)




E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table Correction


Decoder is activated with E = 0 - Not 1

4. Encoding

 

- Encoding - the opposite of decoding
- An encoder converts m input lines to an n -bit output code where $2 \leq m \leq 2^n$ - such that each activated input line produces the corresponding unique output code
- If the input lines have **exactly** only one active line (e.g. at logic 1) → output is the binary code corresponds to the position of that input (**exact opposite of decoder**)
 - If not, we need to consider priority What is the smallest Encoder?


Example: 8-to-3 Encoder

 

- Inputs (D_0, \dots, D_7): 8 lines corresponding to digits 0 through 7
- Outputs (A_2, A_1, A_0): 3 bits of the binary code
- Function: If the i th input line D_i is a 1, the output (A_2, A_1, A_0) = the binary code for i
- Initially for simplicity:
Assume that **at least one** and **only one** of the 8 inputs **is active** at any given time. So we have **only 8 valid input combinations** out of the **$2^8 = 256$** possible combinations. Remaining rows are **don't care** → simplifies the design considerably

Example: 8-to-3 Encoder

Octal-to-binary encoder

 

Truth Table for Octal-to-Binary Encoder

Assuming only 1 (and at least 1) Input line being active at a time

The 256-row truth table is thus reduced to **only these 8 valid rows**

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Ambiguities arise if conditions above are not met:

Equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

1. O/P = 000 for: D0 active, **also** for no active line
2. If two lines become active simultaneously, O/P code is wrong (represents neither of them!)
e.g. if both D3 and D6 are active, output=111 (wrong) → So, We need **priority encoding**!

Priority Encoder

- If **none** or **more than one** input line is active (at logic 1), then the encoder just described does not work properly
- An encoder that can accept **all** possible combinations of input values and still produces **meaningful output** is called a **priority encoder**
- Among all the 1s that appear at the I/Ps simultaneously, it selects the “1” I/P having the highest designated priority **and produces its corresponding binary code- ignoring all other lower-priority “1”s that may exist with it.**
- So the code generated is for the input of the highest priority that is active (=1) (all higher priority inputs = 0), **regardless of the state of all lower priority inputs**

4-to-2 Priority Encoder

Example: 3 ← Higher Priority ← 0




K-map cells Included

- 0
- 1
- 2,3
- 4,5,6,7
- 8,9,10,11,12,13,14,15

Should be $2^4 = 16$ rows/cells in total!

Note the difference Between a don't care (X) in the inputs and a don't care (X) in the outputs!

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
1	0	0	1	0	0	1
2,3	0	1	X	0	1	1
4,5,6,7	0	X	X	1	0	1
8,9,10,11,12,13,14,15	1	X	X	1	1	1

 


Logic and Computer Design Fundamentals
 PowerPoint Slides
 © 2004 Pearson Education, Inc.

4-to-2 Priority Encoder Example

$$A_1 = D_2 + D_3$$

$$A_0 = D_3 + D_1\bar{D}_2$$


$$V = D_0 + D_1 + D_2 + D_3$$

 

5. Selecting (Multiplexing): 2^n -to-1

- A multiplexer (**MUX**) selects **one** of 2^n data input lines based on an **n-bit address**, directing it to one output line
- A typical multiplexer has:
 - 2^n **Information inputs** ($I_{(2^n-1)}, \dots, I_0$) (to select **from**)
 - n Select** (control or address) inputs (S_{n-1}, \dots, S_0) (to select **with**)
 - 1 **Information output Y** (to select **to**)
- Will implement it using a decoder, see next slide
- MUX selection circuits can be **duplicated m times** (with the same selection controls) to provide **m-wide** data widths, e.g. select one of four input **bytes** using 8-wide 4-to-1 MUX

4-to-1 MUX

 

The **Simplest** Multiplexer $n = 1 \rightarrow 2^1$ -to-1 MUX

- The single selection variable **S** has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1
- 3-input K-map optimization gives the output equation:

$$Y = \bar{S}I_0 + SI_1$$

- The circuit:


- Can also be seen As:

1-to-2 decoder

+ Enabling

+ Selection

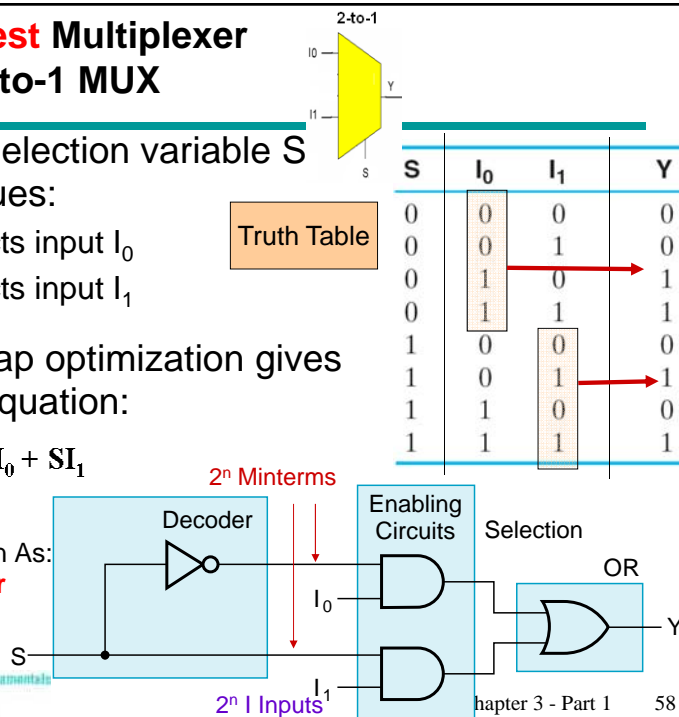Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.




Example: 4-to-1-line Multiplexer, Using

Size of the Select
Inputs = $\log_2(4)$


2-to-4 decoder +

4×2 -I/P AND-OR for Enabling/selection

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Function table

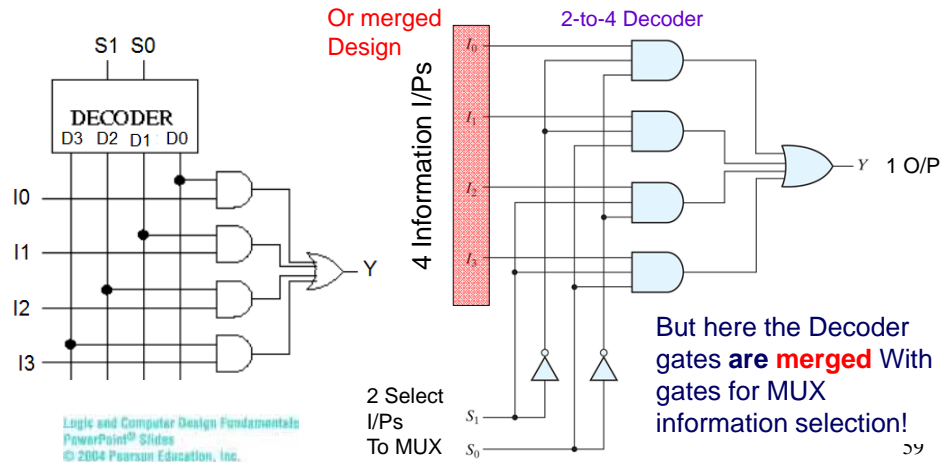


1. Duplicating the MUX in Width: m-wide 2^n -to-1 MUX

Example: Quad 2-to-1 MUX with E

Selection Capability

Is the same


Only widths extended

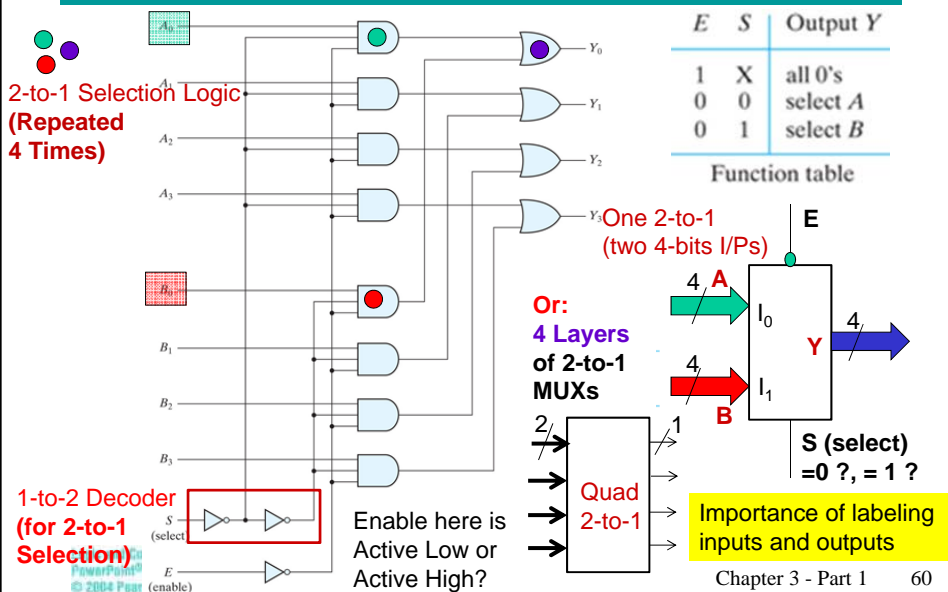

2. MUX Expansion: Expanding the selection capability

Example: Using 2-to-1 MUXs to do 4-to-1 Muxing

S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

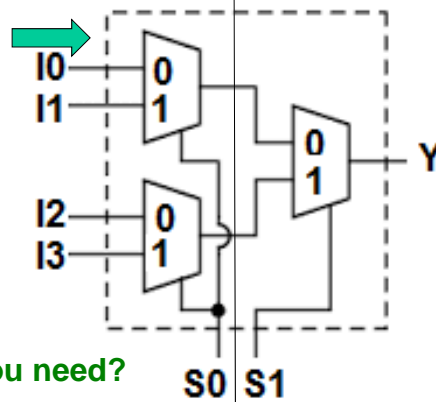

How many 2-to-1 MUXs do you need?


Selection with the **lower** significant bits
(I0 or I1)/(I2 or I3)

Selection with the **higher** significant bits
(I0, I1) or (I2, I3)

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

3. Demultiplexer- Opposite of Multiplexer


MUX: Many-to-One

 


Multiplexer

A decoder with **Enable** is
Called a:
Decoder/Demultiplexer

One-to-Many

 

(Select Destination Line)
Demultiplexer

 


A device that moves data
arriving on a **single** input (E)
to one of m outputs (Ds)
determined by the value of
(log₂ m) select inputs (As)

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 62

2-to-4 Decoder with **Enable** = 1-to-4 Demultiplexer!

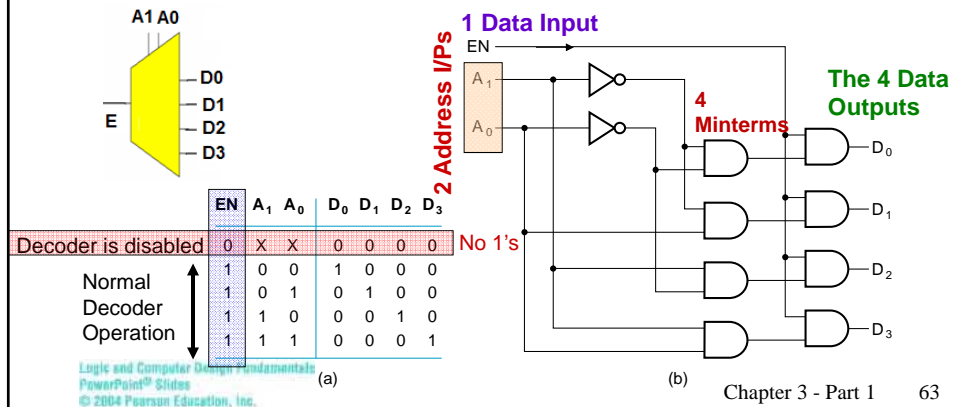- From Truth Table, decoder can be viewed as **distributing** the value of the **EN** input to 1 of 4 outputs
- From this perspective, it is a **Demultiplexer** !




Implementing Combinational Functions Using Functional Blocks

- Two implementation techniques from the SOM canonical form (no simplification):
 - Using a Decoder + OR gates
 - Using a Multiplexer + Inverters (if needed)

We always said **Canonical forms give complex implementations!**

But now we have most of the complexity "hidden" inside the "ready-made" function block !! (e.g. decoder or MUX) → Utilize it!

 **1. Using a Decoder + OR Gates:
From Canonical Form:
Truth Table (or Σm Form)**



- Functions of n inputs and m outputs:
 - Specification:
 - As a Truth Table (has n input columns and m output columns)
 - or m SOfm expressions [$\Sigma m(\dots)$]
 - Implementation requires:
 - One n -to- 2^n -line decoder
 - m "OR" gates: one gate for each output
 - Procedure:
 - From the truth table:
 - For each output: For a '1' in truth table row (i), connect the corresponding D_i output of the decoder to the OR of that output
 - Or → From the m minterm expression [$\Sigma m(\dots)$]:
 - Connect the decoder D_i outputs corresponding to the minterms of each output to the OR of that output

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


**Decoder + OR Gates: Example
1-bit adder (with carries at I/P and O/P)**

Truth Table for 1-bit Binary Adder

3 Inputs			LSB	2 Outputs	
X	Y	Z		C	S
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	2	0	1
0	1	1	3	1	0
1	0	0	4	0	1
1	0	1	5	1	0
1	1	0	6	1	0
1	1	1	7	1	1

3 I/Ps and 2 O/Ps: 2 SOfm expressions
We need:
→ 3-to- 2^3 Decoder
→ 2 "OR" gates of appropriate # of inputs
 $S(x, y, z) = \Sigma_m(1, 2, 4, 7)$
 $C(x, y, z) = \Sigma_m(3, 5, 6, 7)$

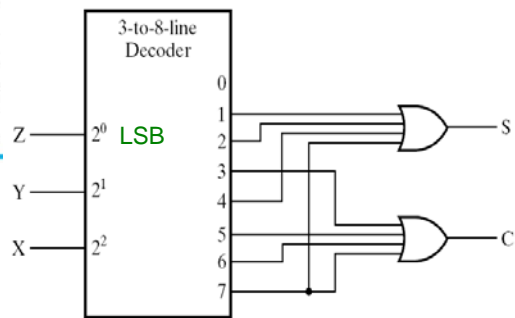Larger # of 1's require larger ORs. If so, Consider expressing F and using a NOR instead of the OR!



Using Multiplexers: from Truth Table, or canonical Form


- Implementing a logic circuit of n inputs and m outputs requires:
 - Specification: Truth table, or Som or PoM forms
 - **Implementation: Use $m \times 2^n$ -to-1 multiplexer**
- Example: 5 input, 3 output circuit:
Need 3 x 2^5 -to-1 MUX**
- Design:
 - In the same order they appear in the truth table:
 - Apply the n **input variables** to the MUX **select** inputs S_{n-1}, \dots, S_0 (i.e. Observe bit significance, i.e. LS variable goes to S_0)
 - Label the outputs of the multiplexer with the output variables
 - Value-fix the **I inputs** to the multiplexer using the values from the truth table. For don't cares, use either 0 or 1.

Light Micrograph: © Pearson Education, Inc.
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1 67

Using Multiplexers: Example:

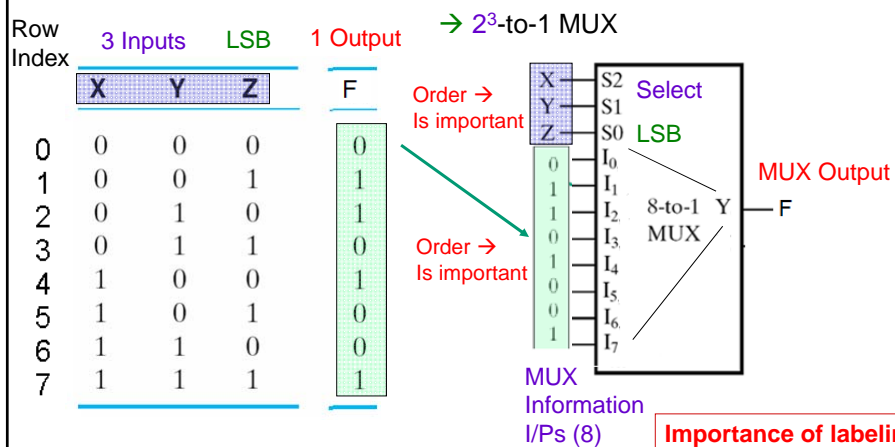1. Conventional approach, n inputs \rightarrow Use 2^n -to-1 MUX



What if we have 2 outputs?
We use a dual (i.e. x 2) 8-to-1 MUX

Chapter 3 - Part 1 68

Using Multiplexers: Example: Full adder-


2. Smarter approach uses a smaller MUX:

n input variables \rightarrow Use 2^{n-1} -to-1 MUX (1/2 previous size)

\rightarrow Use $\frac{1}{2}$ the MUX size needed earlier: 2^2 -to-1 MUX

\rightarrow Connect MS 2 input variables to select, and express F as 1, 0, Z , or \bar{Z} for each value of XY and apply to the I inputs of the MUX.

3 Inputs			Output	
X	Y	LSB XY Index	Z	F
0	0	0	0	$F = z$
0	0	0	1	$F = z'$
0	1	1	0	$F = 0$
0	1	1	1	$F = 0$
1	0	2	0	$F = 0$
1	0	2	1	$F = 0$
1	1	3	0	$F = 1$
1	1	3	1	$F = 1$

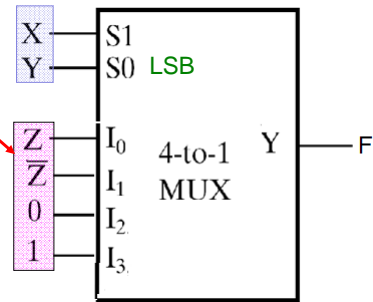

What if we have 2 outputs?
We use a dual 4-to-1 MUX

Using Multiplexers: Example

$$F(A,B,C,D) = \sum m(1,3,4,11,12,13,14,15)$$

\rightarrow 16 rows in truth table


\rightarrow 16-to-1 MUX

(conventional approach)


\rightarrow But using the more efficient

approach ... will use only an 8-to-1 MUX + 1 inverter

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 

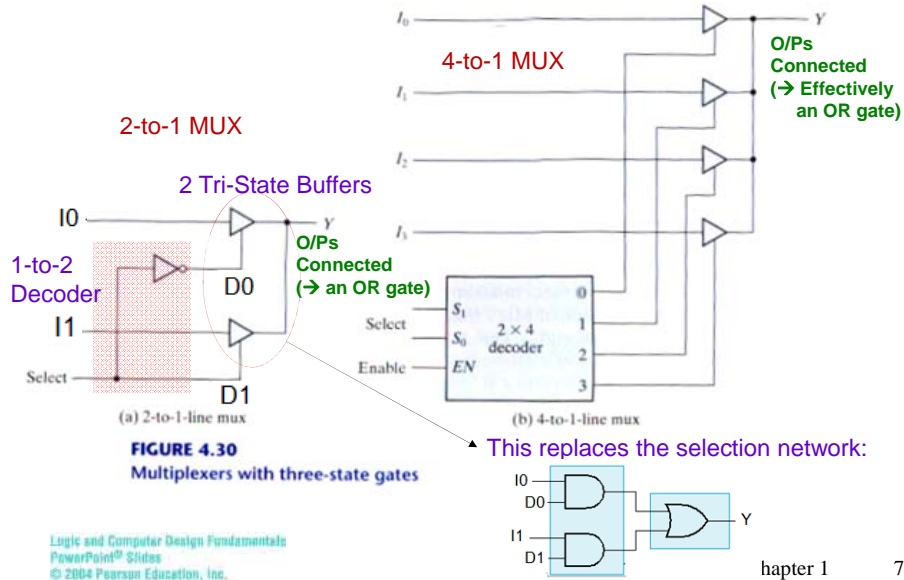Designing MUXes Using 3-State Buffers for Selection



Design Examples Using MSI Combinational Functional Blocks

1. Adding three 4-bit numbers
2. Adding two 16-bit numbers using 4-bit adders
3. Building a 4-to-16 Decoders using several 2-to-4 Decoders (with Enable)
4. Selecting the larger of two 4-bit numbers
5. BCD to Excess-3 Code Converter using **binary** decoders and encoders only
6. Building multi-function combinational circuit (e.g. a cct that adds, subtracts, doubles, etc. according to a set of function select I/Ps)

Important in these problems: Must Label Clearly all inputs/Outputs of all function blocks

Example 1: Adding three unsigned 4-bit digits

Problem: Add three 4-bit numbers (X, Y, Z) using 2 standard MSI 4-bit adders

Solution:

Let the numbers be $X_3X_2X_1X_0$, $Y_3Y_2Y_1Y_0$, $Z_3Z_2Z_1Z_0$,

$$\begin{array}{r}
 X_3X_2X_1X_0 \\
 + Y_3Y_2Y_1Y_0 \\
 \hline
 \end{array}
 +
 \begin{array}{r}
 S_3S_2S_1S_0 \\
 + Z_3Z_2Z_1Z_0 \\
 \hline
 \end{array}$$


D₄ F₃F₂F₁F₀

C₄ S₃S₂S₁S₀

Note: C₄ and D₄ are generated in digit position 4. They must be added in the same position to generate the most significant bits of the result

Logic and Computer Design Fundamentals
 PowerPoint® Slides
 © 2004 Pearson Education, Inc.


Adding three unsigned 4-bit digits

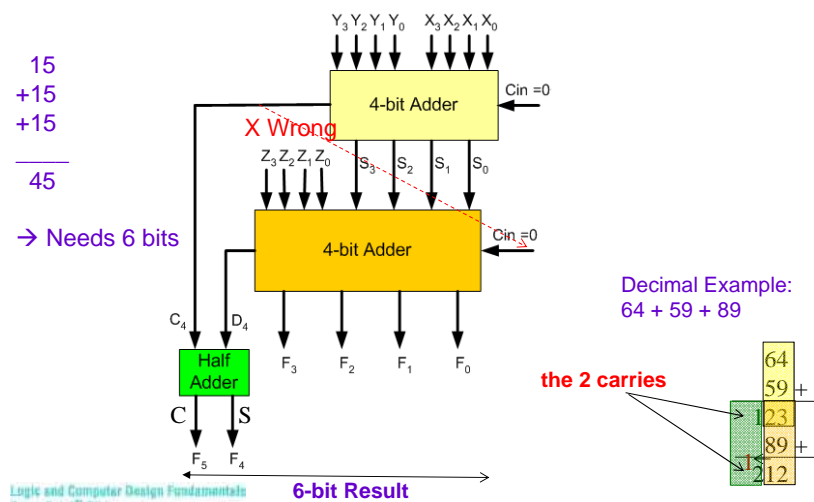

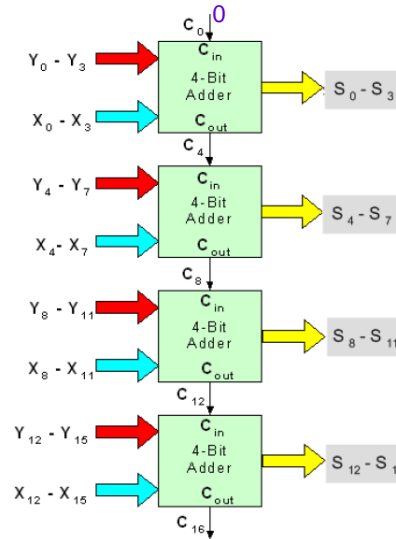Example 2: Adding two 16-bit numbers using a number of 4-bit adders

Solution:

Four 4-bit adder blocks are connected in cascade, with carries rippling in between



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Chapter 3 - Part 1

Example 3: Design a 4-to-16 Decoder Using a number of 2-to-4 Decoders (each with Enable)

Problem: Design a 4-to-16 Decoder using a number of 2-to-4 Decoders with Enable

Solution:


- Four 2-to-4 decoders are fed with A1 A0 (in parallel) to generate the 16 output lines
- The remaining 2 input lines A3 A2 drive a 5th 2-to-4 decoder to select (Enable) one of the 4 decoders to perform decoding for its group of 4 lines

Select 1 of the 4 2-to-4 decoders Common to all 4 2-to-4 decoders

	A ₃	A ₂	A ₁	A ₀	Active Output
A ₃ A ₂ = 00	0	0	0	0	D ₀
	0	0	0	1	D ₁
	0	0	1	0	D ₂
	0	0	1	1	D ₃
A ₃ A ₂ = 01	0	1	0	0	D ₄
	0	1	0	1	D ₅
	0	1	1	0	D ₆
	0	1	1	1	D ₇
A ₃ A ₂ = 10	1	0	0	0	D ₈
	1	0	0	1	D ₉
	1	0	1	0	D ₁₀
	1	0	1	1	D ₁₁
A ₃ A ₂ = 11	1	1	0	0	D ₁₂
	1	1	0	1	D ₁₃
	1	1	1	0	D ₁₄
	1	1	1	1	D ₁₅

Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.


4-to-16 Decoder

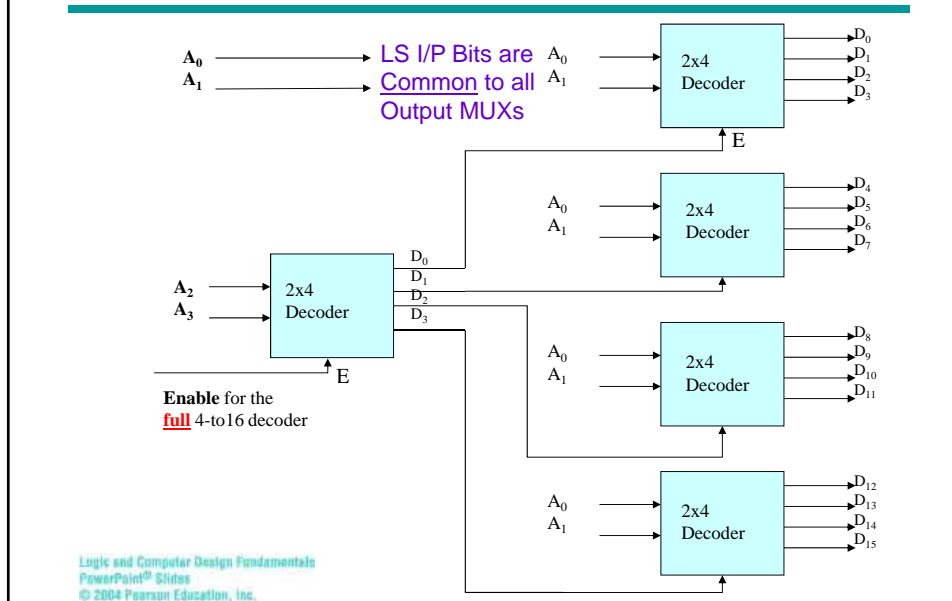

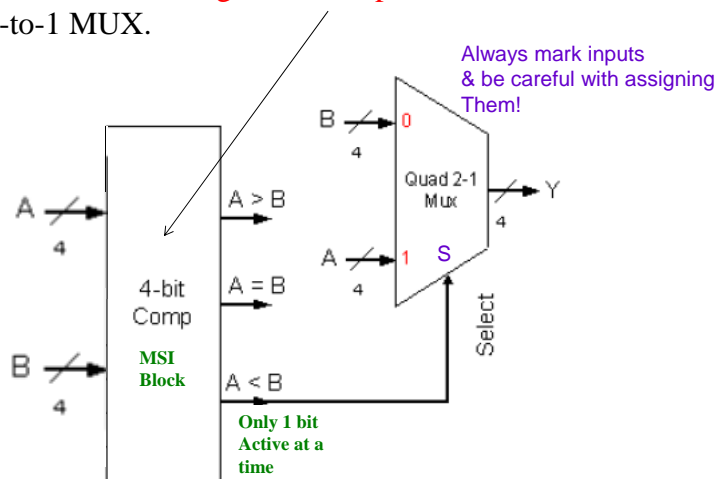Example 4:


Hardware that compares two unsigned 4-bit numbers and selects (passes) the smaller of the two to the O/P

Solution: We will use a magnitude comparator and a Quad 2-to-1 MUX.



Logic and Computer Design Fundamentals
PowerPoint® Slides
© 2004 Pearson Education, Inc.

Example 5: BCD to Excess-3 Code Converter using a decoder and straight binary encoder

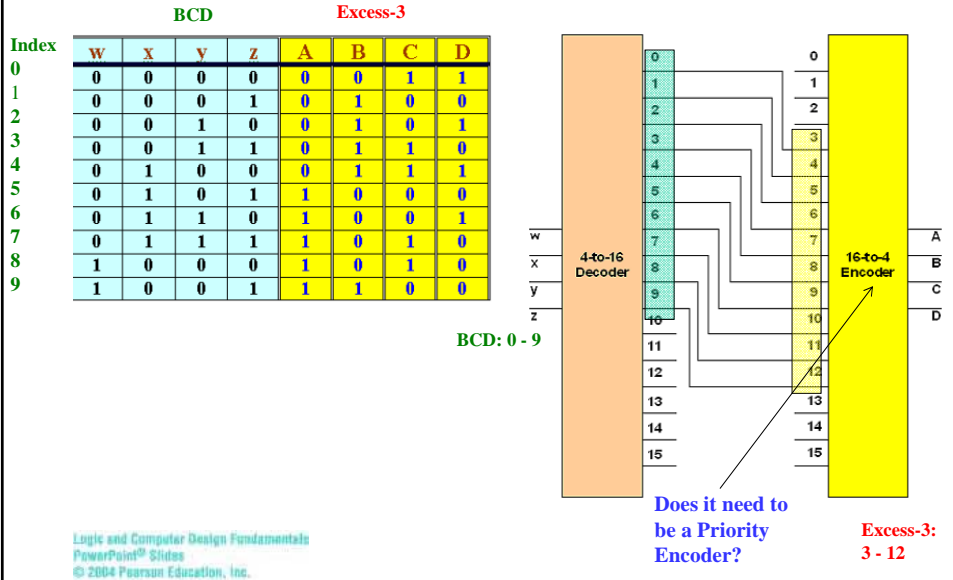

Example 6: Building multiple-function combinational circuit (e.g. add, subtract, Max, ..)

