

# COE 202- Digital Logic

## K-Map Simplification

Dr. Abdulaziz Y. Barnawi

COE Department

KFUPM

# Outline

- Introduction
- Learn to minimize a function using K-Maps
  - 2-Variable K-Maps
  - 3-Variable K-Maps
  - 4-Variable K-Maps
- Prime and essential prime implicants
- SOP and POS simplification
- Simplification using don't care conditions
- 5-Variable K-Maps

# Introduction

- ❑ Even though Boolean expressions can be simplified by algebraic manipulation, such an approach lacks clear regular rules for each succeeding step and it is difficult to determine whether the simplest expression has been achieved. Also, mistakes are easy to make
- ❑ In contrast, **Karnaugh map (K-map)** method provides a straightforward procedure for simplifying Boolean functions.
- ❑ K-maps of up to 4 variables are very common to use. Maps of 5 and 6 variables can be made as well, but are more cumbersome to use.

# Introduction

- ❑ Simplified expressions produced by K-maps are always either in the **SOP** or the **POS** form.
- ❑ The map provides the same information contained in a Truth Table but in a different format.
- ❑ The objectives of this unit are to learn:
  - ❑ How to build a 2, 3, or 4 variables K-map.
  - ❑ How to obtain a minimized SOP or POS function using K-maps.



# Truth Table Adjacencies

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

These minterms are adjacent in a gray code sense – they differ by only one bit.

We can apply the identity  $XY + XY' = X$

$$F = A'B' + A'B = A'(B' + B) = A'(1) = A'$$

A	B	F
0	0	0
0	1	1
1	0	0
1	1	1


Same idea:

$$F = A'B + AB = B$$

Keep common literal only!

 
# 2-Variable K-Maps

- The 2-variable map is a table of 2 rows by 2 columns.
- The 2 rows represent the two values of the first input variable A, while the two columns represent the two values of the second input variable B.
- Thus, all entries (squares) in the first row correspond to input variable  $A=0$ , while entries (squares) of the second row correspond to  $A=1$ .
- Likewise, all entries of the first column correspond to input variable  $B = 0$ , while entries of the second column correspond to  $B=1$ .


 
# 2-Variable K-Maps

- Thus, each map entry (or square) corresponds to a unique value for the input variables A and B.
- For example, the top left square corresponds to input combination  $AB=00$ . In other words, this square represents minterm  $m_0$ .
- Likewise, the top right square corresponds to input combination  $AB=01$ , or minterm  $m_1$ .
- In general, each map entry (or square) corresponds to a particular input combination (or minterm).





# 2-Variable K-Maps

- Two K-map squares are considered **adjacent** if the input codes they represent have a **Hamming distance of 1**.
- A K-map square with a function value of 1 will be referred to as a **1-Square**.
- A K-map square with a function value of 0 will be referred to as a **0-Square**.
- The **simplification procedure** is summarized below:
  - Step 1:** Draw the map according to the number of input variables of the function, i.e.  $2^n$  squares,  $n = \text{\#of variables}$
  - Step 2:** Fill “1’s” in the squares for which the function output is “1”

	<b>B</b>	<b>0</b>	<b>1</b>
<b>A</b>	<b>0</b>	m0	m1
	<b>1</b>	m2	m3

# 2-Variable K-Maps

- **Step 3:** Form as big group of adjacent 1-squares as possible. There are some rules for this which you will learn with bigger maps.
- **Step 4:** Find the common literals for each group and write the simplified expression in SOP.
- **Example:** Consider the given truth table of two variable function. Obtain the simplified function using K-map.

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1


		Y	0	1
X	0	0	0	0
	1	1	1	1

Combining all the 1's in only the adjacent squares

The final reduced expression is given by the common literals from the combination. So, the reduced function is:  $F(X,Y) = X$


# 2-Variable K-Maps

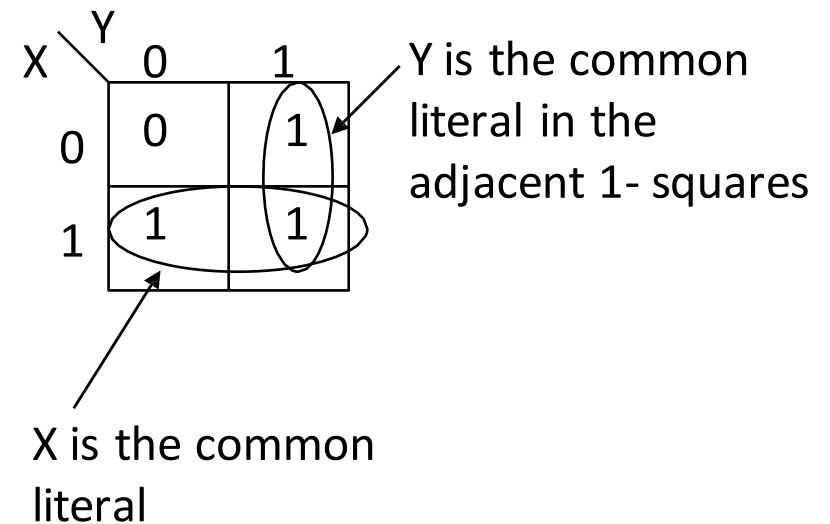- **Question:** Simplify the function  $F(X,Y) = \sum m(1,2,3)$
- **Solution:** This function has 2 variables, and three 1-squares (three minterms where function is 1)
  - $F = m_1 + m_2 + m_3$
  - Note: The 1-squares can be combined more than once
  - The Minimized expression is  **$F = X + Y$**



 
# 2 variable K-Maps (Adjacency)

- In an n-variable map each square is adjacent to “n” other squares, e.g., in a 2-variable map each square is adjacent to two other squares



- Examples of non-adjacent squares

 

# 3-Variable K-Maps

- There are eight minterms for a Boolean function with three-variables, e.g.  $F(A, B, C)$
- Hence, a three-variable map consists of  $2^3 = 8$  squares
- All entries (squares) in the first row correspond to input variable  $A=0$ , while entries (squares) of the second row correspond to  $A=1$ .

		BC			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$


# 3-Variable K-Maps

- █ Likewise, all entries of the first column correspond to input variable  $B = 0, C = 0$ .
- █ All entries of the second column correspond to input variable  $B = 0, C = 1$ .
- █ All entries of the third column correspond to input variable  $B = 1, C = 1$ .
- █ All entries of the fourth column correspond to  $B=1, C = 0$

		BC			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
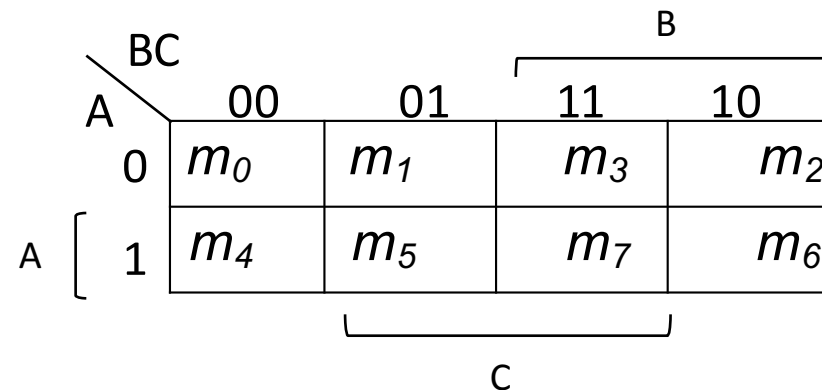
# 3-Variable K-Maps

- To maintain adjacency neighbors don't have more than 1 different bit



- There are cases where two squares in the map are considered to be adjacent even though they do not physically touch each other.
- $m_0$  is adjacent to  $m_2$  and  $m_4$  is adjacent to  $m_6$  because the minterms differ by only one variable.

# 3-Variable K-Maps




## □ How to minimize

- Groups may only consist of 2, 4, 8, 16,... squares (always power of 2). For example, groups may not consist of 3, 6 or 12 squares.
- Members of a group must have a closed loop adjacency, i.e., L-Shaped 4 squares do not form a valid group.
- One square is represented by a minterm (i.e. a product term containing all 3 literals).
- A group of 2 adjacent squares is represented by a product term containing only 2 literals, i.e., 1 literal is dropped.
- A group of 4 adjacent squares is represented by a product term containing only 1 literal, i.e., 2 literals are dropped.





   
# 3 variable K-Maps (Adjacency)

- A 3-variable map has 12 possible groups of 2 minterms. They become product terms with 2 literals



   - A 3-variable map has 6 possible groups of 4 minterms. They become product terms with 1 literal



# 3-Variable K-Maps Examples

A \ BC	00	01	11	10
0		1	1	
1		1	1	

Out = C

A \ BC	00	01	11	10
0			1	1
1			1	1

Out = B

A \ BC	00	01	11	10
0			1	
1			1	


Out = BC

A \ BC	00	01	11	10
0	1	1	1	1
1			1	1

Out =  $\bar{A} + B$

A \ BC	00	01	11	10
0	1			1
1	1			1

Out =  $\bar{C}$

 

A \ BC	00	01	11	10
0	1	1	1	1
1	1			1

Out =  $\bar{A} + \bar{C}$

A \ BC	00	01	11	10
0			1	
1		1	1	1

Output =  $AB + BC + AC$

# 3-Variable K-Maps Examples

- Simplify  $F = \sum m(1, 3, 4, 6)$  using K-map

# 3-Variable K-Maps Examples

- Simplify  $F = \sum m(1, 3, 4, 6)$  using K-map

		BC			
		00	01	11	10
A	0		1	1	
	1	1			1
		C		B	


- Minimized F is  $F = A'C + AC'$

# 3-Variable K-Maps Examples

- Simplify  $F = \sum m(0,1, 2, 4, 6)$  using K-map
 
# 3-Variable K-Maps Examples

- Simplify  $F = \sum m(0,1, 2, 4, 6)$  using K-map



- Minimized F is  $F = A'B' + C'$

# 4-Variable K-Maps

- There are 16 minterms for a Boolean function with four-variables. Hence, four-variable map consists of 16 squares.
- Each square is adjacent to 4 other squares.
- A square by itself will represent a 4-literals output
- Combining 2 squares will generate a 3-literal output
- Combining 4 squares will generate a 2-literal output
- Combining 8 squares will generate a 1-literal output

		<b>CD</b>			
		00	01	11	10
<b>AB</b>	00	m0	m1	m3	m2
	01	m4	m5	m7	m6
	11	m12	m13	m15	m14
	10	m8	m9	m11	m10

# 4-variable K-maps (Adjacency)

- You can only combine a power of 2 adjacent 1-squares. For e.g. 2, 4, 8, 16 squares. You cannot combine 3, 7 or 5 squares
- Right column and left column are adjacent; can be combined
- Top row and bottom row are adjacent; can be combined
- Many possible 2, 4, 8 groupings







AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

B

D



# Four-Variable K-Map Examples

 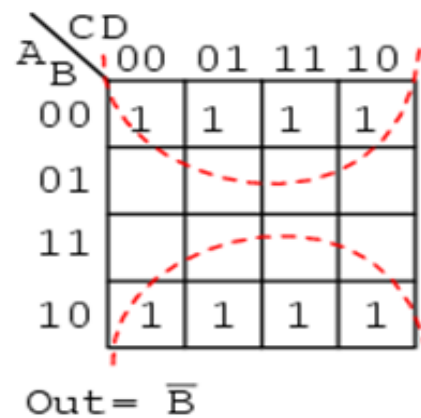 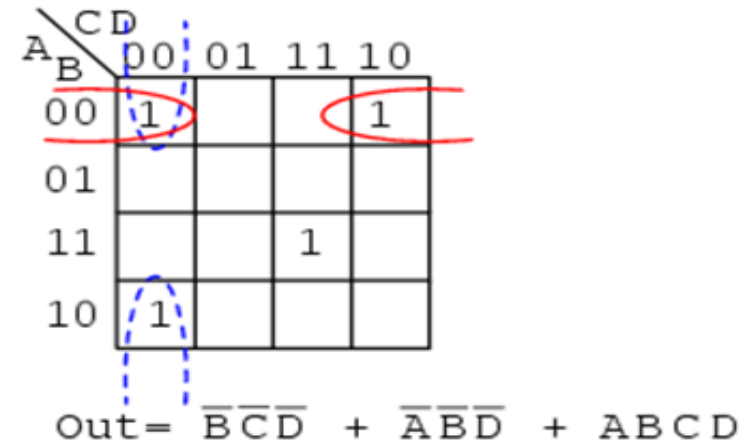  

# Four-Variable K-Map Examples

- Minimize the function  $F(A,B,C,D)=\sum m(1,3,5,6,7,8,9,11,14,15)$

# Four-Variable K-Map Examples

- Minimize the function  $F(A,B,C,D)=\sum m(1,3,5,6,7,8,9,11,14,15)$

AB \ CD		C			
		00	01	11	10
A	00		1	1	
	01		1	1	1
	11			1	1
	10	1	1	1	

Diagram illustrating the Karnaugh map for the function  $F(A,B,C,D) = \sum m(1,3,5,6,7,8,9,11,14,15)$ . The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). The function is 1 for the minterms listed. The map shows several groups of 1s: a group of 4 (minterms 1, 3, 5, 7), a group of 4 (minterms 8, 9, 10, 11), a group of 2 (minterms 1, 3), a group of 2 (minterms 5, 7), a group of 2 (minterms 8, 9), and a group of 2 (minterms 10, 11). The groups are labeled A, B, and C.


- Minimized F is  $F = CD + A'D + BC + AB'C'$

# Four-Variable K-Map Examples

□  $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$

# Four-Variable K-Map Examples

□  $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$

 

□ Minimized F is  $F = B' D' + B' C' + A' C' D$


# Four-Variable K-Map Examples

- Question: What if it is required to write the minimized F in a product of sums (POS) form
  - Two methods:
    - Method 1: You already know one!
    - Method 2: Follow same rule as before but combine the ones of F', then find F.

- $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$

- Minimized  $F' = AB + CD + BD'$



- So,  $F'' = F = (A'+B')(C'+D')(B'+D)$

 

- ❑ A product term of a function is said to be an **implicant**.
- ❑ A **Prime Implicant (PI)** is a product term obtained by combining the maximum possible number of adjacent 1-squares in the map.
- ❑ A **Prime Implicant** is a product that we cannot remove any of its literals.
  - ❑ Largest groups of 1's
  - ❑ Not all prime implicants are needed!
- ❑ If a minterm is covered only by one prime implicant then this prime implicant is said to be an **Essential Prime Implicant (EPI)**.

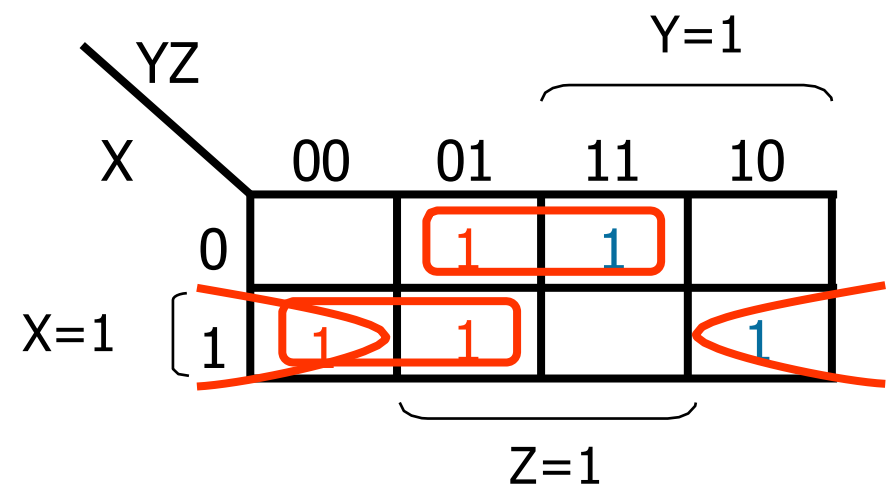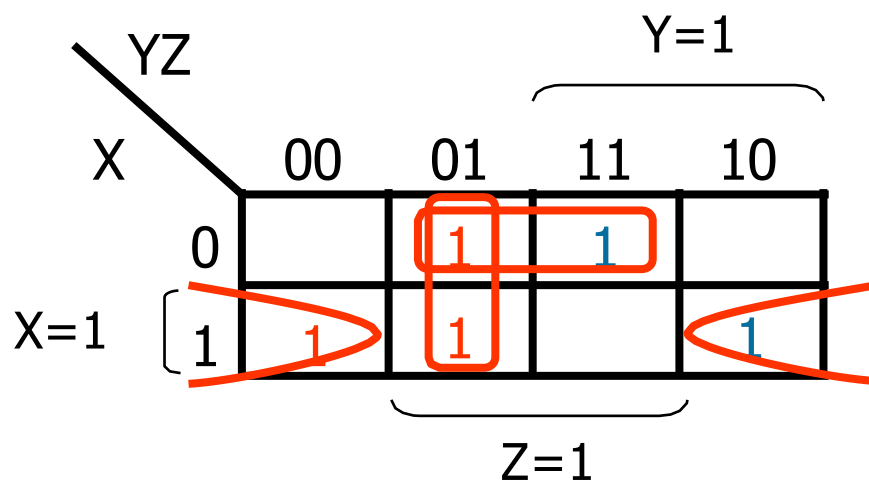
# Examples of Types of Implicants

- Consider  $F(X,Y,Z) = (1,3,4,5,6)$ , List all implicants, prime implicants and essential prime implicants
- Solution:
  - **Implicants:**  $XY'Z'$ ,  $XZ'$ ,  $XY'$ ,  $XY'Z$ ,  $X'Y'Z$ ,  $Y'Z$ , ...
  - **P.Is:**  $XY'$ ,  $XZ'$ ,  $Y'Z$ ,  $X'Z$
  - **E.P.Is:**  $X'Z$ ,  $XZ'$





# Examples of Types of Implicants

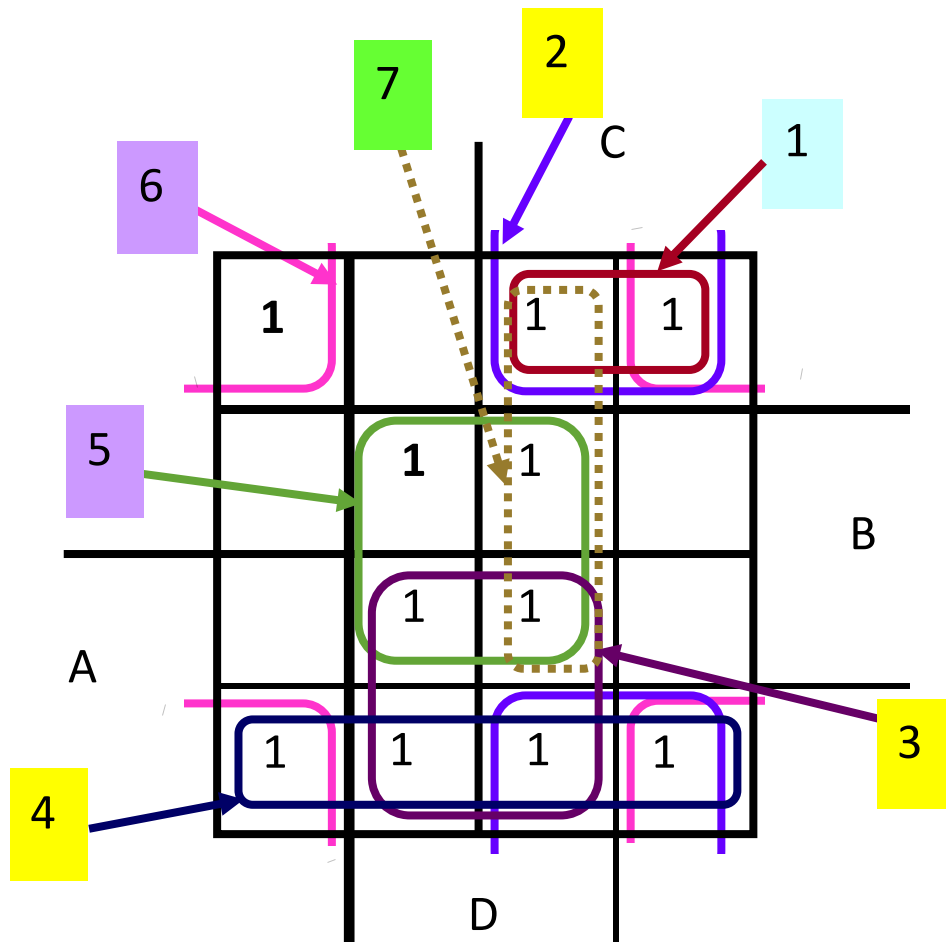


- 1 An implicant
- 2-4 Prime Implicants
- 5-6 Essential Prime Implicants

Give a situation that makes implicant 1 a prime implicant

Does 7 represent a single product term? Is it an implicant? Why?

Minterm covered by only one prime implicant So minterm 5 is .....

# Examples of Types of Implicants

 


# Examples of Types of Implicants

- ❖ Find **all possible** prime implicants for:

$$G(W, X, Y, Z) = \Sigma_m(0, 2, 3, 4, 7, 12, 13, 14, 15)$$

 - ✧ *Hint: There are seven prime implicants!*



# SOP Simplification procedure


- Identify all **prime implicants** covering 1's
  - Example: For a function of 3 variables, group all possible groups of 4, then groups of 2 that are not contained in groups of 4, then minterms that are not contained in a group of 4 or 2.
- Identify all **essential prime implicants** and select them.
- Check all minterms (1's) covered by essential prime implicants
- Repeat until all minterms (1's) are covered:
  - Select the prime implicant covering the largest **uncovered minterms (1's)**

# SOP Simplification procedure

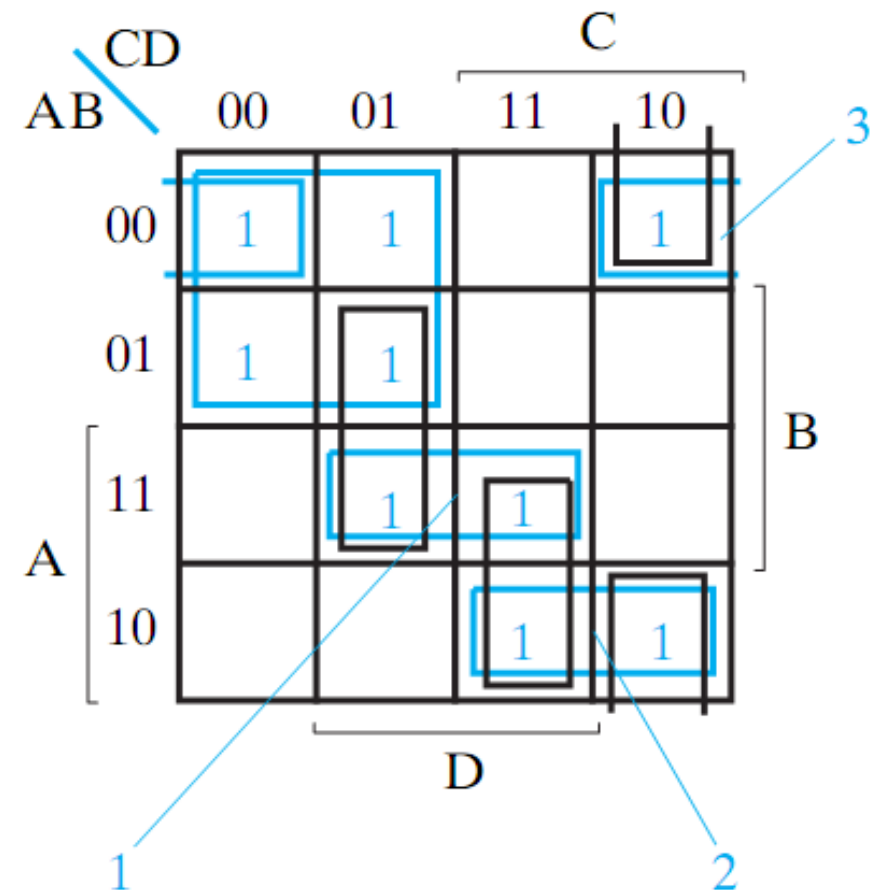Example: Simplify  $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 10, 11, 13, 15)$

Solution:

- Only  $A'C'$  is E.P.I
- For the remaining minterms:
- Choose 1 and 2 (minimize overlap)
- For  $m_2$ , choose either  $A'B'D'$  or  $B'CD'$
- $F = A'C' + ABD + AB'C + A'B'D'$



# Don't Care Conditions

- ❑ In some cases, the function is not specified for certain combinations of input variables as 1 or 0.
- ❑ There are two cases in which it occurs:
  - ❑ The input combination never occurs.
  - ❑ The input combination occurs but we do not care what the outputs are in response to these inputs because the output will not be observed.
- ❑ In both cases, the outputs are called as unspecified and the functions having them are called as **incompletely specified functions**
- ❑ In most applications, we simply do not care what value is assumed by the function for unspecified minterms.

# Don't Care Conditions

- Unspecified minterms of a function are called as **don't care conditions**. They provide further simplification of the function, and they are denoted by **X's** to distinguish them from 1's and 0's.
- In choosing adjacent squares to simplify the function in a map, the don't care minterms can be assumed either 1 or 0, depending on which combination gives the simplest expression.
- A don't care minterm need not be chosen at all if it does not contribute to produce a larger implicant.

# SOP Simplification procedure using Don't Cares

- Identify all prime implicants covering 1's & X's
  - Each prime implicant must contain at least a single 1
- Identify all essential prime implicants and select them.
  - An essential prime implicant must be the only implicant covering at least a "1".
- Check all 1's covered by essential prime implicants
- Repeat until all 1's are covered:
  - Select the prime implicant covering the largest **uncovered 1's**.



# SOP Simplification procedure using Don't Cares

- Example: Minimize  $F = \sum m(1, 3, 7) + \sum d(0, 5)$
- Circle the X's that help get bigger groups of 1's (or 0's if POS).
- Don't circle the X's that don't help.

		B			
		00	01	11	10
A	0	<sup>0</sup> <b>X</b>	<sup>1</sup> <b>1</b>	<sup>3</sup> <b>1</b>	<sup>2</sup>
	1	<sup>4</sup>	<sup>5</sup> <b>X</b>	<sup>7</sup> <b>1</b>	<sup>6</sup>

C

# SOP Simplification procedure using Don't Cares

- **Example:** Minimize  $F = \sum m(1, 3, 7) + \sum d(0, 5)$
- Circle the X's that help get bigger groups of 1's (or 0's if POS).
- Don't circle the X's that don't help.
- $F = C$

		B			
		00	01	11	10
A	0	0 <b>X</b>	1 <b>1</b>	3 <b>1</b>	2
	1	4	5 <b>X</b>	7 <b>1</b>	6
		C			
		00	01	11	10

# SOP Simplification procedure using Don't Cares

- **Example:** Minimize  $F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$ 
  - Two possible solutions!
  - Both acceptable
  - All 1's covered

		C				B
		00	01	11	10	
A	00	X	1	1	X	
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

$$(a) F = CD + \bar{A} \bar{B}$$

		C				B
		00	01	11	10	
A	00	X	1	1	X	
	01	0	X	1	0	
	11	0	0	1	0	
	10	0	0	1	0	
		D				

$$(b) F = CD + \bar{A} D$$


# POS Simplification

- Until now we have derived simplified Boolean functions from the maps in SOP form. Procedure for deriving simplified Boolean functions POS is slightly different. Instead of making groups of 1's, make the groups of 0's.
- Since the simplified expression obtained by making group of 1's of the function (say  $F$ ) is always in SOP form. Then the simplified function obtained by making group of 0's of the function will be the complement of the function (i.e.,  $F'$ ) in SOP form.
- Applying DeMorgan's theorem to  $F'$  (in SOP) will give  $F$  in POS form.
 
# POS Simplification

- Find the optimum POS solution for F, given:

$$F(A, B, C, D) = \Sigma_m(3,9,11,12,13,14,15) + \Sigma_d(1,4,6)$$




# 5-Variable K-Maps

- 32 minterms require 32 squares in the K-map
- Minterms 0-15 belong to the squares with variable  $A=0$ , and minterms 16-32 belong to the squares with variable  $A=1$
- Each square in  $A'$  is also adjacent to a square in  $A$  (one is above the other)
- Minterm 4 is adjacent to 20, and minterm 15 is to 31

BC \ DE		A=0				A=1			
		00	01	11	10	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$	$m_{16}$	$m_{17}$	$m_{19}$	$m_8$ $m_1$	
01	$m_4$	$m_5$	$m_7$	$m_6$	$m_{20}$	$m_{21}$	$m_{23}$	$m_{22}$	
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$	$m_{28}$	$m_{29}$	$m_{31}$	$m_{30}$	
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$	$m_{24}$	$m_{25}$	$m_{27}$	$m_{26}$	

# 5-Variable K-Maps

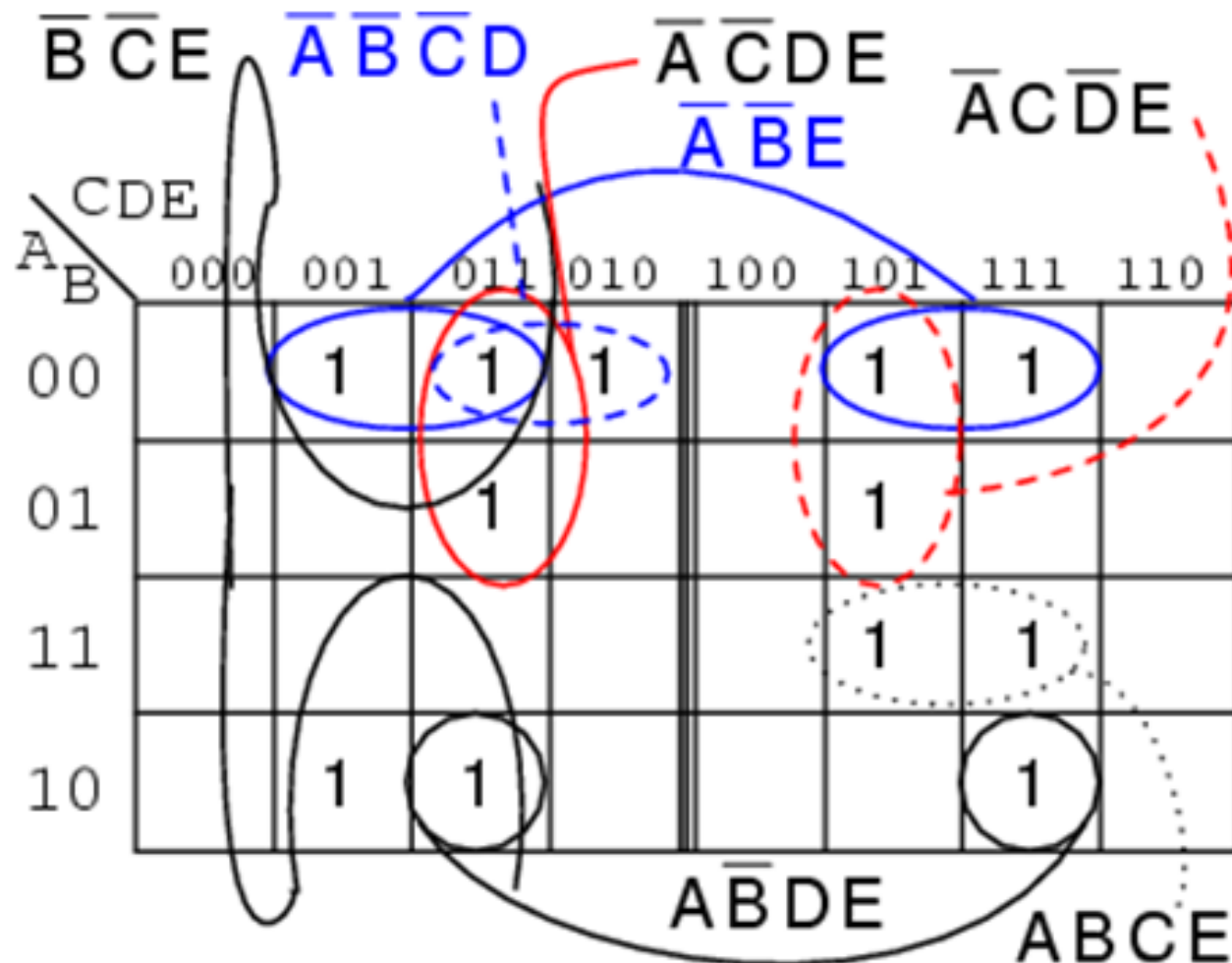

# Conclusion

- A K-Map is simply a folded truth table, where physical adjacency implies logical adjacency
- K-Maps are most commonly used hand method for logic minimization.