

COE 202- Digital Logic

Standard & Canonical Forms

Dr. Abdulaziz Y. Barnawi

COE Department

KFUPM

Outline

- Minterms and Maxterms
- From truth table to Boolean expression
 - Sum of minterms
 - Product of Maxterms
- Standard and Canonical Forms
- Implementation of Standard Forms
- Practical Aspects of Logic Gates

MinTerms

- A **product term** is a term where literals are ANDed.
 - Example: $x'y'$, xz , xyz , ...

- A **minterm** is a product term in which all variables appear exactly once, in normal or complemented form
 - Example: $F(x,y,z)$ has 8 minterms: $\bar{x}\bar{y}\bar{z}, \bar{x}\bar{y}z, \bar{x}y\bar{z}, \bar{x}yz, x\bar{y}\bar{z}, x\bar{y}z, xy\bar{z} & xyz$

- Each minterm equals 1 at exactly one particular input combination and is equal to 0 at all other combinations

- Thus, for example, $\bar{x}\bar{y}\bar{z}$ is always equal to 0 except for the input combination $xyz = 000$, where it is equal to 1.

MinTerms

- In general, minterms are designated m_i , where i corresponds the input combination at which this minterm is equal to 1.
- Accordingly, the minterm $\bar{x}\bar{y}\bar{z}$ is referred to as m_0 .

Minterms for Three Variables

Src: Mano's book

| X | Y | Z | Product Term | Symbol | m_0 | m_1 | m_2 | m_3 | m_4 | m_5 | m_6 | m_7 |
|---|---|---|-------------------------|--------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | $\bar{X}\bar{Y}\bar{Z}$ | m_0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | $\bar{X}\bar{Y}Z$ | m_1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | $\bar{X}Y\bar{Z}$ | m_2 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | $\bar{X}YZ$ | m_3 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | $X\bar{Y}\bar{Z}$ | m_4 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | $X\bar{Y}Z$ | m_5 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | $XY\bar{Z}$ | m_6 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | XYZ | m_7 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

MinTerms

- In general, for n-input variables, the **number of minterms** = the total number of possible input combinations = 2^n .
- **Question:** What is the number of minterms for a function with 5 input variables?
 - Number of minterms = $2^5 = 32$ minterms.

MaxTerms

- A **sum term** is a term where literals are ORed.
 - Example: $x'+y'$, $x+z$, $x+y+z$, ...
- A **maxterm** is a sum term in which all variables appear exactly once, in normal or complemented form
 - Example: $F(x,y,z)$ has 8 Maxterms: $(x+y+z)$, $(x+y+z')$, $(x+y'+z)$, ...
- Each Maxterm equals 0 at exactly one of the 8 possible input combinations and is equal to 1 at all other combinations.
- Thus, for example, $(x + y + z)$ equals 1 at all input combinations except for the combination $xyz = 000$, where it is equal to 0.

MaxTerms

- In general, Maxterms are designated M_i , where i corresponds the input combination at which this Maxterm is equal to 0.
- Accordingly, the minterm $(x + y + z)$ is referred to as M_0 .

Maxterms for Three Variables

Src: Mano's book

| X | Y | Z | Sum Term | Symbol | M_0 | M_1 | M_2 | M_3 | M_4 | M_5 | M_6 | M_7 |
|---|---|---|---------------------------|--------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | $X+Y+Z$ | M_0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | $X+Y+\bar{Z}$ | M_1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | $X+\bar{Y}+Z$ | M_2 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | $X+\bar{Y}+\bar{Z}$ | M_3 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | $\bar{X}+Y+Z$ | M_4 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | $\bar{X}+Y+\bar{Z}$ | M_5 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | $\bar{X}+\bar{Y}+Z$ | M_6 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | $\bar{X}+\bar{Y}+\bar{Z}$ | M_7 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |

MaxTerms

- For n-input variables, the **number of Maxterms** = the total number of possible input combinations = 2^n .
- **Question:** What is the number of Maxterms for a function with 5 input variables?
 - Number of Maxterms = $2^5 = 32$ Maxterms.
- Using De-Morgan's theorem, or truth tables, it can be easily shown that minterms and Maxterms are the complement of each other!

$$M_i = \overline{m_i} \quad \forall i = 0, 1, 2, \dots, (2^n - 1)$$

Expressing Functions as a Sum of Minterms

- A Boolean function can be expressed algebraically from a given truth table by forming the logical sum (OR) of ALL the minterms that produce 1 in the function
- Example: Consider the function defined by the truth table

- $$F(X,Y,Z) = X'Y'Z' + X'YZ' + XY'Z + XYZ$$

$$= m_0 + m_2 + m_5 + m_7$$

$$= \sum m(0,2,5,7)$$

| X | Y | Z | m | F |
|---|---|---|-------|---|
| 0 | 0 | 0 | m_0 | 1 |
| 0 | 0 | 1 | m_1 | 0 |
| 0 | 1 | 0 | m_2 | 1 |
| 0 | 1 | 1 | m_3 | 0 |
| 1 | 0 | 0 | m_4 | 0 |
| 1 | 0 | 1 | m_5 | 1 |
| 1 | 1 | 0 | m_6 | 0 |
| 1 | 1 | 1 | m_7 | 1 |

Expressing Functions as a Product of Sums

- A Boolean function can be expressed algebraically from a given truth table by forming the logical product (AND) of ALL the Maxterms that produce 0 in the function
- Example: Consider the function defined by the truth table

- $F(X,Y,Z) = \prod M(1,3,4,6)$

- Applying DeMorgan

$$F' = m_1 + m_3 + m_4 + m_6$$

$$= \sum m(1,3,4,6)$$

$$F = F'' = [m_1 + m_3 + m_4 + m_6]'$$

$$= m_1' \cdot m_3' \cdot m_4' \cdot m_6'$$

$$= M_1 \cdot M_3 \cdot M_4 \cdot M_6$$

$$= \prod M(1,3,4,6)$$

| X | Y | Z | M | F | F' |
|---|---|---|----------------|---|----|
| 0 | 0 | 0 | M ₀ | 1 | 0 |
| 0 | 0 | 1 | M ₁ | 0 | 1 |
| 0 | 1 | 0 | M ₂ | 1 | 0 |
| 0 | 1 | 1 | M ₃ | 0 | 1 |
| 1 | 0 | 0 | M ₄ | 0 | 1 |
| 1 | 0 | 1 | M ₅ | 1 | 0 |
| 1 | 1 | 0 | M ₆ | 0 | 1 |
| 1 | 1 | 1 | M ₇ | 1 | 0 |

Expressing Functions as Sum of Minterms or Product of Maxterms

- Any function can be expressed both as a sum of minterms ($\sum m_i$) and as a product of Maxterms ($\prod M_j$)
- The product of Maxterms expression ($\prod M_j$) of F contains all Maxterms M_j ($\forall j \neq i$) that do not appear in the sum of minterms expression of F
- The sum of minterms expression of F' contains all minterms that do not appear in the sum of minterms expression of F
- This is true for all complementary functions. Thus, each of the 2^n minterms will appear either in the sum of minterms expression of F or the sum of minterms expression of F' but not both.

Expressing Functions as Sum of Minterms or Product of Maxterms

- The product of Maxterms expression of F' contains all Maxterms that do not appear in the product of Maxterms expression of F
- This is true for all complementary functions. Thus, each of the 2^n Maxterms will appear either in the product of Maxterms expression of F or the product of Maxterms expression of F' but not both

Expressing Functions as Sum of Minterms or Product of Maxterms

- **Example:** Given that $F(a, b, c, d) = \sum (0, 1, 2, 4, 5, 7)$, derive the product of Maxterms expression of F and the two standard form expressions of F'
- Since the system has 4 input variables (a, b, c & d), the number of minterms and Maxterms = $2^4 = 16$
- $F(a, b, c, d) = \sum(0, 1, 2, 4, 5, 7)$
- $F(a, b, c, d) = \prod(3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$
- $F'(a, b, c, d) = \sum(3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$.
- $F'(a, b, c, d) = \prod(0, 1, 2, 4, 5, 7)$

Expressing Functions as Sum of Minterms or Product of Maxterms

□ **Example:** Let $F(X,Y,Z) = Y' + X'Z'$, express F as a sum of minterms and product of Maxterms

$$\begin{aligned}
 \square \quad F &= Y' + X'Z' \\
 &= Y'(X+X')(Z+Z') + X'Z'(Y+Y') \\
 &= (XY'+X'Y')(Z+Z') + X'YZ'+X'Z'Y' \\
 &= XY'Z+X'Y'Z+XY'Z'+X'Y'Z'+ X'YZ'+X'Z'Y' \\
 &= m_5 + m_1 + m_4 + m_0 + m_2 + m_0 \\
 &= m_0 + m_1 + m_2 + m_4 + m_5 \\
 &= \sum m(0,1,2,4,5)
 \end{aligned}$$

□ To find the form $\prod M$, consider the remaining indices

$$\square \quad F = \prod M(3,6,7)$$

□ **What about F'?**

Expressing Functions as Sum of Minterms or Product of Maxterms

- **Question:** $F(a,b,c,d) = \sum m(0,1,2,4,5,7)$, What are the minterms and Maxterms of F and its complement \bar{F} ?
- **Solution:**

Expressing Functions as Sum of Minterms or Product of Maxterms

- **Question:** $F(a,b,c,d) = \sum m(0,1,2,4,5,7)$, What are the minterms and Maxterms of F and its complement \overline{F} ?
- **Solution:**
- F has 4 variables; $2^4 = 16$ possible minterms/Maxterms

$$\begin{aligned}
 F(a,b,c,d) &= \sum m(0,1,2,4,5,7) \\
 &= \prod M(3,6,8,9,10,11,12,13,14,15)
 \end{aligned}$$

$$\begin{aligned}
 \overline{F}(a,b,c,d) &= \sum m(3,6,8,9,10,11,12,13,14,15) \\
 &= \prod M(0,1,2,4,5,7)
 \end{aligned}$$

Operations on Functions

- The AND operation on two functions corresponds to the intersection of the two sets of minterms of the functions
- The OR operation on two functions corresponds to the union of the two sets of minterms of the functions
- Example
 - Let $F(A,B,C) = \sum m(1, 3, 6, 7)$ and $G(A,B,C) = \sum m(0,1, 2, 4,6, 7)$
 - $F \cdot G = \sum m(1, 6, 7)$
 - $F + G = \sum m(0,1, 2, 3, 4,6, 7)$
 - $F' \cdot G = ?$
 - $F' = \sum m(0, 2, 4, 5)$
 - $F' \cdot G = \sum m(0, 2, 4)$

Canonical Forms

- The sum of minterms and the product of Maxterms forms of Boolean expressions are known as **canonical** forms.
- Canonical form means that all equivalent functions will have a unique and equal representation.
- Two functions are equal if and only if they have the same sum of minterms and the same product of Maxterms.
- Example:
 - Are the functions $F1 = a' b' + a c + b c'$ and $F2 = a' c' + a b + b' c$ Equal?
 - $F1 = a' b' + a c + b c' = \Sigma m(0, 1, 2, 5, 6, 7)$
 - $F2 = a' c' + a b + b' c = \Sigma m(0, 1, 2, 5, 6, 7)$
 - They are equal as they have the same set of minterms.

Standard Forms

- **Remember:** a **product term** is a term with ANDed literals. Thus, AB , $A'B$, $A'CD$ are all product terms
- A minterm is a special case of a product term where all input variables appear in the product term either in the true or complement form
- **Remember:** a **sum term** is a term with ORed literals. Thus, $(A+B)$, $(A'+B)$, $(A'+C+D)$ are all sum terms
- A maxterm is a special case of a sum term where all input variables, either in the true or complement form, are ORed together

Standard Forms

- Boolean functions can generally be expressed in the form of a **Sum of Products (SOP)** or in the form of a **Product of Sums (POS)**
- The sum of minterms form is a special case of the SOP form where all product terms are minterms.
- The product of Maxterms form is a special case of the POS form where all sum terms are Maxterms.
- The **SOP** and **POS** forms are **Standard forms** for representing Boolean functions.

SOP and POS Conversion

SOP \rightarrow POS

$$\begin{aligned}
 F &= AB + CD \\
 &= (AB+C)(AB+D) \\
 &= (A+C)(B+C)(AB+D) \\
 &= (A+C)(B+C)(A+D)(B+D)
 \end{aligned}$$

POS \rightarrow SOP

$$\begin{aligned}
 F &= (A'+B)(A'+C)(C+D) \\
 &= (A'+BC)(C+D) \\
 &= A'C+A'D+BCC+BCD \\
 &= A'C+A'D+BC+BCD \\
 &= A'C+A'D+BC
 \end{aligned}$$

Question1: How to convert SOP to sum of minterms?

Question2: How to convert POS to product of Maxterms?


Two-Level Implementations of Standard Forms

- ❑ **Sum of Products Expressions (SOP):**
- ❑ Any SOP expression can be implemented in 2-levels of gates.
- ❑ The first level consists of a number of **AND gates** which equals the number of product terms in the expression.
- ❑ Each AND gate implements one of the product terms in the expression.
- ❑ The second level consists of a **single OR gate** whose number of inputs equals the number of product terms in the expression.

Two-Level Implementations of Standard Forms

- Example: Implement the following SOP function

$$F = XZ + Y'Z + X'YZ$$

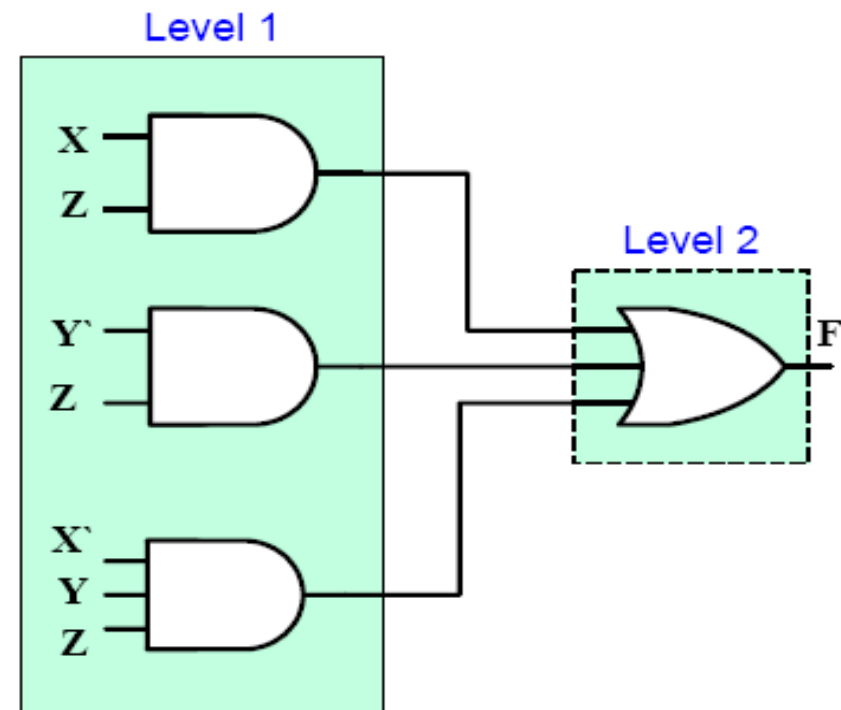

Two-Level Implementation ($F = XZ + Y'Z + X'YZ$)

Level-1: AND-Gates ; Level-2: One OR-Gate


Two-Level Implementations of Standard Forms

- **Product of Sums Expression (POS):**
- Any POS expression can be implemented in 2-levels of gates.
- The first level consists of a number of **OR gates** which equals the number of sum terms in the expression.
- Each gate implements one of the sum terms in the expression.
- The second level consists of a **single AND gate** whose number of inputs equals the number of sum terms.

Two-Level Implementations of Standard Forms

- Example: Implement the following POS function

$$F = (X+Z)(Y'+Z)(X'+Y+Z)$$

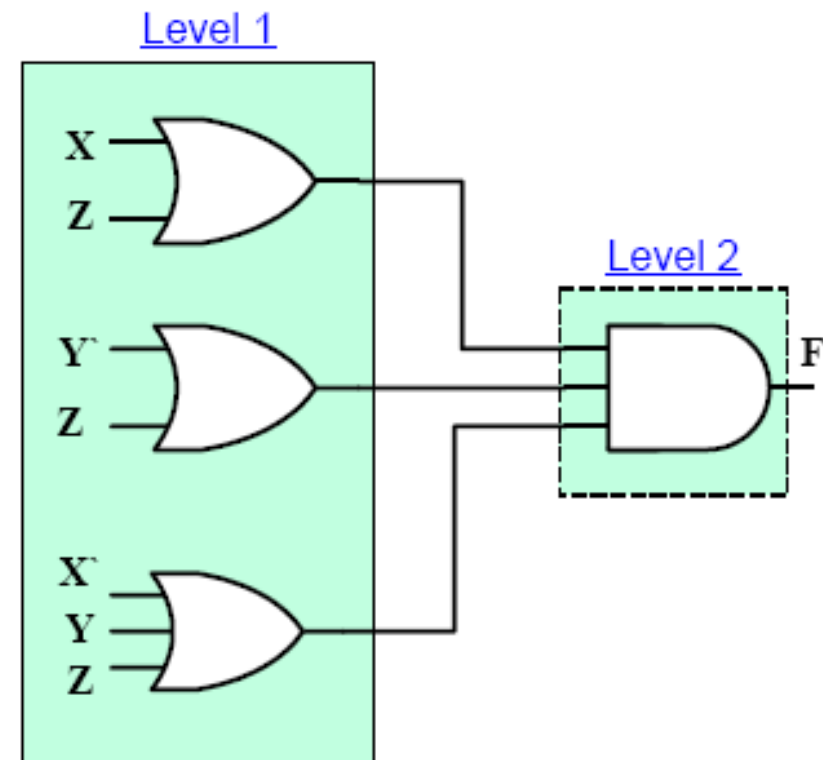


Two-Level Implementation { $F = (X+Z)(Y'+Z)(X'+Y+Z)$ }

Level-1: OR-Gates ; Level-2: One AND-Gate


Practical Aspects of Logic Gates

- Logic gates are built with transistors as integrated circuits (IC) or chips.
- ICs are digital devices built using various technologies.
- Complementary metal oxide semiconductor (CMOS) technology
- Levels of Integration:
 - Small Scale Integrated (SSI) < 10 gates
 - Medium Scale Integrated (MSI) < 100 gates
 - Large Scale Integrated (LSI) < 1000 gates
 - Very Large Scale Integrated (VLSI) < 10⁶ gates

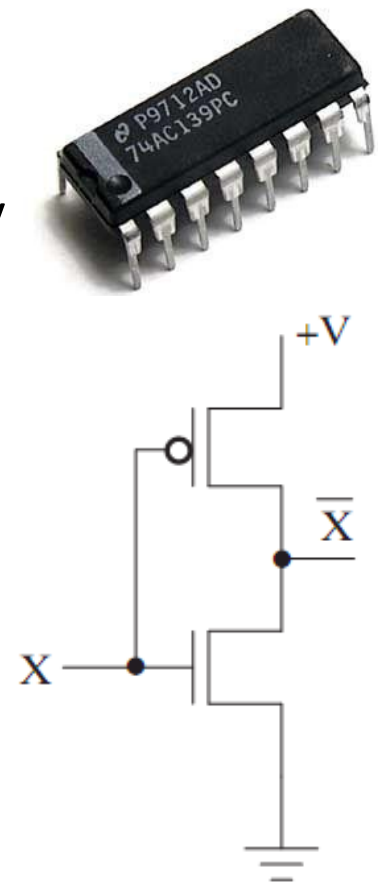


Practical Aspects of Logic Gates

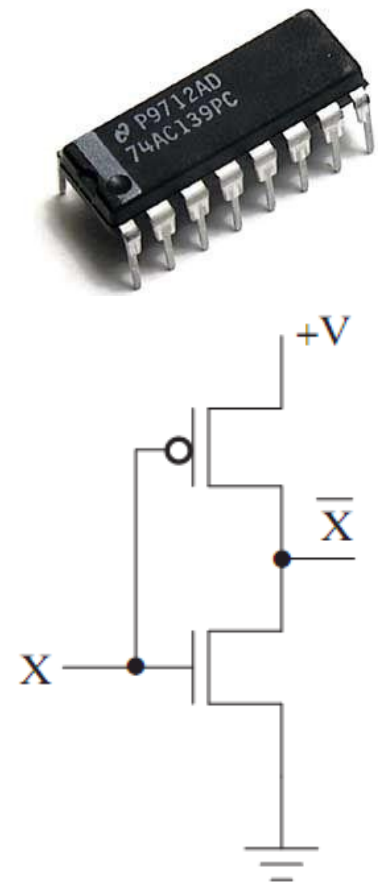- Key characteristics of ICs are:
 - Voltages ranges
 - Noise Margin
 - Gate propagation delay/speed
 - Fan-in and Fan-out
 - Buffers
 - Tri-state Gates




Voltage Levels

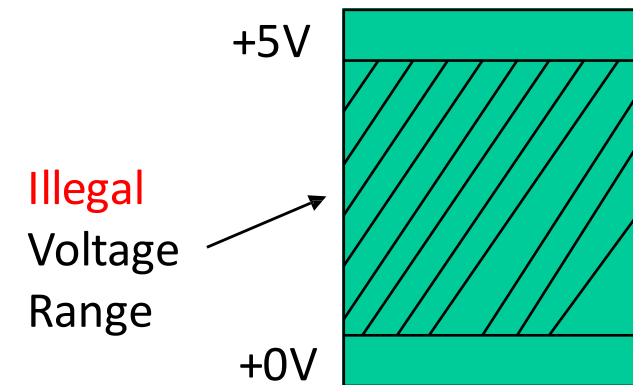- Logic values of 0 & 1 corresponds to voltage level
- A range of voltage defines logic 0 and logic 1
- Any value outside this range is invalid




Noise Margins

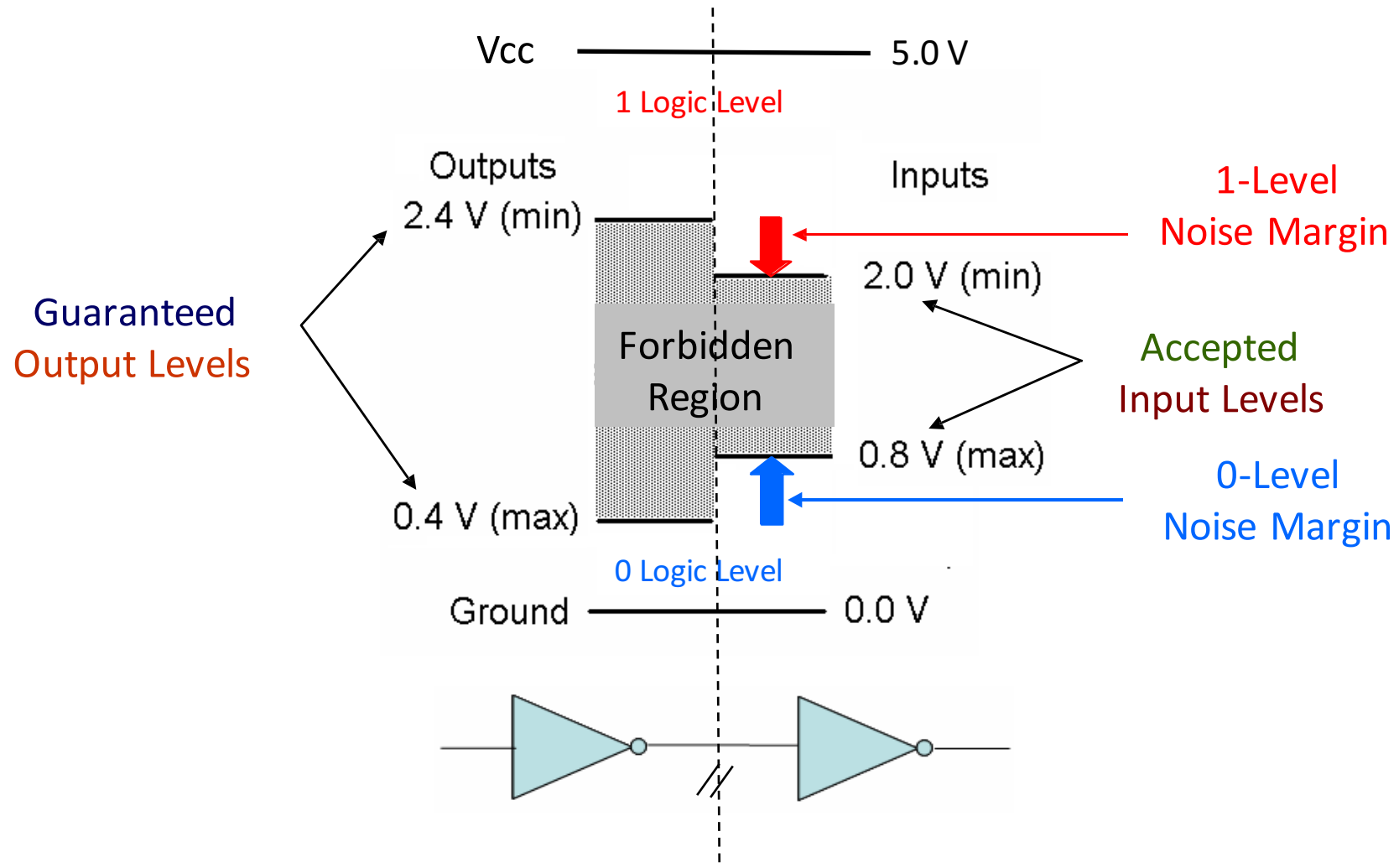


Propagation Delay

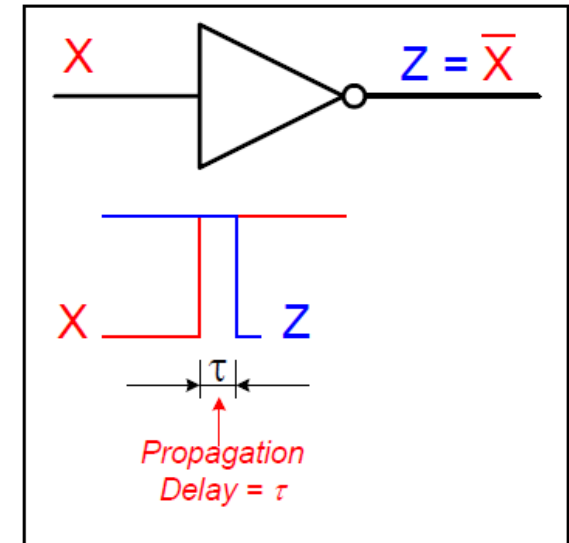- Consider the shown inverter with input X and output Z.
 - A change in the input (X) from 0 to 1 causes the inverter output (Z) to change from 1 to 0.
 - The change in the output (Z), however is not instantaneous. Rather, it occurs slightly after the input change.
 - This delay between an input signal change and the corresponding output signal change is what is known as the **propagation delay**



Propagation Delay

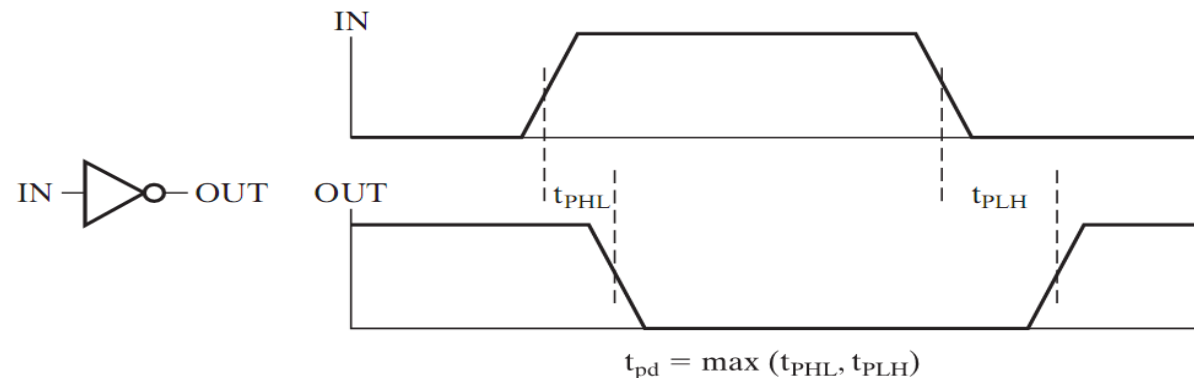
- Formally, the **propagation delay** (t_{pd}) is the time for a change in the input of a gate to propagate to the output
 - High-to-low** (t_{phl}) and **low-to-high** (t_{plh}) output signal changes may have different propagation delays
 - $t_{pd} = \max \{t_{phl}, t_{plh}\}$



- Faster circuits are characterized by smaller propagation delays
- Higher performance systems require higher speeds, i.e. smaller propagation delays

Propagation Delay

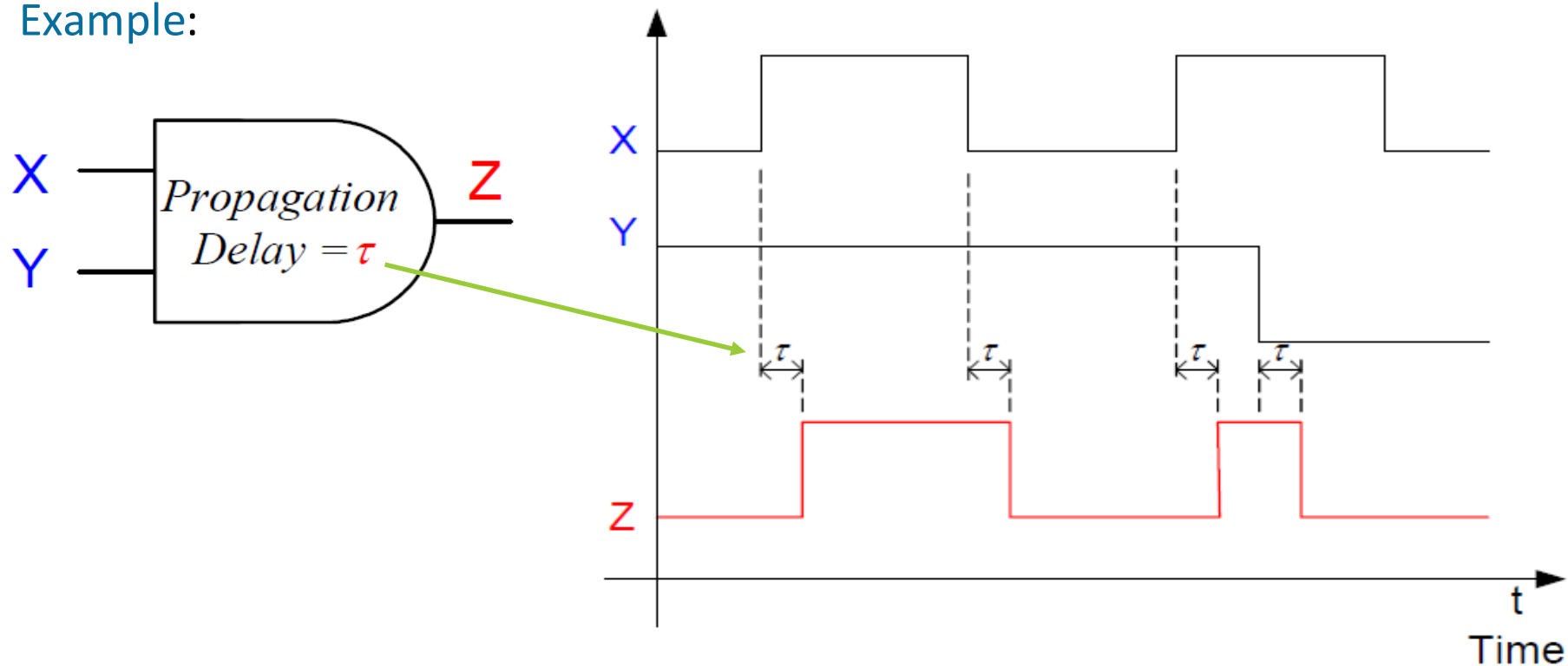- A timing diagram shows the logic values of signals in a circuit versus time.
- A signal shape versus time is typically referred to as **Waveform**.
- **Example:**




Computing Longest Delay

- Each gate has a given propagation delay
- We start at the inputs and compute the delay at the output of each gate as follows:
 - The delay at the output of a gate = gate propagation delay + maximum delay at its inputs
- Maximum propagation delay from any input to any output is called the **Critical Path**
- The critical path determines the minimum clock period (T) and the maximum clock frequency (f)
- Clock frequency $(f) = 1 / T$

Computing Longest Delay

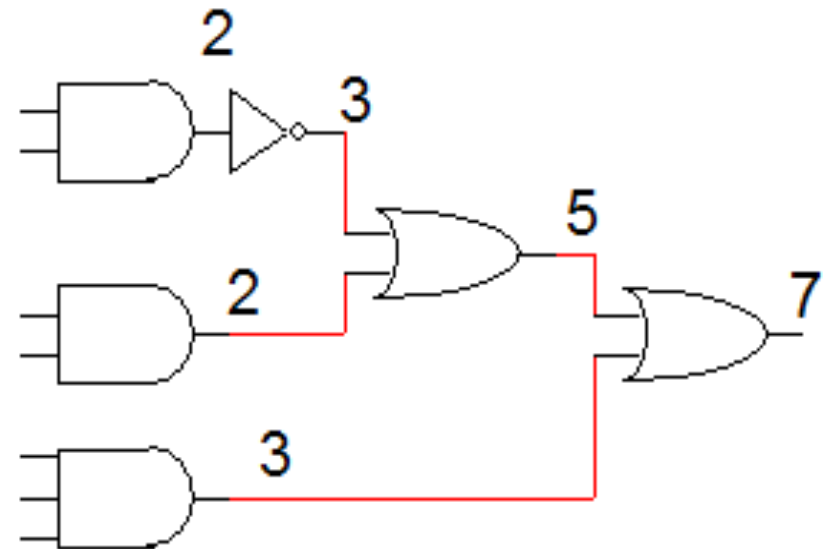
- **Example:** Assume that delay of each gate is related to number of its inputs i.e. delay of 1 input gate is 1 ns, delay of 2-input gate is 2 ns. Compute longest propagation delay and maximum frequency.



- Longest propagation delay = 7 ns
- Maximum frequency = $1 / 7\text{ns} = 143 \text{ MHz}$

Fanin

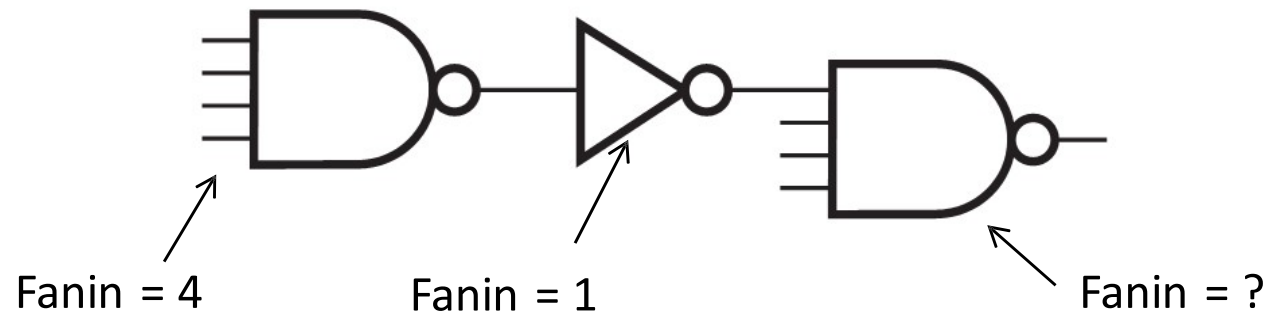- Fan in of a gate is the number of inputs to the gate
 - A 3-input OR gate has a fanin = 3
- There is a limitation on the fanin
- Larger fanin generally implies slower gates (higher propagation delays)



Fanout

- Fan out of a gate is the number of gates that it can drive
 - The driven gate is called a load
- Fan out is limited due to
 - Current in TTL
 - Propagation delays in CMOS

