

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 111 (Fall 2011)
Major Exam 2
Thursday December 8, 2011

Time: 120 minutes, Total Pages: 10

Name: Key **ID:** **Section:**

Notes:

- Do not open the exam book until instructed
- **Calculators are not allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	16	
2	20	
3	20	
4	34	
Total	90	

Question 1.**(points)**

I.


a. What are the conditions for a gate to be universal?

[1 Point]

Can implement Any Boolean expression without need for any other type gates. This is equivalent to ability to perform any of the following:

1. {AND, NOT}
2. {OR, NOT},
3. {AND, OR, NOT}

Show that a two input gate performing the function $f(A, B) = A'B$ is a universal gate.

 [3 Points]

1. Can Implement {NOT} $\rightarrow B=1, f = A'$
2. Can Implement {AND} \rightarrow Use two such gates; one acts as inverter generating A' and a 2nd with it's a-input = A' , B= B and, $f = AB$

II. Let $F(x, y, z) + G(x, y, z) = H(x, y, z)$, where F , G and H are Boolean functions of three variables x , y , and z . Given that

$$F(x, y, z) = x'z' + yz' \quad \text{and} \quad H(x, y, z) = z' + xy'$$

- a- Find a possible function $G(x, y, z)$ that will satisfy the above relation. [3 Points]
 b- Is the solution unique? If not, what is the number of possible $G(x, y, z)$ functions that can satisfy the above relation? [2 Points]

(Hint: Draw the K-maps of the functions above)

(Hint: Draw the K-maps of the functions above)

$$\begin{array}{c}
 z \\
 \swarrow \downarrow \\
 yz \\
 \begin{array}{c|c|c|c}
 & 00 & 01 & 11 & 10 \\
 \hline
 0 & 1 & 0 & 0 & 1 \\
 \hline
 1 & 0 & 0 & 0 & 1 \\
 \hline
 \end{array}
 \end{array}
 +
 \begin{array}{c|c|c|c}
 & a & b & c & d \\
 \hline
 & e & f & g & h \\
 \hline
 \end{array}
 =
 \begin{array}{c|c|c|c}
 & 1 & 0 & 0 & 1 \\
 \hline
 & 1 & 1 & 0 & 1 \\
 \hline
 \end{array}$$

• Since $F + G = H$, then

1) IF $H = 0$ then $F = 0$ & $G = 0$

2) IF $H = 1$ and $F = 0$ then

$$\boxed{G \text{ must be } 1} \Rightarrow b = c = 1$$

3) IF $H = 1$ and $F = 1$ Then

G can be either 0, or 1

$$\text{i.e. } \boxed{G = X = \text{Don't Care}}$$

$$\Rightarrow a = d = e = X$$

$$\begin{array}{c}
 z \\
 \swarrow \downarrow \\
 yz \\
 \begin{array}{c|c|c|c}
 & 00 & 01 & 11 & 10 \\
 \hline
 0 & X & & & X \\
 \hline
 1 & 1 & 1 & & X \\
 \hline
 \end{array}
 \end{array}$$



3-don't cares
 means 8-possible
 expressions for G will
 satisfy the above relation.

- III. Using the K-Map method, give a simplified SOP expression for the Boolean function $F(A, B, C, D) = \sum(0, 1, 4, 10, 14)$ subject to don't care conditions $d(A, B, C, D) = \sum(2, 5, 8, 15)$. [8 Points]
 <SHOW your WORK>

$$F(A, B, C, D) = A'C' + ACD'$$

		CD			
		00	01	11	10
AB	00	1	1		X
	01	1	X		
	11			X	1
	10	X			1

(20 Points)

Question 2.

Given a 4-bit unsigned number X ($x_3 x_2 x_1 x_0$), the function $F(X)$ is defined as:

$$F(X) = \begin{cases} X - 1, & X \text{ is odd} \\ \frac{X}{2}, & X \text{ is even} \end{cases}$$

You are to design a digital circuit that takes X as an input and produces $Z = F(X)$ as output;

- (a) How many bits are required to represent the output Z ? [2 points]

The maximum unsigned # representable in 4 bits is 15 which is an odd #
 $\Rightarrow F(15) = 14$ which is also representable in 4 bits
 \Rightarrow # of bits for Z is 4

- (b) Derive the truth table for the output function Z . [5 points]

X_3	X_2	X_1	X_0	Z_3	Z_2	Z_1	Z_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	1	0	0
1	0	0	1	0	1	0	0
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	0
1	1	0	1	0	1	1	0
1	1	1	0	0	1	1	1
1	1	1	1	0	1	1	0

- (c) If Z is to be implemented using only NAND gates, derive minimized expressions for the output bits of the circuit. [8 points]

Z_0

AB \ CD	00	01	11	10
00				1
01				1
11				1
10				1

$$Z_0 = A\bar{B}$$

AB \ CD	00	01	11	10
00			1	
01	1		1	1
11	1		1	1
10			1	

$$Z_1 = B\bar{D} + CB + CD$$





AB \ CD	00	01	11	10
00				
01				
11		1	1	
10		1	1	

$$Z_3 = AD$$

AB \ CD	00	01	11	10
00				
01		1	1	
11	1	1	1	1
10	1			1

$$Z_2 = AB + A\bar{D} + BD$$

- (d) Implement the output expressions obtained in (c) using NAND gates only [5 points]

    

Question 3.

(20 Points)

a. In each of the following problems, first represent the numbers in brackets in binary in the signed-2's complement notation using 5 bits then perform the indicated arithmetic operation using only binary addition. [8 points]

In each case check if you have obtained the correct results and indicate clearly if overflow occurred or not.

<p style="text-align: center;">Same sign → No overflow</p> $\begin{array}{r} (-6) \quad -00110 \\ +(-7) \quad + -00111 \\ \hline -13 \end{array}$ <p style="text-align: center;">-ive result = -01101 = -13 ✓</p>	<p style="text-align: center;">sign of result is different → overflow</p> $\begin{array}{r} (+5) \quad 00101 \\ -(-12) \quad -10100 \\ \hline +17 > 15 \end{array}$ <p style="text-align: center;">overflow</p>
<p style="text-align: center;">Same sign → No overflow</p> $\begin{array}{r} (+5) \quad 00101 \\ +(+9) \quad +01001 \\ \hline +14 \end{array}$ <p style="text-align: center;">01110 = +14 ✓</p>	<p style="text-align: center;">sign of result is different → overflow</p> $\begin{array}{r} (+6) \quad 00110 \\ -(+8) \quad -01000 \\ \hline -2 \end{array}$ <p style="text-align: center;">= -00010 = -2 ✓</p>

b. Interpret each of the following 5-bit binary numbers in the format indicated: [6 points]

Binary Number	Is equal to (in decimal)	When interpreted as:
11011	-11	Signed-magnitude
01101	+13	Signed-1's complement
10110	01010 -10	Signed-2's complement
11010	26	Unsigned

c. When doing signed-2's complement arithmetic in 6-bits: (Fill in the spaces with signed decimal values) [6 points]

- The range of numbers that can be represented extends from -32 to +31.
- The largest positive number that can be added to +13 without causing an overflow is +18.


$$31 - 13 = 18$$
- Overflow may occur when (circle all that applies):
 - i. Adding a positive number to a negative number
 - ii. Subtracting a negative number from a negative number
 - iii. Subtracting a negative number from a positive number

Question 1. Given the function

$$F(X,Y,Z) = \prod M(1,2,4,5,7)$$


a. Implement F using 2 2-to-4 decoders and any other gates you need

$$F(X,Y,Z) = \sum m(0,3,6)$$

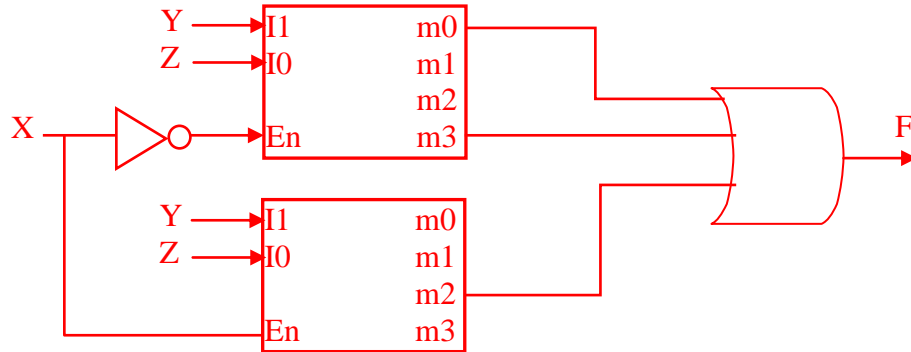

b. Implement F using the 4-to-1 MUX shown below (see steps for obtaining the solution)



X	Y	Z	F	F
0	0	0	1	Z'
0	0	1	0	
0	1	0	0	Z
0	1	1	1	
1	0	0	0	0
1	0	1	0	
1	1	0	1	Z'
1	1	1	0	

 

c. It is required to design a circuit that adds two **5-bit numbers**, A and B, that are represented in **signed-magnitude**. The result **O**, also 5-bits, should also be represented in signed-magnitude notation. **Ignore overflow. You can Design this circuit in anyway you like or follow the suggested sequence below.**

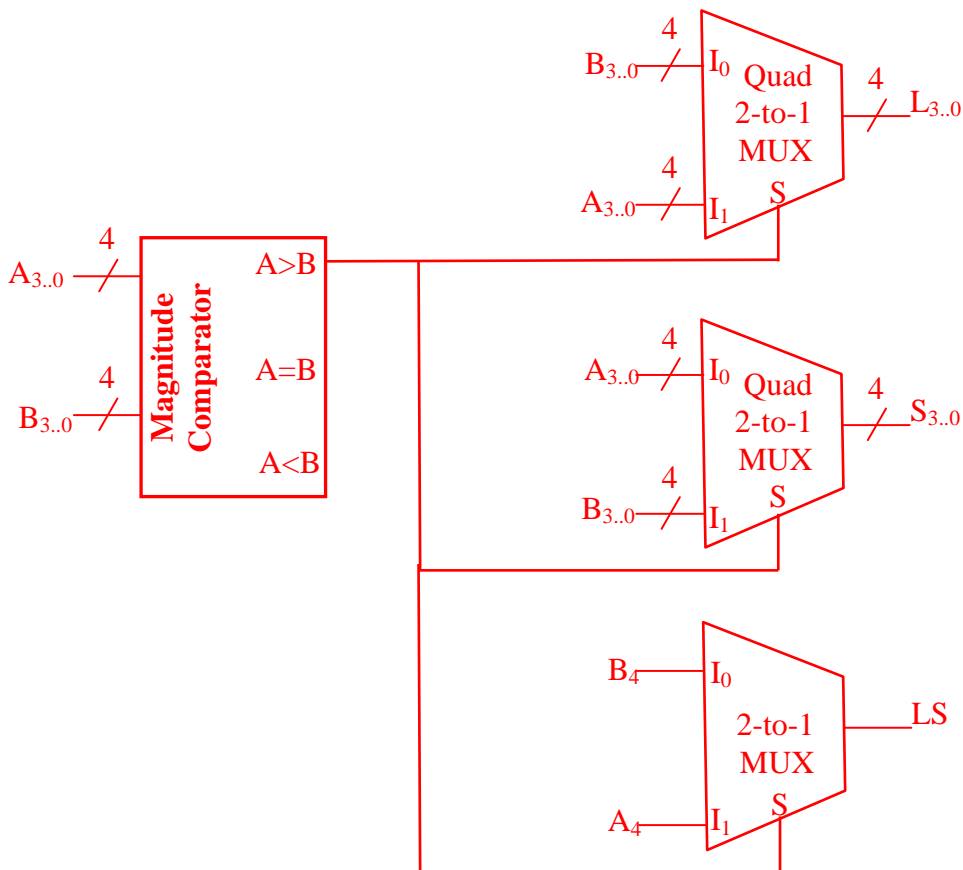 - (I) Using MSI parts, design a circuit that receives two 5-bit signed numbers A & B (represented in **signed-magnitude**) and produces three outputs **L**, **S** and **LS**, where:
- **L**: a 4-bit number which equals the larger *magnitude* of either A or B irrespective of their signs (e.g, A=-5 and B=+4 then L=5 but if A=-3 and B=+7 then L=7)
 - **S**: a 4-bit number which equals the smaller *magnitude* of either A or B irrespective of their signs (e.g, A=-5 and B=+4 then S=4 but if A=-3 and B=+7 then S=3)
 - **LS**: a single bit which equals the sign of larger magnitude number of either A or B (e.g, A=-5 and B=+4 then LS=1 or if A=-3 and B=+7 then LS=0).

Magnitude of A = $A_3A_2A_1A_0 = A_{3..0}$
 same with B ...
 Sign of A is A_4 ... same with B ...



(II) Using MSI parts, design a Signed-Magnitude Adder that will take as input **L**, **S**, **LS** (produced by the circuit in I above), **A** and **B**, and generates **A+B**

Hint: to add two signed-magnitude numbers **A** and **B** we can do the following:

1. If $\text{sign}(\mathbf{A}) = \text{Sign}(\mathbf{B}) \rightarrow$ then $\text{magnitude}(\mathbf{O}) = \text{magnitude}(\mathbf{A}) + \text{magnitude}(\mathbf{B})$, $\text{sign}(\mathbf{O}) = \text{Sign}(\mathbf{A})$
2. else (i.e. $\text{sign}(\mathbf{A}) \neq \text{Sign}(\mathbf{B})$) \rightarrow subtract the smaller number from the larger number $\text{magnitude}(\mathbf{O}) = \max[\text{magnitude}(\mathbf{A}), \text{magnitude}(\mathbf{B})] - \min[\text{magnitude}(\mathbf{A}), \text{magnitude}(\mathbf{B})]$, $\text{sign}(\mathbf{O}) = \text{Sign}$ of the number with the larger magnitude

Sign of output (O_4) is **LS**
 Magnitude is either $L+S$ (when signs are equal)
 or $L-S$ when signs are different
 The Adder/Subtractor performs $A+B$ if
 the Add/Sub input is 1 and $A-B$ otherwise

