

King Fahd University of Petroleum and Minerals
 College of Computer Sciences and Engineering
 Department of Computer Engineering


COE 202 – Digital Logic Design (T121)

Homework # 04 (due date & time: Saturday 17/11/2012 during class period)

*** Show all your work. No credit will be given if work is not shown! ***

Problem # 1 (20 points): The Full-Adder circuit is shown to the right. Given the following gate delays;

Gate/ Circuit	Propagation Delay
Inverter	1 τ
AND, OR	2 τ
XOR	4 τ

 

- (i) (5 points) What is the carry propagation delay per Full adder stage?
- (ii) (15 points) For an n -bit Ripple-Carry **Adder-Subtractor**, what is the total delay for the n^{th} sum bit and the $(n+1)^{\text{th}}$ carry-out bit?

Problem # 2 (20 points): Use a 4×16 non-inverted-output decoder and external gate(s) to implement the following function:

$$F(A, B, C, D) = \sum (1, 3, 5, 8, 10, 14)$$

Problem # 3 (20 points): Repeat problem # 3 but use a 4×16 inverted-output decoder and external gate(s).

Problem # 4 (20 points): Repeat problem # 3 but use a 16×1 **MUX** and external gate(s).

Problem # 5 (20 points): Repeat problem # 3 but use an 8×1 **MUX** and external gate(s). Connect C , A , and D to S_2 , S_1 , and S_0 , respectively.