

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Digital Logic Design (T161)

Homework # 03 (due date & time: Thursday 10/11/2016 during class period)

*** Show all your work. No credit will be given if work is not shown! ***

Problem 1 (15 points):

Consider the Boolean function $F(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 7, 10, 12, 13, 14, 15)$.

1. (9 points) Identify all the prime implicants and the essential prime implicants of F .
2. (3 points) Simplify the Boolean function F into a minimal sum-of-products expression.
3. (3 points) Simplify the Boolean function F into a minimal product-of-sums expression.

Problem 2 (20 points): Consider the Boolean function $F(A, B, C, D) = \sum m(0, 10, 15)$, together with the don't care conditions $d(A, B, C, D) = \sum m(1, 2, 4, 8, 11, 14)$.

1. (10 points) Simplify the Boolean function F together with the don't care conditions d , into minimal sum-of-products expression.
2. (5 points) Starting with the sum-of-products expression, implement the function using only **NAND** gates and **Inverters**.
3. (5 points) Starting with the sum-of-products expression, implement the function using only **NOR** gates and **Inverters**.

Problem 3 (30 points): Design an **all NAND** circuit that accepts two 2-bit unsigned numbers $A = A_1A_0$ and $B = B_1B_0$. The circuit produces $2 \times A$ when $A < B$, and produces A otherwise. Derive the simplified Boolean expressions of all outputs, and show the logic diagram implementation of the **all NAND** circuit.

Problem 4 (35 points):

(a) (10 points) If **6-bit registers** are used, show the binary number representation of the decimal numbers (+23), (-23), (+14), and (-14) using the following representation systems:

- i. Signed magnitude system
- ii. Signed 1's complement system
- iii. Signed 2's complement system

(b) (10 points) Provide the decimal equivalent of each of the following **signed 2's complement** numbers:

- i. 001101
- ii. 011011
- iii. 100101
- iv. 110011

(c) (15 points) If **6-bit registers** are used, perform the following **signed 2's complement** arithmetic operations on the provided signed 2's complement numbers. For each case, state whether the result is correct or an **overflow** has occurred.

- i. 001101 – 111101
- ii. 110011 – 011101
- iii. 101111 + 110011