

# EE 200- Digital Logic Circuit Design

## 1.9 Binary Logic

Dr. Muhammad Mahmoud

جامعة الملك فهد للبترول والمعادن  
King Fahd University of Petroleum & Minerals



September 12, 2013



# Entry Questions

- What is logic?
- What is **binary** logic?



# Objectives

- 1 Binary Logic
  - Basic Logic Operations
  - Logic Circuits
  - Logic Gates



# Introduction

- Binary logic deals with binary quantities which can take one of two values (0 & 1, True & False, ... etc).
- A binary number can be represented by a variable ( $x$ ,  $y$ ,  $z$ ,  $A$ ,  $B$ ,  $C$  ... etc).



# Basic Logic Operations

- AND:  $x \cdot y = z$  (or  $xy = z$ ), reads x **AND** y is equal to z.
- OR :  $x + y = z$ , reads x **OR** y is equal to z.
- NOT:  $x' = z$  (or  $\bar{x} = z$ ), reads **NOT** x is equal to z.



# Truth Tables

Example:

$$\text{AND } (xy = z) \begin{array}{c|c|c} x & y & z \\ \hline F & F & F \\ \hline F & T & F \\ \hline T & F & F \\ \hline T & T & T \end{array}$$
$$\text{OR } (x + y = z) \begin{array}{c|c|c} x & y & z \\ \hline F & F & F \\ \hline F & T & T \\ \hline T & F & T \\ \hline T & T & T \end{array}$$
$$\text{NOT } (\bar{x} = z) \begin{array}{c|c} x & z \\ \hline F & T \\ \hline T & F \end{array}$$



# Truth Tables

Example:

AND	x	y	z
	0	0	0
	0	1	0
	1	0	0
	1	1	1


OR	x	y	z
	0	0	0
	0	1	1
	1	0	1
	1	1	1

NOT	x	z
	0	1
	1	0



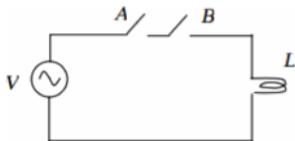
# Logic Circuits

- Binary logic can be demonstrated by switching circuits as follows:



$$L = A \cdot B$$

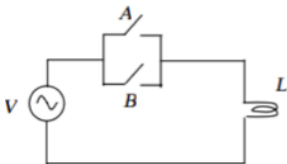

$$L = A + B$$





# Logic Voltage levels





# Binary Arithmetic vs. Binary Logic

- Binary Arithmetic:  $1+1=10$  (one plus one is equal to two).
- Binary Logic:  $1+1=1$  (one OR one is equal to one).



# Logic Gates


- Conventional symbols for logic gates.



2-input AND gate



2-input OR gate

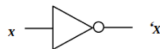


Inverter

- AND & OR** gates can have more than two inputs.


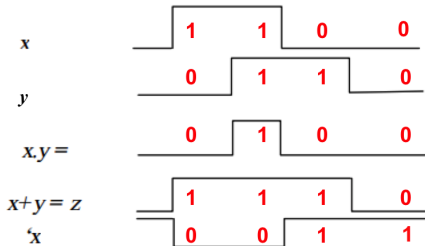
# Basic Logic Gates and Signal Waveforms

- Signals for logic gates may be represented in a signal waveform.





# Properties of Boolean Algebra

- |    |   |   |                  |
|----|---|---|------------------|
| 1. | $x + 0 = x$   | $x \cdot 1 = x$                             | Identity         |
| 2. | $x + x' = 1$  | $x \cdot x' = 0$                            | Complement       |
| 3. | $x + y = y + x$   | $x \cdot y = y \cdot x$                     | Commutative Law  |
| 4. | $x + (y + z) = (x + y) + z$   | $x \cdot (y \cdot z) = (x \cdot y) \cdot z$ | Associative Law  |
| 5. | $x + (y \cdot z) = (x + y) \cdot (x + z)$ $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$ |   | Distributive Law |



# Summary

- 1 Binary Logic
  - Basic Logic Operations
  - Logic Circuits
  - Logic Gates



# Next Lecture

- Boolean Algebra