

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 171 (Fall 2017)**  
**Major Exam 2**  
**Saturday, November 25th, 2017**

**Time: 120 minutes, Total Pages: 9**

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

<b>Question</b>	<b>Maximum Points</b>	<b>Your Points</b>
<b>1</b>	<b>15</b>	
<b>2</b>	<b>15</b>	
<b>3</b>	<b>15</b>	
<b>4</b>	<b>10</b>	
<b>5</b>	<b>20</b>	
<b>6</b>	<b>15</b>	
<b>7</b>	<b>10</b>	
<b>Total</b>	<b>100</b>	

**Question 1:**

[15 points]

Given the following two 8-bit binary numbers **A** and **B**:

$$A = 1010\ 0011$$

$$B = 1000\ 0010$$

- a) What are the decimal values of A and B if they are unsigned numbers? (2 pts)
- b) What are the decimal values of A and B if they are signed numbers in signed-magnitude? (2 pts)
- c) What are the decimal values of A and B if they are signed numbers in 2's complement? (2 pts)
- d) If A and B are signed numbers in 2's complement, Compute A + B and specify if there is an overflow (4 pts)
- e) If A and B are signed numbers in 2's complement, Compute A - B and specify if there is an overflow (5 pts)

**Question 2.** Let  $f(a, b, c, d) = \sum m(0, 2, 3, 4, 5, 8, 11, 12, 13, 14, 15)$

**[15 Points]**

a) Draw the Karnaugh map of the function  $f$ . **(2 points)**

b) Write the terms of ALL the prime Implicants and indicate which ones are Essential. **(7 points)**

c) Find ALL minimum sum-of-product expressions of  $f$  **(3 solutions)**. **(6 points)**

**Question 3.****[15 Points]**Given the following function  $g(a, b, c, d) = \sum m(0, 1, 6, 15)$ with the *don't care conditions*  $= \sum d(3, 5, 7, 11, 14)$ ,a) Find the minimal **Sum-of-Product** expressions of  $g$  (**1 Solution**).**(5 points)**b) Find the minimal **Product-of-Sum** expressions of the function  $g$  (**2 Solutions**).**(6 points)**c) Assuming that all inputs are available as true and complement, implement  $g$  using minimum number of the same gate type (**i.e. using only one type of gates**)**(4 points)**

**Question 4.**

**[10 Points]**

It is required to design a circuit that receives a BCD input  $N$  and compute two outputs;  $Q$  is the quotient  $= N/3$ , and  $R$  = remainder. e.g. if the input  $N=7$ , then  $Q=2$ , and  $R=1$ .

Determine the number of bits in  $N$ ,  $Q$ , and  $R$ , and draw the truth table for this circuit.

**Question 5. Label all your components, inputs, and outputs**

**[20 Points]**

1) Given the function  $F(A,B,C) = AB' + AC + A'B'C + A'BC'$  ,

Implement F using minimum number of 2-to-1 Multiplexors.

**(10 Points)**


2) Given the functions  $G(X,Y,Z) = \prod M(0, 2,3,5,7)$  , and  $H = \sum m(0,1,4,6,7)$

Implement **G** and **H** using minimum number of 2-to-4 Decoders and other gates with minimum sizes (i.e. number of inputs per gate).

**(10 Points)**

Question 6. For the logic diagram below:

[15 Points]

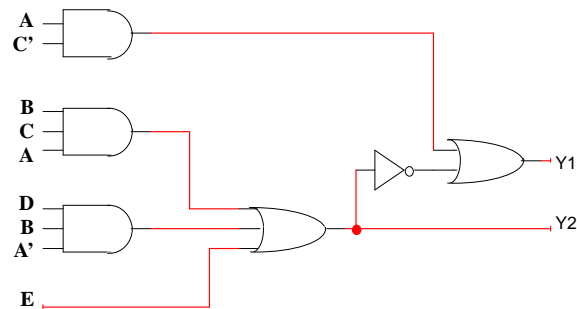

- Complete the Gate level Verilog description of this circuit using the Gate delays in the table below (6 Points)

Gate	Delay
NOT	1 ns
2-IP AND	2 ns
2-IP OR	3 ns
3-IP AND	3 ns
3-IP OR	4 ns

- Describe the same circuit again (including the delay) in Verilog, but using the *assign* statement. (4 Points)

- Convert it to NAND-only gates (using minimum number of NAND gates) (5 Points)

**Question 7.      Label all your components, inputs, and outputs****[10 Points]**

1. Using any standard functional block (Adders, Multiplexors, decoders ...etc.) design a circuit that compute the absolute difference between two unsigned 4-bit numbers A and B (If  $A \geq B$ ,  $\text{Diff}(A,B) = A - B$ , else  $\text{Diff}(A,B) = B - A$ ). **(4 Points)**

2. Now using your circuit above, and any other components, design an ALU that has two 4-bit data inputs A and B, two control bits C1 and C0, and performs the following functions: **(6 Points)**

**(for the bitwise ANDing and ORing of A and B, Y4 should be 0)**

<b>C1 C0</b>	<b>Functionality</b>
<b>0 0</b>	<b><math>Y \leftarrow A \&amp; B</math> (Y= bitwise ANDing of A and B)</b>
<b>0 1</b>	<b><math>Y \leftarrow A   B</math> (Y= bitwise ORing of A and B)</b>
<b>1 0</b>	<b><math>Y \leftarrow A + B</math> (Y= SUM of A and B)</b>
<b>1 1</b>	<b><math>Y \leftarrow \text{Diff}(A,B)</math> (Y= the absolute difference between A and B, i.e. <math> A-B </math>)</b>