

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 171 (Fall 2017)
Major Exam 2
Saturday, November 25th, 2017

Time: 120 minutes, Total Pages: 9

Name: _____ **ID:** _____ **Section:** _____

Notes:

Do not open the exam book until instructed


Calculators are not allowed (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	15	
2	15	
3	15	
4	10	
5	20	
6	15	
7	10	
Total	100	

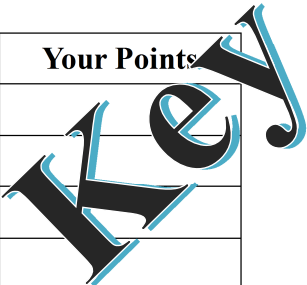

[15 points]

Question 1:Given the following two 8-bit binary numbers **A** and **B**:

$$A = 1010\ 0011 \quad B = 1000\ 0010$$

a) What are the decimal values of A and B if they are unsigned numbers? (2 pts)

$$A = (1010\ 0011)_{\text{unsigned}} = 128+32+2+1 = 163$$

$$B = (1000\ 0010)_{\text{unsigned}} = 128+2 = 130$$

b) What are the decimal values of A and B if they are signed numbers in signed-magnitude? (2 pts)

$$A = 1010\ 0011 = -(32+2+1) = -35$$

$$B = 1000\ 0010 = -2$$

c) What are the decimal values of A and B if they are signed numbers in 2's complement? (2 pts)

$$A = 1010\ 0011 = -128+32+2+1 = -93$$

$$B = 1000\ 0010 = -128+2 = -126$$

d) If A and B are signed numbers in 2's complement, Compute A + B and specify if there is an overflow (4 pts)
$$\begin{array}{r} 1 \quad 1 \\ A = 1010\ 0011 \\ + B = 1000\ 0010 \\ \hline 0010\ 0101 \end{array}$$

Overflow? Yes

e) If A and B are signed numbers in 2's complement, Compute A - B and specify if there is an overflow (5 pts)d) $A - B = A + (2\text{'s complement of } B)$

Carry 1 1111 11

$$A = 1010\ 0011$$

$$+ (2\text{'s complement of } B) = 0111\ 1110$$

$$\hline 0010\ 0001$$

Overflow? No

Question 2. Let $f(a, b, c, d) = \sum m(0, 2, 3, 4, 5, 8, 11, 12, 13, 14, 15)$

[15 Points]

a) Draw the Karnaugh map of the function f.

(2 points)

a b \ c d	0 0	0 1	1 1	1 0
0 0	1		1	1
0 1	1	1		
1 1	1	1	1	1
1 0	1		1	

b) Write the terms of ALL the prime Implicants and indicate which ones are Essential. (7 points)

There are Seven Prime Implicants: $ab, c'd', bc', a'b'c, a'b'd', acd, b'cd$

Only three prime implicants are Essential: $ab, c'd', bc'$

c) Find ALL minimum sum-of-product expressions of f (**3 solutions**).

(6 points)

$$f = ab + c'd' + bc' + \underline{a'b'c} + \underline{acd} \text{ (Solution 1)}$$

$$f = ab + c'd' + bc' + \underline{a'b'c} + \underline{b'cd} \text{ (Solution 2)}$$

$$f = ab + c'd' + bc' + \underline{a'b'd'} + \underline{b'cd} \text{ (Solution 3)}$$

[15 Points]

Question 3.

Given the following function $g(a, b, c, d) = \sum m(0, 1, 6, 15)$
with the *don't care conditions* = $\sum d(3, 5, 7, 11, 14)$,

a) Find the minimal **Sum-of-Product** expressions of g (**1 Solution**).

(5 points)

a b \ c d	0 0	0 1	1 1	1 0
0 0	1	1	x	
0 1		x	x	1
1 1			1	x
1 0			x	

Minimal SOP expression: $g = a' b' c' + b c$ (minimum terms \rightarrow minimum # of NAND gates)

b) Find the minimal **Product-of-Sum** expressions of the function g (**2 Solutions**).

(6 points)

a b \ c d	0 0	0 1	1 1	1 0
0 0			x	1
0 1	1	x	x	
1 1	1	1		x
1 0	1	1	x	1


Minimal POS expressions of g :

$g' = b c' + b' c + a b' \rightarrow g = (b' + c)(b + c')(a' + b)$ (Solution 1)

$g' = b c' + b' c + a c' \rightarrow g = (b' + c)(b + c')(a' + c)$ (Solution 2)

c) Assuming that all inputs are available as true and complement, implement g using minimum number of the same gate type (**i.e. using only one type of gates**)

(4 points)

 

Question 4.**[10 Points]**

It is required to design a circuit that receives a BCD input N and compute two outputs; Q is the quotient $= N/3$, and R = remainder. e.g. if the input $N=7$, then $Q=2$, and $R=1$.

Determine the number of bits in N , Q , and R , and draw the truth table for this circuit.

Solution: N is 4-bits, Q max value is 3 \rightarrow 2 bits, R max value is also 2 \rightarrow 2 bits

Truth Table

Input N $N_3 N_2 N_1 N_0$	Output Q $Q_1 Q_0$	Output R $R_1 R_0$
0 0 0 0	0 0	0 0
0 0 0 1	0 0	0 1
0 0 1 0	0 0	1 0
0 0 1 1	0 1	0 0
0 1 0 0	0 1	0 1
0 1 0 1	0 1	1 0
0 1 1 0	1 0	0 0
0 1 1 1	1 0	0 1
1 0 0 0	1 0	1 0
1 0 0 1	1 1	0 0
1 0 1 0	x x	x x
1 0 1 1	x x	x x
1 1 0 0	x x	x x
1 1 0 1	x x	x x
1 1 1 0	x x	x x
1 1 1 1	x x	x x


Question 5. Label all your components, inputs, and outputs

[20 Points]

1) Given the function $F(A,B,C) = AB' + AC + A'B'C + A'BC'$,

Implement F using minimum number of 2-to-1 Multiplexors.

(10 Points)

 

2) Given the functions $G(X,Y,Z) = \prod M(0, 2,3,5,7)$, and $H = \sum m(0,1,4,6,7)$


Implement G and H using minimum number of 2-to-4 Decoders and other gates with minimum sizes (i.e. number of inputs per gate).

(10 Points)


We need to construct a 3-to-8 decoder from two 2-to-4 decoders and an inverter.

Since G has only 3 minterms (1,4,6) we will use a decoder + OR design,

Since H has only 3 Maxterms (2,3,5) we will use a decoder + NOR design:

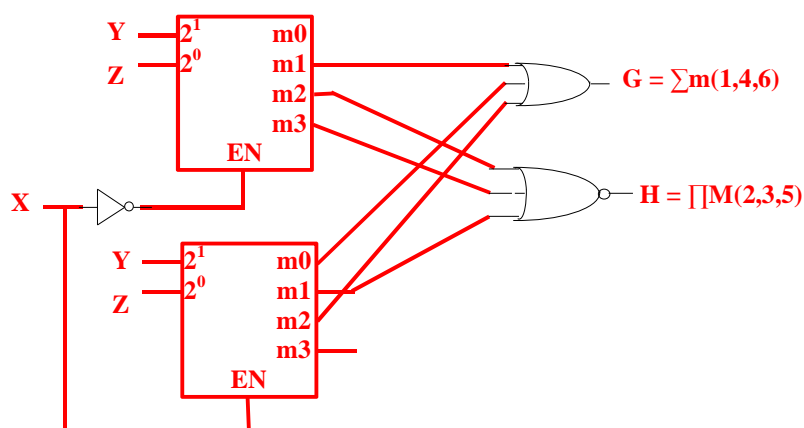

Question 6. For the logic diagram below:

 

1. Complete the Gate level Verilog description of this circuit using the Gate delays in the table below (6 Points)

```

module Y1_Y2 (input A,B,C,D,E, output Y1,Y2);
wire n1,n2,n3,A_b,C_b,Y2_b ;
not #1 (A_b,A) ; not #1 (C_b,C) ; and #2 (n1,A_b,C) ;
and #3 (n2,B,C,A) ; and #3 (n3,D,B,A_b) ;
not # 1 (Y2_b,Y2) ; or #3 (Y1,n1,Y2_b) ; or #4 (Y2,n2,n3,E) ;
endmodule
    
```


Gate	Delay
NOT	1 ns
2-IPAND	2 ns
2-IP OR	3 ns
3-IPAND	3 ns
3-IP OR	4 ns

2. Describe the same circuit again (including the delay) in Verilog, but using the assign statement. (4 Points)

```

module Y1_Y2 (input A,B,C,D,E, output Y1,Y2);
assign #8 Y2 = E | ~A & B & D | A & B & C ;
assign #12 Y1 = ~( E | ~A & B & D | A & B & C ) | A & ~C ; // if Y1 is defined as a
endmodule // function of Y2, the delay would be wrong!
    
```

3. Convert it to NAND-only gates (using minimum number of NAND gates) (5 Points)

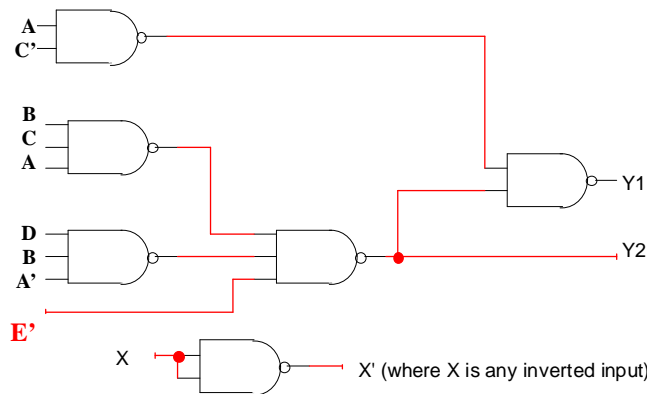


Question 7. Label all your components, inputs, and outputs


[10 Points]

1. Using any standard functional block (Adders, Multiplexors, decoders ...etc.) design a circuit that compute the absolute difference between two unsigned 4-bit numbers A and B (If $A \geq B$, $\text{Diff}(A,B) = A - B$, else $\text{Diff}(A,B) = B - A$). **(4 Points)**

SOLUTION 1

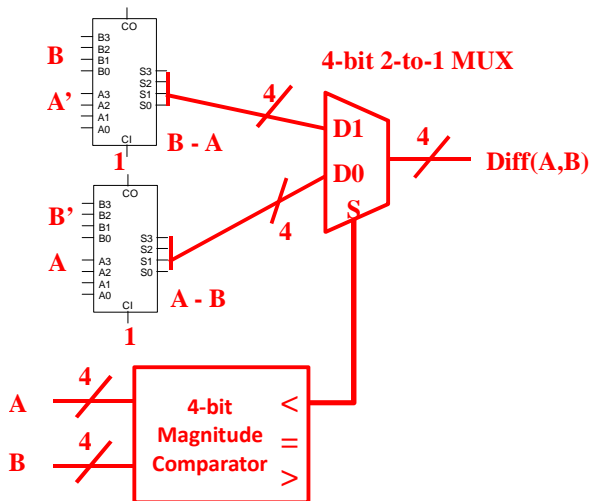

SOLUTION 2

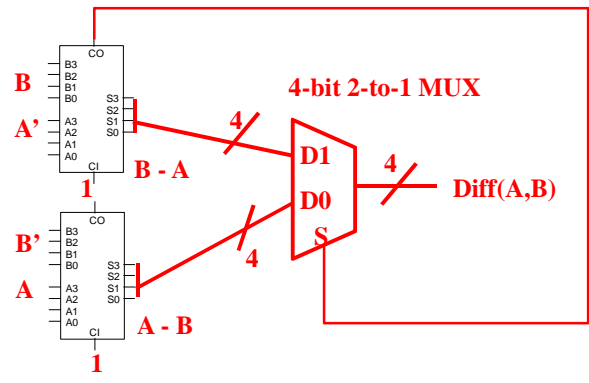

The CO (output carry) of (B - A) is 1 when $(B - A \geq 0)$ and 0 otherwise. It is used as the select input of the mux. It works only when A and B are unsigned.

2. Now using your circuit above, and any other components, design an ALU that has two 4-bit data inputs A and B, two control bits C1 and C0, and performs the following functions: **(6 Points)**

(for the bitwise ANDing and ORing of A and B, Y4 should be 0)

C1 C0	Functionality
0 0	$Y \leftarrow A \& B$ (Y= bitwise ANDing of A and B)
0 1	$Y \leftarrow A B$ (Y= bitwise ORing of A and B)
1 0	$Y \leftarrow A + B$ (Y= SUM of A and B)
1 1	$Y \leftarrow \text{Diff}(A,B)$ (Y= the absolute difference between A and B, i.e. $ A-B $)

