

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 181 (Fall 2018)**  
**Major Exam 2**  
**Saturday, November 11th, 2018**

**Time: 120 minutes, Total Pages: 9**

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

Clearly label all inputs and outputs of any circuit component

<b>Question</b>	<b>Maximum Marks</b>	<b>Your Marks</b>
<b>1</b>	<b>18</b>	
<b>2</b>	<b>19</b>	
<b>3</b>	<b>20</b>	
<b>4</b>	<b>13</b>	
<b>Total</b>	<b>70</b>	

(18 Marks)

**Question 1.**

a) Consider the following Boolean function and its don't care conditions:

$$F(A, B, C, D) = \prod M(3,11,12,13) + \sum d(2,6,10,14)$$

Represent F on a K-map along with its don't care conditions.

(4 Marks)

b) The K-map below represents a function G(X,Y,Z,W):

		ZW			
		00	01	11	10
XY	00	1	1	0	1
	01	1	X	X	1
	11	0	X	X	0
	10	1	1	0	0

1. List all the **prime implicants** and **essential prime implicants** of G.

(4 Marks)

2. Minimize G to a minimal SOP expression

**(2 Marks)**

3. Minimize G to a minimal POS expression

**(4 Marks)**

c) Let  $F = A'(B' + C')(A+C)$  Implement F using minimum number of NOR gates **only**. **(4 Marks)**

**Question 2:****(19 Marks)**

It is required to design a circuit that receives a **3-bit signed** number in **signed-magnitude** representation, **X**, and computes the equation  $Y = 3 * X - 2$  where **Y** is also **represented in signed-magnitude** representation.

a. Determine the number of bits needed for the output Y. Justify your answer. **(2 Marks)**


b. Fill the table below with the truth table for the output Y. **(5 Marks)**

<b>X2 X1 X0</b>	<b>Decimal Value of Y</b>	<b>Output Y</b>

c. If the output of the circuit Y is fed as input to another circuit that will compute the equation:  $Z = Y^2$ , what will be the don't care conditions for Z. **(2 Marks)**

- d. Implement the following two functions using a **decoder** and **additional gates**, each with the **smallest possible Fan-in (i.e. number of inputs)**. Clearly mark all inputs and outputs of the **decoder**.  $F1(A,B,C) = \sum m(0,4,5,6,7)$        $F2(A,B,C) = \sum m(4,5,7)$       **(5 Marks)**

- e. Convert the circuit below to **2-input NAND gates only**. Redraw the circuit to obtain a multi-level NAND circuit implementation. Assume that **both the true and complement** forms of each input variable are available. **Use the circuit as is and do not attempt to simplify it.** (5 Marks)

 



**Question 3.****(20 Marks)**

- a) Represent the given signed numbers using **8-bit** signed binary numbers in the specified representations in the table below: **(6 Marks)**

<b>Decimal Value</b>	<b>Sign-Magnitude representation</b>	<b>1's complement representation</b>	<b>2's complement representation</b>
<b>-34</b>			
<b>-67</b>			

- b) **A** and **B** below are 8-bit signed integers represented in the 2's complement representation:

$$\mathbf{A = 11011000 \quad B = 01110101}$$

1. What are the decimal values of **A** and **B**? **(2 Marks)**

2. Compute  $A + B$  in binary and indicate whether there is overflow or not. **(3 Marks)**

3. Compute  $A - B$  by converting subtraction into binary addition. Indicate whether there is overflow or not. Show all the steps. **(3 Marks)**

c) Suppose that  $X$ ,  $Y$ , and  $Z$  are 4-bit unsigned integers. Let  $S = X+Y+Z$  be the unsigned sum.


1. What is the number of bits required to represent the output  $S$ ? **(1 Mark)**

2. Draw a circuit that computes  $S = X+Y+Z$  using only full adders and half adders. **(5 Marks)**



 **Question 4**

Consider the following implementation of a full-adder circuit:



- a) Write a **gate-level** Verilog description of the above full adder using the Inputs, Outputs, and wire names and gate delays shown on the diagram above. **(5 Marks)**
- b) Write another Verilog description of the full adder, with delay modeling, using a **single assign statement per output (i.e. two assign statements)**. **(3 Marks)**
- c) Using the full adder in (a) above, write a testbench to test a **2-bit adder** (i.e. uses two of the full adder in (a)) to add two 2-bit numbers **A** and **B** with a carry in **Ci**, and produces a 2-bit Sum **S** and carry out **Co**. The testbench should test the 2-bit adder for the following input values (with 10 time units delay in-between the two input patterns): **(5 Marks)**
- A = 00, B = 00, Cin = 0**, and the second input is **A = 10, B = 01, Cin = 1**.