

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 181 (Fall 2018)**  
**Major Exam 2**  
**Saturday, November 11th, 2018**

**Time: 120 minutes, Total Pages: 9**

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

Clearly label all inputs and outputs of any circuit component

<b>Question</b>	<b>Maximum Marks</b>	<b>Your Marks</b>
<b>1</b>	<b>18</b>	
<b>2</b>	<b>19</b>	
<b>3</b>	<b>20</b>	
<b>4</b>	<b>13</b>	
<b>Total</b>	<b>70</b>	

(18 Marks)

**Question 1.**

a) Consider the following Boolean function and its don't care conditions:

$$F(A, B, C, D) = \prod M(3,11,12,13) + \sum d(2,6,10,14)$$

Represent F on a K-map along with its don't care conditions.

(4 Marks)

CD \ AB	00	01	11	10
00	1	1	0	X
01	1	1	1	X
11	0	0	1	X
10	1	1	0	X

b) The K-map below represents a function G(X,Y,Z,W):

ZW \ XY	00	01	11	10
00	1	1	0	1
01	1	X	X	1
11	0	X	X	0
10	1	1	0	0

1. List all the **prime implicants** and **essential prime implicants** of G. (4 Marks)

PIs:  $X'Z'$ ,  $X'Y$ ,  $Z'W$ ,  $Y'Z'$ ,  $X'W'$       EPIs:  $Y'Z'$  and  $X'W'$

**Note that  $Z'W$  is not EPI because only the don't care is not in any other PI – Don't cares do not have to be covered so they don't make an EPI!**

2. Minimize G to a minimal SOP expression (2 Marks)

**$G = Y'Z' + X'W'$**

3. Minimize G to a minimal POS expression


(4 Marks)

$$G = (Z' + W')(X' + Y')(X' + Z')$$


ZW \ XY	00	01	11	10
00	1	1	0	1
01	1	X	X	1
11	0	X	X	0
10	1	1	0	0

c) Let  $F = A'(B' + C')(A + C)$  Implement F using minimum number of NOR gates **only**. (4 Marks)

 **F is actually = m1 =  $A'B'C = (A + B + C')$**



**Another solution (you lose 1 mark!)**

 

**Question 2:****(18 Marks)**

It is required to design a circuit that receives a **3-bit signed** number in **signed-magnitude** representation, **X**, and computes the equation  $Y = 3*X - 2$  where **Y** is also **represented in signed-magnitude** representation.

- a. Determine the number of bits needed for the output Y. Justify your answer. **(2 Marks)**

The smallest negative value is -3. Thus,  $3 * -3 - 2 = -11$ . This implies that we need **5 bits** to represent the output correctly (1-bit for the sign, and 4-bits for the magnitude).

- b. Fill the table below with the truth table for the output Y. **(5 Marks)**

<b>X2 X1 X0</b>	<b>Decimal Value of Y</b>	<b>Output Y: Y4 Y3 Y2 Y1 Y0</b>
0 0 0	-2	1 0 0 1 0
0 0 1	+1	0 0 0 0 1
0 1 0	+4	0 0 1 0 0
0 1 1	+7	0 0 1 1 1
1 0 0	-2	1 0 0 1 0
1 0 1	-5	1 0 1 0 1
1 1 0	-8	1 1 0 0 0
1 1 1	-11	1 1 0 1 1


- c. If the output of the circuit Y is fed as input to another circuit that will compute the equation:  $Z = Y^2$ , what will be the don't care conditions for Z. **(2 Marks)**

The don't care conditions include all the values that do not occur at the output of Y, i.e. 0, +2, +3, +5, +6, +8 to +15, -1, -3, -4, -6, -7, -9, -10, -12, -13, -15, -16


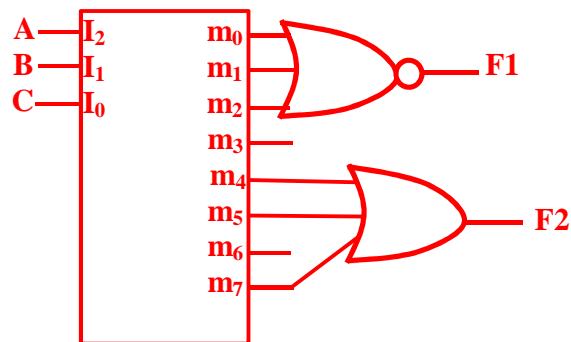
- d. Implement the following two functions using a decoder and additional gates, each with the smallest possible Fan-in (i.e. number of inputs). Clearly mark all inputs and outputs of the decoder.  $F1(A,B,C) = \sum m(0,4,5,6,7)$   $F2(A,B,C) = \sum m(4,5,7)$  (5 Marks)

$F1(A,B,C) = \sum m(0,4,5,6,7) = \prod M(1,2,3) \rightarrow$  it is better to implement it as POM  
 3 I/Ps  $\rightarrow$  3-to-8 decoder & a 3-I/Ps NOR Gate

$F2(A,B,C) = \sum m(4,5,7) = \prod M(0,1,2,3,6) \rightarrow$  it is better to implement it as SOM  
 3 I/Ps  $\rightarrow$  3-to-8 decoder & a 3-I/Ps OR Gate



- e. Convert the circuit below to 2-input NAND gates only. Redraw the circuit to obtain a multi-level NAND circuit implementation. Assume that both the true and complement forms of each input variable are available. Use the circuit as is and do not attempt to simplify it. (5 Marks)

  

**Question 3.****(20 Marks)**

- a) Represent the given signed numbers using **8-bit** signed binary numbers in the specified representations in the table below: **(6 Marks)**

Decimal Value	Sign-Magnitude representation	1's complement representation	2's complement representation
-34	<b>1 010 0010</b>	<b>1101 1101</b>	<b>1101 1110</b>
-67	<b>1 100 0011</b>	<b>1011 1100</b>	<b>1011 1101</b>

- b) **A** and **B** below are 8-bit signed integers represented in the 2's complement representation:

$$A = 11011000 \quad B = 01110101$$

1. What are the decimal values of A and B? **(2 Marks)**

$$\text{Decimal Value of A} = -128 + 64 + 16 + 8 = -40$$

$$\text{Decimal Value of B} = 64 + 32 + 16 + 4 + 1 = +117$$

2. Compute A + B in binary and indicate whether there is overflow or not. **(3 Marks)**

$$\begin{array}{r}
 1\ 1\ 1\ 1 \\
 1\ 1\ 0\ 1\ 1\ 0\ 0\ 0 \\
 +\ 0\ 1\ 1\ 1\ 0\ 1\ 0\ 1 \\
 \hline
 0\ 1\ 0\ 0\ 1\ 1\ 0\ 1
 \end{array}$$

**There is NO overflow because  $C_7$  and  $C_8$  are identical. Last carry is ignored.**

**The result = +77**

3. Compute A - B by converting subtraction into binary addition. Indicate whether there is overflow or not. Show all the steps. **(3 Marks)**

$$A - B = A + (2\text{'s complement of } B) = A + (1\text{'s complement of } B) + 1$$

$$\begin{array}{r}
 1\ 1\ 1\ 1 \\
 1\ 1\ 0\ 1\ 1\ 0\ 0\ 0 \\
 +\ 1\ 0\ 0\ 0\ 1\ 0\ 1\ 0 \\
 \hline
 0\ 1\ 1\ 0\ 0\ 0\ 1\ 1
 \end{array}$$

**Yes, there is overflow because  $C_7$  and  $C_8$  are different. The result is positive, while it is supposed to be negative. The exact result -157 cannot be represented using 8 bits only.**


c) Suppose that  $X$ ,  $Y$ , and  $Z$  are 4-bit unsigned integers. Let  $S = X+Y+Z$  be the unsigned sum.

1. What is the number of bits required to represent the output  $S$ ? (1 Mark)


**S should have 6 bits to represent the largest sum:  $15+15+15 = 45$  in binary**

2. Draw a circuit that computes  $S = X+Y+Z$  using only full adders and half adders. (5 Marks)

**Solution:**

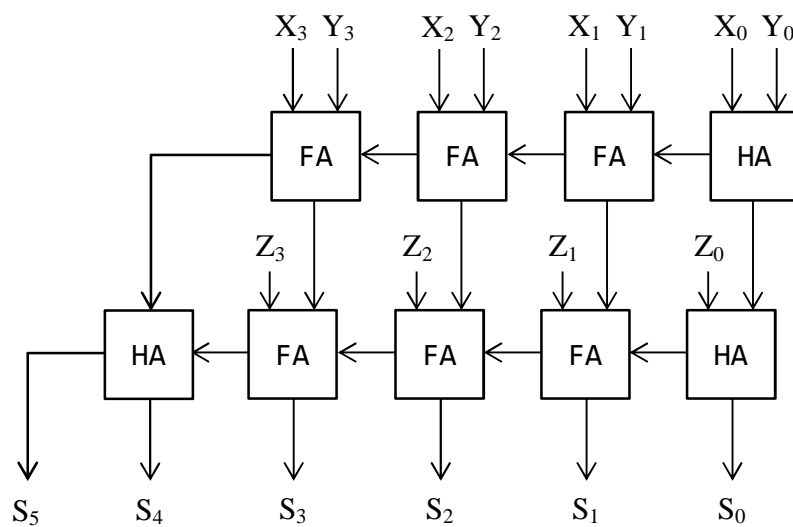


**Better Solution:**

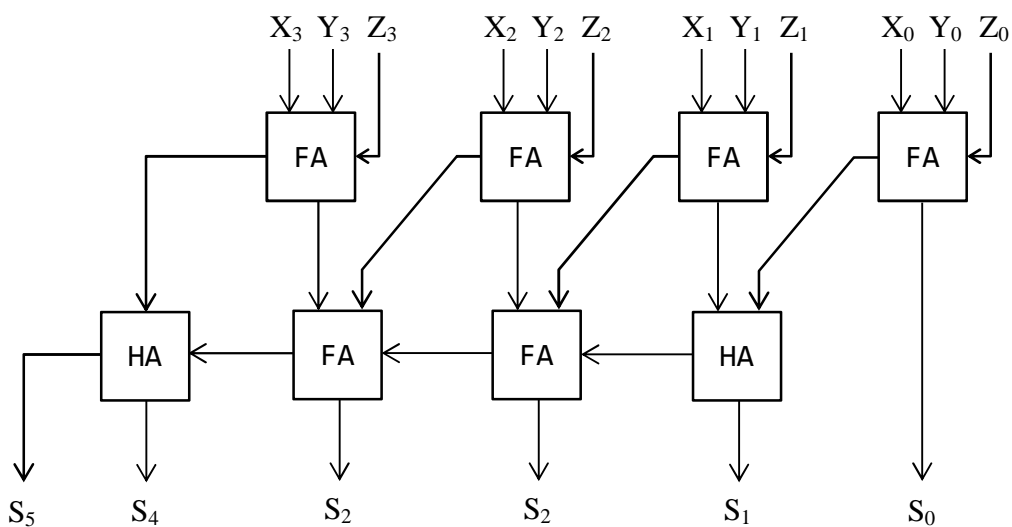

 **Question 4****(13 Marks)**

Consider the following implementation of a full-adder circuit:



- a) Write a **gate-level** Verilog description of the above full adder using the Inputs, Outputs, and wire names and gate delays shown on the diagram above. **(5 Marks)**

```

module full_adder(output S, Cout, input A, B, Cin);
    wire P, X, G;

    xor    #3 (P, A, B);           // or assign #3 P = A^B
    xor    #3 (S, P, Cin);         // or assign #3 S = P^Cin
    and    #2 (X, P, Cin);         // or assign #2 X = P & Cin
    and    #2 (G, A, B);          // or assign #2 G = A & B
    or     #2 (Cout, X, G);       // or assign #3 Cout = X | G

endmodule

```

- b) Write another Verilog description of the full adder, with delay modeling, using a **single assign statement per output** (i.e. two assign statements). **(3 Marks)**

```

module full_adder(output S, Cout, input A, B, Cin);

    assign #6 S = A^B^Cin ;
    assign #7 Cout = (A^B)& Cin | A & B;

endmodule

```

if someone does assign #6 {Cout,S} = A + B + Cin ; he loses 1 mark for wrong delay modeling of Ci and even if he uses #7

- c) Using the full adder in (a) above, write a testbench to test a **2-bit adder** (i.e. uses two of the full adder in (a)) to add two 2-bit numbers **A** and **B** with a carry in **Ci**, and produces a 2-bit Sum **S** and carry out **Co**.



The testbench should test the 2-bit adder for the following input values (with 10 time units delay in-between the two input patterns):

(5 Marks)

**A = 00, B = 00, Cin = 0, and the second input is A = 10, B = 01, Cin = 1.**

```

module tb;

    reg [1:0] A, B;
    reg Ci;
    wire [1:0] S, Co;

    full_adder fa1(S[0], Co[0], A[0], B[0], Ci);
    full_adder fa2(S[1], Co[1], A[0], B[0], Co[0]);

    initial begin
        A[0]= 0 ; A[1]= 0 ;
        B[0]= 0 ; B[1]= 0 ;
        Ci= 0 ;
        #10 A[0]= 0 ; A[1]= 1 ;
        B[0]= 1 ; B[1]= 0 ;
        Ci= 1 ;
    end

endmodule

```

OR

```

module tb;

    reg A1,A0, B1,B0;
    reg Ci;
    wire S1, S0, Co0, Co1;

    full_adder fa1(S0, Co0, A0, B0, Ci);
    full_adder fa2(S1, Co1, A1, B1, Co0);

    initial begin
        A0= 0 ; A1= 0 ;
        B0= 0 ; B1= 0 ;
        Ci= 0 ;
        #10 A0= 0 ; A1= 1 ;
        B0= 1 ; B1= 0 ;
        Ci= 1 ;
    end

endmodule

```