

**King Fahd University of Petroleum and Minerals**  
**College of Computer Science and Engineering**  
**Computer Engineering Department**

**COE 202: Digital Logic Design (3-0-3)**  
**Term 161 (Fall 2016)**  
**Final Exam**  
**Wednesday, December 11, 2017**

**Time: 120 minutes, Total Pages: 14**

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**

Do not open the exam book until instructed

**Calculators are not allowed** (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown


Any assumptions made must be clearly stated

<b>Question</b>	<b>Maximum Points</b>	<b>Your Points</b>
<b>1</b>	<b>16</b>	
<b>2</b>	<b>7</b>	
<b>3</b>	<b>6</b>	
<b>4</b>	<b>15</b>	
<b>5</b>	<b>9</b>	
<b>6</b>	<b>6</b>	
<b>7</b>	<b>6</b>	
<b>8</b>	<b>15</b>	
<b>9</b>	<b>10</b>	
<b>Total</b>	<b>90</b>	

**Question 1: Fill in the Spaces: (Show all work needed to obtain your answer) (16 points)**


1. A high value to the two R and S inputs of the NAND-gate latch will \_\_\_\_\_ (Change/No Change) the state/output of the latch. **(1 point)**
2. Asynchronous reset to a flip flop doesn't depend on the clock input \_\_\_\_\_ (True/False). **(1 point)**
3. Given a synchronous sequential circuit with 9 states, the minimum number of flip flops required to implement the circuit is \_\_\_\_\_ flip flops and the number of unused states is \_\_\_\_\_ states. **(2 points)**

 4. The following circuit shows a parallel load binary counter, the range of the counter is \_\_\_\_\_ to \_\_\_\_\_. **(2 points)**




5. The below figure shows connections to the *D* input of stage *i* in a multi-function register of D-type flip flops. Study the circuit and fill in the missing information in the table below (empty slots) **only for supported register functions.** **(2 points)**


$S_1 S_0$	Register Function (where applicable)
	Shift right
	Clear register
	No change in output
	Load Data input

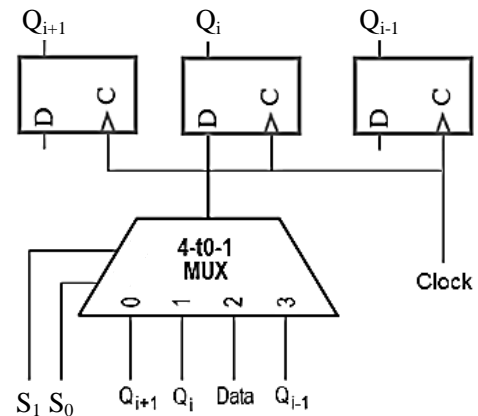

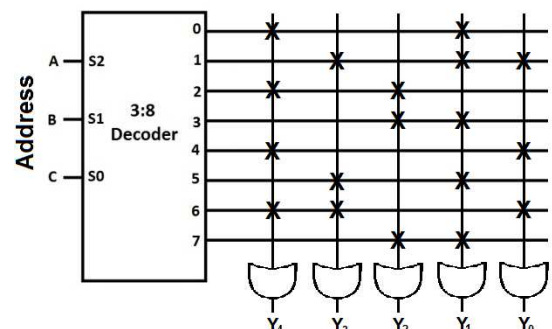6. In the ROM circuit shown, **X** indicates a connection. At address  $ABC = 110$ , the ROM stores the data  $Y_4 Y_3 Y_2 Y_1 Y_0 =$  \_\_\_\_\_. **(1 point)**



 7. For a 4-bit synchronous binary counter (outputs  $Q_3$ ,  $Q_2$ ,  $Q_1$  and  $Q_0$ ), with input clock frequency of 48 MHz, the frequency of  $Q_1$  is \_\_\_\_\_ MHz and the frequency of  $Q_3$  is \_\_\_\_\_ MHz. **(2 points)**
8. Two RS level sensitive latches and one inverter are used to make an edge triggered flip flop which can be used to store up to two bits \_\_\_\_\_ (True/False). **(1 point)**
9. Consider the below 4-bit register. If the initial register contents (Q outputs)  $ABCD$  are  $0111$  and the serial input is kept at 1, show the contents  $ABCD =$  \_\_\_\_\_ of the register after two clock pulses. **(2 points)**



10. A state machine with two inputs and three outputs will have \_\_\_\_\_ (how many) arcs going out from each state to any other states. **(1 point)**
11. For any given problem/requirement, the number of states required by a Mealy machine or a Moore machine is always the same \_\_\_\_\_ (True/False). **(1 point)**

**Question 2:**

**(7 points)**

Derive the state diagram of a synchronous Moore sequential circuit that receives a serial input  $Y$  and produces a serial output  $F$  that is set to **1** when the circuit detects the sequence **11X0**, where **X** represents don't care.

**Question 3:****(6 points)**

Design a combinational circuit using a ROM. The circuit accepts a 3-bit number  $X = X_2X_1X_0$  and generates an output binary number  $Y$  equal to  $3X + 4$ . The ROM should contain a minimum number of columns. Fill the truth table and ROM table below and draw the block diagram.

**Truth Table**



**ROM Table**

**Question 4:****(15 points)**

Given the following state table:

- a) Obtain minimal sum-of-products equations for the next state and output.  
 b) Draw the circuit diagram.


**(12 points)****(3 points)**

Present State	Next State		Output
	x = 0	x = 1	
A B C	x = 0	x = 1	z
0 0 0	0 0 1	0 0 0	0
0 0 1	0 1 0	0 0 0	1
0 1 0	0 1 1	0 0 0	1
0 1 1	1 0 0	0 0 0	1
1 0 0	1 0 1	0 0 1	0
1 0 1	1 0 1	0 1 1	1



(9 points)

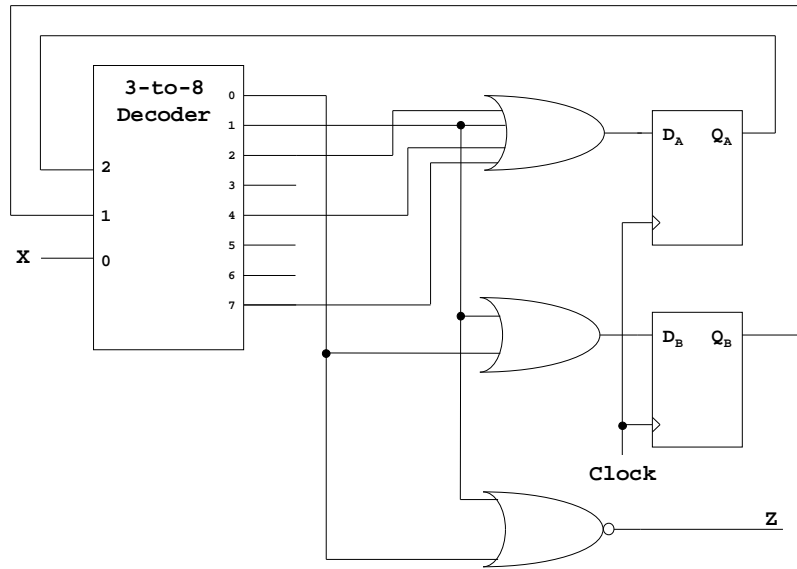Question 5: Consider the following sequential circuit:



a) Provide a state table for the given circuit showing the Present State, the input **X**, the Next State, and the output **Z**. (8 points)

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---


b) Is the circuit type *Mealy* or *Moore*? Justify your answer. (1 point)



**Question 6:****(6 points)**


Consider the following state table. Assume that the initial state of the circuit implementation of the given state table is ( $Q_A Q_B = 10$ ). Draw the waveforms of  $Q_A$ ,  $Q_B$ , and  $Z$  for the given 2 clock cycles in response to the shown applied input  $X$ . *Ignore propagation delays, setup times, and hold times. Assume that the circuit uses rising edge-triggered D-FF(s).*

Present State		$X$	Next State		$Z$
$Q_A$	$Q_B$		$D_A$	$D_B$	
0	0	0	0	1	1
0	0	1	1	1	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	1	0	0	0	1
1	1	1	1	0	1

 

 **Question 7:****(6 points)**

Use minimal external gates and as many of the following counter as necessary to design a counter that counts from **1** to **52** and then repeats. Note that the operation of the provided counter is according to the table to the right of the counter. Note also that CO stands for Carry-output which gets set to 1 when the maximum count of 15 is reached. Assume that the counter is initially loaded with the value 1. Properly label (Q0 – Q7) and (D0 – D7) of the designed counter.




<i>LOAD</i>	<i>EN</i>	<i>Operation</i>
0	0	Hold count
0	1	Increment count
1	X	Parallel load

**Question 8:****(15 points)**

Using D-FFs and any other components, design a 4-bit rotator register with direct asynchronous reset that has two control inputs; Load and Rot with the functionality shown in the table below:

Reset	Load	Rot	Function
0	0	0	No Change (Q stay as is)
1	X	X	asynchronous reset: Q = 0
0	1	X	Load: Q = D
0	0	1	Rotate Left: Q3=Q2, Q2=Q1, Q1=Q0, Q0=Q3

 

a) Draw the circuit diagram

**(5 points)**

b) Write a **behavioral** Verilog description of the above rotator register

**(6 points)**


c) Write a test bench to test the above rotator register. Let the clock cycle = 20 time units. First, reset the register, then load the register with **1010**, then do nothing for two clock cycles, then rotate the register **3** times.

**(4 points)**



**Question 9:****(10 points)**

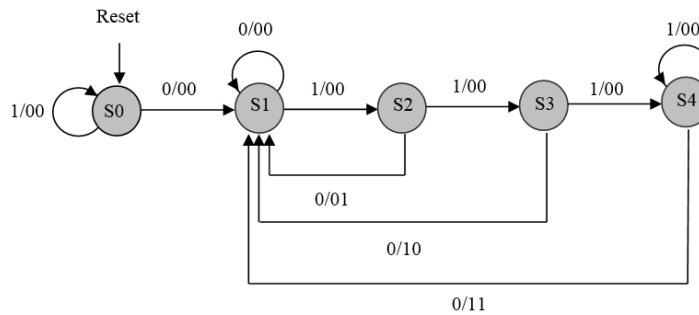- a) Write a **behavioral** Verilog description of a sequential circuit with the state diagram below. The circuit has an asynchronous **Reset** input, one input **X**, and two outputs: **Y** and **Z**. Use the following state encodings: **S0=000**, **S1=001**, **S2=010**, **S3=100**, **S4=111**. If the circuit ever gets into any of the unused states, it will go to state **S0** no matter what the input value is. **(6 points)**



- b) Write a test bench to test the circuit. Let the clock cycle = 20 time units. First, reset the circuit, then apply the following input sequence to **X**: **0, 1, 0, 1, 1, 1, 0**. **(4 points)**

