

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 171 (Fall 2017)
Final Exam
Monday, January 8th, 2018

Time: 120 minutes, Total Pages: 10

Name: _____ **ID:** _____ **Section:** _____

Notes:

Do not open the exam book until instructed


Calculators are not allowed (*basic, advanced, cell phones, etc.*)

Answer all questions

All steps must be shown

Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	25	
2	10	
3	15	
4	12	
5	8	
6	10	
7	15	
Total	95	

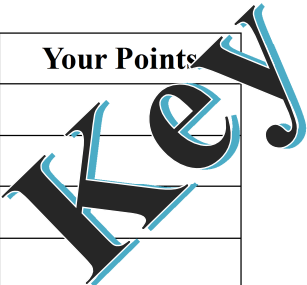


[25 points]

Question 1:


a) For a basic NOR SR latch the input SR = **00** keeps the state of the latch unchanged, while the forbidden input is SR = **11** (2 points).

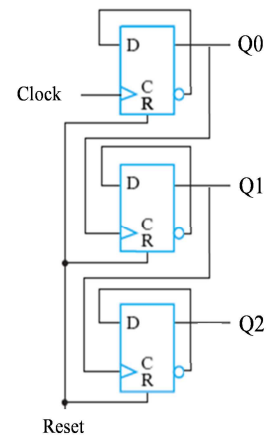b) The shown 3-bit binary counter counts **upwards/downward** (circle one).
 The counter has a maximum count of **7** and a minimum count of **0** (3 points).



 c) Given the following block diagram below:

If the output Q is 1 during the current cycle t , shown the output Q at $(t+1)$ after 1 cycle, and at $(t+2)$ after 2 cycles. (2 points)




$Q(t)$	$Q(t+1)$	$Q(t+2)$
0001	0100 = 4	0111 = 7

Describe the function of the above circuit diagram: (1 points)

The above circuit is a counter that increments its output Q by 3 each cycle (modulo 16).


d) The 4-bit shift register shown was initially loaded with ABCD = 0100. List in the table below the contents of the register after receiving each of the clock pulses indicated. (2 points).

	Register Contents A B C D (Binary)
Initial	0 1 0 0
After Clock Pulse 1	1 0 0 0
After Clock Pulse 2	1 1 1 0


 


 e) A sequential circuit has two inputs; X and Y , and one output Z and the state diagram below:



- The *synchronous reset* input is X (X or Y ?) The circuit is reset when this input is *High/Low* (circle one) and the *reset state* is 00. The *unused state* is 11 (4 points)
- For the input sequence **00 then 11 then 11 then 10**, the circuit would **end up in state** 01 (1 point)



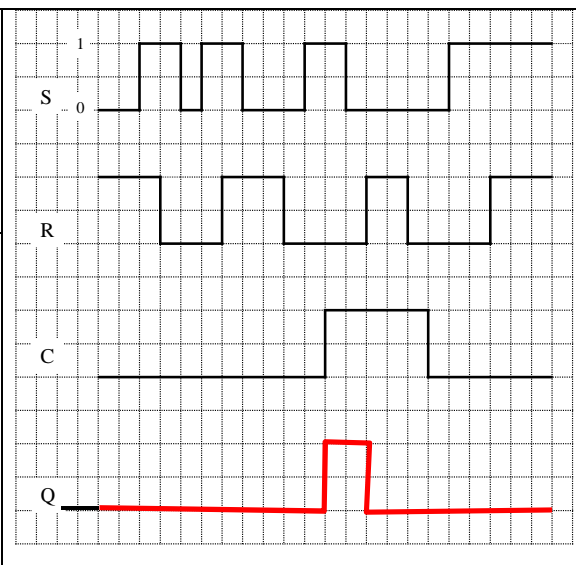 f) For the clocked SR latch shown, complete the waveform of the Q output for the given S, R, and clock (C) inputs. Initially, Q is 0. Ignore any propagation delays. (2 points).



 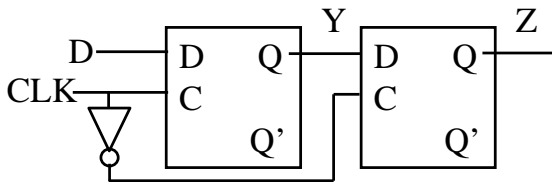g) Given the master-slave D-FF shown in Figure, complete the timing diagram for signals Y and Z (assume they are both initially at 0 and ignore any propagation delays). (4 points).



h) Given a synchronous sequential circuit with 13 states, the minimum number of flip flops required to implement the circuit is 4 flip flops and the number of unused states is 3 states. (2 points)

 
i) For a 5-bit synchronous binary counter with outputs Q₄, Q₃, Q₂, Q₁, and Q₀ (where Q₀ is the least-significant bit), if the clock frequency is 800 MHz then the frequency of Q₂ is 100 MHz and the frequency of Q₄ is 25 MHz. (2 points)

Question 2.

[10 points]


Draw the state diagram of a **Moore** synchronous sequential circuit that receives a serial input y and produces a serial output z . The output z should be **1** when the circuit detects the sequence **01100**. Overlapping sequences **are allowed**. A sample input/output trace after a reset is shown below:

y	0	1	1	0	0	1	1	0	0	0	1	
z	0	0	0	0	0	1	0	0	0	1	0	0

Solution:

Question 3. A sequential circuit has one input x and one output z , and has the state diagram shown below. **[15 Points]**

 a) Design the circuit using minimum number of logic gates and positive-edge triggered D Flip-Flops. **(10 points).**



Solution:

State table and K-maps are as shown:

Bx \ A	00	01	11	10
0	0	0	1	1
1	1	1	0	0

$$D_A = AB' + AB' = A \oplus B$$

Bx \ A	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D_B = A \oplus B + x$$


The circuit is as shown.

PS		Input	NS		Output
A	B	x	A+	B+	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

Bx \ A	00	01	11	10
0	0	0	0	0
1	1	0	1	0


$$z = ABx + AB'x'$$

b) Using the timing diagram below, draw the output waveform z . Assume the circuit starts at state **00**. **(5 points)**

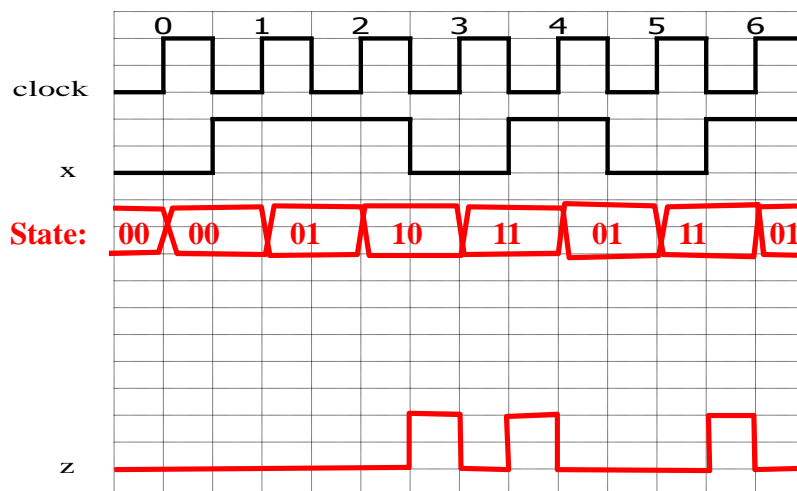

Question 4.

For the sequential circuit shown below:

 


1. Specify the inputs, outputs, reset state, and the type (Mealy or Moore). (2 points)

inputs; X, reset, clk, outputs; Z, Reset state:00, circuit type: Mealy

2. Derive the state diagram of the circuit. (9 points)

$B+ = B \text{ XOR } X + AB$ $A+ = A + BX$ $Z = X + AB$

A B X	A+ B+ Z
0 0 0	0 0 0
0 0 1	0 1 1
0 1 0	0 1 0
0 1 1	1 0 1
1 0 0	1 0 0
1 0 1	1 1 1
1 1 0	1 1 1
1 1 1	1 1 1

 

3. Does this circuit has any unused states? Briefly explain your answer (1 points)


No – All states can be reached using the circuit's inputs

Question 5. Label all your components, inputs, and outputs

[8 Points]

Using D flip-flop(s) and MUX(s) only (i.e., other components are not allowed), design a 4-bit register with mode selection inputs **S1** and **S0**. The register should operate according to the following table:

S1	S0	Function
0	0	No change
0	1	Parallel load (load inputs into register in parallel)
1	0	Rotate Right (i.e., shift register contents to the right feeding in the shifted bit out from the last bit location as a serial input to the first location)
1	1	Load register with 1's complement of its current content

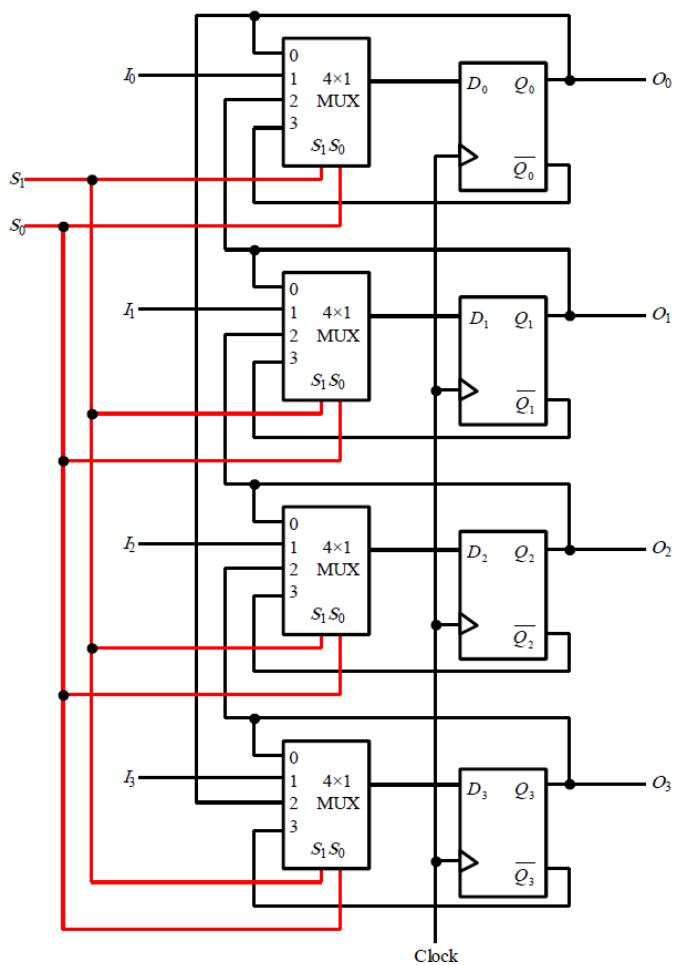


Question 6.

[10 Points]


Use as many as you need of the 4-bit binary counter shown below (with the table explaining its operation) and minimal gates to design a counter that counts up from 5 to 125 in binary and then back to 5. Label properly the inputs and outputs of your designed counter.

LD	EN	Operation of the counter
0	0	Hold count
0	1	Increment count
1	X	Parallel load

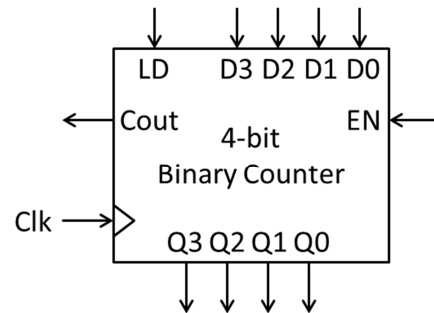

Solution:


$$125 = 8'b0111_1101$$

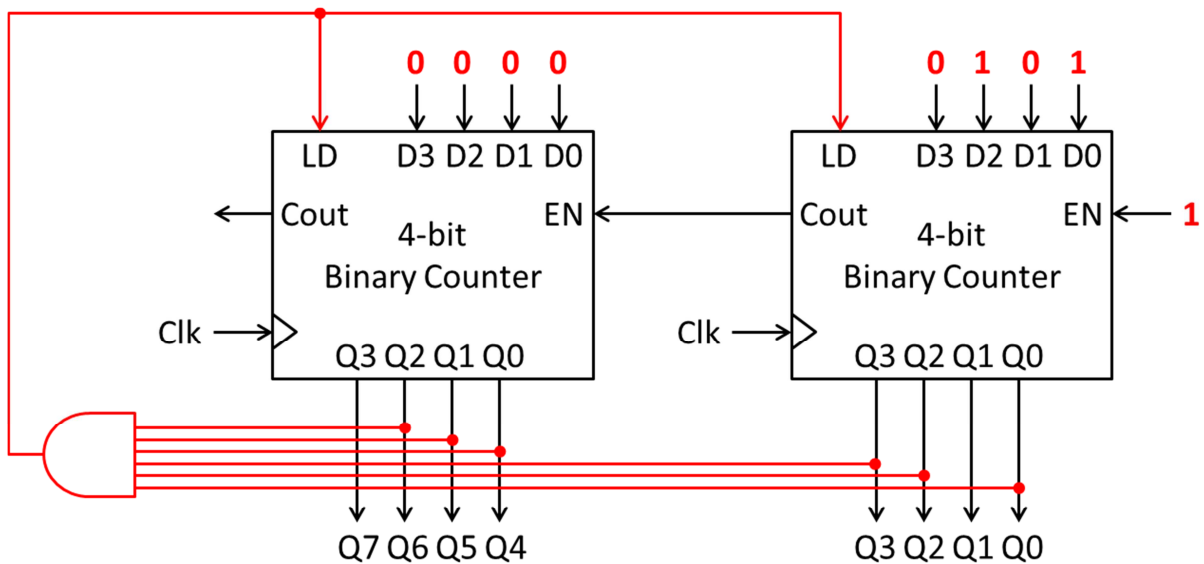

Question 7.

[15 Points]

 1. The state diagram below is for a sequential circuit that one input **X** (in addition to the asynchronous Reset) and one output **Y**. Write a **behavioral** Verilog description of this circuit. (10 points)



```

module FSM (input x, clk, reset, output y);
reg [1:0] state;
assign y = (state==2'b01) | (state==2'b10);
// this could also be simply written as
// assign y = (state==1) | (state==2);
always @(posedge clk, posedge reset)
if (reset) state<=0; //or state<= 2'b00
else case (state)
0: if (x) state <= 1; //could be 2'b00: if (x) state <= 2'b01;
1: if (x) state <= 2;
2: if (x) state <= 2;
   else state <= 0;
3: if (!x) state <= 1;
   else state <= 0;
endcase
endmodule

```

2. Write a **behavioral** Verilog description of a universal register that has three control inputs in addition to the clock input; Clr, LD, and Count, **and 4-bit input Din and output Q**, with the following functionality: **(the counter does not have asynchronous inputs)** (5 points)

Clr	LD	Count	Functionality
0	0	0	No change (i.e. Q stay the same)
1	X	X	Clear register no matter what LD and Count are (i.e. Q=0)
0	1	X	Load the register with Din (i.e. Q=Din)
0	0	1	Count up till Q=9, then go back to 0

```

module cntr (input clr, LD, count, clk, input [3:0] Din, output reg [3:0] Q);
always @(posedge clk)
if (clr) Q<=0; //or Q<= 4'b0000
else if (LD) Q<= Din;
else if (count)
if (Q==9) Q<=0; //or if (Q==4'b1001) Q<= 4'b0000
else Q<=Q+1;
endmodule

```