

*King Fahd University of Petroleum and Minerals*  
*College of Computer Science and Engineering*  
*Computer Engineering Department*

**COE 202: Digital Logic Design (3-0-3)**  
**Term 172 (Spring 2018)**  
**Final Exam**  
**Sunday May 13, 2018**

**Time: 120 minutes, Total Pages: 14**

Name: KEY ID: \_\_\_\_\_ Section: \_\_\_\_\_

**Notes:**

- Do not open the exam book until instructed
- **No Calculators are allowed** (*basic, advanced, cell phones, etc.*)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	13	
2	15	
3	15	
4	10	
5	10	
6	12	
<b>Total</b>	<b>75</b>	


**Question 1.**

**(13 points)**

Answer the following questions by **filling** the spaces with the correct answers:


 
- a) (2 points) The following circuit implements an edge-triggered D flip flop. Is it a positive or negative edge-triggered and why?

It is a negative edge-triggered D-FF because when CLK=1 the master latch is active capturing input changes and the slave latched is inactive while when CLK=0, the master is turned off and the slave is turned on copying the last value captured by the master.



  - b) (3 points) In the circuit shown, A is a D-type latch and B is a D-type flip flop. For the input waveforms given for the clock signal (Clk) and the input X, accurately draw the resulting waveforms at outputs  $Q_A$  and  $Q_B$ .


Assume that both  $Q_A$  and  $Q_B$  are initially at 0.




- c) (2 points) Given a synchronous sequential circuit with 5 states, the minimum number of flip-flops required to implement the circuit is 3 flip flops and the number of unused states is 3 states.

d) (2 points) For a 3-bit synchronous binary counter (outputs  $Q_2$ ,  $Q_1$  and  $Q_0$ ), with input clock frequency of 64 MHz, the frequency of  $Q_0$  is 32 MHz and the frequency of  $Q_2$  is 8 MHz.

 e) (2 points) Consider the sequential circuit given below with the 4-bit register ABCD . Initially the register has the contents ABCD = 1001 and the serial input line is kept at 1. After the first rising-edge of the clock, the register contents become ABCD = 0110. After the second rising-edge, the register contents become ABCD = 1011.




f) (2 points) Consider the given synchronous counter circuit. The LOAD input is synchronous and the Clear (reset to 0) input is asynchronous. Initially one short 0 pulse is applied at the clear input. The circuit implements a modulo-9 counter. With a clock input signal having a frequency of 720 cycles/sec, the frequency at the output signal is 80 cycles/sec.

 

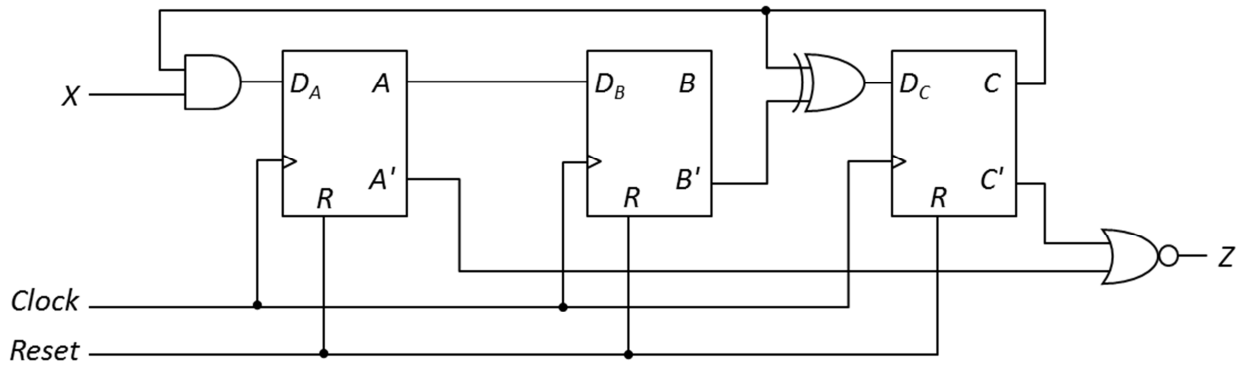**Question 2.****(15 points)**

Given the following synchronous sequential circuit with input  $X$  and output  $Z$  and asynchronous *Reset*:



- (1 point) Is it a Mealy or Moore sequential circuit and why?
- (2 points) Write the equations at the inputs of all flip-flops.
- (1 point) Write the output equation.
- (5 points) Draw the state table showing the present state, next state, and output  $Z$ .
- (1 point) Are there any unused states? Which ones?


**Solution:**

- Moore sequential circuit, because output  $Z$  does not depend on input  $X$ .**
- $D_A = X \cdot C$        $D_B = A$        $D_C = B' \oplus C$**
- $Z = (A' + C')' = A \cdot C$**
- 

Present State $A, B, C$	Next State when $X = 0$	Next State when $X = 1$	Output $Z$
0 0 0	0 0 1	0 0 1	0
0 0 1	0 0 0	1 0 0	0
0 1 0	0 0 0	0 0 0	0
0 1 1	0 0 1	1 0 1	0
1 0 0	0 1 1	0 1 1	0
1 0 1	0 1 0	1 1 0	1
1 1 0	0 1 0	0 1 0	0
1 1 1	0 1 1	1 1 1	1

- State 111 is unused. It is unreachable from the other states.**

- f) (5 points) Complete the timing diagram, starting at the initial state ( $ABC = 000$ ). Note that all the flip-flops are positive edge-triggered.

 

**Question 3.****(15 points)**

The state transition table below is for a sequential circuit with one input **X** and one output **Y**. The circuit has two state variables **A** and **B**, and **synchronous** input Reset that resets the circuit to state **AB=01** when Reset=1:

	Present State		Next State		Output	
	A	B	X=0	X=1	X=0	X=1
			A B	A B	A B	Y
	0	0	0 0	0 1	0	1
Reset State →	0	1	0 0	1 0	1	0
	1	0	0 1	1 0	0	1

- a) (9 points) Implement the sequential circuit using minimum number of logic gates and rising-edge triggered D-FFs and draw the logic diagram of the implemented circuit. The circuit should have **synchronous** reset that resets it to state **01**.

	00	01	11	10
0	0	1	? 3	2
1	4	5	? 7	6


$$D_A = X A + X B = X (A + B)$$

	00	01	11	10
0	0	1	? 3	2
1	4	5	? 7	6

$$D_B = X' A + X A' B'$$

	00	01	11	10
0	0	1	? 3	2
1	4	5	? 7	6

$$Z = X' B + X B' = X \oplus B$$

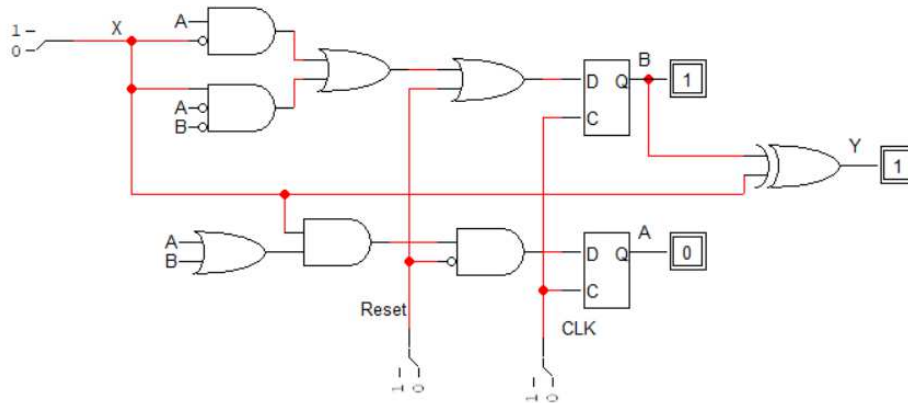

- b) (6 points) It is required to write a **behavioral** Verilog module to model the given sequential circuit. Complete the given Verilog code to achieve that.

```

module FinalQ3 (output reg Y, input X, Reset, CLK);

reg [1:0] state, next_state;

always @(posedge CLK) //synch reset
  if (Reset) state <= 2'b01;
  else state <= next_state; // the state transition

always @(state, X) begin //comb. Logic
  Y = 0;    next_state=2'b00; //Default value of Y and next_state
  case (state)
    2'b00: if (X) begin next_state=2'b01; Y=1; end
    2'b01: if (X) next_state=2'b10; else Y=1;
    2'b10: if (X) begin next_state=2'b10; Y=1; end else next_state=2'b01;
  endcase
end

endmodule

 
```

**Question 4.****(10 points)**

Draw the state diagram of a Mealy sequence detector with input  $X$ , output  $Z$ , and a *reset* input, that detects the input sequences **0110** or **1100**. The sequence detector should detect overlapping sequences.

The following is an example of an input/output stream, starting at the initial state:

Clock Cycle	0	1	2	3	4	5	6	7	8	9	10	11	12	13
Input $X$	0	1	1	0	0	1	1	0	1	1	0	1	1	1
Output $Z$	0	0	0	1	1	0	0	1	0	0	1	0	0	0



**Solution:**



**Question 5.**

**(10 points)**

- a) (5 points) Using 4-bit synchronous binary counters, with synchronous load input (LD), enable input (EN), and Cout output, as shown in the graphic symbol below, show how to implement a counter that counts up from 7 to 77 and then back to 7, repeatedly. You may use multiple instances of the 4-bit counter and additional gates as needed to implement the 7 to 77 counter. Include an external preset input that initializes the counter to 7.

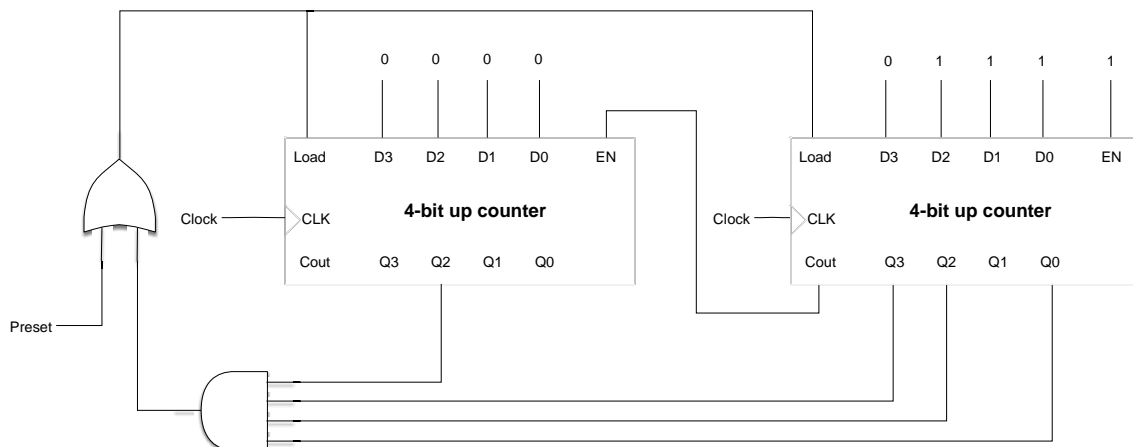 




**Question 6:**


**(12 marks)**

Using positive edge-triggered D-FFs and any other components, you are required to design a 3-bit multi-function register with direct **asynchronous** reset. The register operates according to the following function table:

Reset	F1	F0	Function
1	X	X	Asynchronous reset: $Q = 0$
0	0	0	No change
0	0	1	Rotate left: $Q2 \leftarrow Q1, Q1 \leftarrow Q0, Q0 \leftarrow Q2$
0	1	X	Load: $Q = D$

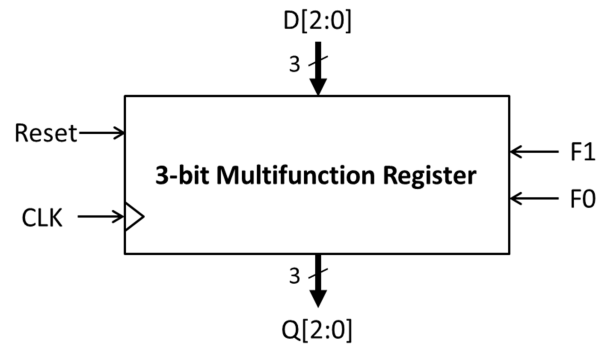

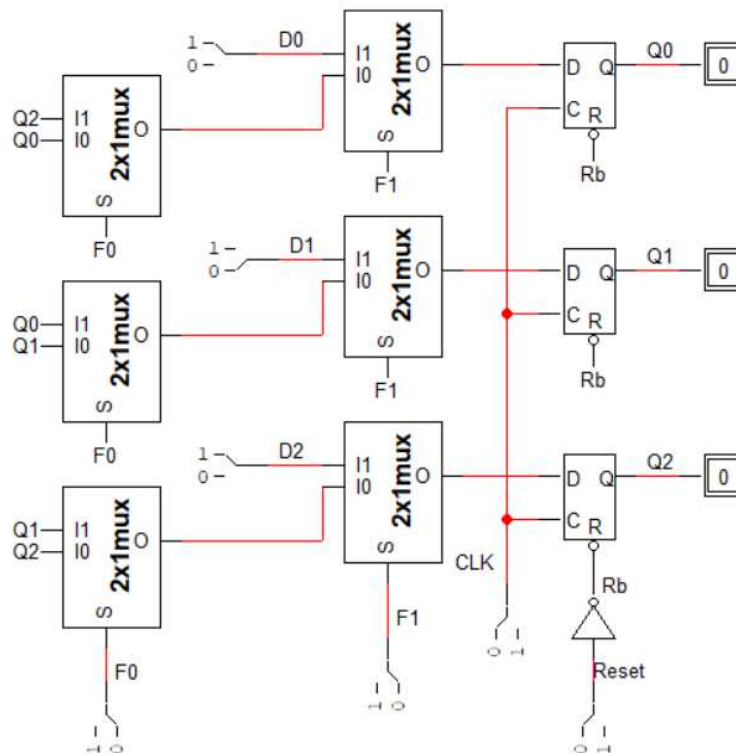a) (4 points) Draw the circuit diagram of this register.



- b) (4 points) The following Verilog module is supposed to model the register described above. Complete the module by filling the blanks in the following code:

```
// mfr: multi-function register
module mfr (input [2:0] D, input reset, clk, F1, F0,
           output reg [2:0] Q);
always @(  posedge clk, posedge reset          )
begin

    if (reset) Q <= 0;
    else if (F1) Q <= D;
    else if (F0) Q <= {Q[1:0],Q[2]};

end

endmodule
```

- c) (4 points) Write a test bench module to verify the functionality of Module **mfr**. Use the following test patterns for verification:

Clock Cycle	1	2	3	4
Reset	1	0	0	0
F1	X	0	1	0
F0	X	0	0	1
D[2:0]	X	X	3	X

Complete the missing parts of the following test bench module.

```

module tb;
reg clk, rst, F1, F0;
reg [2:0] D;
wire [2:0] Q;
// instantiate Module mfr below this line
mfr mfr1(D, rst, clk, F1, F0, Q);

// In the space provided below, setup the clock
// and apply the test patterns shown above.

always #5 clk = ~clk;

initial begin

    rst=1; clk=0;
    #10 rst=0;
    @(negedge clk) F1=1'b0; F0=1'b0;
    @(negedge clk) F1=1'b1; F0=0; D=3'b011;
    @(negedge clk) F1=1'b0; F0=1'b1;

end

endmodule

```