

# Boolean Algebra and Logic Gates

COE 233

Digital Logic and Computer Organization

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals

# Presentation Outline

- ❖ Boolean Algebra, truth tables, and DeMorgan's theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ From truth table to logic expression: minterms and maxterms
- ❖ Logic gates, logic diagrams, and standard forms
- ❖ Additional gates: NAND, NOR, XOR, XNOR

# Boolean Algebra

- ❖ Introduced by George Boole in 1854
- ❖ A set of two values:  $B = \{0, 1\}$
- ❖ Three basic operations: **AND**, **OR**, and **NOT**
- ❖ The **AND** operator is denoted by a dot ( $\cdot$ )
  - ❖  $x \cdot y$  or  $xy$  is read:  $x$  **AND**  $y$
- ❖ The **OR** operator is denoted by a plus ( $+$ )
  - ❖  $x + y$  is read:  $x$  **OR**  $y$
- ❖ The **NOT** operator is denoted by a quotation ' or an overbar  $\bar{\phantom{x}}$ 
  - ❖  $x'$  or  $\bar{x}$  is the complement of  $x$
- ❖ Today, Boolean algebra is being used to design digital circuits

# Postulates of Boolean Algebra

1. Closure: the result of any Boolean operation is in  $B = \{0, 1\}$
2. Identity element with respect to  $+$  is 0:  $x + 0 = 0 + x = x$   
Identity element with respect to  $\cdot$  is 1:  $x \cdot 1 = 1 \cdot x = x$
3. Commutative with respect to  $+$ :  $x + y = y + x$   
Commutative with respect to  $\cdot$ :  $x \cdot y = y \cdot x$
4.  $\cdot$  is distributive over  $+$ :  $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$   
 $+$  is distributive over  $\cdot$ :  $x + (y \cdot z) = (x + y) \cdot (x + z)$
5. For every  $x$  in  $B$ , there exists  $x'$  in  $B$  (called complement of  $x$ ) such that:  $x + x' = 1$  and  $x \cdot x' = 0$

# AND, OR, and NOT Operators

- ❖ The following tables define  $x \cdot y$ ,  $x + y$ , and  $x'$
- ❖  $x \cdot y$  is the **AND** operator
- ❖  $x + y$  is the **OR** operator
- ❖  $x'$  is the **NOT** operator

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	$x'$
0	1
1	0

# Boolean Functions

- ❖ Boolean functions are described by expressions that consist of:
  - ✧ Boolean variables, such as:  $x$ ,  $y$ , etc.
  - ✧ Boolean constants: 0 and 1
  - ✧ Boolean operators: AND ( $\cdot$ ), OR ( $+$ ), NOT ( $'$ )
  - ✧ Parentheses, which can be nested
- ❖ Example:  $f = x(y + w'z)$ 
  - ✧ The dot operator is implicit and need not be written
- ❖ Operator precedence: to avoid ambiguity in expressions
  - ✧ Expressions within parentheses should be evaluated first
  - ✧ The NOT ( $'$ ) operator should be evaluated second
  - ✧ The AND ( $\cdot$ ) operator should be evaluated third
  - ✧ The OR ( $+$ ) operator should be evaluated last

# Truth Table

- ❖ A truth table can represent a Boolean function
- ❖ List all possible combinations of 0's and 1's assigned to variables
- ❖ If  $n$  variables then  $2^n$  rows
- ❖ Example: Truth table for  $f = xy' + x'z$

x	y	z	y'	xy'	x'	x'z	f = xy' + x'z
0	0	0	1	0	1	0	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

# DeMorgan's Theorem

$$\diamond (x + y)' = x' y'$$

$$\diamond (x y)' = x' + y'$$

Can be verified  
Using a Truth Table

x	y	x'	y'	x+y	(x+y)'	x'y'	x y	(x y)'	x'+ y'
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

Identical

Identical

$\diamond$  Generalized DeMorgan's Theorem:

$$\diamond (x_1 + x_2 + \dots + x_n)' = x_1' \cdot x_2' \cdot \dots \cdot x_n'$$

$$\diamond (x_1 \cdot x_2 \cdot \dots \cdot x_n)' = x_1' + x_2' + \dots + x_n'$$



# Complementing Boolean Functions

- ❖ What is the complement of  $f = x'yz' + xy'z'$  ?
- ❖ Use DeMorgan's Theorem:
  - ✧ Complement each variable and constant
  - ✧ Interchange AND and OR operators
- ❖ So, what is the complement of  $f = x'yz' + xy'z'$  ?

**Answer:**  $f' = (x + y' + z)(x' + y + z)$

- ❖ **Example 2:** Complement  $g = (a' + bc)d' + e$

- ❖ **Answer:**  $g' = (a(b' + c') + d)e'$

# Algebraic Manipulation of Expressions

❖ The objective is to acquire skills in manipulating Boolean expressions, to transform them into simpler form.

❖ **Example 1:** prove  $x + xy = x$  (absorption theorem)

❖ **Proof:**  $x + xy = x \cdot 1 + xy$

$$= x \cdot (1 + y)$$

$$= x \cdot 1 = x$$

$$x \cdot 1 = x$$

Distributive  $\cdot$  over  $+$

$$(1 + y) = 1$$

❖ **Example 2:** prove  $x + x'y = x + y$  (simplification theorem)

❖ **Proof:**  $x + x'y = (x + x')(x + y)$

$$= 1 \cdot (x + y)$$

$$= x + y$$

Distributive  $+$  over  $\cdot$

$$(x + x') = 1$$

# Expression Simplification

- ❖ Using Boolean algebra to simplify expressions
- ❖ Expression should contain the smallest number of **literals**
- ❖ A **literal** is a variable that may or may not be complemented

❖ **Example:** simplify  $ab + a'cd + a'bd + a'cd' + abcd$

❖ **Solution:**  $ab + a'cd + a'bd + a'cd' + abcd$  (15 literals)

$= ab + abcd + a'cd + a'cd' + a'bd$  (15 literals)

$= ab + ab(cd) + a'c(d + d') + a'bd$  (13 literals)

$= ab + \underbrace{a'c + a'bd}$  (7 literals)

$= ba + ba'd + a'c$  (7 literals)

$= b(a + a'd) + a'c$  (6 literals)

$= b(a + d) + a'c$  (5 literals only)

# Summary of Boolean Algebra

	Property	Dual Property
Identity	$x + 0 = x$	$x \cdot 1 = x$
Complement	$x + x' = 1$	$x \cdot x' = 0$
Null	$x + 1 = 1$	$x \cdot 0 = 0$
Idempotence	$x + x = x$	$x \cdot x = x$
Involution	$(x')' = x$	
Commutative	$x + y = y + x$	$x y = y x$
Associative	$(x + y) + z = x + (y + z)$	$(x y) z = x (y z)$
Distributive	$x (y + z) = xy + xz$	$x + yz = (x + y)(x + z)$
Absorption	$x + xy = x$	$x(x + y) = x$
Simplification	$x + x'y = x + y$	$x(x' + y) = xy$
De Morgan	$(x + y)' = x' y'$	$(x y)' = x' + y'$

# Importance of Boolean Algebra

- ❖ Our objective is to learn how to design digital circuits
- ❖ These circuits use signals with two possible values
- ❖ Logic **0** is a **low** voltage signal (0 volts)
- ❖ Logic **1** is a **high** voltage signal (for example, 1.2 volts)
- ❖ The physical value of a signal is the actual voltage it carries, while its logic value is either 0 (low) or 1 (high)
- ❖ Having only two logic values (0 and 1) simplifies the implementation of the digital circuit

# Next . . .

- ❖ Boolean Algebra, truth tables, and DeMorgan's theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ From truth table to logic expression: minterms and maxterms
- ❖ Logic gates, logic diagrams, and standard forms
- ❖ Additional gates: NAND, NOR, XOR, XNOR

# From a Truth Table to Logic Expression

- ❖ Given the truth table of a Boolean function  $f$ , how to obtain the logic expression ?

## Truth Table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

What is the logic expression of  $f$ ?

To answer this question, we need to define Minterms and Maxterms

# Minterms and Maxterms

- ❖ **Minterms** are AND terms with every variable present in either true or complement form
- ❖ **Maxterms** are OR terms with every variable present in either true or complement form

Minterms and Maxterms for 2 variables  $x$  and  $y$

<b>x</b>	<b>y</b>	<b>index</b>	<b>Minterm</b>	<b>Maxterm</b>
0	0	0	$m_0 = x'y'$	$M_0 = x + y$
0	1	1	$m_1 = x'y$	$M_1 = x + y'$
1	0	2	$m_2 = xy'$	$M_2 = x' + y$
1	1	3	$m_3 = xy$	$M_3 = x' + y'$

- ❖ For  $n$  variables, there are  $2^n$  Minterms and Maxterms



# Minterms and Maxterms for 3 Variables

x	y	z	index	Minterm	Maxterm
0	0	0	0	$m_0 = x'y'z'$	$M_0 = x + y + z$
0	0	1	1	$m_1 = x'y'z$	$M_1 = x + y + z'$
0	1	0	2	$m_2 = x'yz'$	$M_2 = x + y' + z$
0	1	1	3	$m_3 = x'yz$	$M_3 = x + y' + z'$
1	0	0	4	$m_4 = xy'z'$	$M_4 = x' + y + z$
1	0	1	5	$m_5 = xy'z$	$M_5 = x' + y + z'$
1	1	0	6	$m_6 = xyz'$	$M_6 = x' + y' + z$
1	1	1	7	$m_7 = xyz$	$M_7 = x' + y' + z'$

Maxterm  $M_i$  is the **complement** of Minterm  $m_i$

$$M_i = m_i' \quad \text{and} \quad m_i = M_i'$$

# Sum-Of-Minterms (SOM) Canonical Form

## Truth Table

x	y	z	f	Minterm
0	0	0	0	
0	0	1	0	
0	1	0	1	$m_2 = x'yz'$
0	1	1	1	$m_3 = x'yz$
1	0	0	0	
1	0	1	1	$m_5 = xy'z$
1	1	0	0	
1	1	1	1	$m_7 = xyz$

Sum of Minterm entries  
that evaluate to '1'

Focus on the '1' entries

$$f = m_2 + m_3 + m_5 + m_7$$

$$f = \sum (2, 3, 5, 7)$$

$$f = x'yz' + x'yz + xy'z + xyz$$

# Product-Of-Maxterms (POM) Canonical Form

## Truth Table

x	y	z	f	Maxterm
0	0	0	0	$M_0 = x + y + z$
0	0	1	0	$M_1 = x + y + z'$
0	1	0	1	
0	1	1	1	
1	0	0	0	$M_4 = x' + y + z$
1	0	1	1	
1	1	0	0	$M_6 = x' + y' + z$
1	1	1	1	

Product of Maxterm entries  
that evaluate to '0'

Focus on the '0' entries

$$f = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$f = \prod (0, 1, 4, 6)$$

$$f = (x + y + z)(x + y + z')(x' + y + z)(x' + y' + z)$$

# Purpose of the Index

- ❖ Minterms and Maxterms are designated with an index
- ❖ The **index** for the Minterm or Maxterm, expressed as a **binary number**, is used to determine whether the variable is shown in the true or complemented form
- ❖ For Minterms:
  - ✧ '1' means the variable is **Not Complemented**
  - ✧ '0' means the variable is **Complemented**
- ❖ For Maxterms:
  - ✧ '0' means the variable is **Not Complemented**
  - ✧ '1' means the variable is **Complemented**

# Examples of Sum-Of-Minterms

$$\diamond f(a, b, c, d) = \Sigma(2, 3, 6, 10, 11)$$

$$\diamond f(a, b, c, d) = m_2 + m_3 + m_6 + m_{10} + m_{11}$$

$$\diamond f(a, b, c, d) = a'b'cd' + a'b'cd + a'bcd' + ab'cd' + ab'cd$$

$$\diamond g(a, b, c, d) = \Sigma(0, 1, 12, 15)$$

$$\diamond g(a, b, c, d) = m_0 + m_1 + m_{12} + m_{15}$$

$$\diamond g(a, b, c, d) = a'b'c'd' + a'b'c'd + abc'd' + abcd$$

# Examples of Product-Of-Maxterms

$$\diamond f(a, b, c, d) = \prod(1, 3, 11)$$

$$\diamond f(a, b, c, d) = M_1 \cdot M_3 \cdot M_{11}$$

$$\diamond f(a, b, c, d) = (a + b + c + d')(a + b + c' + d')(a' + b + c' + d')$$

$$\diamond g(a, b, c, d) = \prod(0, 5, 13)$$

$$\diamond g(a, b, c, d) = M_0 \cdot M_5 \cdot M_{13}$$

$$\diamond g(a, b, c, d) = (a + b + c + d)(a + b' + c + d')(a' + b' + c + d')$$

# Conversions between Canonical Forms

❖ The same Boolean function  $f$  can be expressed in two ways:

❖ Sum-of-Minterms  $f = m_0 + m_2 + m_3 + m_5 + m_7 = \Sigma(0, 2, 3, 5, 7)$

❖ Product-of-Maxterms  $f = M_1 \cdot M_4 \cdot M_6 = \Pi(1, 4, 6)$

## Truth Table

x	y	z	f	Minterms	Maxterms
0	0	0	1	$m_0 = x'y'z'$	
0	0	1	0		$M_1 = x + y + z'$
0	1	0	1	$m_2 = x'yz'$	
0	1	1	1	$m_3 = x'yz$	
1	0	0	0		$M_4 = x' + y + z$
1	0	1	1	$m_5 = xy'z$	
1	1	0	0		$M_6 = x' + y' + z$
1	1	1	1	$m_7 = xyz$	

To convert from one canonical form to another, interchange the symbols  $\Sigma$  and  $\Pi$  and list those numbers missing from the original form.

# Function Complement

## Truth Table

x	y	z	f	f'
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

Given a Boolean function  $f$

$$f(x, y, z) = \sum (0, 2, 3, 5, 7) = \prod (1, 4, 6)$$

Then, the complement  $f'$  of function  $f$

$$f'(x, y, z) = \prod (0, 2, 3, 5, 7) = \sum (1, 4, 6)$$

The complement of a function expressed by a Sum of Minterms is the Product of Maxterms with the same indices. Interchange the symbols  $\Sigma$  and  $\Pi$ , but keep the same list of indices.




# Summary of Minterms and Maxterms

- ❖ There are  $2^n$  Minterms and Maxterms for Boolean functions with  $n$  variables, indexed from 0 to  $2^n - 1$
- ❖ Minterms correspond to the **1-entries** of the function
- ❖ Maxterms correspond to the **0-entries** of the function
- ❖ Any Boolean function can be expressed as a Sum-of-Minterms and as a Product-of-Maxterms
- ❖ For a Boolean function, given the list of Minterm indices one can determine the list of Maxterms indices (and vice versa)
- ❖ The complement of a Sum-of-Minterms is a Product-of-Maxterms with the same indices (and vice versa)


# Next . . .

- ❖ Boolean Algebra, truth tables, and DeMorgan's theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ From truth table to logic expression: minterms and maxterms
- ❖ Logic gates, logic diagrams, and standard forms
- ❖ Additional gates: NAND, NOR, XOR, XNOR


# Logic Gates and Symbols

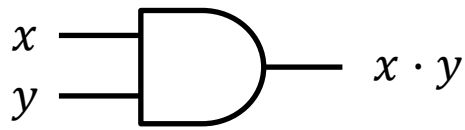


AND gate

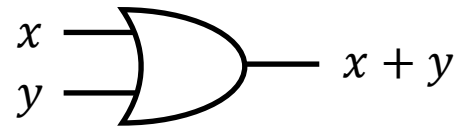


OR gate

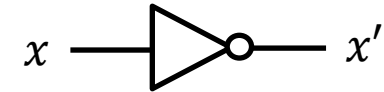


NOT gate (inverter)

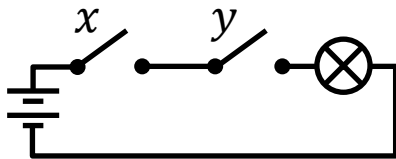

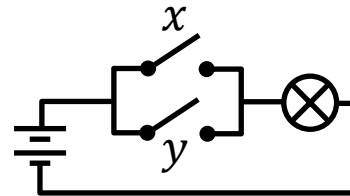AND: Switches in series  
logic 0 is open switch



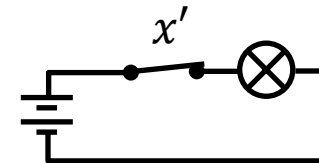OR: Switches in parallel  
logic 0 is open switch



NOT: Switch is normally  
closed when  $x$  is 0

- ❖ In the earliest days of computers, relays were used as mechanical switches controlled by electricity (coils)
- ❖ Today, tiny transistors are used as electronic switches that implement the logic gates (CMOS technology)


# Truth Table and Logic Diagram

- ❖ Given the following logic function:  $f = x(y' + z)$
- ❖ Draw the corresponding truth table and logic diagram

## Truth Table

x	y	z	$y' + z$	$f = x(y' + z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

## Logic Diagram

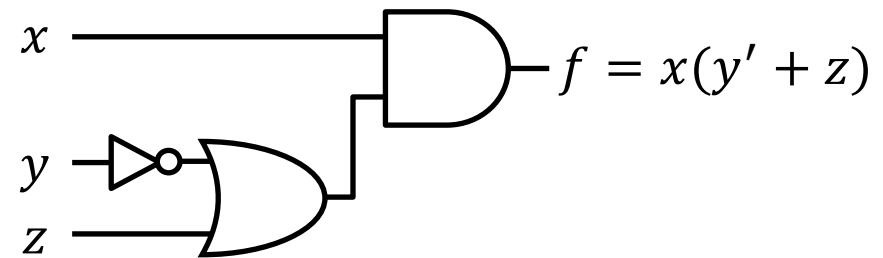

Truth Table and Logic Diagram describe the same function  $f$ . Truth table is unique, but logic expression and logic diagram are not. This gives flexibility in implementing logic functions.

# Standard Forms

- ❖ Boolean functions are usually expressed in **standard** form
- ❖ Two standard forms: **Sum-of-Products** and **Product-of -Sums**
- ❖ Sum of Products (**SOP**)
  - ✧ Boolean expression is the **ORing** (sum) of **AND terms** (products)
  - ✧ Examples:  $f_1 = x'y + xz$                        $f_2 = y + w'xz$
- ❖ Products of Sums (**POS**)
  - ✧ Boolean expression is the **ANDing** (product) of **OR terms** (sums)
  - ✧ Examples:  $f_3 = (x + z)(x' + y')$                        $f_4 = x(w' + y' + z)$

# From Sum-of-Minterms to Sum-of-Products

- ❖ Simplify  $f(x, y, z) = \sum(2, 3, 5, 7)$  into minimal sum-of-products
- ❖ First, write  $f$  as sum-of-minterms canonical form
- ❖  $f(x, y, z) = \sum(2, 3, 5, 7) = x'yz' + x'yz + xy'z + xyz$
- ❖ Then, simplify expression using properties of Boolean Algebra

$$f = x'yz' + x'yz + xy'z + xyz \quad (12 \text{ literals})$$


$$f = x'y(z' + z) + xz(y' + y)$$

$$f = x'y (1) + x z (1)$$

$$f = x'y + xz \quad (4 \text{ literals})$$


# Two-Level Gate Implementation

$$f_1 = x'y + xz$$

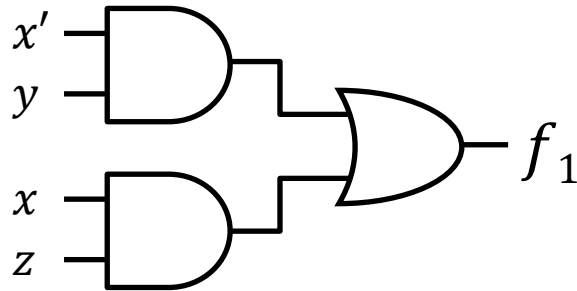


**AND-OR  
implementations**

$$f_2 = y + w'xz$$

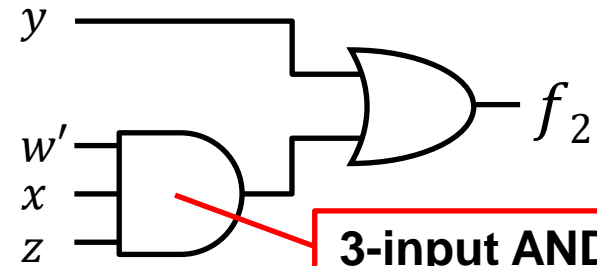


**3-input AND gate**

$$f_3 = (x + z)(x' + y')$$

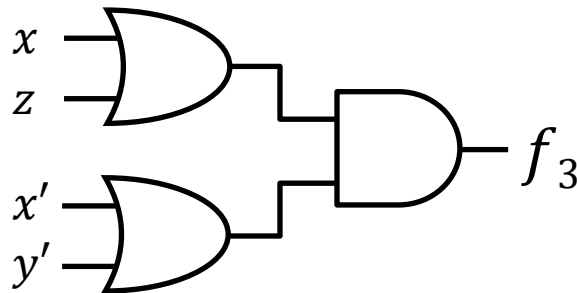

**OR-AND  
implementations**

$$f_4 = x(w' + y' + z)$$

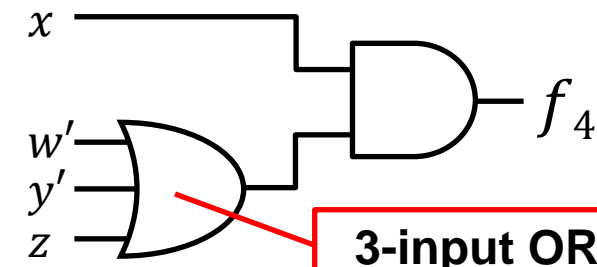


**3-input OR gate**

# Two-Level vs. Three-Level Implementation

- ❖  $h = ab + cd + ce$  (6 literals) is a sum-of-products
- ❖  $h$  may also be written as:  $h = ab + c(d + e)$  (5 literals)
- ❖ However,  $h = ab + c(d + e)$  is a non-standard form
  - ✧  $h = ab + c(d + e)$  is not a sum-of-products nor a product-of-sums


## 2-level implementation

$$h = ab + cd + ce$$

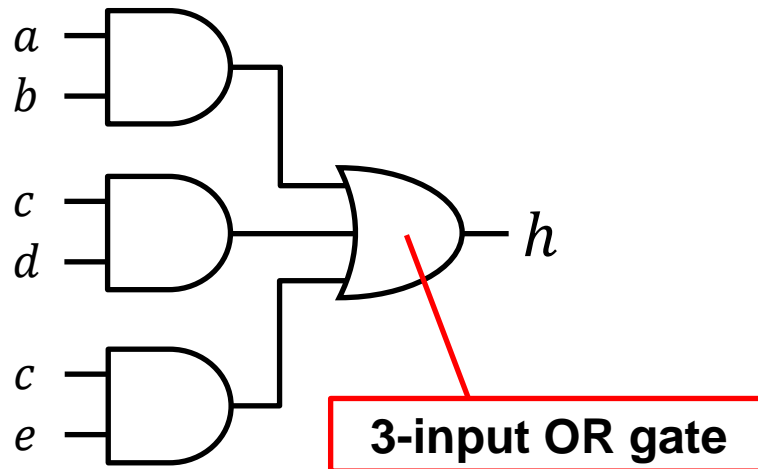

## 3-level implementation

$$h = ab + c(d + e)$$

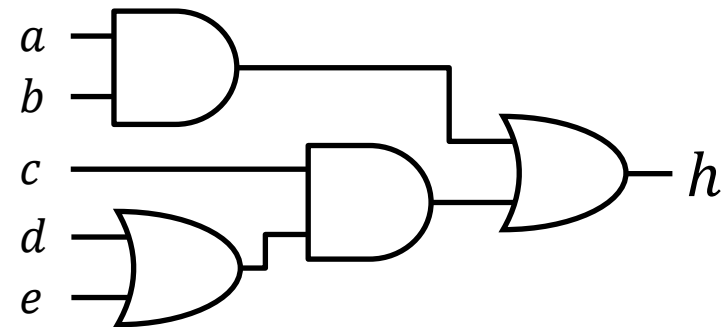




# Next . . .

- ❖ Boolean Algebra, truth tables, and DeMorgan's theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ From truth table to logic expression: minterms and maxterms
- ❖ Logic gates, logic diagrams, and standard forms
- ❖ Additional gates: NAND, NOR, XOR, XNOR


# Additional Logic Gates and Symbols
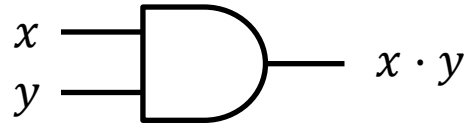
## ❖ Why?


- ❖ Low-cost implementation
- ❖ Useful in implementing Boolean functions




AND gate

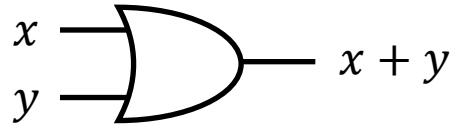


OR gate

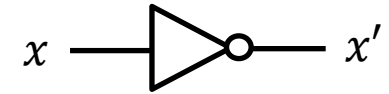


NOT gate (inverter)

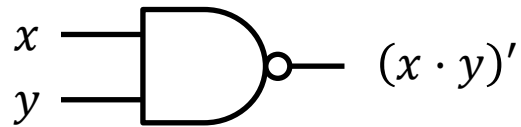


NAND gate

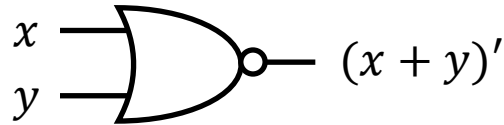

NOR gate

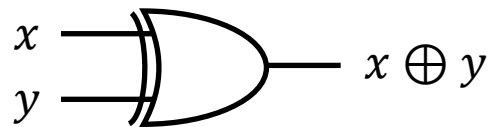


XOR gate

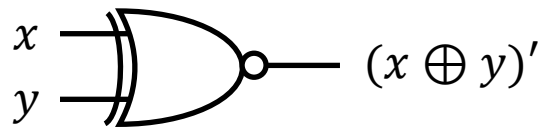


XNOR gate
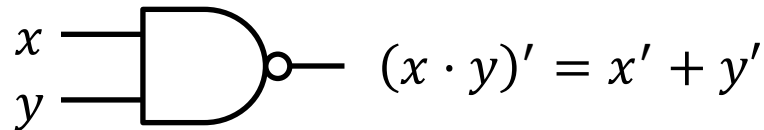
# NAND Gate

- ❖ The NAND gate has the following symbol and truth table
- ❖ NAND represents **NOT AND**
- ❖ The small bubble circle represents the invert function



NAND gate

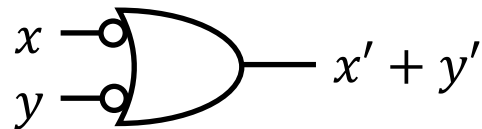


Another symbol for NAND

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


- ❖ NAND gate is implemented efficiently in CMOS technology
  - ✧ In terms of chip area and speed
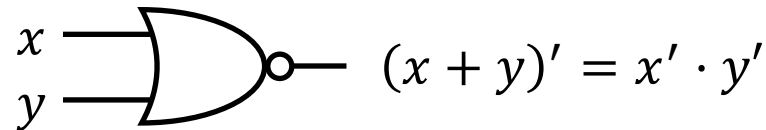
# NOR Gate

- ❖ The NOR gate has the following symbol and truth table
- ❖ NOR represents **NOT OR**
- ❖ The small bubble circle represents the invert function



NOR gate

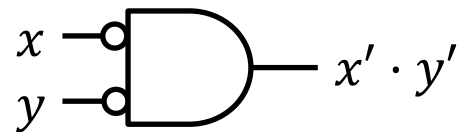


Another symbol for NOR

x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0


- ❖ NOR gate is implemented efficiently in CMOS technology
  - ✧ In terms of chip area and speed
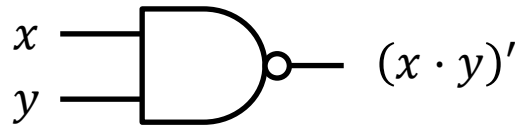
# Multiple-Input NAND / NOR Gates


NAND/NOR gates can have multiple inputs, similar to AND/OR gates




2-input NAND gate

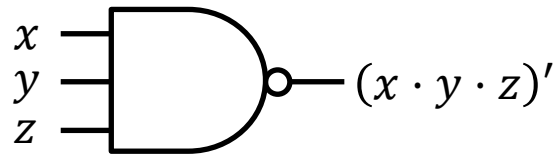


3-input NAND gate

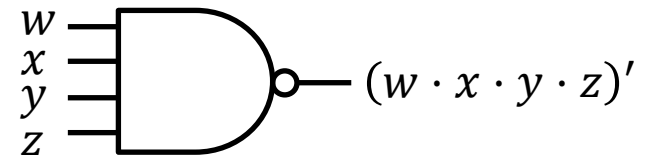


4-input NAND gate

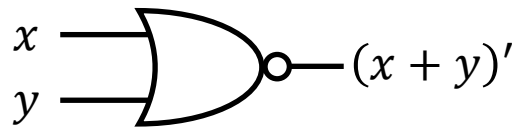

2-input NOR gate

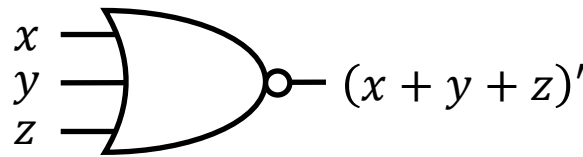

3-input NOR gate

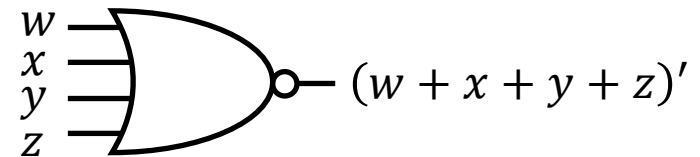

4-input NOR gate

Note: a 3-input NAND is a single gate, NOT a combination of two 2-input gates. The same can be said about other multiple-input NAND/NOR gates.


# NAND - NAND Implementation

- ❖ Consider the following sum-of-products expression:


$$f = bd + a'cd'$$

- ❖ A 2-level **AND-OR** circuit can be converted easily to a 2-level **NAND-NAND** implementation


2-Level AND-OR

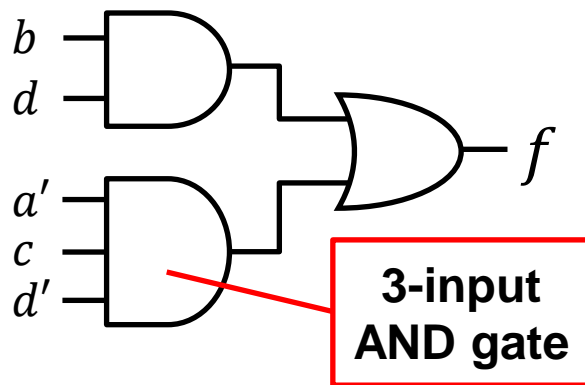

Inserting Bubbles

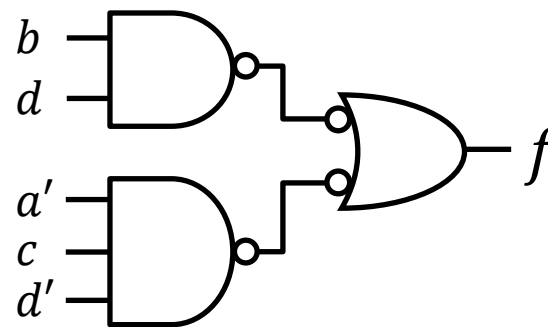

2-Level NAND-NAND

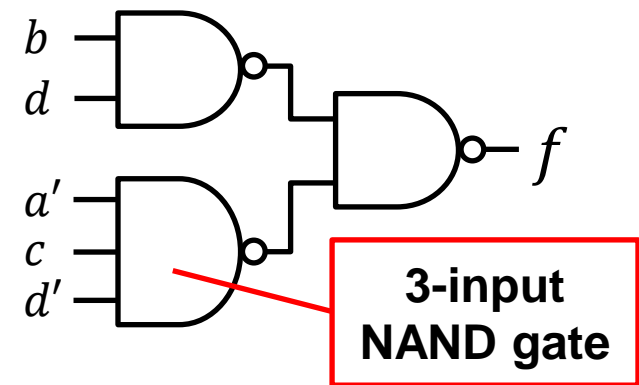

Two successive bubbles on same line cancel each other


# NOR - NOR Implementation

- ❖ Consider the following product-of-sums expression:


$$g = (a + d)(b + c + d')$$

- ❖ A 2-level **OR-AND** circuit can be converted easily to a 2-level **NOR-NOR** implementation


2-Level OR-AND

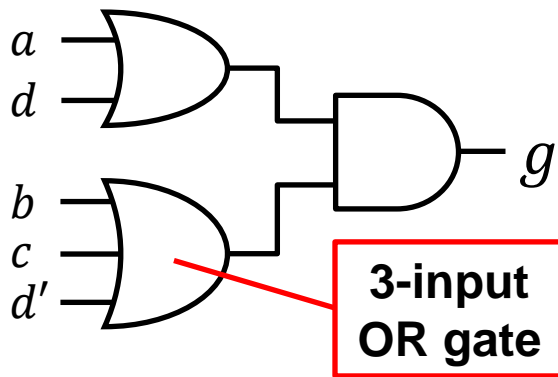

Inserting Bubbles

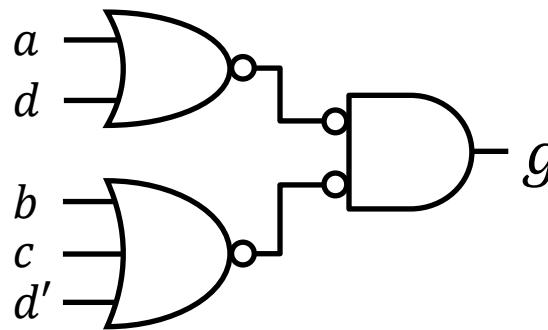

2-Level NOR-NOR

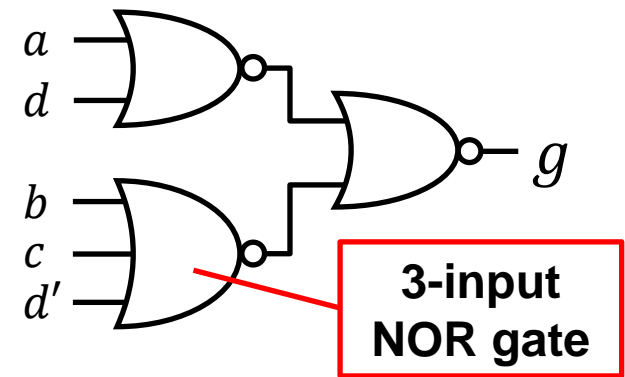

Two successive bubbles on same line cancel each other



# Exclusive OR / Exclusive NOR

- ❖ Exclusive OR (XOR) is an important Boolean operation used extensively in logic circuits
- ❖ Exclusive NOR (XNOR) is the complement of XOR

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

XNOR is also known  
as **equivalence**

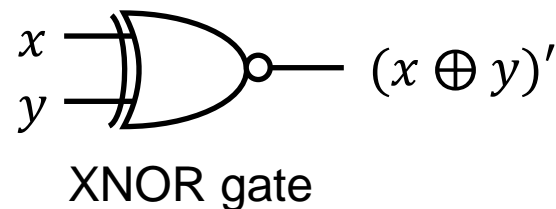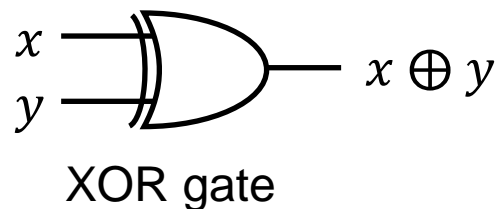



# XOR / XNOR Functions

- ❖ The XOR function is:  $x \oplus y = xy' + x'y$
- ❖ The XNOR function is:  $(x \oplus y)' = xy + x'y'$
- ❖ XOR and XNOR gates are complex
  - ✧ Can be implemented as a true gate, or by
  - ✧ Interconnecting other gate types
- ❖ XOR and XNOR gates do not exist for more than two inputs
  - ✧ For 3 inputs, use two XOR gates
  - ✧ The cost of a 3-input XOR gate is greater than the cost of two XOR gates
- ❖ Uses for XOR and XNOR gates include:
  - ✧ Adders, subtractors, multipliers, incrementers, and decrementers

# XOR and XNOR Properties

$$\diamond x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$\diamond x \oplus x = 0$$

$$x \oplus x' = 1$$

$$\diamond x \oplus y = y \oplus x$$

$$\diamond x' \oplus y' = x \oplus y$$

$$\diamond (x \oplus y)' = x' \oplus y = x \oplus y'$$

XOR is an **associative** operation

$$\diamond (x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$$

# Odd Function

- ❖ Output is 1 if the **number of 1's is odd in the inputs**
- ❖ Output is the XOR operation on all input variables


Odd Function with 3 inputs

x	y	z	fodd
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$fodd = \sum (1, 2, 4, 7)$$

$$fodd = x'y'z + x'yz' + xy'z' + xyz$$

$$fodd = x \oplus y \oplus z$$

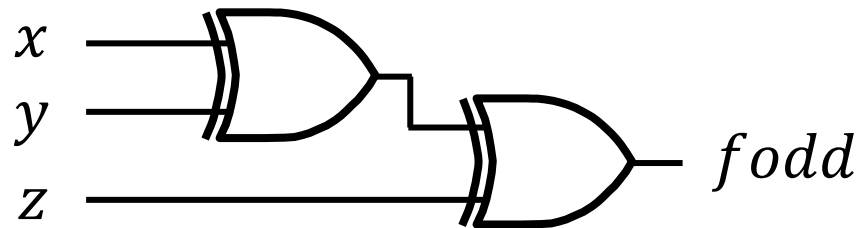

Implementation using two XOR gates

# Even Function


Even Function with 4 inputs

w	x	y	z	feven
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

- ❖ Output is 1 if the **number of 1's is even** in the inputs (complement of odd function)
- ❖ Output is the XNOR operation on all inputs

$$feven = \sum (0, 3, 5, 6, 9, 10, 12, 15)$$
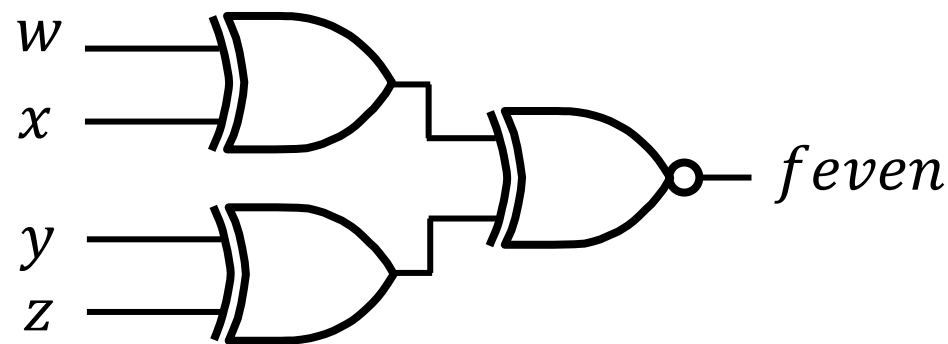
$$feven = (w \oplus x \oplus y \oplus z)'$$



Implementation using two XOR gates and one XNOR