

# Integer Multiplication and Division

COE 301

Computer Organization

Prof. Muhamed Mudawar

College of Computer Sciences and Engineering  
King Fahd University of Petroleum and Minerals

# Presentation Outline

- ❖ **Unsigned Integer Multiplication**
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS

# Unsigned Integer Multiplication

❖ Paper and Pencil Example:

$$\begin{array}{r} \text{Multiplicand} \quad 1100_2 = 12 \\ \text{Multiplier} \quad \times 1101_2 = 13 \\ \hline \phantom{0000} 1100 \\ \phantom{0000} 0000 \\ \phantom{00} 1100 \\ \phantom{00} 1100 \\ \hline \text{Product} \quad 10011100_2 = 156 \end{array}$$

Binary multiplication is easy  
 $0 \times \text{multiplicand} = 0$   
 $1 \times \text{multiplicand} = \text{multiplicand}$

- ❖ **n-bit multiplicand × n-bit multiplier = (2n)-bit product**
- ❖ Accomplished via **shifting** and **addition**
- ❖ Consumes more time and more chip area than addition

# Unsigned Sequential Multiplication

- ❖ Initialize Product = 0
- ❖ Check each bit of the Multiplier
- ❖ If Multiplier bit = 1 then **Product = Product + Multiplicand**
- ❖ Rather than shifting the multiplicand to the left,

**Shift the Product to the Right**



Has the same net effect and produces the same result

Minimizes the hardware resources

- ❖ One cycle per iteration (for each bit of the Multiplier)
  - ✧ Addition and shifting can be done simultaneously
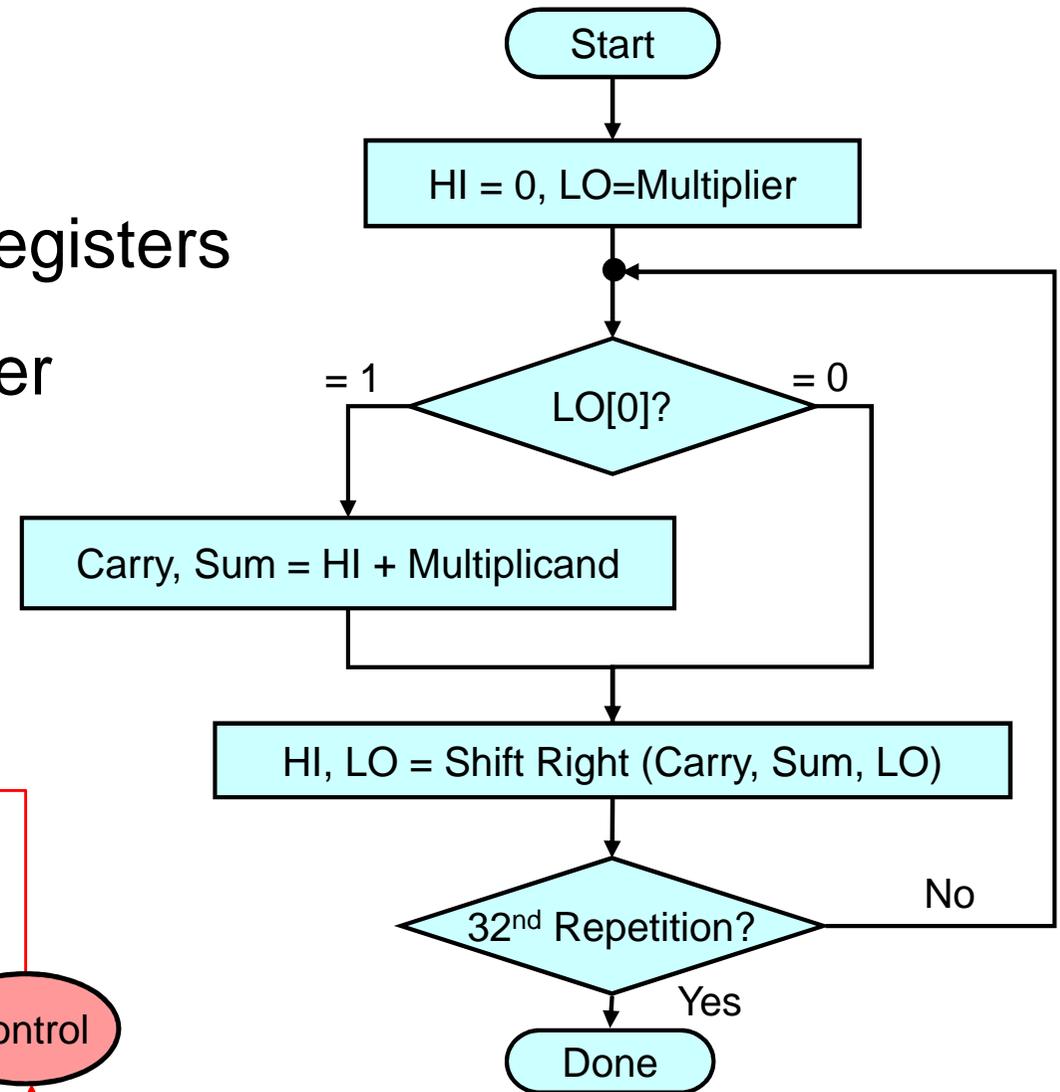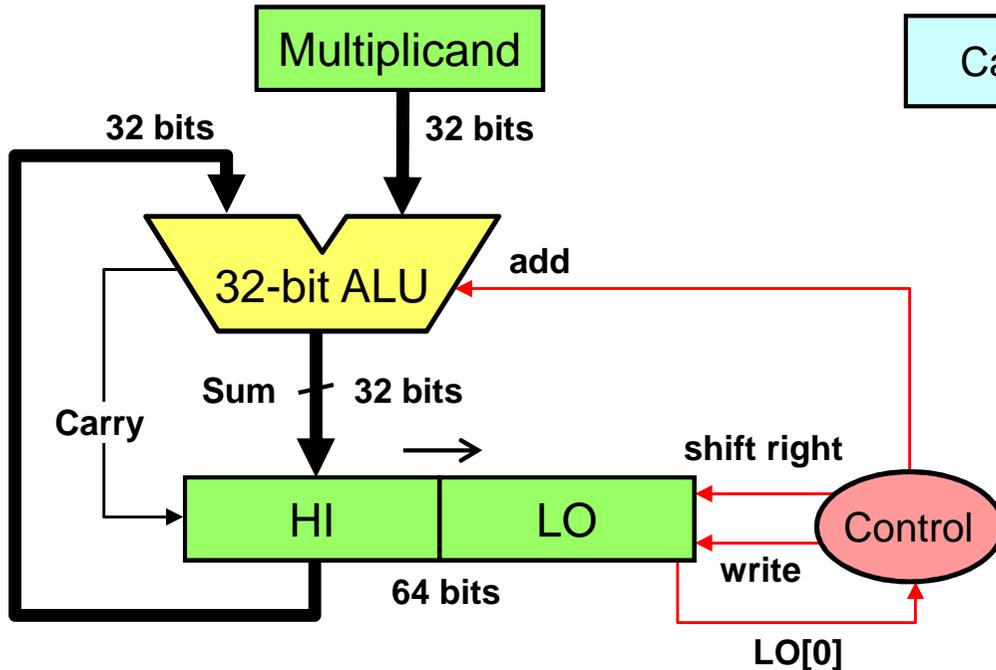
# Unsigned Sequential Multiplier

- ❖ Initialize: **HI = 0**
- ❖ Initialize: **LO = Multiplier**
- ❖ **Final Product** in **HI** and **LO** registers
- ❖ Repeat for each bit of Multiplier



# Sequential Multiplier Example

- ❖ Consider:  $1100_2 \times 1101_2$  , Product =  $10011100_2$
- ❖ 4-bit multiplicand and multiplier are used in this example
- ❖ 4-bit adder produces a **4-bit Sum + Carry bit**

Iteration		Multiplicand	Carry	Product = HI, LO
0	Initialize (HI = 0, LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 <b>1</b>
1	LO[0] = <b>1</b> => <b>ADD</b>		<b>0</b>	<b>1 1 0 0</b> 1 1 0 1
	Shift Right (Carry, Sum, LO) by 1 bit	1 1 0 0		<b>0 1 1 0</b> <b>0 1 1 0</b>
2	LO[0] = <b>0</b> => NO addition			
	Shift Right (HI, LO) by 1 bit	1 1 0 0		<b>0 0 1 1</b> <b>0 0 1 1</b>
3	LO[0] = <b>1</b> => <b>ADD</b>		<b>0</b>	<b>1 1 1 1</b> <b>0 0 1 1</b>
	Shift Right (Carry, Sum, LO) by 1 bit	1 1 0 0		<b>0 1 1 1</b> <b>1 0 0 1</b>
4	LO[0] = <b>1</b> => <b>ADD</b>		<b>1</b>	<b>0 0 1 1</b> <b>1 0 0 1</b>
	Shift Right (Carry, Sum, LO) by 1 bit	1 1 0 0		<b>1 0 0 1</b> <b>1 1 0 0</b>

# Next . . .

- ❖ Unsigned Integer Multiplication
- ❖ **Signed Integer Multiplication**
- ❖ Faster Integer Multiplication
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS

# Signed Integer Multiplication

## ❖ First attempt:

- ❖ Convert multiplier and multiplicand into positive numbers
  - If negative then obtain the 2's complement and remember the sign
- ❖ Perform unsigned multiplication
- ❖ Compute the sign of the product
- ❖ If product sign  $< 0$  then obtain the 2's complement of the product
- ❖ Drawback: additional steps to compute the 2's complement

## ❖ Better version:

- ❖ Use the unsigned multiplication hardware
- ❖ When shifting right, **extend the sign** of the product
- ❖ If multiplier is negative, the **last step** should be a **subtract**

# Signed Multiplication (Paper & Pencil)

## ❖ Case 1: Positive Multiplier

Multiplicand  $1100_2 = -4$

Multiplier  $\times 0101_2 = +5$

Sign-extension  $\left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \end{array} \right.$

Product  $11101100_2 = -20$

## ❖ Case 2: Negative Multiplier

Multiplicand  $1100_2 = -4$

Multiplier  $\times 1101_2 = -3$



Sign-extension  $\left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \end{array} \right.$

$00100$  (2's complement of 1100)

Product  $00001100_2 = +12$
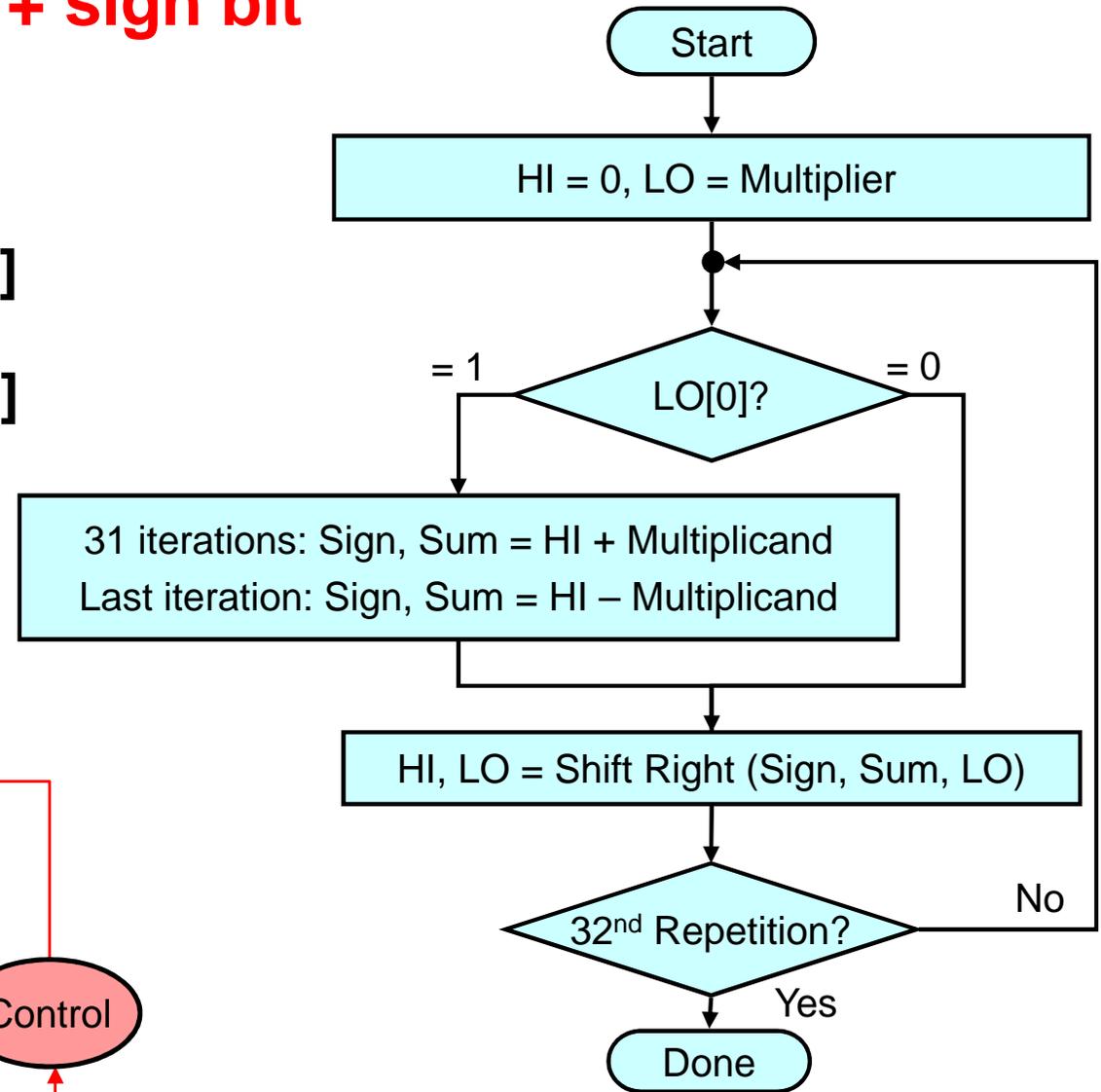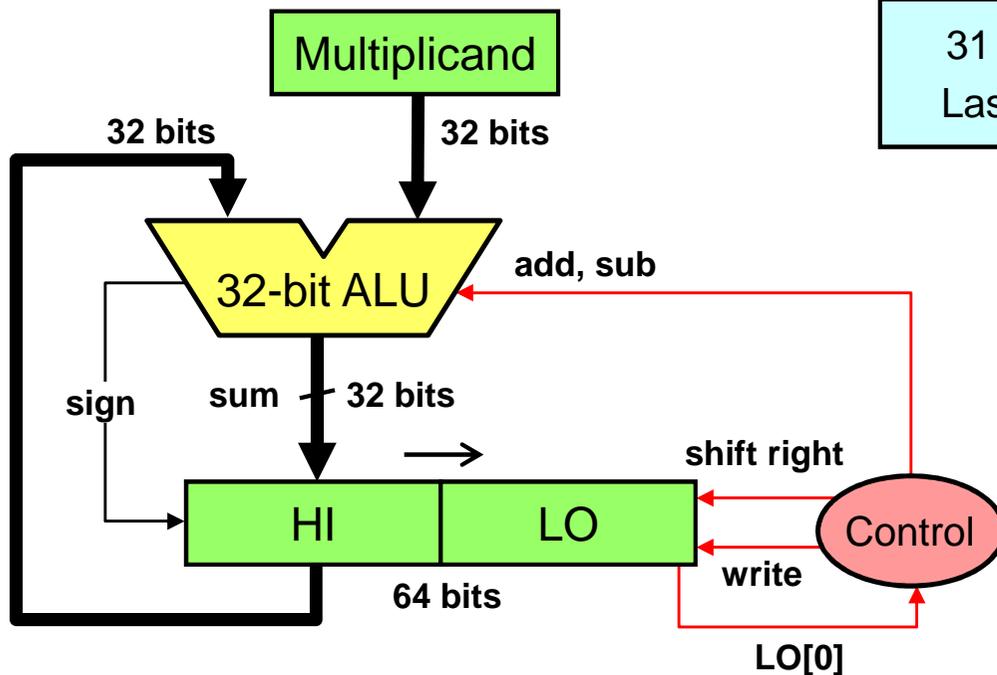
# Signed Sequential Multiplier

- ❖ ALU produces: **32-bit sum + sign bit**
- ❖ Sign bit can be computed:
  - ✧ No overflow:  $\text{sign} = \text{sum}[31]$
  - ✧ If Overflow:  $\text{sign} = \sim \text{sum}[31]$



# Signed Multiplication Example

- ❖ Consider:  $1100_2$  (-4)  $\times$   $1101_2$  (-3), Product =  $00001100_2$
- ❖ Check for overflow: No overflow  $\rightarrow$  Extend sign bit
- ❖ Last iteration: add 2's complement of Multiplicand


Iteration		Multiplicand	Sign	Product = HI, LO
0	Initialize (HI = 0, LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 <b>1</b>
1	LO[0] = <b>1</b> $\Rightarrow$ ADD	1 1 0 0	<b>1</b>	<b>1 1 0 0</b> 1 1 0 1
	Shift Right (Sign, Sum, LO) by 1 bit	1 1 0 0		<b>1 1 1 0</b> <b>0 1 1 0</b>
2	LO[0] = <b>0</b> $\Rightarrow$ NO addition			
	Shift Right (Sign, HI, LO) by 1 bit	1 1 0 0		<b>1 1 1 1</b> <b>0 0 1 1</b>
3	LO[0] = <b>1</b> $\Rightarrow$ ADD	1 1 0 0	<b>1</b>	<b>1 0 1 1</b> <b>0 0 1 1</b>
	Shift Right (Sign, Sum, LO) by 1 bit	1 1 0 0		<b>1 1 0 1</b> <b>1 0 0 1</b>
4	LO[0] = <b>1</b> $\Rightarrow$ SUB (ADD 2's compl)	<b>0 1 0 0</b>	<b>0</b>	<b>0 0 0 1</b> <b>1 0 0 1</b>
	Shift Right (Sign, Sum, LO) by 1 bit			<b>0 0 0 0</b> <b>1 1 0 0</b>

# Next . . .

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ **Faster Integer Multiplication**
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS
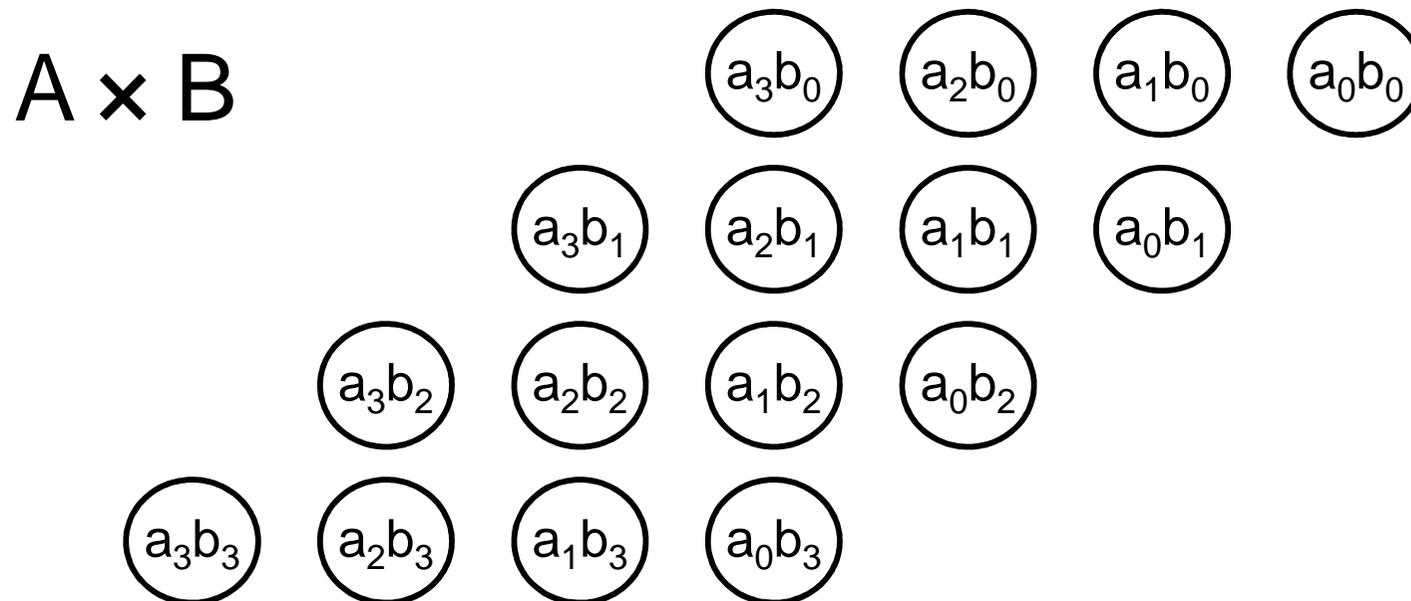
# Faster Multiplier


- ❖ Suppose we want to multiply two numbers A and B
  - ✧ Example on 4-bit numbers:  $A = a_3 a_2 a_1 a_0$  and  $B = b_3 b_2 b_1 b_0$
- ❖ Step 1: AND (multiply) each bit of A with each bit of B
  - ✧ Requires  $n^2$  AND gates and produces  $n^2$  product bits
  - ✧ Position of  $a_i b_j = (i+j)$ . For example, Position of  $a_2 b_3 = 2+3 = 5$



# Adding the Partial Products

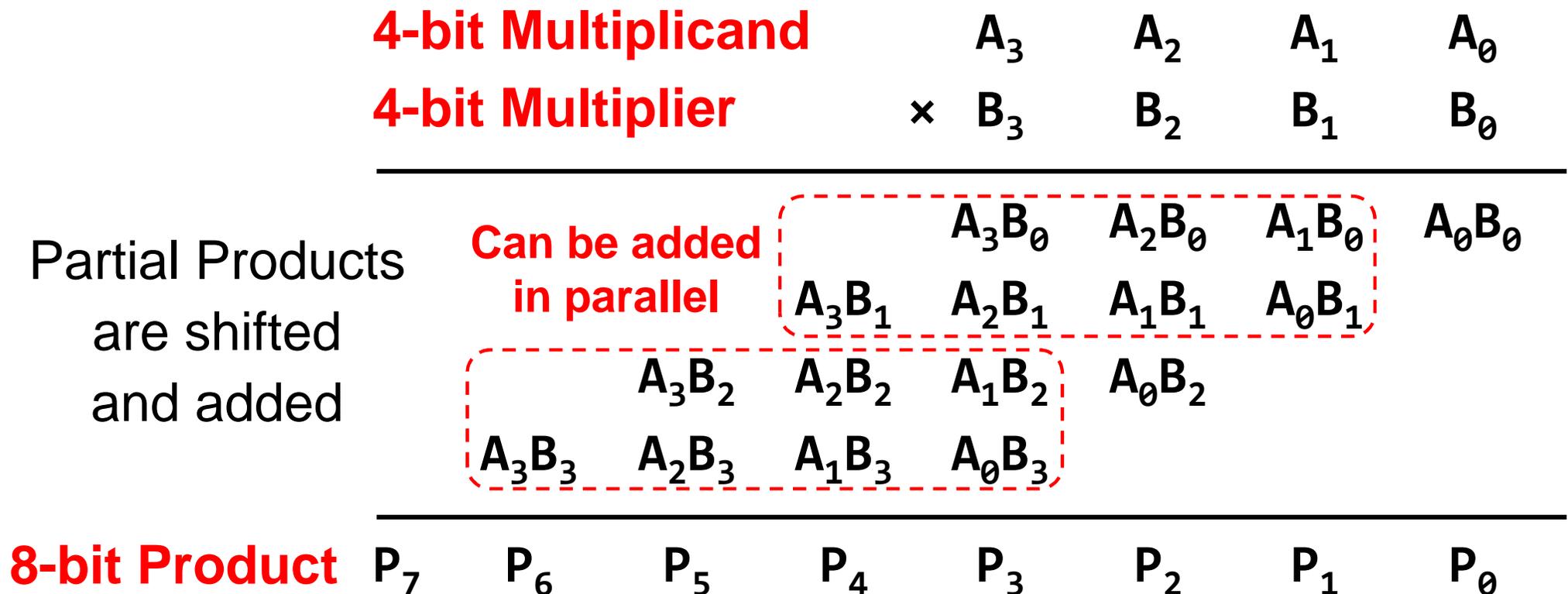
## ❖ Step 2: Add the partial products

- ❖ The partial products are shifted and added to compute the product P
- ❖ The partial products can be added in parallel
- ❖ Different implementations are possible



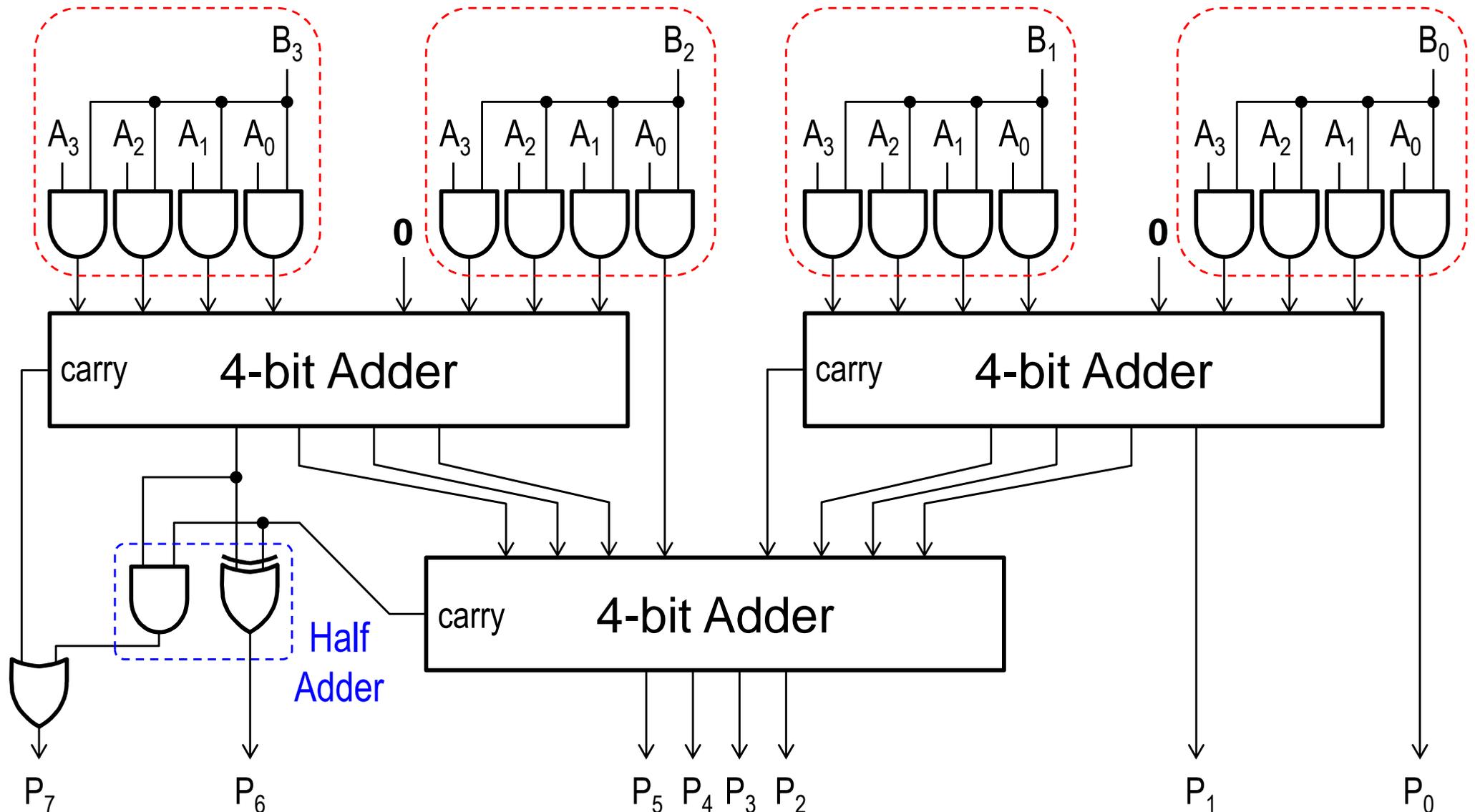
# 4-bit × 4-bit Binary Multiplier

**16** AND gates, **Three** 4-bit adders, a half-adder, and an OR gate



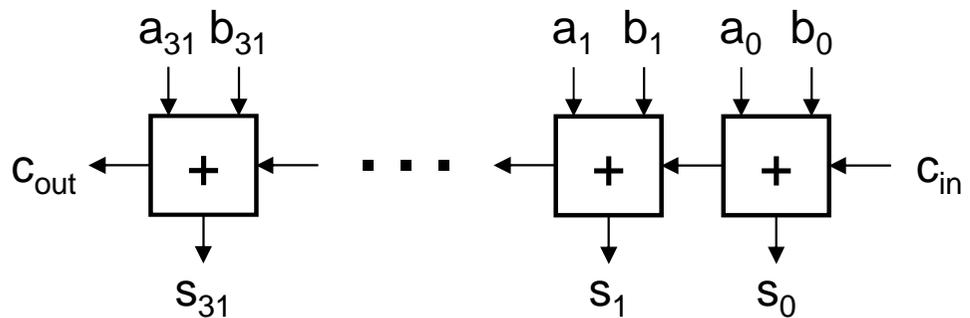
# Carry Save Adders

- ❖ A n-bit carry-save adder produces two n-bit outputs
  - ✧ n-bit partial sum bits and n-bit carry bits
- ❖ All the n bits of a carry-save adder work in parallel
  - ✧ The carry does not propagate as in a carry-propagate adder
  - ✧ This is why a carry-save is faster than a carry-propagate adder
- ❖ Useful when adding multiple numbers (as in multipliers)




Carry-Propagate Adder

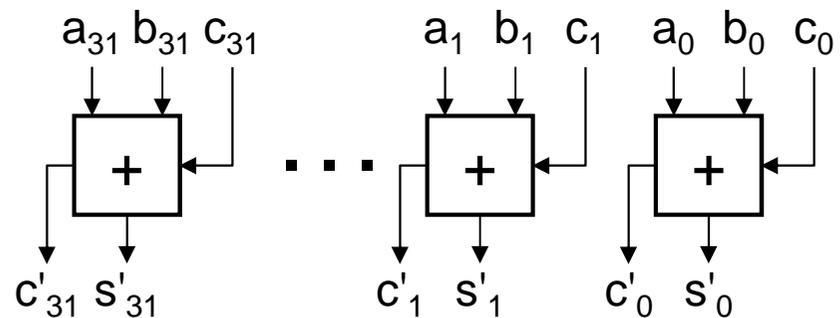

Carry-Save Adder
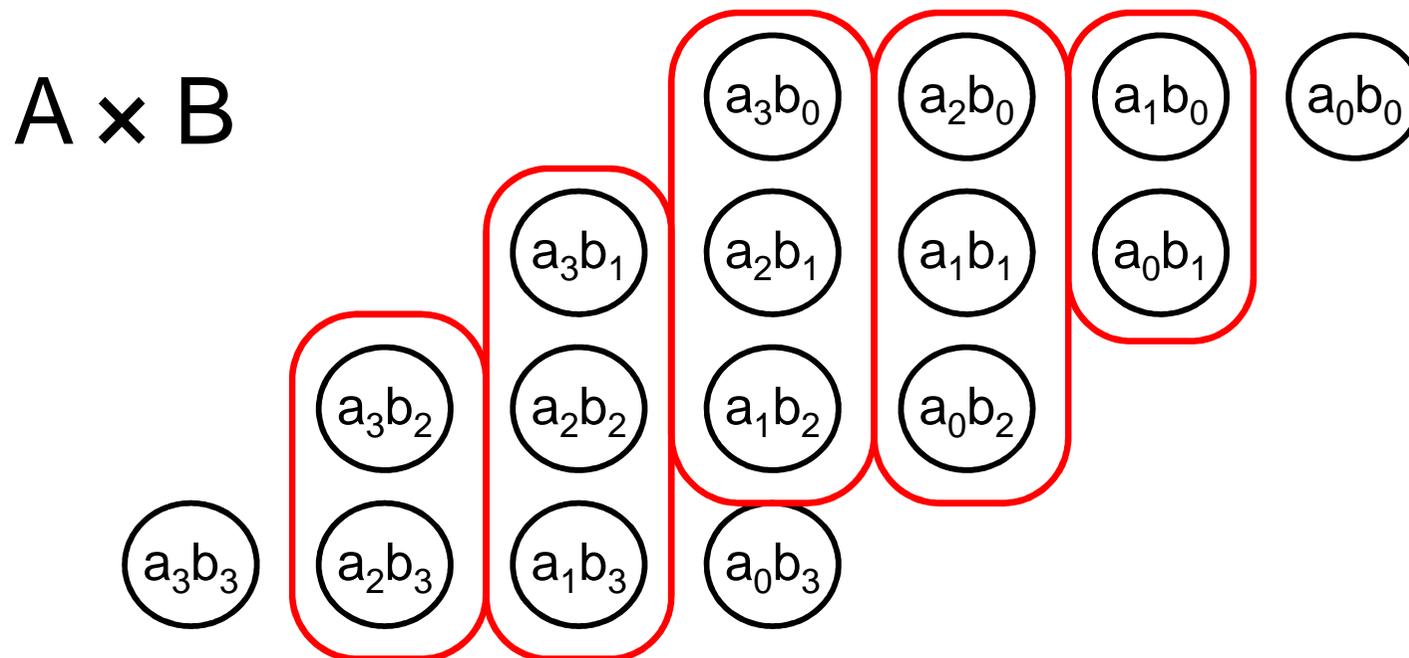
# Carry-Save Adders in a Multiplier

- ❖ ADD the product bits vertically using **Carry-Save adders**
  - ✧ Full Adder adds three vertical bits
  - ✧ Half Adder adds two vertical bits
  - ✧ Each adder produces a partial sum and a carry
- ❖ Use **Carry-propagate adder** for final addition




# Carry-Save Adders in a Multiplier

Step 1: Use **carry save adders** to add the partial products

✧ Reduce the partial products to just two numbers

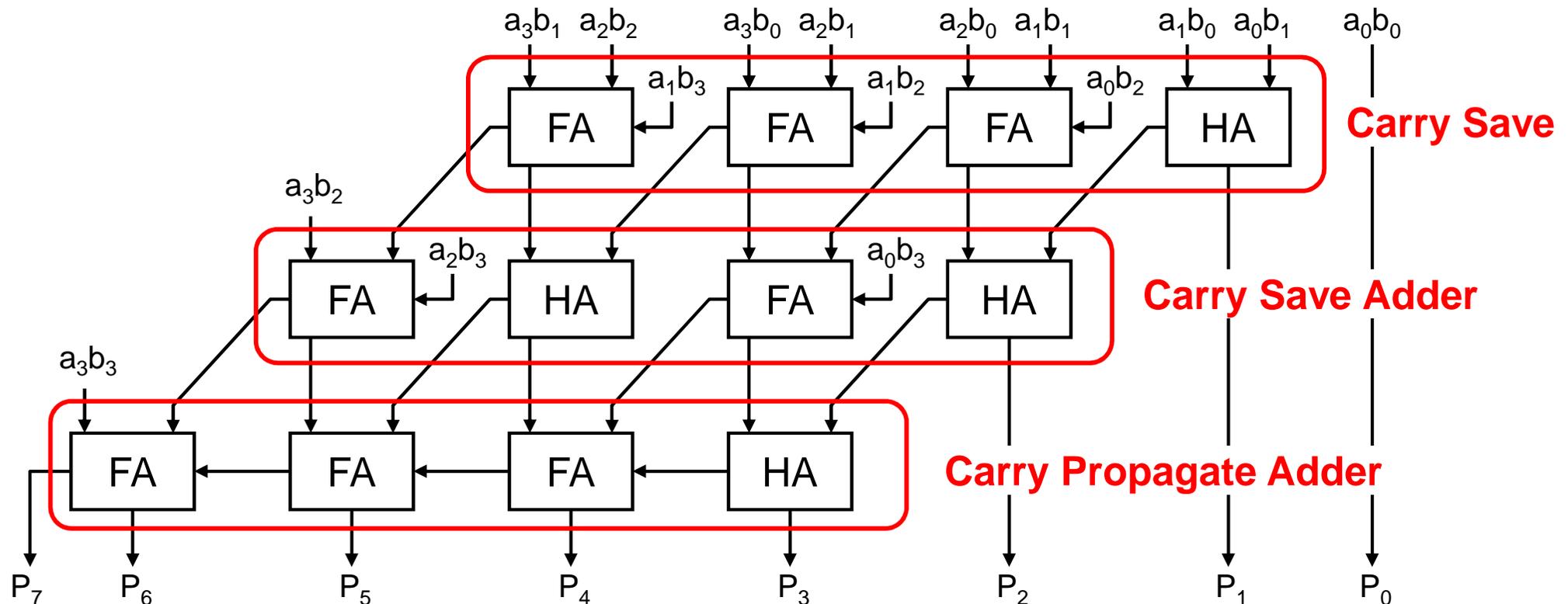Step 2: Use **carry-propagate adder** to add last two numbers



# Summary of a Fast Multiplier

- ❖ A fast  $n$ -bit  $\times$   $n$ -bit multiplier requires:
  - ✧  $n^2$  AND gates to produce  $n^2$  product bits in parallel
  - ✧ Many adders to perform additions in parallel
- ❖ Uses carry-save adders to reduce delays
- ❖ Higher cost (more chip area) than sequential multiplier
- ❖ Higher performance (faster) than sequential multiplier

# Next . . .

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ **Integer Division**
- ❖ Integer Multiplication and Division in MIPS

# Unsigned Division (Paper & Pencil)

$$\begin{array}{r}
 \text{Divisor } 1011_2 \bigg) \overline{11011001_2} \\
 \text{Quotient } 10011_2 = 19 \\
 \text{Dividend } 11011001_2 = 217
 \end{array}$$

$$\begin{array}{r}
 \text{---} \\
 -1011 \\
 \text{---} \\
 10 \\
 101 \\
 1010 \\
 10100 \\
 -1011 \\
 \text{---} \\
 1001 \\
 10011 \\
 -1011 \\
 \text{---} \\
 1000_2 = 8
 \end{array}$$

Check how big a number can be subtracted, creating a bit of the quotient on each attempt

Binary division is done via **shifting** and **subtraction**

Dividend =  
 Quotient × Divisor  
 + Remainder  
 217 = 19 × 11 + 8

**Remainder**

# Sequential Division

- ❖ Uses two registers: HI and LO
- ❖ Initialize: HI = Remainder = 0 and LO = Dividend
- ❖ Shift (HI, LO) LEFT by 1 bit (also Shift Quotient LEFT)
  - ❖ Shift the remainder and dividend registers together LEFT
  - ❖ Has the same net effect of shifting the divisor RIGHT
- ❖ Compute: Difference = Remainder – Divisor
- ❖ If (Difference  $\geq$  0) then
  - ❖ Remainder = Difference
  - ❖ Set Least significant Bit of Quotient
- ❖ Observation to Reduce Hardware:
  - ❖ LO register can be also used to store the computed Quotient

# Sequential Division Hardware



## ❖ Initialize:

❖  $HI = 0$ ,  $LO = \text{Dividend}$

## ❖ Results:

❖  $HI = \text{Remainder}$

❖  $LO = \text{Quotient}$

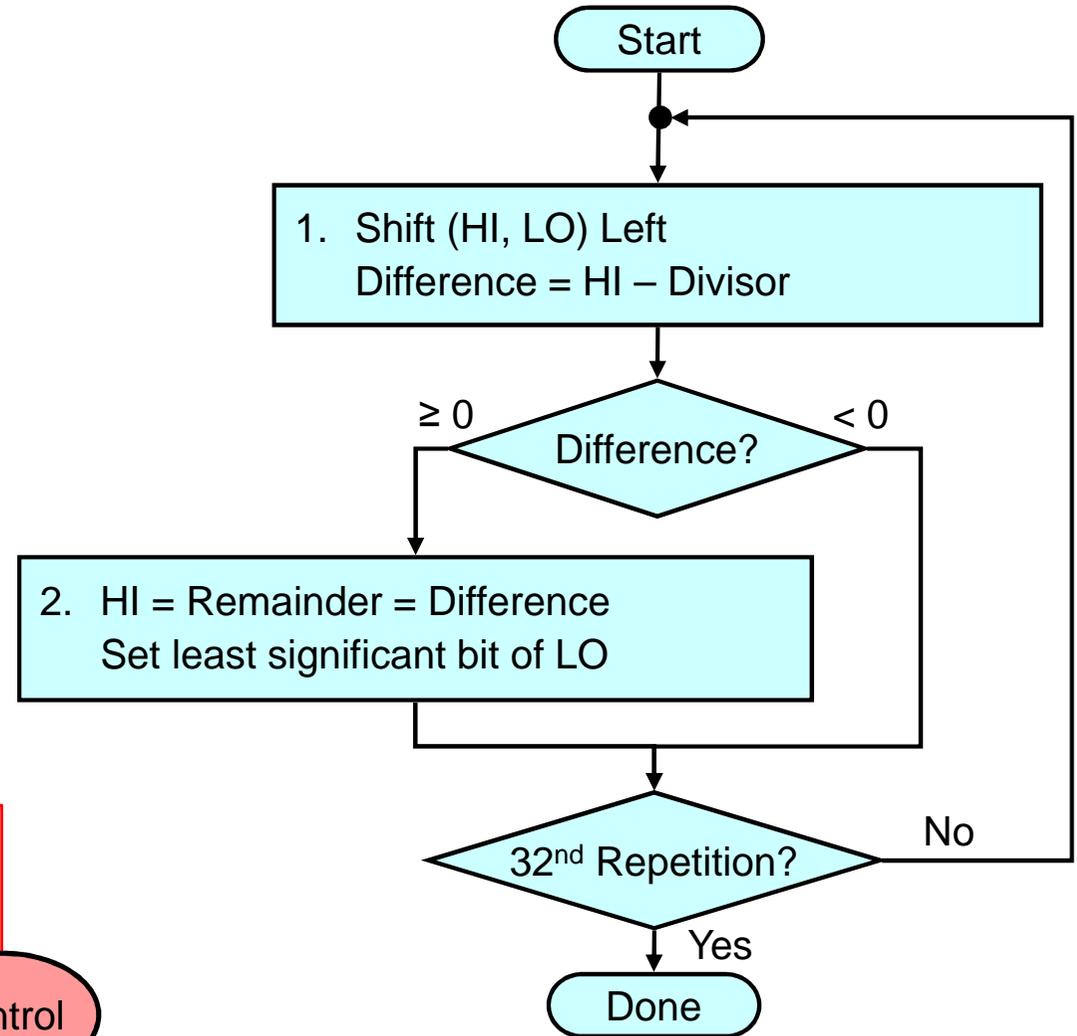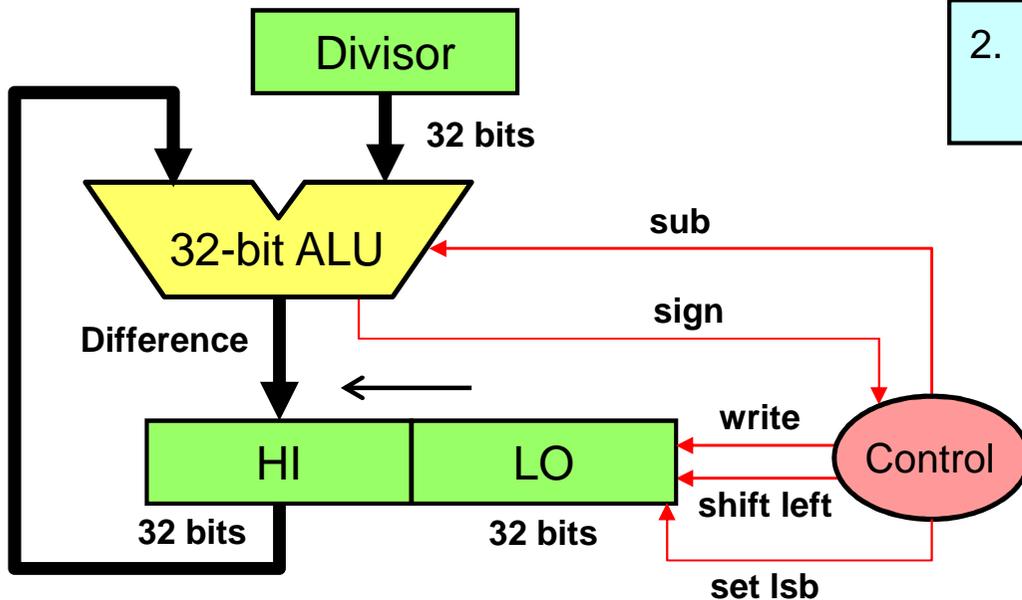

# Unsigned Integer Division Example

- ❖ Example:  $1110_2 / 0100_2$  (4-bit dividend & divisor)
- ❖ Result Quotient =  $0011_2$  and Remainder =  $0010_2$
- ❖ 4-bit registers for Remainder and Divisor (4-bit ALU)

Iteration		HI	LO	Divisor	Difference
0	Initialize	0 0 0 0	1 1 1 0	0 1 0 0	
1	Shift Left, Diff = HI - Divisor	0 0 0 1 ←	1 1 0 0	0 1 0 0	< 0
	Diff < 0 => Do Nothing				
2	Shift Left, Diff = HI - Divisor	0 0 1 1 ←	1 0 0 0	0 1 0 0	< 0
	Diff < 0 => Do Nothing				
3	Shift Left, Diff = HI - Divisor	0 1 1 1 ←	0 0 0 0	0 1 0 0	0 0 1 1
	HI = Diff, set <b>lsb</b> of LO	0 0 1 1	0 0 0 1		
4	Shift Left, Diff = HI - Divisor	0 1 1 0 ←	0 0 1 0	0 1 0 0	0 0 1 0
	HI = Diff, set <b>lsb</b> of LO	0 0 1 0	0 0 1 1		

# Signed Integer Division

- ❖ Simplest way is to remember the signs
- ❖ Convert the dividend and divisor to positive
  - ✧ Obtain the 2's complement if they are negative
- ❖ Do the unsigned division
- ❖ Compute the signs of the quotient and remainder
  - ✧ Quotient sign = Dividend sign XOR Divisor sign
  - ✧ Remainder sign = Dividend sign
- ❖ Negate the quotient and remainder if their sign is negative
  - ✧ Obtain the 2's complement to convert them to negative

# Signed Integer Division Examples

## 1. **Positive** Dividend and **Positive** Divisor

✧ Example:  $+17 / +3$       Quotient =  $+5$     Remainder =  $+2$

## 2. **Positive** Dividend and **Negative** Divisor

✧ Example:  $+17 / -3$       Quotient =  $-5$     Remainder =  $+2$

## 3. **Negative** Dividend and **Positive** Divisor

✧ Example:  $-17 / +3$       Quotient =  $-5$     Remainder =  $-2$

## 4. **Negative** Dividend and **Negative** Divisor

✧ Example:  $-17 / -3$       Quotient =  $+5$     Remainder =  $-2$

The following equation must always hold:

$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$

# Next . . .

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ Integer Division
- ❖ **Integer Multiplication and Division in MIPS**

# Integer Multiplication in MIPS

## ❖ Multiply instructions

❖ `mult Rs, Rt`      **Signed multiplication**

❖ `multu Rs, Rt`      **Unsigned multiplication**

## ❖ 32-bit multiplication produces a 64-bit Product

## ❖ Separate pair of 32-bit registers

❖ **HI = high-order 32-bit of product**


❖ **LO = low-order 32-bit of product**

## ❖ MIPS also has a special `mul` instruction

❖ `mul Rd, Rs, Rt`       **$Rd = Rs \times Rt$**

❖ Copy **LO** into destination register **Rd**

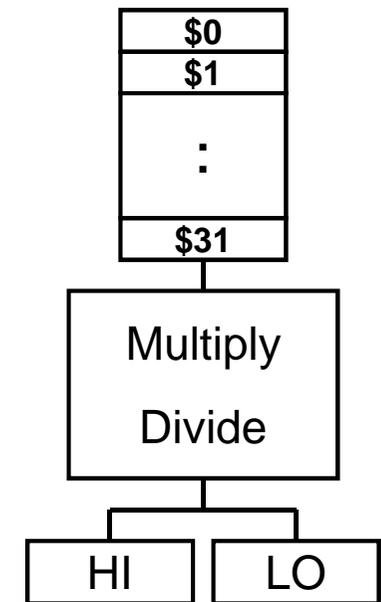❖ Useful when the product is small (32 bits) and **HI** is not needed



# Integer Division in MIPS

## ❖ Divide instructions

❖ `div Rs, Rt`                      **Signed division**

❖ `divu Rs, Rt`                      **Unsigned division**

## ❖ Division produces quotient and remainder

## ❖ Separate pair of 32-bit registers

❖ **HI = 32-bit remainder**


❖ **LO = 32-bit quotient**

❖ If divisor is 0 then result is **unpredictable**

## ❖ Moving data from **HI**, **LO** to MIPS registers

❖ `mfhi Rd` ( $Rd = HI$ )

❖ `mflo Rd` ( $Rd = LO$ )

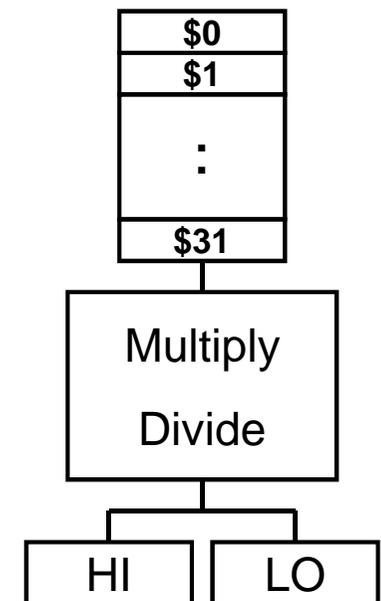

# Integer Multiply and Divide Instructions

Instruction		Meaning	Format					
<code>mult</code>	<code>Rs, Rt</code>	$HI, LO = Rs \times_s Rt$	$Op = 0$	<code>Rs</code>	<code>Rt</code>	<code>0</code>	<code>0</code>	<code>0x18</code>
<code>multu</code>	<code>Rs, Rt</code>	$HI, LO = Rs \times_u Rt$	$Op = 0$	<code>Rs</code>	<code>Rt</code>	<code>0</code>	<code>0</code>	<code>0x19</code>
<code>mul</code>	<code>Rd, Rs, Rt</code>	$Rd = Rs \times_s Rt$	<code>0x1c</code>	<code>Rs</code>	<code>Rt</code>	<code>Rd</code>	<code>0</code>	<code>2</code>
<code>div</code>	<code>Rs, Rt</code>	$HI, LO = Rs /_s Rt$	$Op = 0$	<code>Rs</code>	<code>Rt</code>	<code>0</code>	<code>0</code>	<code>0x1a</code>
<code>divu</code>	<code>Rs, Rt</code>	$HI, LO = Rs /_u Rt$	$Op = 0$	<code>Rs</code>	<code>Rt</code>	<code>0</code>	<code>0</code>	<code>0x1b</code>
<code>mfhi</code>	<code>Rd</code>	$Rd = HI$	$Op = 0$	<code>0</code>	<code>0</code>	<code>Rd</code>	<code>0</code>	<code>0x10</code>
<code>mflo</code>	<code>Rd</code>	$Rd = LO$	$Op = 0$	<code>0</code>	<code>0</code>	<code>Rd</code>	<code>0</code>	<code>0x12</code>
<code>mthi</code>	<code>Rs</code>	$HI = Rs$	$Op = 0$	<code>Rs</code>	<code>0</code>	<code>0</code>	<code>0</code>	<code>0x11</code>
<code>mtlo</code>	<code>Rs</code>	$LO = Rs$	$Op = 0$	<code>Rs</code>	<code>0</code>	<code>0</code>	<code>0</code>	<code>0x13</code>

$\times_s$  = Signed multiplication,       $\times_u$  = Unsigned multiplication

$/_s$  = Signed division,       $/_u$  = Unsigned division

**NO arithmetic exception** can occur

# String to Integer Conversion

- ❖ Consider the conversion of string "91052" into an integer

'9'	'1'	'0'	'5'	'2'
-----	-----	-----	-----	-----

- ❖ How to convert the string into an integer?
- ❖ Initialize: **sum = 0**
- ❖ Load each character of the string into a register
  - ✧ Check if the character is in the range: '0' to '9'
  - ✧ Convert the character into a **digit** in the range: 0 to 9
  - ✧ Compute: **sum = sum \* 10 + digit**
  - ✧ Repeat until end of string or a non-digit character is encountered
- ❖ To convert "91052", initialize sum to 0 then ...
  - ✧ sum = 9, then 91, then 910, then 9105, then 91052

# String to Integer Conversion Function

```
#-----  
# str2int: Convert a string of digits into unsigned integer  
# Input:   $a0 = address of null terminated string  
# Output:  $v0 = unsigned integer value  
#-----  
str2int:  
    li    $v0, 0           # Initialize: $v0 = sum = 0  
    li    $t0, 10          # Initialize: $t0 = 10  
L1:   lb   $t1, 0($a0)     # load $t1 = str[i]  
      blt $t1, '0', done   # exit loop if ($t1 < '0')  
      bgt $t1, '9', done   # exit loop if ($t1 > '9')  
      addiu $t1, $t1, -48  # Convert character to digit  
      mul  $v0, $v0, $t0   # $v0 = sum * 10  
      addu $v0, $v0, $t1   # $v0 = sum * 10 + digit  
      addiu $a0, $a0, 1   # $a0 = address of next char  
      j    L1             # loop back  
done: jr   $ra            # return to caller
```

# Integer to String Conversion

- ❖ Convert an unsigned 32-bit integer into a string
- ❖ How to obtain the decimal digits of the number?
  - ✧ Divide the number by 10, Remainder = decimal digit (0 to 9)
  - ✧ Convert decimal digit into its ASCII representation ('0' to '9')
  - ✧ Repeat the division until the quotient becomes zero
  - ✧ Digits are computed **backwards** from least to most significant
- ❖ Example: convert 2037 to a string
  - ✧ Divide 2037/10    quotient = 203    remainder = 7    char = '7'
  - ✧ Divide 203/10    quotient = 20    remainder = 3    char = '3'
  - ✧ Divide 20/10    quotient = 2    remainder = 0    char = '0'
  - ✧ Divide 2/10    quotient = 0    remainder = 2    char = '2'

# Integer to String Conversion Function

```
#-----  
# int2str:  Converts an unsigned integer into a string  
# Input:   $a0 = value, $a1 = buffer address (12 bytes)  
# Output:  $v0 = address of converted string in buffer  
#-----  
int2str:  
    li      $t0, 10          # $t0 = divisor = 10  
    addiu  $v0, $a1, 11     # start at end of buffer  
    sb     $zero, 0($v0)    # store a NULL character  
L2:   divu   $a0, $t0        # L0 = value/10, HI = value%10  
    mflo   $a0              # $a0 = value/10  
    mfhi   $t1              # $t1 = value%10  
    addiu  $t1, $t1, 48     # convert digit into ASCII  
    addiu  $v0, $v0, -1    # point to previous byte  
    sb     $t1, 0($v0)     # store character in memory  
    bnez   $a0, L2         # loop if value is not 0  
    jr     $ra             # return to caller
```