

# Integer Multiplication and Division

ICS 233

Computer Architecture & Assembly Language

Prof. Muhamed Mudawar

College of Computer Sciences and Engineering

King Fahd University of Petroleum and Minerals

## Presentation Outline

- ❖ **Unsigned Integer Multiplication**
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS

## Unsigned Integer Multiplication

- ❖ Paper and Pencil Example:

**Multiplicand**             $1100_2 = 12$   
**Multiplier**             $\times 1101_2 = 13$

```

      1100
      0000
      1100
      1100
      -----

```

Binary multiplication is easy

$0 \times \text{multiplicand} = 0$

$1 \times \text{multiplicand} = \text{multiplicand}$

**Product**             $10011100_2 = 156$



- ❖  $m$ -bit multiplicand  $\times$   $n$ -bit multiplier =  $(m+n)$ -bit product
- ❖ Accomplished via **shifting** and **addition**
- ❖ Consumes more time and more chip area than addition

## Sequential Unsigned Multiplication

- ❖ Initialize Product = 0
- ❖ Check each bit of the Multiplier
- ❖ If Multiplier bit = 1 then **Product = Product + Multiplicand**
- ❖ Rather than shifting the multiplicand to the left  
 Instead, **Shift the Product to the Right**  
 Has the same net effect and produces the same result  
 Minimizes the hardware resources
- ❖ One cycle per iteration (for each bit of the Multiplier)
  - ❖ Addition and shifting can be done simultaneously
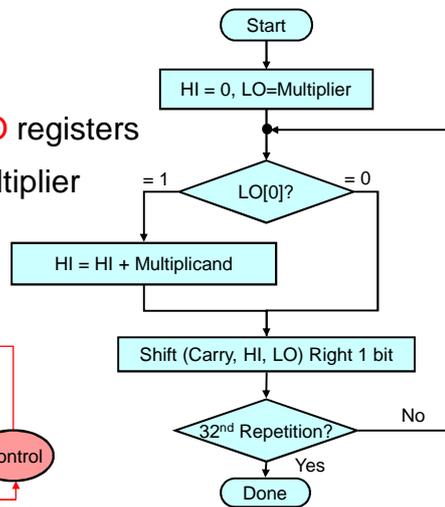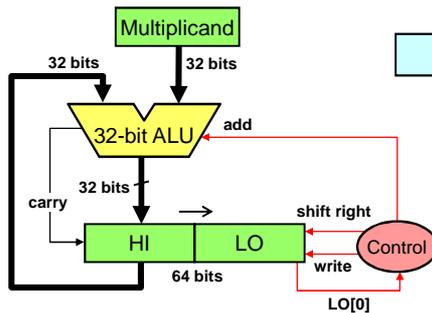
## Sequential Multiplication Hardware

- ❖ Initialize HI = 0
- ❖ Initialize LO = Multiplier
- ❖ Final Product = HI and LO registers
- ❖ Repeat for each bit of Multiplier



Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 5

## Sequential Multiplier Example

- ❖ Consider:  $1100_2 \times 1101_2$ , Product =  $10011100_2$
- ❖ 4-bit multiplicand and multiplier are used in this example
- ❖ 4-bit adder produces a 5-bit sum (with carry)

Iteration		Multiplicand	Carry	Product = HI, LO
0	Initialize (HI = 0, LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 1
1	LO[0] = 1 => ADD		0	1 1 0 0 1 1 0 1
	Shift Right (Carry, HI, LO) by 1 bit	1 1 0 0		0 1 1 0 0 1 1 0
2	LO[0] = 0 => Do Nothing			
	Shift Right (Carry, HI, LO) by 1 bit	1 1 0 0		0 0 1 1 0 0 1 1
3	LO[0] = 1 => ADD		0	1 1 1 1 0 0 1 1
	Shift Right (Carry, HI, LO) by 1 bit	1 1 0 0		0 1 1 1 1 0 0 1
4	LO[0] = 1 => ADD		1	0 0 1 1 1 0 0 1
	Shift Right (Carry, HI, LO) by 1 bit	1 1 0 0		1 0 0 1 1 1 0 0

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 6

## Next ...

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS

## Signed Integer Multiplication

- ❖ So far, we have dealt with unsigned integer multiplication
- ❖ First Attempt:
  - ❖ Convert multiplier and multiplicand into positive numbers
    - If negative then obtain the 2's complement and remember the sign
  - ❖ Perform unsigned multiplication
  - ❖ Compute the sign of the product
  - ❖ If product sign < 0 then obtain the 2's complement of the product
- ❖ Better Version:
  - ❖ Use the unsigned multiplication hardware
  - ❖ When shifting right, **extend the sign** of the product
  - ❖ If multiplier is negative, the **last step** should be a **subtract**

## Signed Multiplication (Pencil & Paper)

### ❖ Case 1: Positive Multiplier

Multiplicand  $1100_2 = -4$   
 Multiplier  $\times 0101_2 = +5$

Sign-extension  $\left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \end{array} \right.$

Product  $11101100_2 = -20$

### ❖ Case 2: Negative Multiplier

Multiplicand  $1100_2 = -4$   
 Multiplier  $\times 1101_2 = -3$

Sign-extension  $\left\{ \begin{array}{l} \rightarrow 11111100 \\ \rightarrow 111100 \end{array} \right.$

$00100$  (2's complement of 1100)

Product  $00001100_2 = +12$

Integer Multiplication and Division

ICS 233 – KFUPM



© Muhamed Mudawar – slide 9

## Sequential Signed Multiplier

### ❖ ALU produces 32-bit result + Sign bit
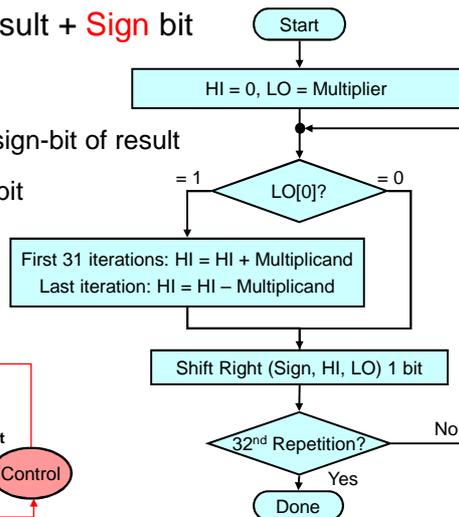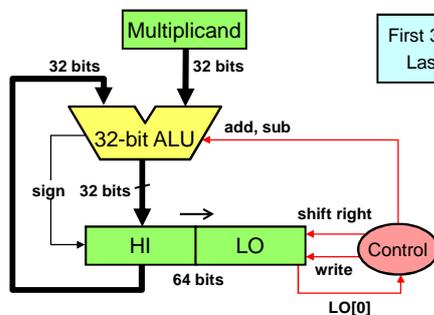
### ❖ Check for overflow

- ❖ No overflow  $\rightarrow$  Extend sign-bit of result
- ❖ Overflow  $\rightarrow$  Invert sign bit



Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 10

## Signed Multiplication Example

- ❖ Consider:  $1100_2$  (-4)  $\times$   $1101_2$  (-3), Product =  $00001100_2$
- ❖ Check for overflow: No overflow  $\rightarrow$  Extend sign bit
- ❖ Last iteration: add 2's complement of Multiplicand

Iteration		Multiplicand	Sign	Product = HI, LO
0	Initialize (HI = 0, LO = Multiplier)	1 1 0 0		0 0 0 0 1 1 0 1
1	LO[0] = 1 $\Rightarrow$ ADD		+	1 1 1 0 0 1 1 0 1
	Shift (Sign, HI, LO) right 1 bit	1 1 0 0		1 1 1 0 0 1 1 0
2	LO[0] = 0 $\Rightarrow$ Do Nothing			
	Shift (Sign, HI, LO) right 1 bit	1 1 0 0		1 1 1 1 0 0 1 1
3	LO[0] = 1 $\Rightarrow$ ADD		+	1 0 1 1 0 0 1 1
	Shift (Sign, HI, LO) right 1 bit	1 1 0 0		1 1 0 1 1 0 0 1
4	LO[0] = 1 $\Rightarrow$ SUB (ADD 2's compl)	0 1 0 0	-	0 0 0 1 1 0 0 1
	Shift (Sign, HI, LO) right 1 bit			0 0 0 0 1 1 0 0

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 11

## Next ...

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ **Faster Integer Multiplication**
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS


Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 12
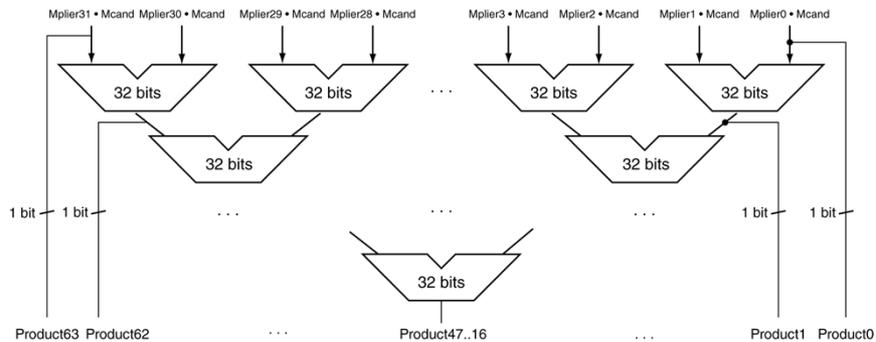
## Faster Integer Multiplier

❖ Uses Multiple Adders (Cost vs. Performance)



■ Can be pipelined

## Using Multiple Adders

❖ 32-bit adder for each bit of the multiplier

- ❖ AND multiplicand with each bit of multiplier
- ❖ Product = accumulated shifted sum

❖ Each adder produces a 33-bit output


- ❖ Most significant bit is a carry bit

❖ Array multiplier can be optimized

- ❖ Additions can be done in parallel
- ❖ Multiple-level tree reduction to produce final product
- ❖ Carry save adders reduce delays
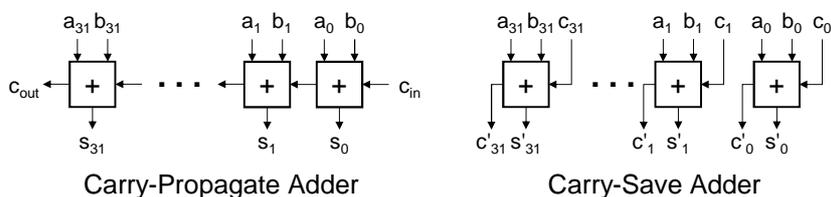
## Carry Save Adders

- ❖ Used when adding multiple numbers (as in multipliers)
- ❖ All the bits of a carry-save adder work in parallel
  - ❖ The carry does not propagate as in a carry-propagate adder
  - ❖ This is why a carry-save is faster than a carry-propagate adder
- ❖ A carry-save adder has 3 inputs and produces two outputs
  - ❖ It adds 3 numbers and produces partial sum and carry bits




Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 15
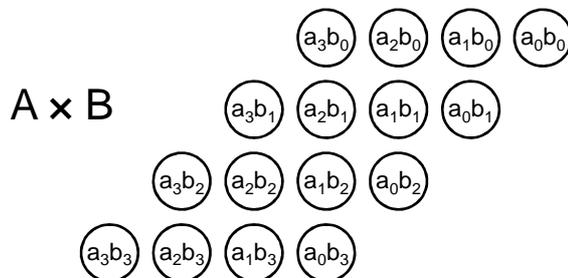
## Tree Multiplier - 1 of 2

- ❖ Suppose we want to multiply two numbers A and B
  - ❖ Example on 4-bit numbers:  $A = a_3 a_2 a_1 a_0$  and  $B = b_3 b_2 b_1 b_0$
- ❖ Step 1: AND (multiply) each bit of A with each bit of B
  - ❖ Requires  $n^2$  AND gates and produces  $n^2$  product bits
  - ❖ Position of  $a_i b_j = (i+j)$ . For example, Position of  $a_2 b_3 = 2+3 = 5$



Integer Multiplication and Division

ICS 233 – KFUPM


© Muhamed Mudawar – slide 16

## Tree Multiplier - 2 of 2

Step 2: Use **carry save adders** to add the partial products

✧ Reduce the partial products to just two numbers

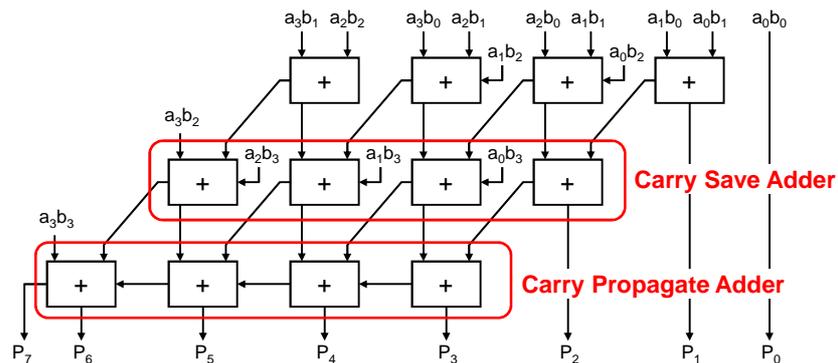Step 3: Add last two numbers using a **carry-propagate adder**



Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 17

## Next ...

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ Faster Integer Multiplication
- ❖ **Integer Division**
- ❖ Integer Multiplication and Division in MIPS

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 18

## Unsigned Division (Paper & Pencil)

$$\begin{array}{r}
 \text{Divisor } 1011_2 \quad ) \quad 11011001_2 \\
 \underline{-1011} \phantom{0000} \\
 10 \phantom{0000} \\
 \underline{101} \phantom{000} \\
 1010 \phantom{00} \\
 \underline{10100} \\
 -1011 \phantom{00} \\
 \underline{1001} \phantom{00} \\
 10011 \\
 \underline{-1011} \\
 1000_2
 \end{array}$$

$10011_2 = 19$     **Quotient**  
 $11011001_2 = 217$     **Dividend**  
 $1000_2 = 8$     **Remainder**

Dividend =  
 Quotient × Divisor  
 + Remainder  
 $217 = 19 \times 11 + 8$

Try to see how big a number can be subtracted, creating a digit of the quotient on each attempt



Binary division is accomplished via **shifting** and **subtraction**

## Sequential Division

- ❖ Uses two registers: HI and LO
- ❖ Initialize: HI = Remainder = 0 and LO = Dividend
- ❖ Shift (HI, LO) LEFT by 1 bit (also Shift Quotient LEFT)
  - ❖ Shift the remainder and dividend registers together LEFT
  - ❖ Has the same net effect of shifting the divisor RIGHT
- ❖ Compute: Difference = Remainder – Divisor
- ❖ If (Difference ≥ 0) then
  - ❖ Remainder = Difference
  - ❖ Set Least significant Bit of Quotient
- ❖ Observation to Reduce Hardware:
  - ❖ LO register can be also used to store the computed Quotient
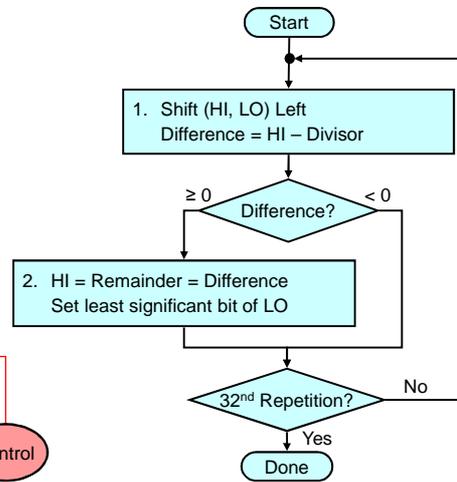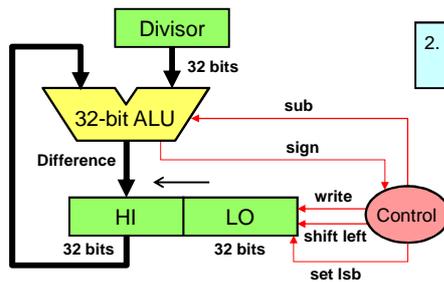
## Sequential Division Hardware

- ❖ Initialize:
  - ❖ HI = 0, LO = Dividend
- ❖ Results:
  - ❖ HI = Remainder
  - ❖ LO = Quotient



Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 21

## Unsigned Integer Division Example

- ❖ Example:  $1110_2 / 0011_2$  (4-bit dividend & divisor)
- ❖ Result Quotient =  $0100_2$  and Remainder =  $0010_2$
- ❖ 4-bit registers for Remainder and Divisor (4-bit ALU)

Iteration		HI	LO	Divisor	Difference
0	Initialize	0000	1110	0011	
1	1: Shift Left, Diff = HI - Divisor	0001	← 1100	0011	1110
	2: Diff < 0 => Do Nothing				
2	1: Shift Left, Diff = HI - Divisor	0011	← 1000	0011	0000
	2: Rem = Diff, set <b>lsb</b> of LO	0000	1001		
3	1: Shift Left, Diff = HI - Divisor	0001	← 0010	0011	1110
	2: Diff < 0 => Do Nothing				
4	1: Shift Left, Diff = HI - Divisor	0010	← 0100	0011	1111
	2: Diff < 0 => Do Nothing				

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 22

## Signed Integer Division

- ❖ Simplest way is to remember the signs
- ❖ Convert the dividend and divisor to positive
  - ❖ Obtain the 2's complement if they are negative
- ❖ Do the unsigned division
- ❖ Compute the signs of the quotient and remainder
  - ❖ Quotient sign = Dividend sign XOR Divisor sign
  - ❖ Remainder sign = Dividend sign
- ❖ Negate the quotient and remainder if their sign is negative
  - ❖ Obtain the 2's complement to convert them to negative

## Signed Integer Division Examples

1. **Positive** Dividend and **Positive** Divisor
  - ❖ Example:  $+17 / +3$       Quotient = +5    Remainder = +2
2. **Positive** Dividend and **Negative** Divisor
  - ❖ Example:  $+17 / -3$       Quotient = -5    Remainder = +2
3. **Negative** Dividend and **Positive** Divisor
  - ❖ Example:  $-17 / +3$       Quotient = -5    Remainder = -2
4. **Negative** Dividend and **Negative** Divisor
  - ❖ Example:  $-17 / -3$       Quotient = +5    Remainder = -2

The following equation must always hold:


$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$

## Next ...

- ❖ Unsigned Integer Multiplication
- ❖ Signed Integer Multiplication
- ❖ Faster Multiplication
- ❖ Integer Division
- ❖ Integer Multiplication and Division in MIPS

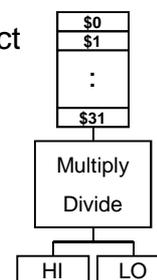
## Integer Multiplication in MIPS

- ❖ Multiply instructions
  - ❖ `mult $s1,$s2` **Signed multiplication**
  - ❖ `multu $s1,$s2` **Unsigned multiplication**
- ❖ 32-bit multiplication produces a 64-bit Product
- ❖ Separate pair of 32-bit registers
  - ❖ **HI = high-order 32-bit of product**
  - ❖ **LO = low-order 32-bit of product**
- ❖ MIPS also has a special `mul` instruction
  - ❖ `mul $s0,$s1,$s2`  **$\$s0 = \$s1 \times \$s2$**
  - ❖ **Put low-order 32 bits into destination register**
  - ❖ **HI & LO are undefined**


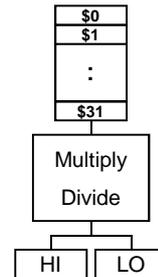
## Integer Division in MIPS

- ❖ Divide instructions
  - ✧ `div $s1,$s2`      **Signed division**
  - ✧ `divu $s1,$s2`      **Unsigned division**
- ❖ Division produces quotient and remainder
- ❖ Separate pair of 32-bit registers
  - ✧ **HI = 32-bit remainder**
  - ✧ **LO = 32-bit quotient**
  - ✧ If divisor is 0 then result is **unpredictable**
- ❖ Moving data from HI/LO to MIPS registers
  - ✧ `mfhi Rd` (move from HI to Rd)
  - ✧ `mflo Rd` (move from LO to Rd)



Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 27

## Integer Multiply/Divide Instructions

Instruction	Meaning	Format						
<code>mult Rs, Rt</code>	Hi, Lo = $Rs \times Rt$	$op^6 = 0$	$Rs^5$	$Rt^5$	0	0	0x18	
<code>multu Rs, Rt</code>	Hi, Lo = $Rs \times Rt$	$op^6 = 0$	$Rs^5$	$Rt^5$	0	0	0x19	
<code>mul Rd, Rs, Rt</code>	$Rd = Rs \times Rt$	0x1c	$Rs^5$	$Rt^5$	$Rd^5$	0	0x02	
<code>div Rs, Rt</code>	Hi, Lo = $Rs / Rt$	$op^6 = 0$	$Rs^5$	$Rt^5$	0	0	0x1a	
<code>divu Rs, Rt</code>	Hi, Lo = $Rs / Rt$	$op^6 = 0$	$Rs^5$	$Rt^5$	0	0	0x1b	
<code>mfhi Rd</code>	$Rd = Hi$	$op^6 = 0$	0	0	$Rd^5$	0	0x10	
<code>mflo Rd</code>	$Rd = Lo$	$op^6 = 0$	0	0	$Rd^5$	0	0x12	

- ❖ Signed arithmetic: `mult`, `div` (Rs and Rt are signed)
  - ✧ LO = 32-bit low-order and HI = 32-bit high-order of multiplication
  - ✧ LO = 32-bit quotient and HI = 32-bit remainder of division
- ❖ Unsigned arithmetic: `multu`, `divu` (Rs and Rt are unsigned)
- ❖ **NO arithmetic exception** can occur

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 28

## Integer to String Conversion

- ❖ Objective: convert an unsigned 32-bit integer to a string
- ❖ How to obtain the decimal digits of the number?
  - ◇ Divide the number by 10, Remainder = decimal digit (0 to 9)
  - ◇ Convert decimal digit into its ASCII representation ('0' to '9')
  - ◇ Repeat the division until the quotient becomes zero
  - ◇ Digits are computed **backwards** from least to most significant
- ❖ Example: convert 2037 to a string
  - ◇ Divide 2037/10    quotient = 203    remainder = 7    char = '7'
  - ◇ Divide 203/10    quotient = 20    remainder = 3    char = '3'
  - ◇ Divide 20/10    quotient = 2    remainder = 0    char = '0'
  - ◇ Divide 2/10    quotient = 0    remainder = 2    char = '2'

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 29

## Integer to String Procedure

```
#-----  
# int2str: Converts an unsigned integer into a string  
# Input:   $a0 = unsigned integer  
# In/Out:  $a1 = address of string buffer (12 bytes)  
#-----  
int2str:  
    move    $t0, $a0           # $t0 = dividend = unsigned integer  
    li     $t1, 10             # $t1 = divisor = 10  
    addiu  $a1, $a1, 11        # start at end of string buffer  
    sb     $zero, 0($a1)       # store a NULL byte  
convert:  
    divu   $t0, $t1            # LO = quotient, HI = remainder  
    mflo  $t0                  # $t0 = quotient  
    mfhi  $t2                  # $t2 = remainder  
    addiu $t2, $t2, 0x30       # convert digit to a character  
    addiu $a1, $a1, -1         # point to previous byte  
    sb    $t2, 0($a1)         # store digit character  
    bnez  $t0, convert         # loop if quotient is not 0  
    jr   $ra                  # return to caller
```

Integer Multiplication and Division

ICS 233 – KFUPM

© Muhamed Mudawar – slide 30