


Problem 1:

a) For the circuit shown above find the node equations necessary to solve (DO NOT SOLVE THE EQUATIONS) for the nodes v_1 , v_2 and v_3 then write

them in the matrix form $GV = I$ where

$$V = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$v_2 - v_1 = 5 \quad \text{--- (1)}$$

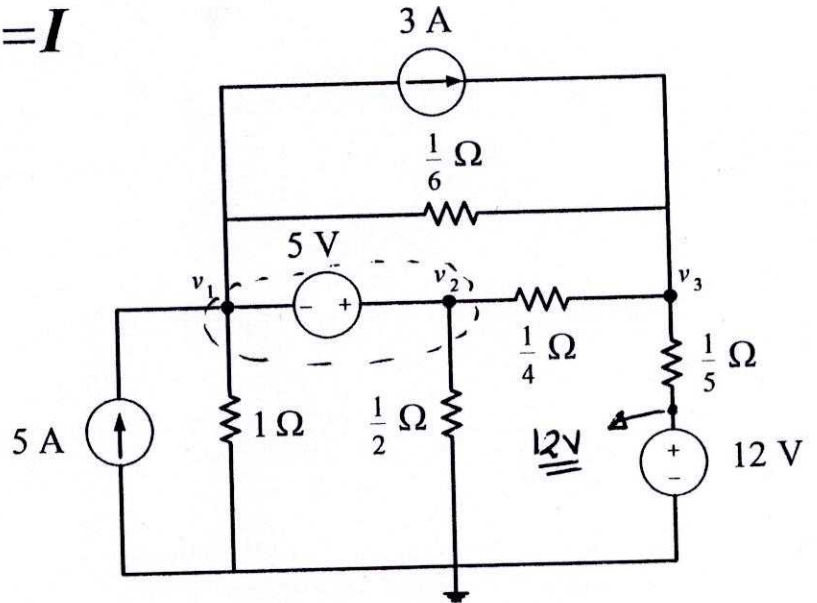

Kcl on Super Node

$$\frac{v_1}{1} - 5 + \frac{v_1 - v_3}{1/6} + 3 + \frac{v_2}{1/2} + \frac{v_2 - v_3}{1/4} = 0$$

$$\Rightarrow 7v_1 + 6v_2 - 10v_3 = 2 \quad \text{--- (2)}$$

Kcl on Node v_3

$$\frac{v_3 - v_2}{1/4} + \frac{v_3 - 12}{1/5} + \frac{v_3 - v_1}{1/6} - 3 = 0$$

$$\Rightarrow -6v_1 - 4v_2 + 15v_3 = 63 \quad \text{--- (3)}$$

$$\begin{bmatrix} -1 & 1 & 0 \\ 7 & 6 & -10 \\ -6 & -4 & 15 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 2 \\ 63 \end{bmatrix}$$


b) For the circuit shown, if the nodes voltages are found to be
 $v_1 = 7.4135 \text{ V}$ $v_2 = 6.5279 \text{ V}$ $v_3 = 8.9062 \text{ V}$

Find the following:

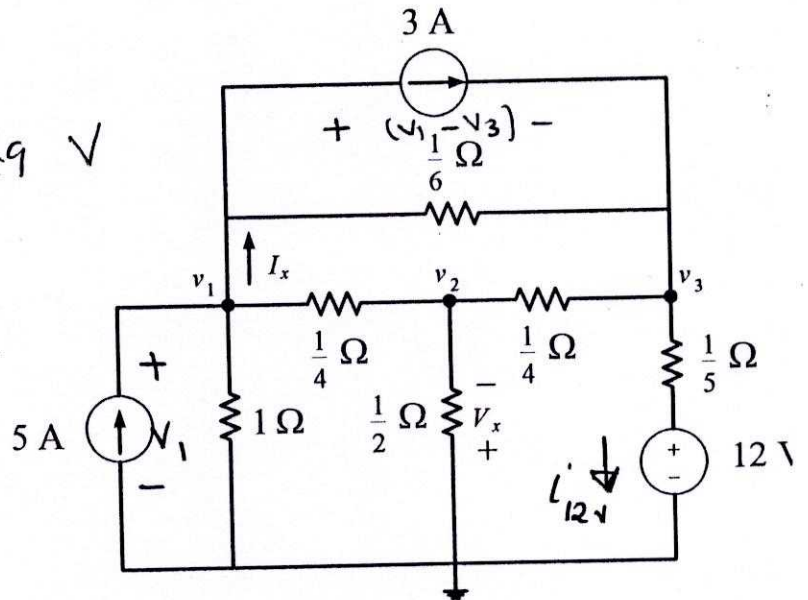1. The voltage V_x and the current I_x ?
2. The power **absorbed** by each of the three independent sources?

$$V_x = -v_2 = -6.5279 \text{ V}$$

$$\begin{aligned} I_x &= 5 + \frac{0 - v_1}{1} + \frac{v_2 - v_1}{1/4} \\ &= 5 - v_1 - 4(v_1 - v_2) \\ &= -5.9559 \text{ A} \end{aligned}$$





$$P_{5A} = -(v_1)(5) = -37.0675 \text{ W}$$

$$P_{3A} = (v_1 - v_3)(3) = -4.4781 \text{ W}$$


$$P_{12V} = 12 I'_{12V} = 12 \left[\frac{v_3 - 12}{1/5} \right] = -185.628 \text{ W}$$

Problem 2:

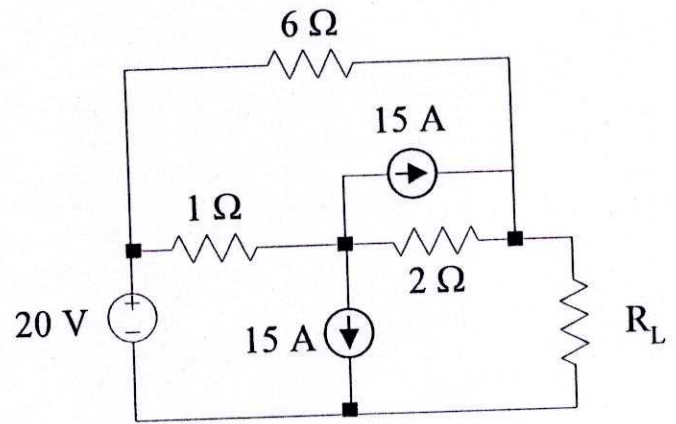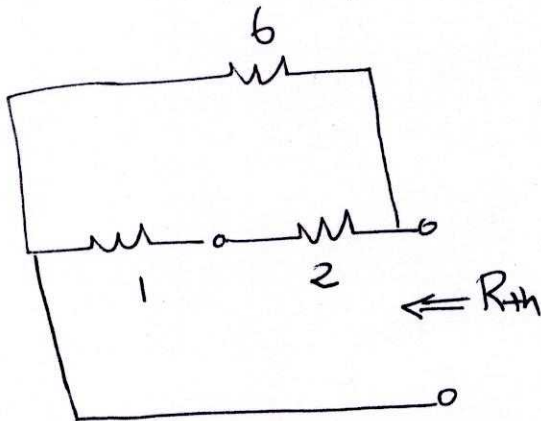- a) In the circuit shown, determine the value of the resistor R_L that absorbs maximum power from the circuit.
 b) Calculate the maximum power that is absorbed by R_L


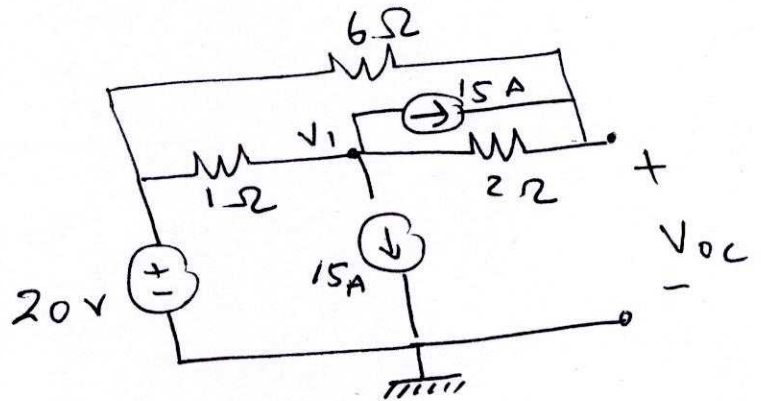
$$R_L = R_{th} = 3 \parallel 6 = \boxed{2 \Omega}$$



using Nodal analysis to find V_{oc}

$$\frac{V_1 - 20}{1} + 15 + 15 + \frac{V_1 - V_{oc}}{2} = 0$$

$$\Rightarrow 3V_1 - V_{oc} = -20 \quad \text{--- (1)}$$






$$\frac{V_{oc} - V_1}{2} + \frac{V_{oc} - 20}{6} = 15$$

$$\Rightarrow -3V_1 + 4V_{oc} = 110 \quad \text{--- (2)}$$

From (1) and (2) $\Rightarrow 3V_{oc} = 90 \Rightarrow V_{oc} = \boxed{30 \text{ V}}$



$$\Rightarrow P_{max} = \frac{V_{oc}^2}{4R_{th}} = \frac{(30)^2}{4(2)} = \boxed{112.5 \text{ W}}$$

Problem 3

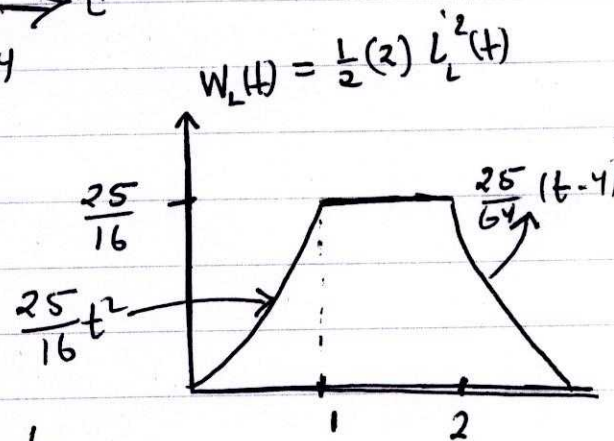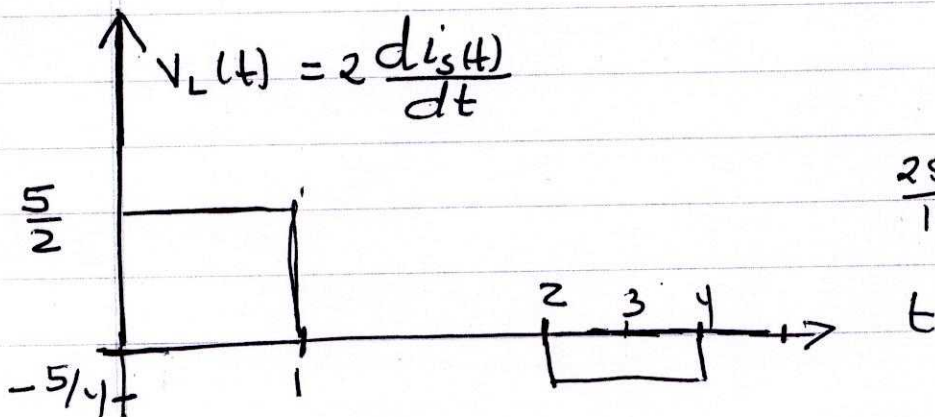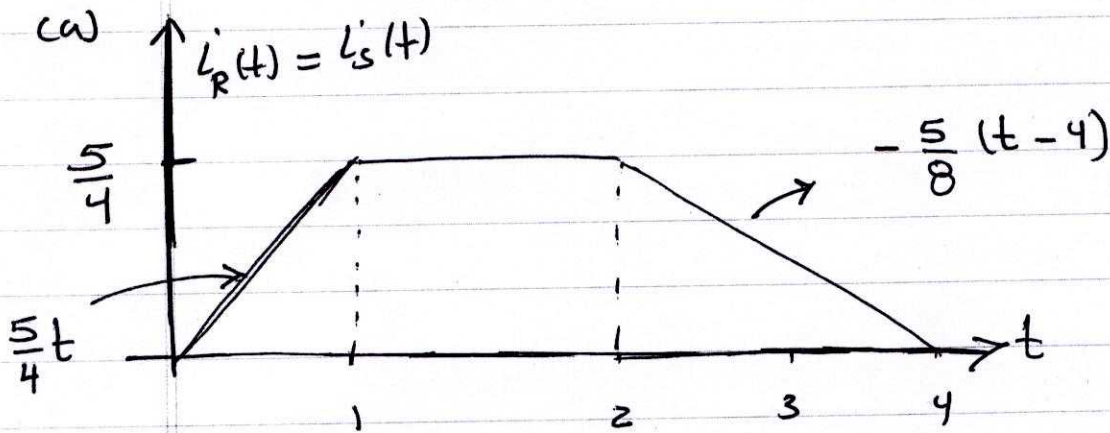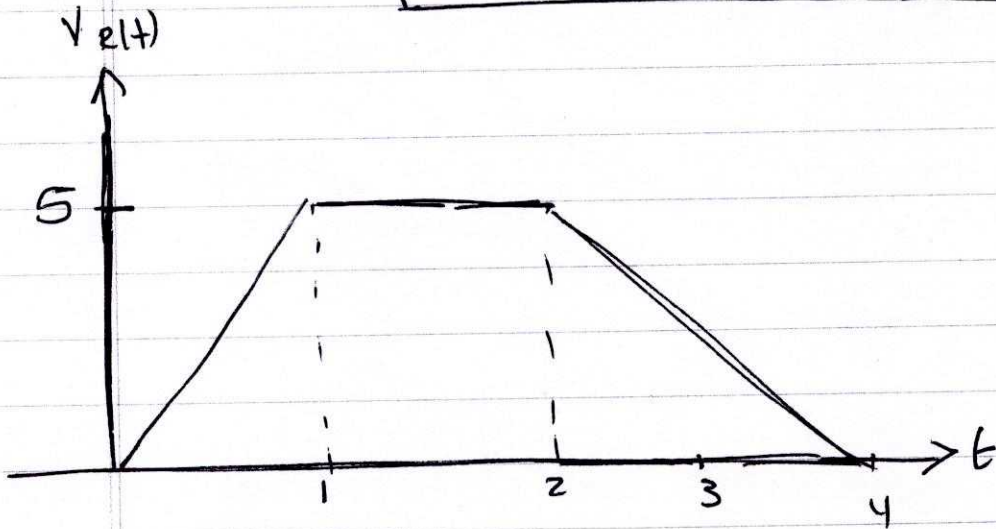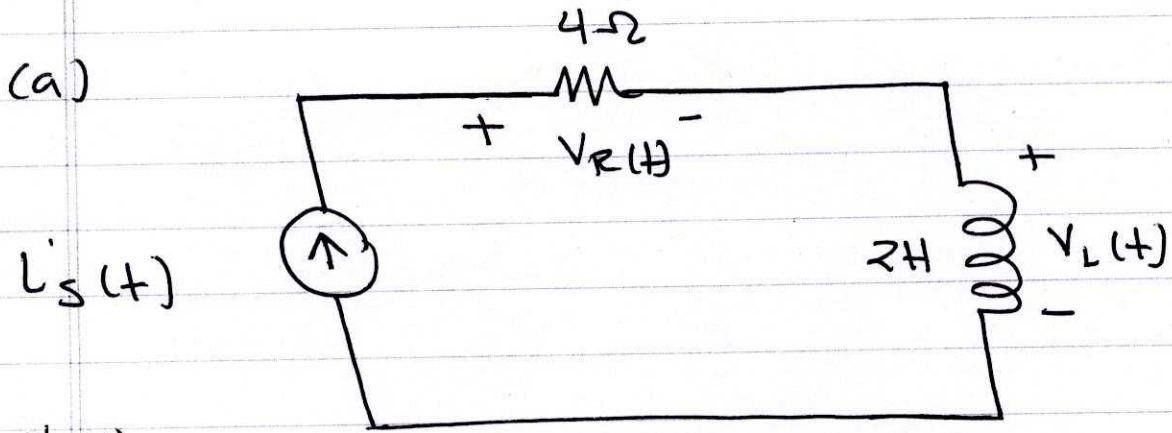


Problem 3

(b)

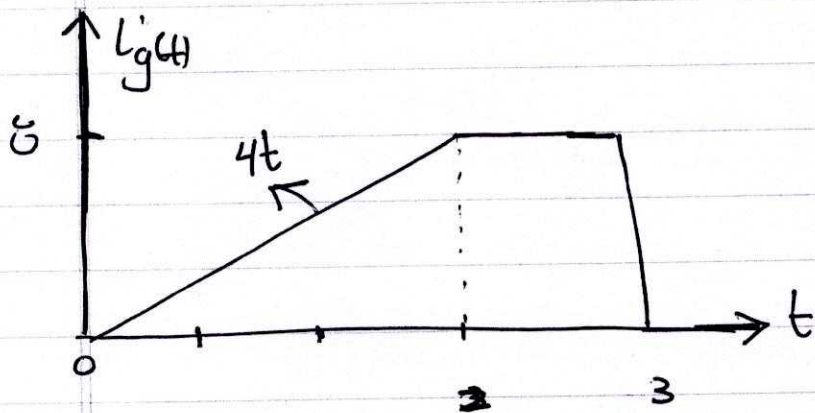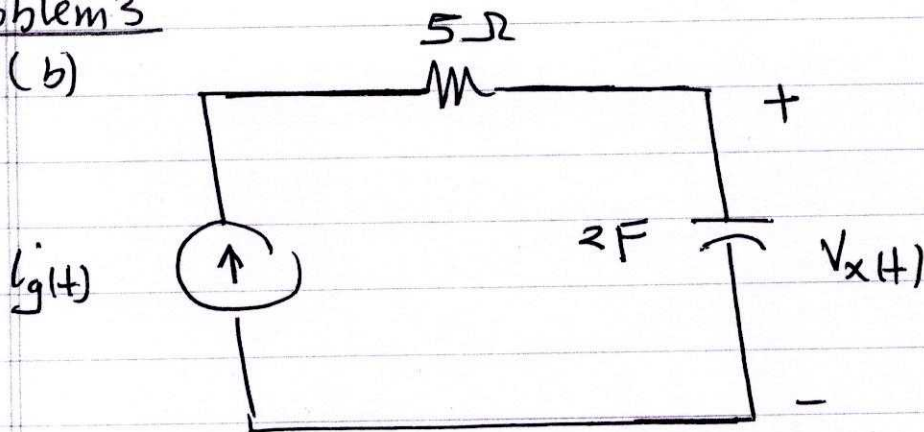
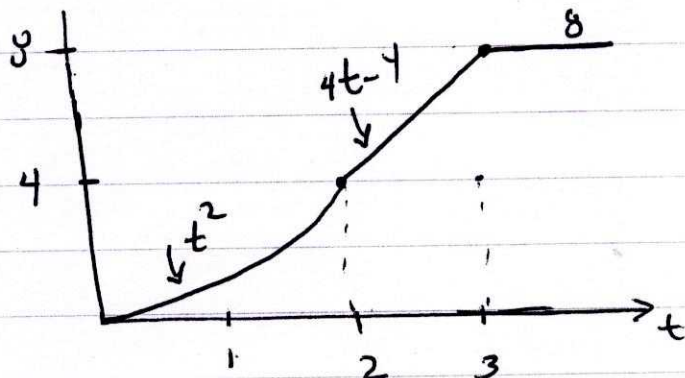
$$v_x(t) = \frac{1}{2} \int_{-\infty}^t i_g(t') dt'$$



$$t < 0 \Rightarrow v_x(t) = 0$$

$$0 < t < 2 \Rightarrow v_x(t) = \frac{1}{2} \int_0^t (4t') dt' = t^2$$

$$2 < t < 3 \Rightarrow v_x(t) = \frac{1}{2} \int_0^2 (4t') dt' + \frac{1}{2} \int_2^t 8 dt' = 4t - 4$$

$$t > 3 \Rightarrow v_x(t) = v_x(3) + \frac{1}{2} \int_3^t 0 dt' = 8$$